



# Diode Applications

## Clippers (Limiters)

# Diode Clipping Circuits

- Used in various circuit configurations to clip signal waveforms
- Always remember is that in the **forward** direction the voltage across a diode will always **be limited** to approximately 0.7V for silicon and 0.3 for Germanium
- In the **reverse** direction the diode behaves like an **open circuit**

# CLIPPER (Limiter) :Series diode



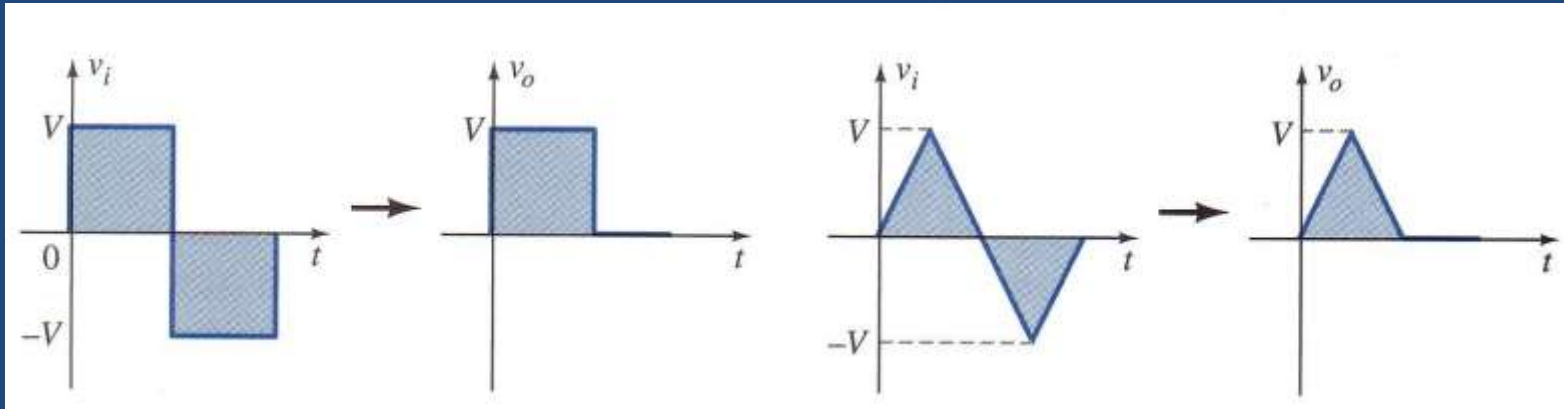
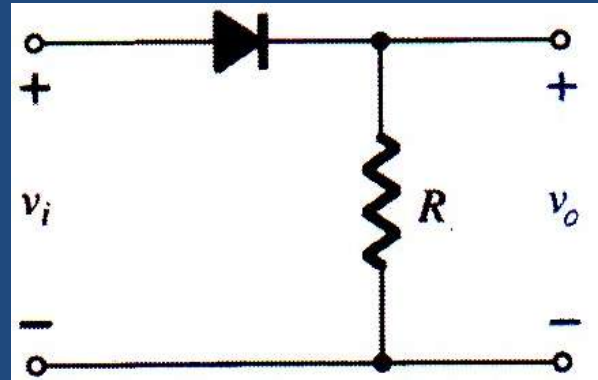


# CLIPPER (Limiter) :Series diode

- **Steps for analysis:**



1. Note direction of the diode and the applied voltage levels
2. Determine the applied voltage that will cause a change in state for the diode.
3. Be continually aware of the defined terminals and polarity of  $v_o$
4. It can be helpful to sketch the input signal above the output at instantaneous values of the input.

# CLIPPER (Limiter) : Series diode

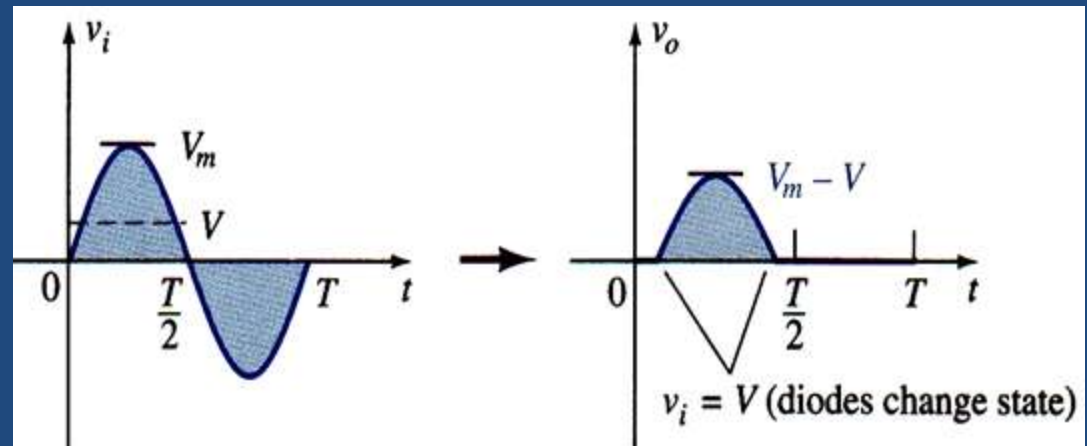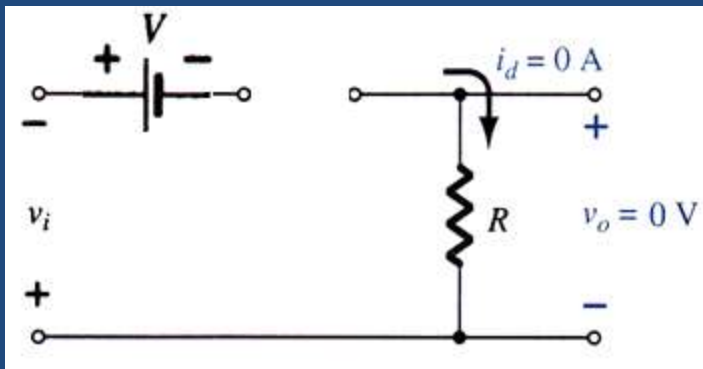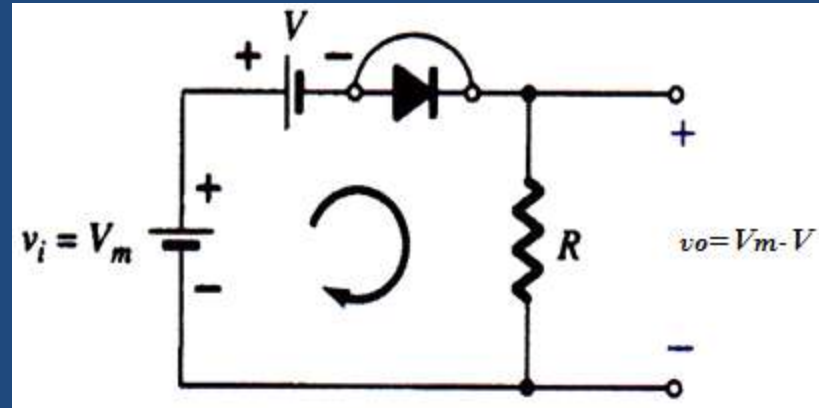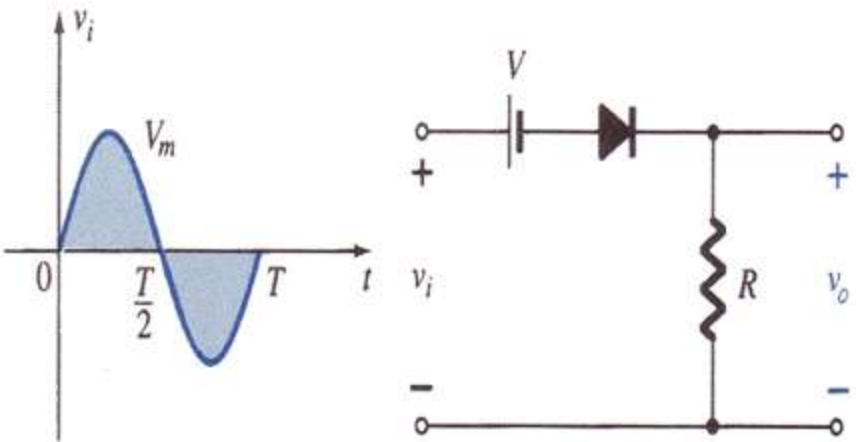


# CLIPPER (Limiter) :Series diode

- Example 2.20

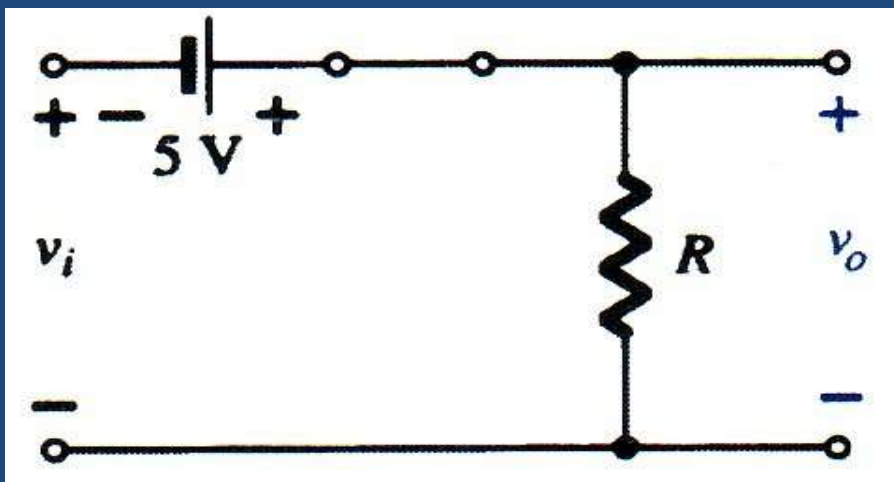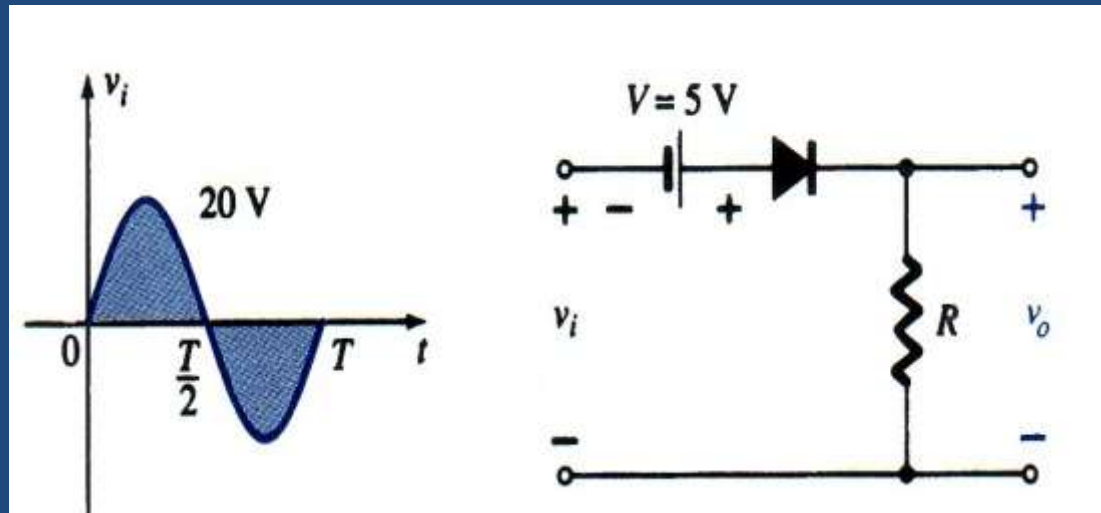

Make a mental sketch of the response of the network based on the direction of the diode and the applied voltage levels


# CLIPPER (Limiter) :Series diode

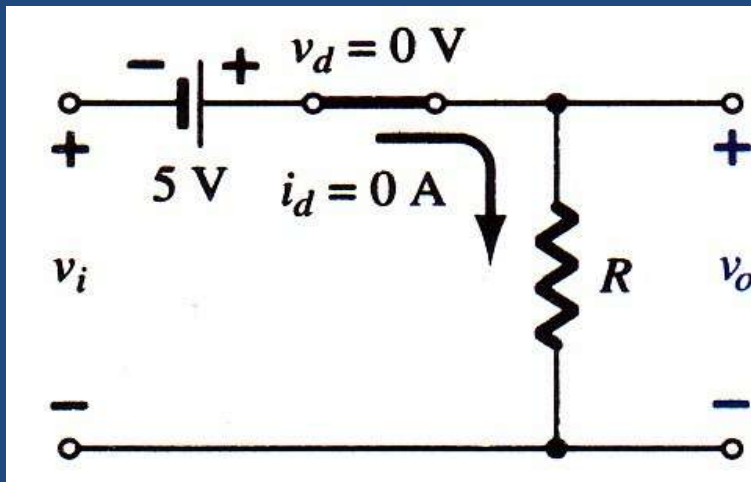

- Determine the applied voltage that will cause a change in state for the diode.






$$v_i \geq -5\text{ V}$$

$$v_o = v_i + V$$

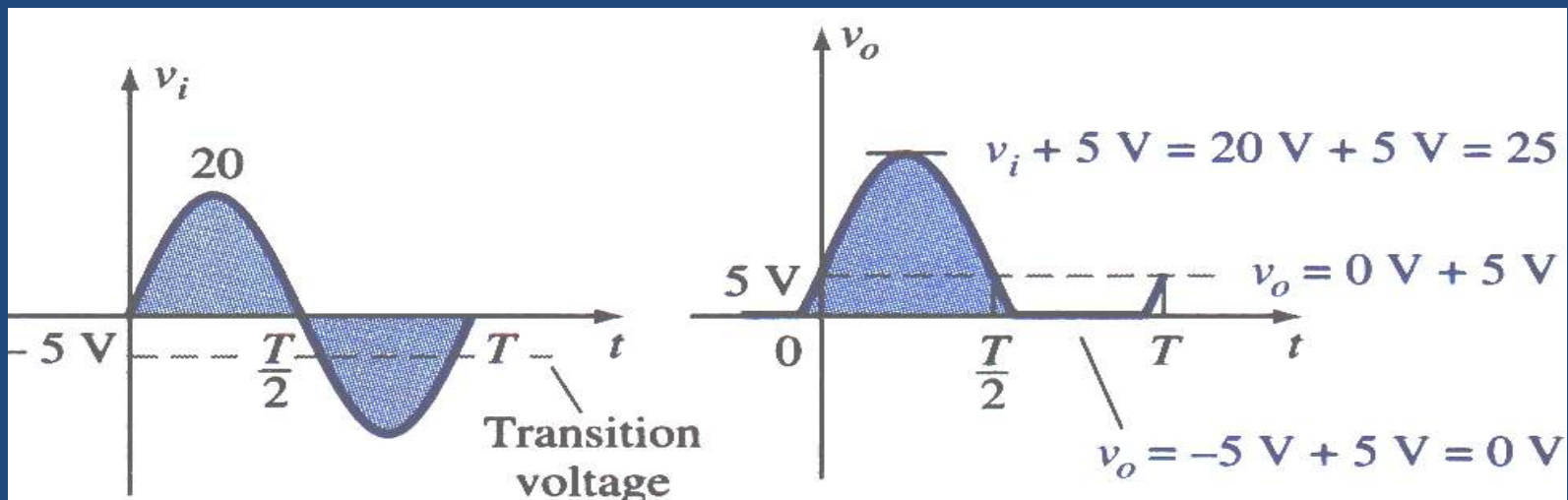







# CLIPPER (Limiter) : Series diode

## Example 2.21

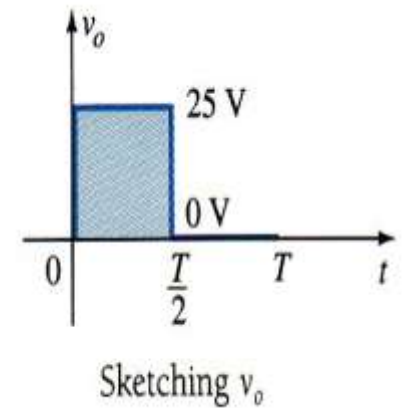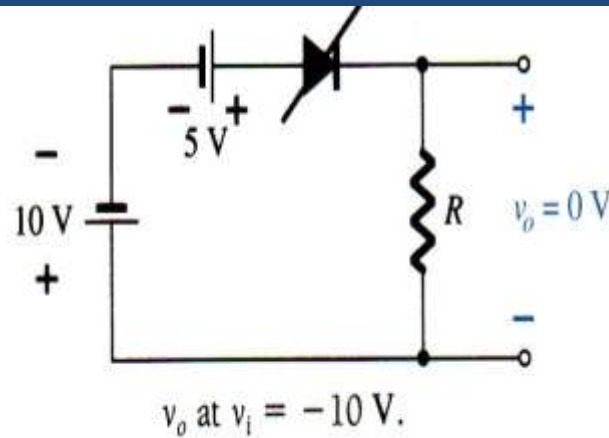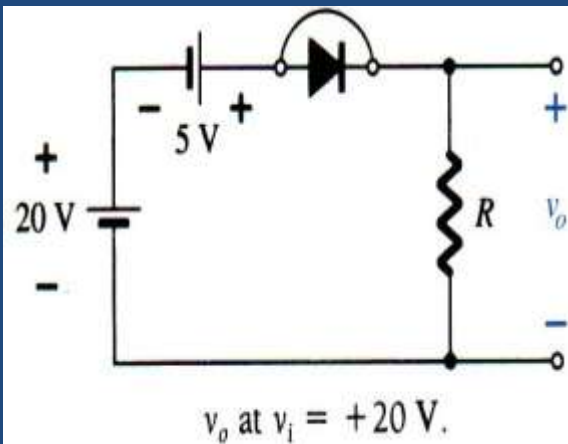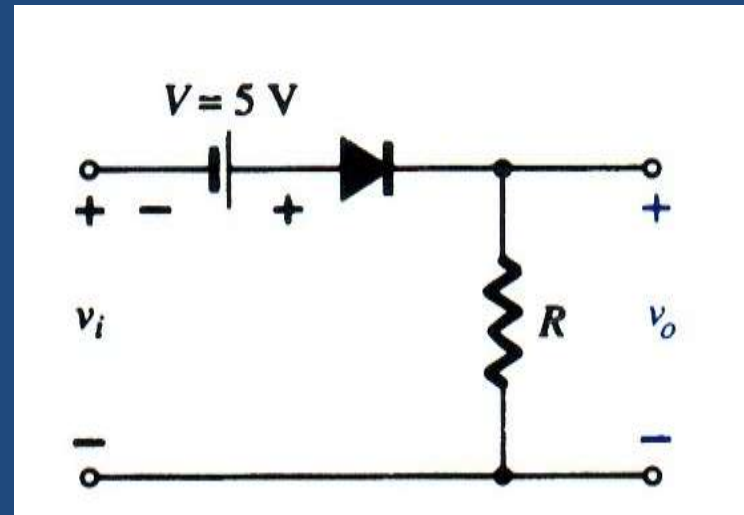
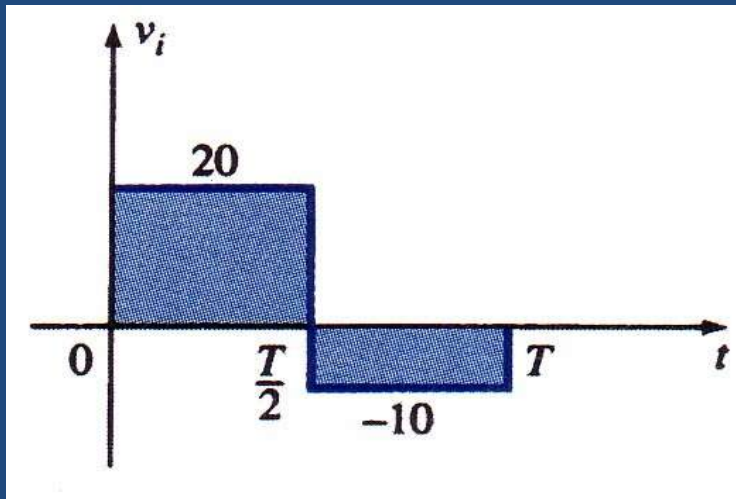





# CLIPPER : Series diode

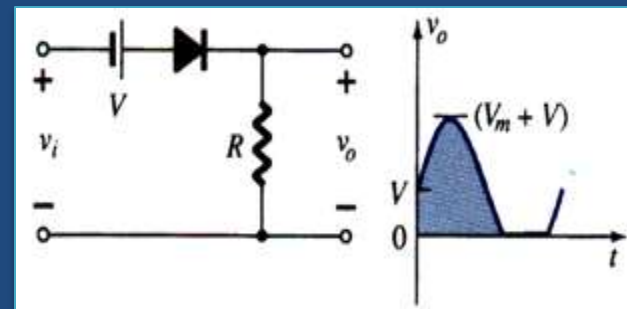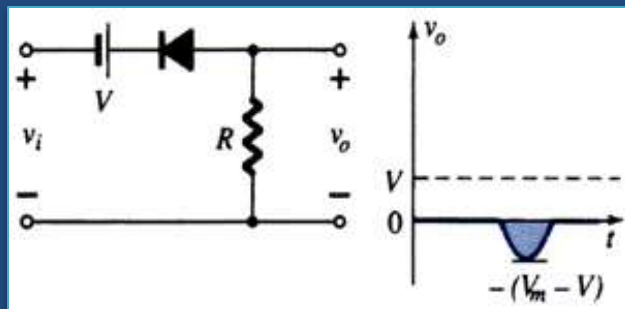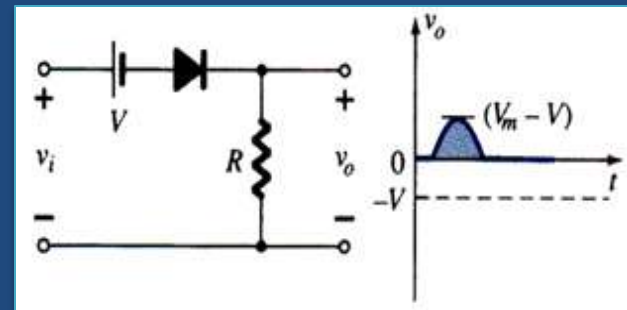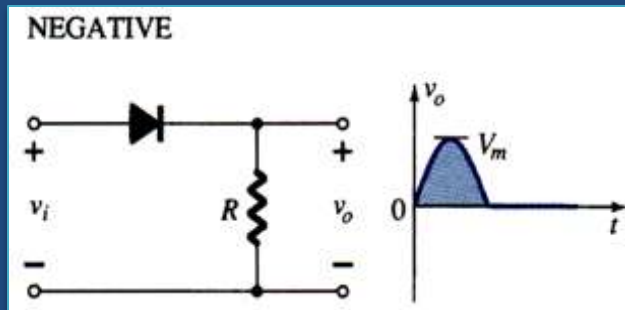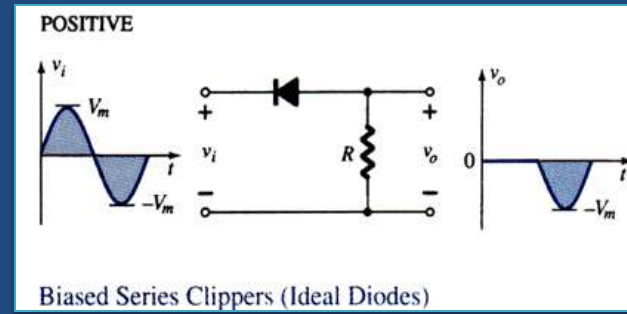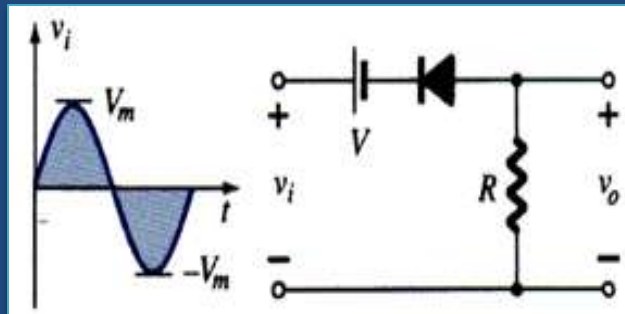

# CLIPPER (Limiter) : Parallel diode


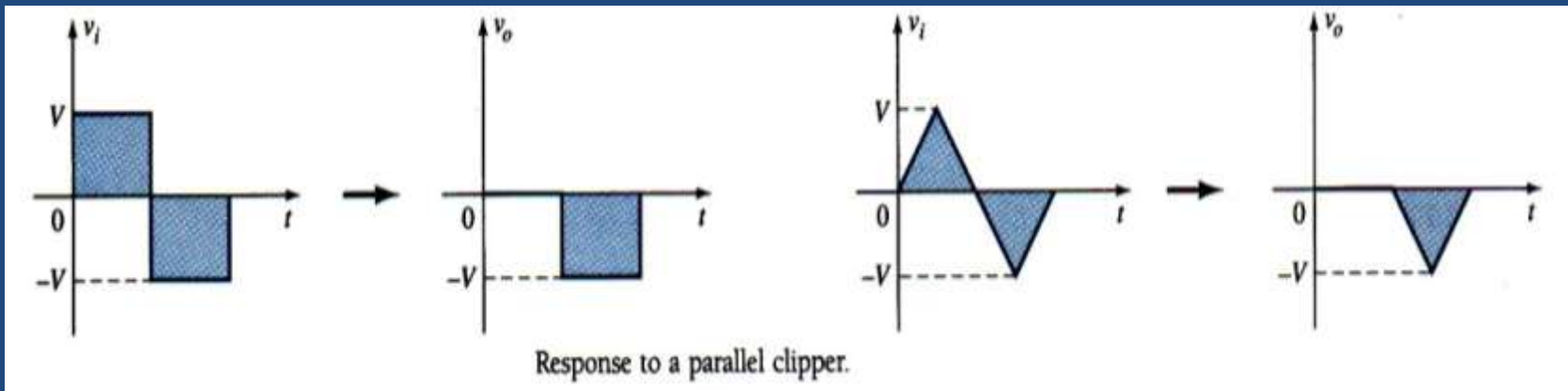
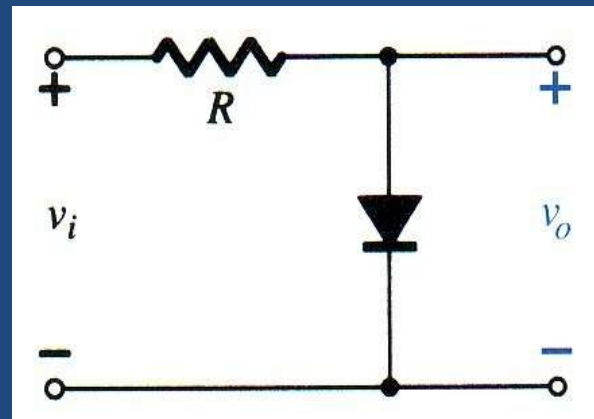


# CLIPPER (Limiter) : Parallel diode

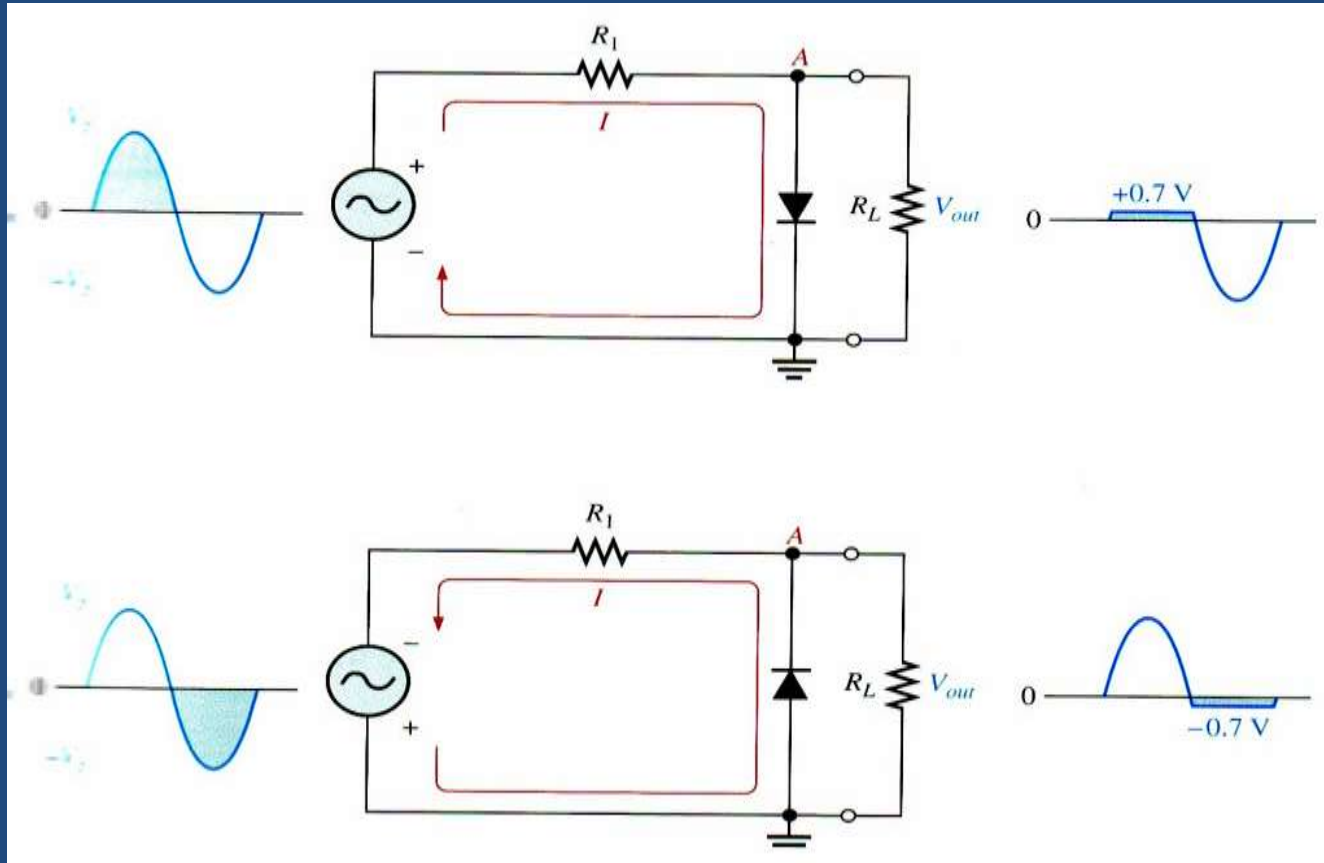


# CLIPPER : Parallel diode

## Example 2.22

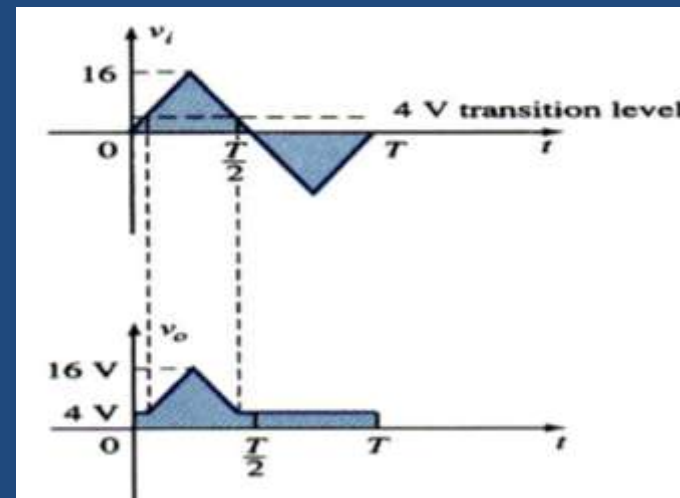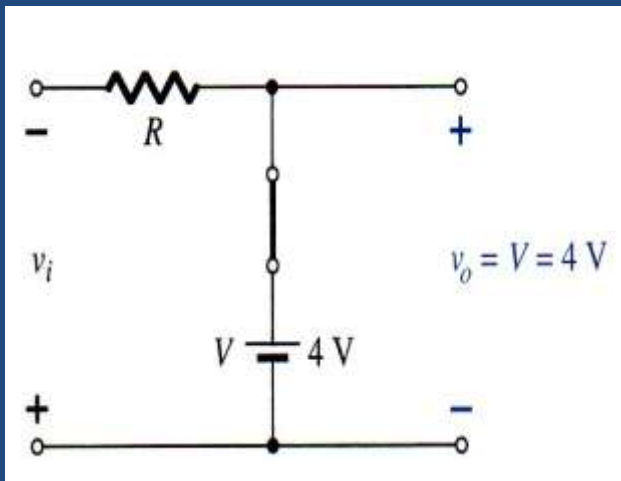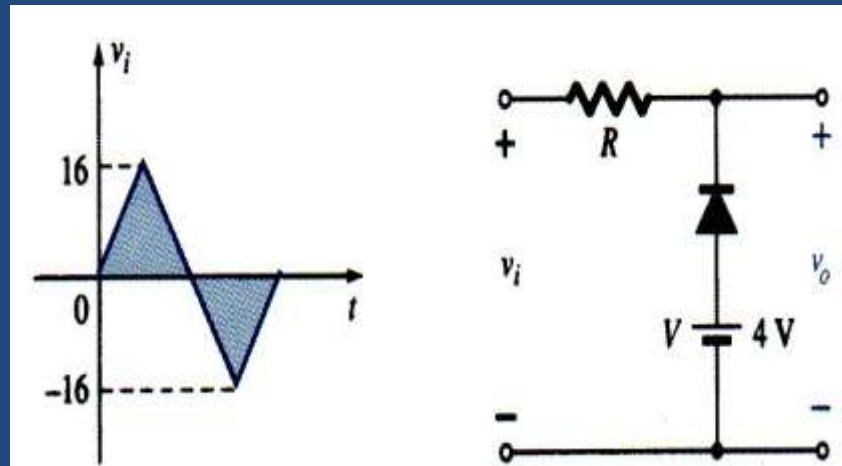


# CLIPPER : Parallel diode

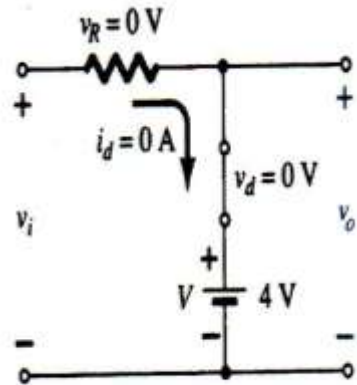


Determining the transition level

$$v_i = V$$

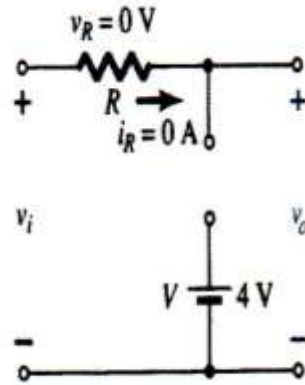

Determining  $v_o$



$$V_o = V_i$$

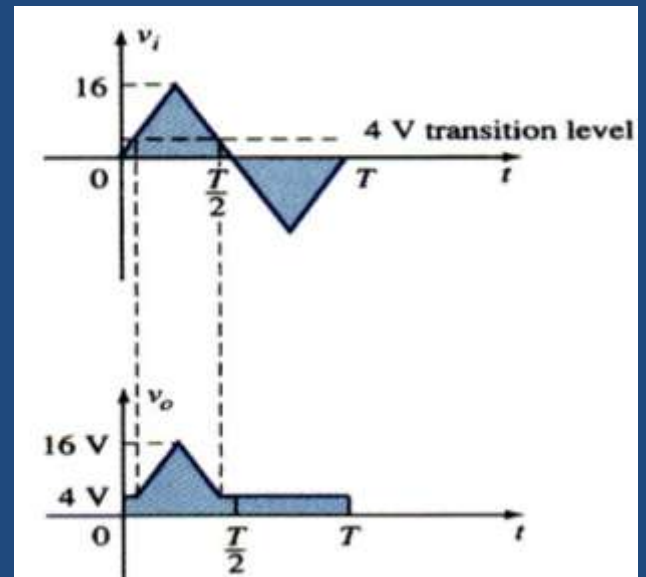

# CLIPPER : Parallel diode

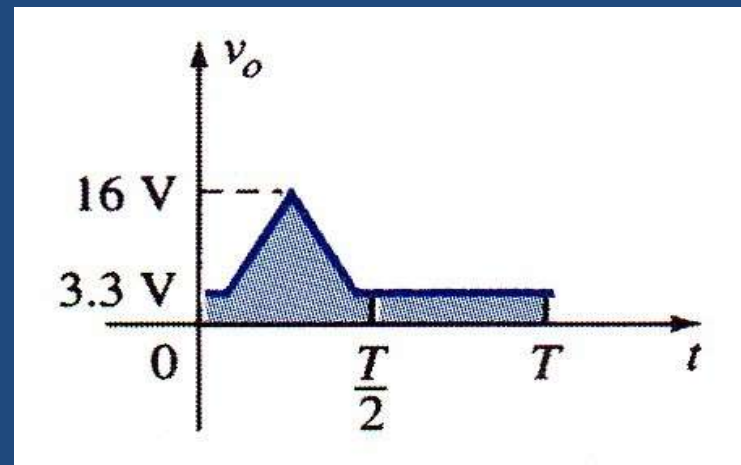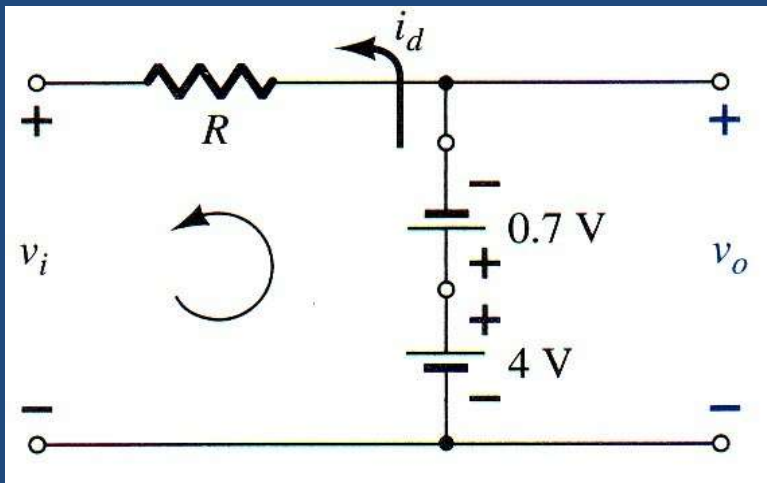
## Example 2.23

- Determining  $v_o$  the transition levels of the network
- For Input voltage less than 3.3 V the diode will be in the on state




$$v_o = 4 - 0.7\text{V} = 3.3$$

# Positive limiter


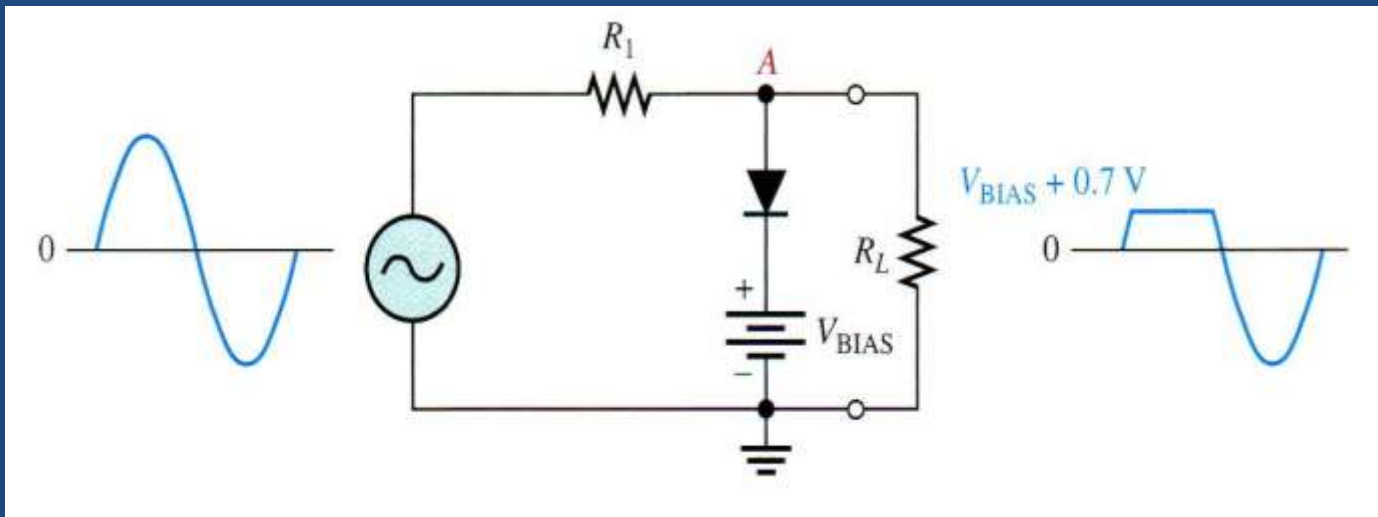


# Negative limiter







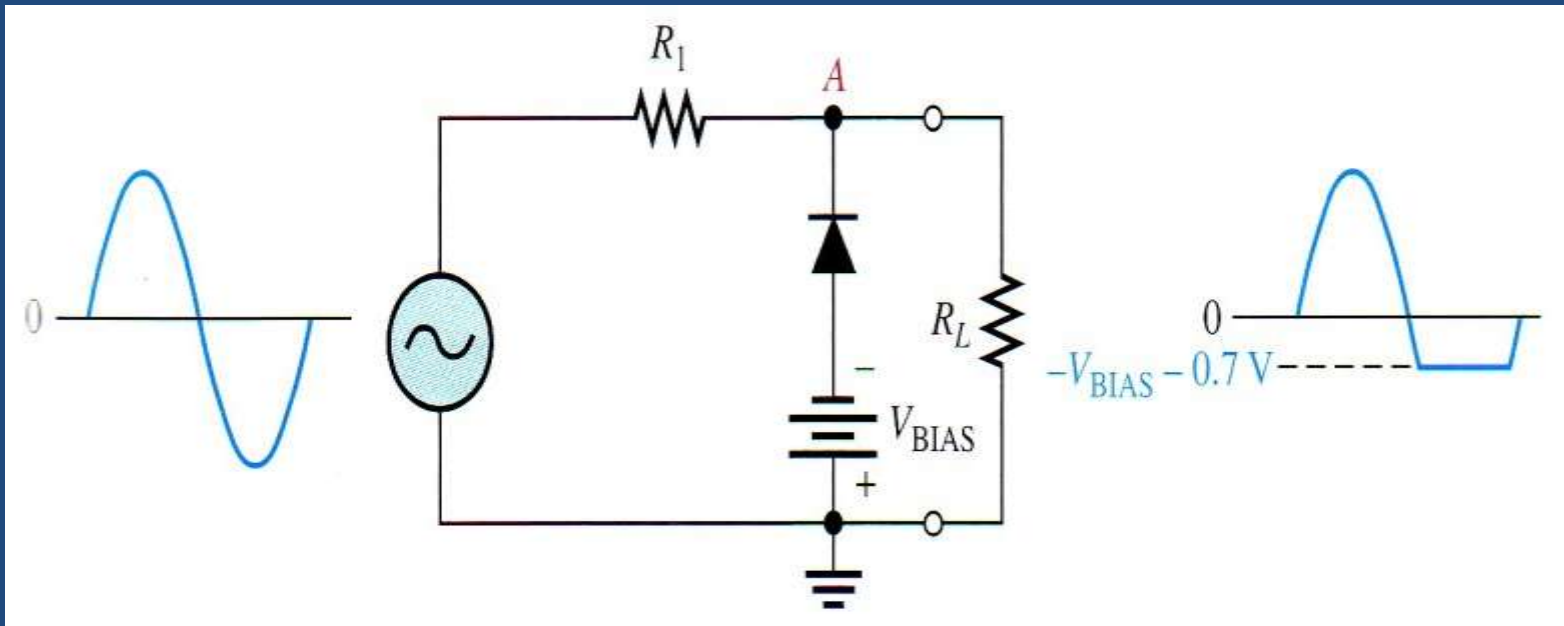






# Biased Limiter

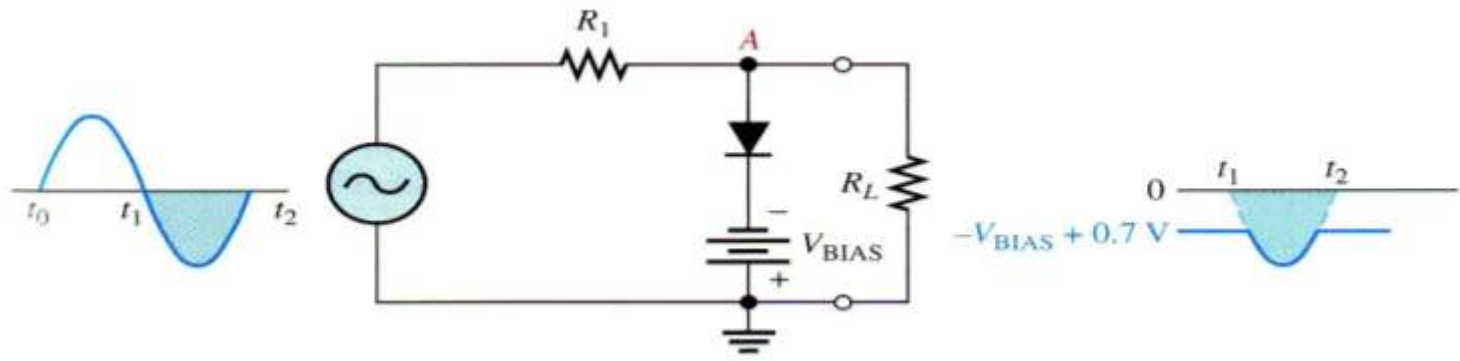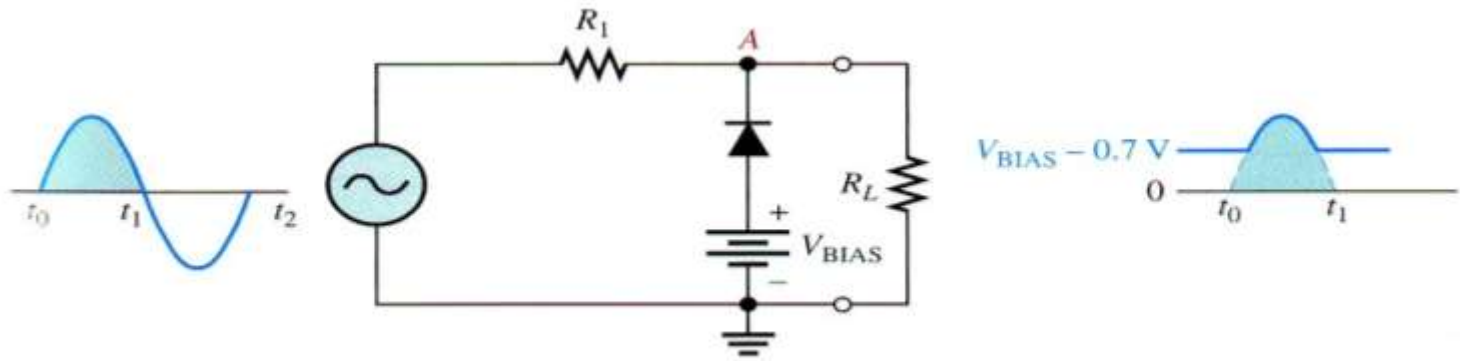

# CLIPPERS : Parallel diode

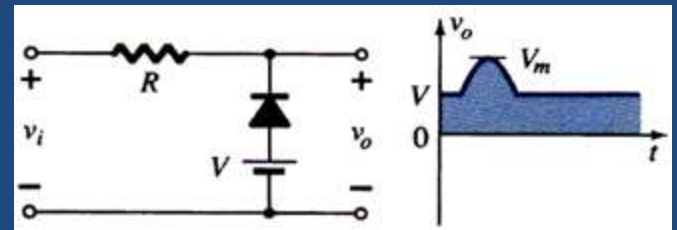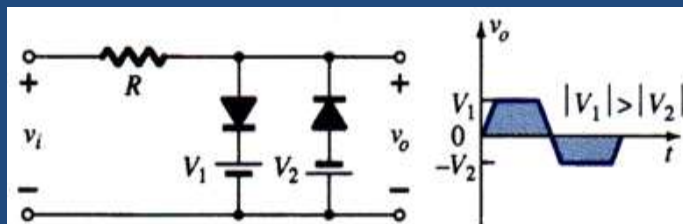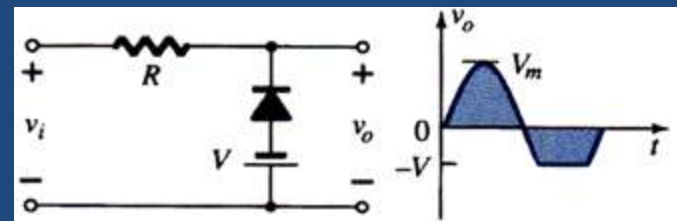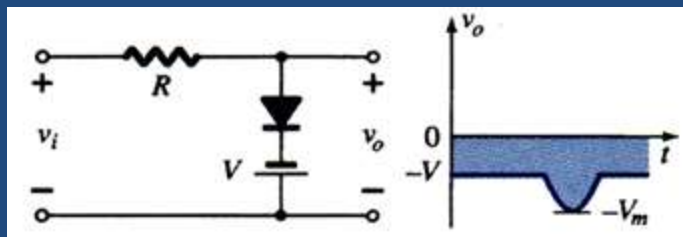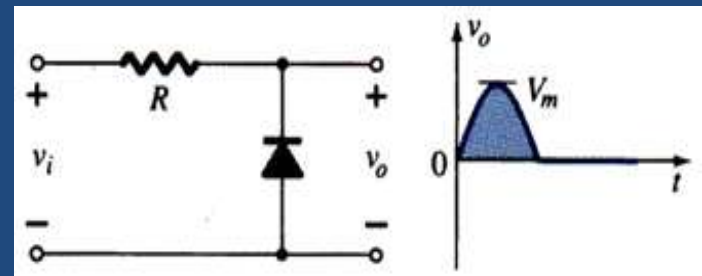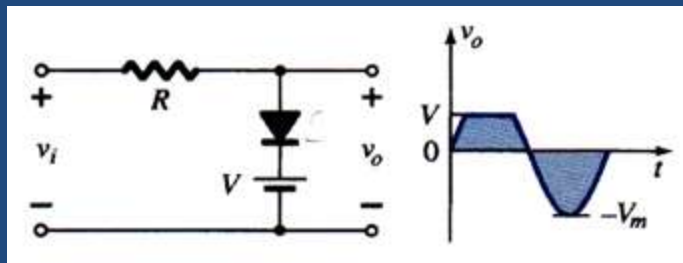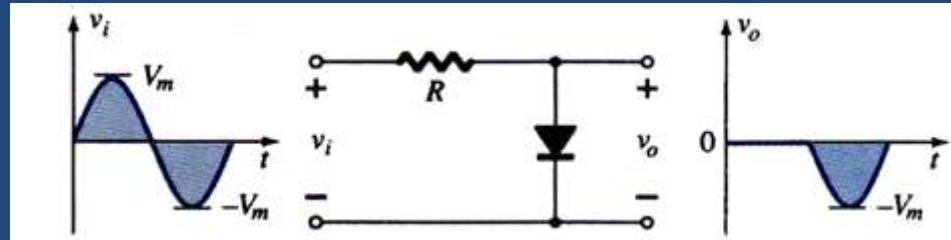

# Clippers

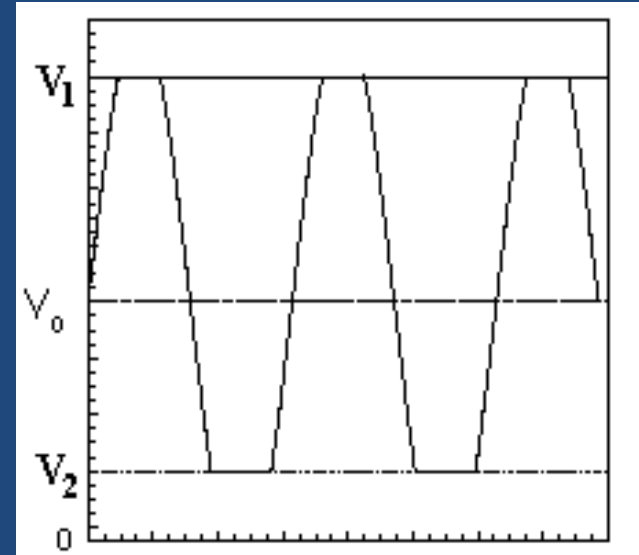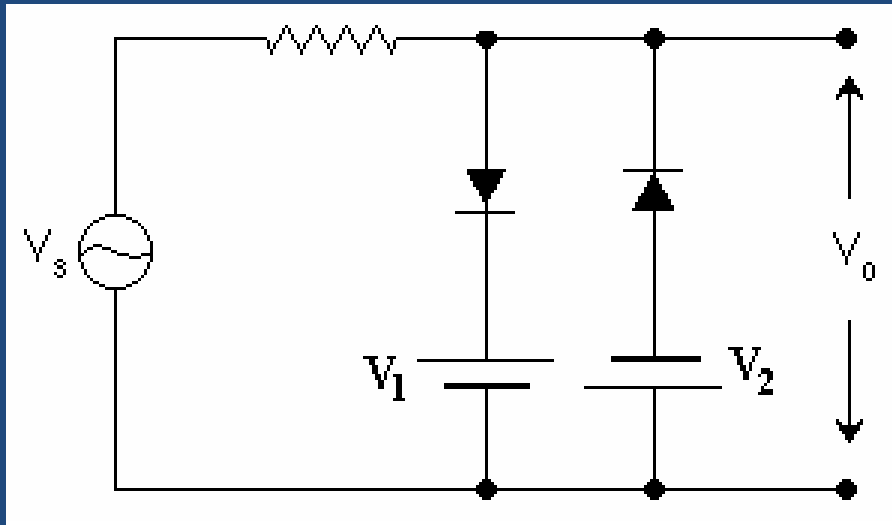

Notice that the dc sources  $V_1$  and  $V_2$  are reverse biasing the diodes in each branch.




Clockwise half cycle -  $V_s$  flows to the output until it becomes equal to  $V_1$ . At that point diode 1 can conduct, another path is found, and any voltage above  $V_1$  goes through the first diode branch.

Counter Clockwise half cycle -  $V_s$  flows to the output until it becomes equal to  $V_2$ . Excess voltage flows then through diode 2.

Output is “clipped” at  $V_1$  and  $V_2$ .
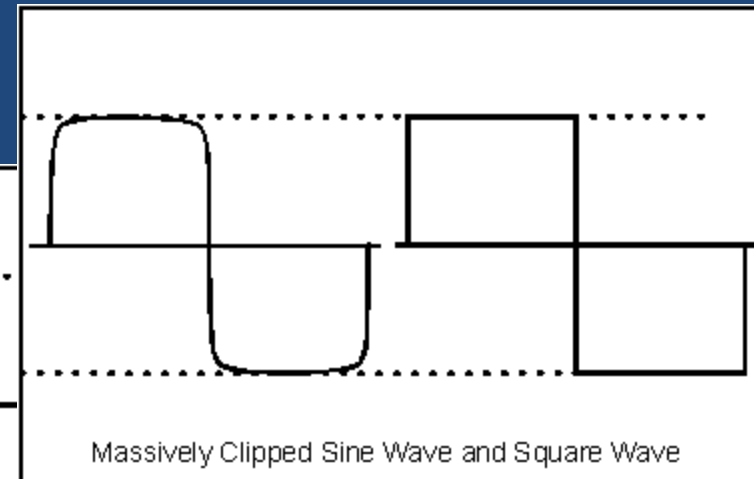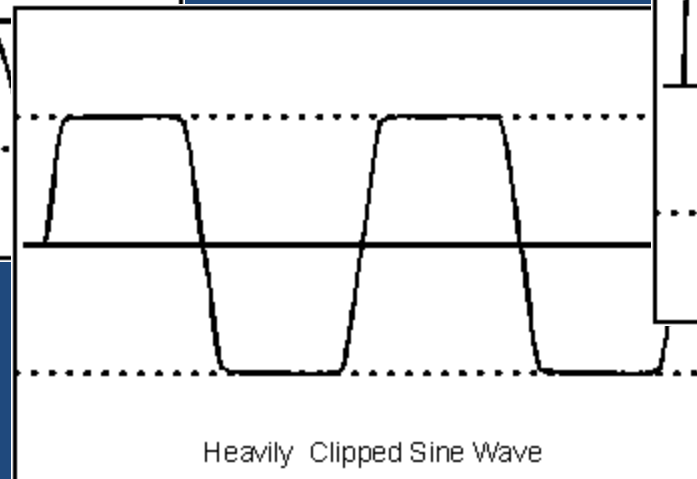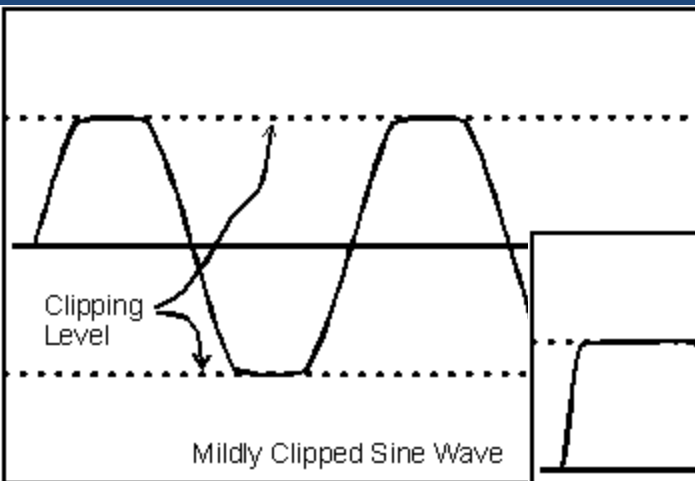
# Special Clipper

- If  $V_1 = V_2$  and  $V_s \gg V_1$ , then you can make a good square wave output.



# Other Clipper Uses

- Surge protection
- Noise reduction