

HW # 2


5.7) $I_C = I_S e^{\frac{V_{BE}}{V_T}} \Rightarrow I_S = I_C e^{-\frac{V_{BE}}{V_T}} ; V_T = 25mV$
 $\alpha = \frac{\beta}{1+\beta} ; \beta = \frac{\alpha}{1-\alpha} ; I_C = \beta I_B = \alpha I_E$
 $I_C + I_B = I_E$

Transistor	a	b	c	d	e
$V_{BE} (mV)$	690	690	580	780	820
$I_C (mA)$	1.00	1.00	0.13	10.10	73.95
$I_B (\mu A)$	50	70	7	120	1050
$I_E (mA)$	1.05	1.07	0.137	10.22	75.00
α	0.952	0.935	0.949	0.988	0.986
β	20	14.286	18.571	84.167	70.429
$I_S (A)$	1.03×10^{-15}	1.03×10^{-15}	1.09×10^{-14}	2.85×10^{-16}	4.2×10^{-16}


5.21)

$\beta = ?$

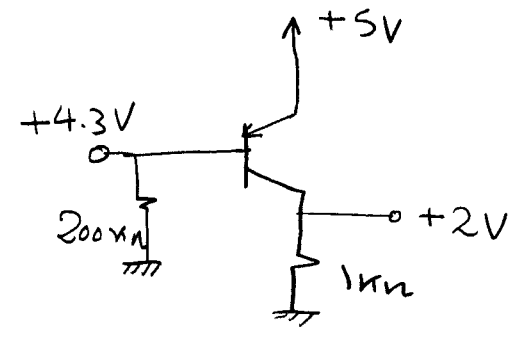
a) $I_B = \frac{4.3}{200} = 0.0215 mA$
 $I_C = \frac{2}{1} = 2 mA$
 $\beta = \frac{I_C}{I_B} = \frac{2}{0.0215} = 93$



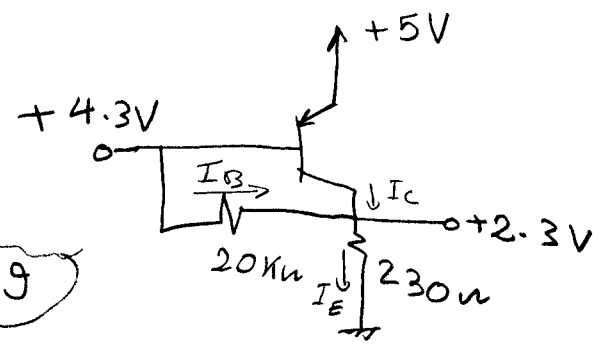b) $I_E = \frac{2.3}{0.23} = 10 mA$
 $I_B = \frac{4.3 - 2.3}{20} = 0.1 mA$
 $1 + \beta = \frac{I_E}{I_B} = 100 \Rightarrow \beta = 99$



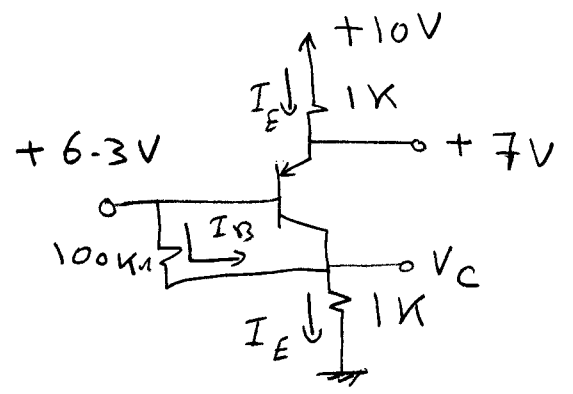c) $I_E = \frac{10 - 7}{1K} = 3 mA$
 $V_C = I_E \times 1K = 3V$
 $I_B = \frac{6.3 - 3}{100} = 0.033 mA$
 $1 + \beta = \frac{I_E}{I_B} = 90.91$
 $\Rightarrow \beta = 89.91$



5.39) $r_o = \frac{V_A}{I_C} = \frac{200}{I_C}$

$I_C = 1 \text{ mA} \Rightarrow r_o = 200 \text{ k}\Omega$

$I_C = 100 \mu\text{A} \Rightarrow r_o = 2 \text{ M}\Omega$

5.66) $R_E = ?$; $\beta_{\text{forced}} = 10$; $V_{EB} = 0.7 \text{ V}$


$V_{EC\text{sat}} = 0.2 \text{ V}$

$I_C = \frac{0.5 - (-5)}{1} = 5.5 \text{ mA}$

$I_B = \frac{I_C}{\beta_{\text{forced}}} = \frac{5.5}{10} = 0.55 \text{ mA}$

$I_E = I_C + I_B = 6.05 \text{ mA}$

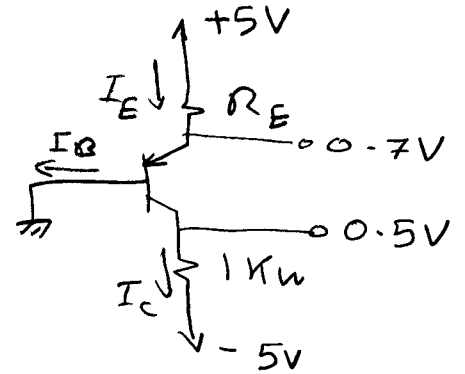$R_E = \frac{5 - 0.7}{I_E} = \frac{4.3}{6.05} = 0.71 \text{ k}\Omega$



5.86) $\beta = 100$

$V_B = ?$, $V_E = ?$

for $V_I = 0, +3, -5, -10 \text{ V}$


note that Q_1 & Q_2 can't be on at the same time

\Rightarrow this is push-pull

for Q_1 to be on $\Rightarrow V_I > 0.7 \text{ V}$

for Q_2 to be on $\Rightarrow V_I < -0.7 \text{ V}$

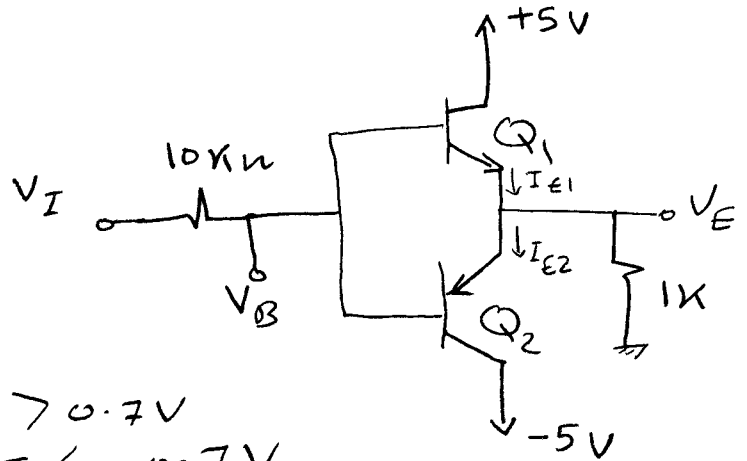$-0.7 < V_I < 0.7 \text{ V} \Rightarrow$ both Q_1 & Q_2 off



$V_I = 0 \text{ V}$

Q_1, Q_2 are off $\Rightarrow V_E = 0 \text{ V}$, $V_B = 0 \text{ V}$

$V_I = +3 \text{ V}$

Q_1 on & Q_2 off $\Rightarrow I_E = \frac{3 - 0.7}{1 + \frac{10}{101}} = 2.09 \text{ mA}$

$\therefore V_E = 2.09 \text{ V}$, $V_B = 2.79 \text{ V}$

$V_I = -5 \text{ V}$ Q_1 off & Q_2 on $\Rightarrow I_{E2} = \frac{5 - 0.7}{1 + \frac{10}{101}} = 3.91 \text{ mA}$

$V_E = -3.91 \text{ V}$; $V_B = -4.61 \text{ V}$


$V_I = -10 \text{ V}$ Q_1 off & Q_2 on (sat)

$\therefore V_E = -4.8 \text{ V}$; $V_B = -5.5 \text{ V}$

H.W # 3

(1)

5.89)

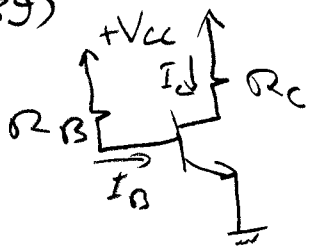

$$R_C = 3 \text{ k}\Omega, \quad V_{CC} = +5 \text{ V}, \quad \beta = 100$$
$$R_B = ? \quad \text{for } I_C = 1 \text{ mA}$$

Solution:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{I_C}{\beta} \Rightarrow \frac{5 - 0.7}{R_B} = \frac{1}{100}$$

$$\therefore R_B = 430 \text{ k}\Omega$$

Now $I_C = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right) = 0.01 \beta \text{ mA}$

$$50 \leq \beta \leq 150$$

$$0.5 \text{ mA} \leq I_C \leq 1.5 \text{ mA}$$

Also, $V_{CE} = V_{CC} - I_C R_C$

$$0.5 \text{ V} \leq V_{CE} \leq 3.5 \text{ V}$$

$\beta = 150$ \Rightarrow $\beta = 50$


Note that for $\beta = 150$ the transistor is near saturation.

Comment:

This design is not recommended since it is too sensitive to β variations.

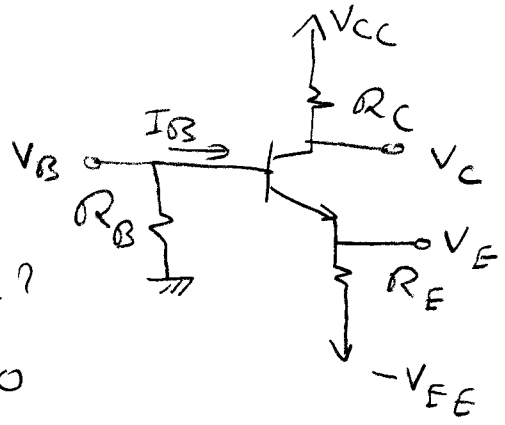5.93) $V_{CC} = V_{EE} = 3V$

$I_C = 3mA$; V_C is placed midway between V_{CC} & V_E



a) For $\beta = \infty$; Calculate R_E & R_C ?

Since $\beta = \infty \Rightarrow I_B = 0 \Rightarrow V_B = 0$

$$\therefore V_E = -0.7V \Rightarrow R_E = \frac{V_E - (-V_{EE})}{I_E}$$

$$\therefore R_E = \frac{-0.7 - (-3)}{3} = 0.767 \text{ k}\Omega$$

$$V_C = \frac{V_E + V_{CC}}{2} = \frac{-0.7 + 3}{2} = 1.15V$$

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{3 - 1.15}{3} = 0.617 \text{ k}\Omega$$

b) $\beta_{min} = 90$; find R_B to limit the voltage drop across R_B to 0.1 the voltage drop across R_E .

$$I_B R_B \leq 0.1 I_E R_E \Rightarrow R_B \leq 0.1 (1 + \beta) R_E$$

$$R_B \leq 0.1 (1 + \beta_{min}) R_E \Rightarrow R_B \leq 0.1 * 91 * 0.767$$

$$\therefore \text{largest } R_B = 6.98 \text{ k}\Omega$$

c) using Appendix G (5% resistor values)

$$\therefore R_B = 6.8 \text{ k}\Omega \quad R_E = 750 \Omega \quad R_C = 620 \Omega$$

d) For the values in part "c" find I_C , V_B , V_E & V_C for $\beta = \infty$ & $\beta = 90$

i) $\beta = \infty \Rightarrow V_B = 0V, V_E = -0.7V$

$$I_C = I_E = \frac{-0.7 - (-3)}{0.75} = 3.07 \text{ mA}; V_C = 3 - I_C R_C = 1.1V$$

ii) $\beta = 90 \Rightarrow I_B = \frac{V_{EE} - V_{BE}}{R_B + (1 + \beta) R_E} = \frac{3 - 0.7}{6.8 + 91 * 0.75} = 30.6 \mu A$

$$\therefore I_C = \beta I_B = 2.76 \text{ mA}$$

$$V_B = -I_B R_B = -0.208V; V_E = -0.908V$$

$$V_C = V_{CC} - I_C R_C = 1.29V$$

5.107) $g_{m \text{ nom}} = 60 \text{ mA/V}$, $50 \leq \beta \leq 200$, I_c has $\pm 20\%$ vari.

extreme values for $r_{\pi} = ?$

$$g_m = \frac{I_c}{V_T} \Rightarrow 0.8 \times 60 \leq g_m \leq 1.2 \times 60 \text{ mA/V}$$

$$48 \leq g_m \leq 72 \text{ mA/V}$$

$$50 \leq \beta \leq 200$$

$$r_{\pi} = \frac{\beta}{g_m} \Rightarrow \frac{50}{72} \leq r_{\pi} \leq \frac{200}{48}$$

$$0.694 \leq r_{\pi} \leq 4.167 \text{ k}\Omega$$

$$r_{\pi \text{ max}} = 4.167 \text{ k}\Omega$$

$$r_{\pi \text{ min}} = 694 \Omega$$

5.116) $\beta = 200$, dc voltage at collector = ?


$R_{ib} = ?$, $R_{in} = ?$, $\frac{V_o}{V_{sig}} = ?$

D.C. operation:

$$V_c = I_c \times R_c = \alpha I_E R_c$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{200}{201} = 0.995$$
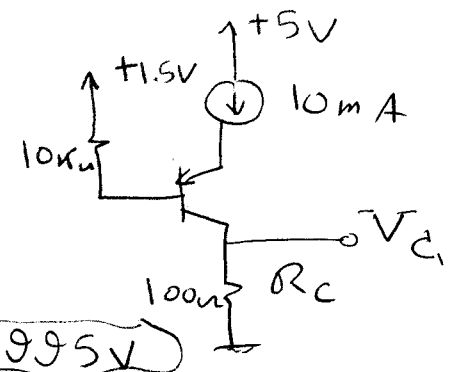
$$\therefore V_c = 0.995 \times 10 \times 0.1 = 0.995 \text{ V}$$



A.C. operation:

$$r_{\pi} = \frac{\beta}{g_m} = \frac{\beta V_T}{I_c}$$

$$= \frac{200 \times 0.025}{9.95} = 0.5 \text{ k}\Omega$$

$$R_{ib} = r_{\pi} = 0.5 \text{ k}\Omega$$

$$R_{in} = 10 \text{ k}\Omega \parallel r_{\pi} = 0.476 \text{ k}\Omega$$



$$\frac{V_o}{V_{sig}} = \frac{V_o}{i_L} \cdot \frac{i_L}{i_b} \cdot \frac{i_b}{V_{be}} \cdot \frac{V_{be}}{V_{sig}}$$

$$= R_c \times (-\beta) \times \frac{1}{r_{\pi}} \times \frac{R_{in}}{R_{in} + R_{sig}}$$

$$= -0.1 \times 200 \times \frac{1}{0.5} \times \frac{0.476}{0.476 + 1} = -12.9 \text{ V/V}$$

$$\text{for } V_o = \pm 0.4 \text{ V} \Rightarrow V_{sig} = \pm 31 \text{ mV}$$

$$V_b = \pm 10 \text{ mV}$$

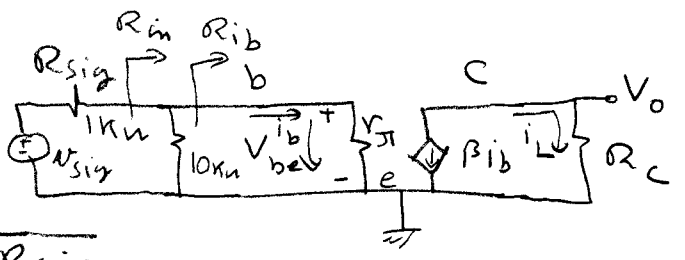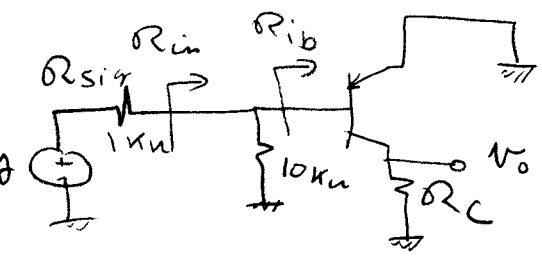

130) $V_{CC} = 9V$, $R_1 = 27k\Omega$, $R_2 = 15k\Omega$, $R_E = 1.2k\Omega$, $R_C = 2.2k\Omega$ (4)
 $\beta = 100$, $V_A = 100V$, $R_{sig} = 10k\Omega$, $R_L = 2k\Omega$.

$I_E = ?$; $R_{in} = ?$; $\frac{V_o}{V_{sig}} = ?$ & $\frac{I_o}{I_i} = ?$

* D.C Analysis:

All c's open; all a.c zero

$R_{th} = R_1 || R_2 = 9.64k\Omega$

$V_{th} = V_{CC} * \frac{R_2}{R_1 + R_2} = 3.21V$

applying KVL at E-B loop

$V_{th} = I_B R_{th} + V_{BE} + I_E R_E \Rightarrow I_E = \frac{V_{th} - V_{BE}}{R_E + \frac{R_{th}}{1 + \beta}}$

$\therefore I_E = \frac{3.21 - 0.7}{1.2 + \frac{9.64}{101}} = 1.94mA$

$I_C = \alpha I_E = 0.99 * 1.94 = 1.92mA$

check: $V_{CE} = V_{CC} - I_C R_C - I_E R_E = 2.45V > V_{CEsat}$

* small signal parameters:


$r_{\pi} = \frac{I_C}{V_T} = 40 I_C = 76.8 mA/V$; $r_{\pi} = \frac{\beta}{g_m} = 1.3k\Omega$

* A.C Analysis:

All c's short, all d.c zero

$R_{in} = \frac{V_{be}}{I_i} = R_{th} || r_{\pi}$
 $= 9.64k || 1.3k$
 $= 1.15k\Omega$

$R_L' = r_o || R_C || R_L$
 $= 1.03k\Omega$

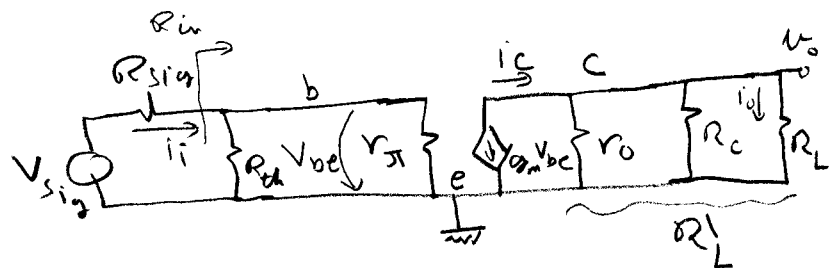

$\frac{V_o}{V_{sig}} = \frac{V_o}{I_c} \cdot \frac{I_c}{V_{be}} \cdot \frac{V_{be}}{V_{sig}} = R_L' * (-g_m) * \frac{R_{in}}{R_{in} + R_{sig}}$

$= 1.03 * (-76.8) * \frac{1.15}{1.15 + 10} = -8.16 V/V$


$\frac{I_o}{I_i} = \frac{V_o / R_L}{V_{sig} / (R_{sig} + R_{in})} = \frac{V_o}{V_{sig}} * \frac{R_{sig} + R_{in}}{R_L}$

$= -8.16 * \frac{10 + 1.15}{2} = -45.5 A/A$

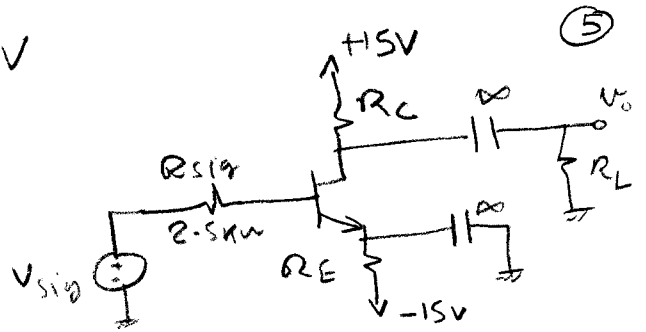134) $\beta = 100$, $I_E \approx 0.5 \text{ mA}$, $V_C = +5 \text{ V}$

$R_L = 10 \text{ k}\Omega$, $v_o = 200 \text{ mV}$

$R_C = ?$, $R_E = ?$, $A_v = \frac{v_o}{v_{sig}} = ?$



* D.C circuit:


All C's open, all a.c sources are zero
applying KVL at B-E loop

$$\therefore R_{sig} I_B + V_{BE} + R_E I_E - V_{EE} = 0$$

$$\therefore R_E = \frac{V_{EE} - V_{BE} - \frac{I_E}{\beta} R_{sig}}{I_E}$$

$$= \frac{15 - 0.7 - \frac{0.5}{101} * 2.5}{0.5} = 28.6 \text{ k}\Omega$$
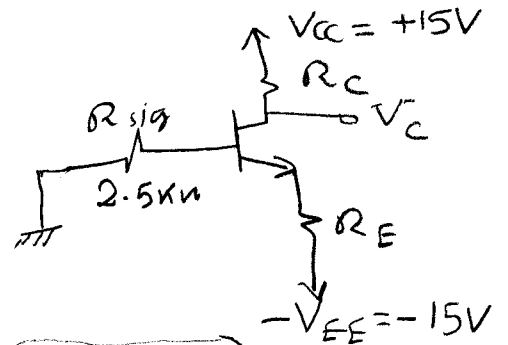
$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{V_{CC} - V_C}{\approx I_E} = \frac{15 - 5}{0.99 * 0.5} = 20.2 \text{ k}\Omega$$




* A.C Analysis:

All C's short, all d.c zero

$$g_m = \frac{I_C}{V_T} = 40 I_C = 40 * I_E$$

$$= 19.8 \text{ mA/V}$$
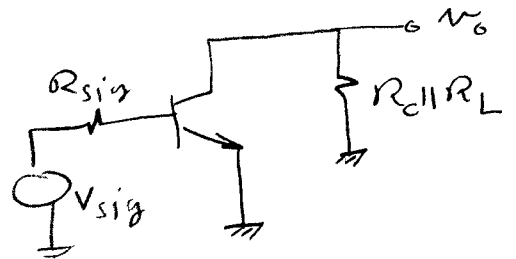
$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{19.8} = 5.05 \text{ k}\Omega$$




$$\frac{v_o}{v_{sig}} = \frac{v_o}{i_c} \cdot \frac{i_c}{v_{be}} - \frac{v_{be}}{v_{sig}}$$

$$= R_L' * (-g_m) * \frac{r_{\pi}}{r_{\pi} + R_{sig}}$$

$$= 6.47 * (-19.8) * \frac{5.05}{7.55}$$

$$= -85.72 \text{ V/V}$$

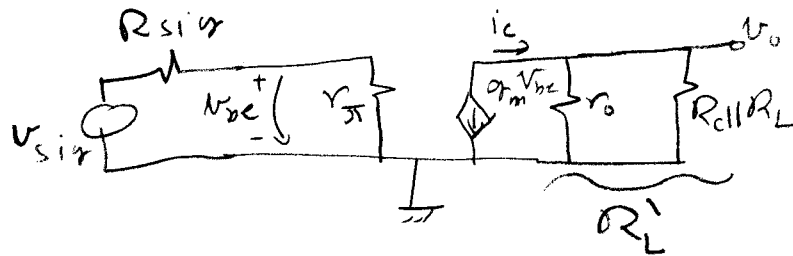

$$R_L' = R_C || R_L || r_o = 6.47 \text{ k}\Omega$$

5.143) $\beta_{min} = 40, \beta_{max} = 200$

(6)

for both values of β find: $I_E, V_E, V_B, R_{in}, \frac{V_o}{V_{sig}}$

* D.C Analysis:

All c's open, a.c sources zero

$$I_E = \frac{9 - V_{BE}}{R_E + \frac{R_B}{1+\beta}} = \frac{8.3}{1 + \frac{100}{1+\beta}} \text{ mA}$$

$$V_E = I_E R_E \text{ V}$$


$$V_B = V_E + V_{BE} = V_E + 0.7 \text{ V}$$

for $\beta = 40$

$$I_E = 2.41 \text{ mA} ; V_E = 2.41 \text{ V} ; V_B = 3.11 \text{ V}$$

for $\beta = 200$
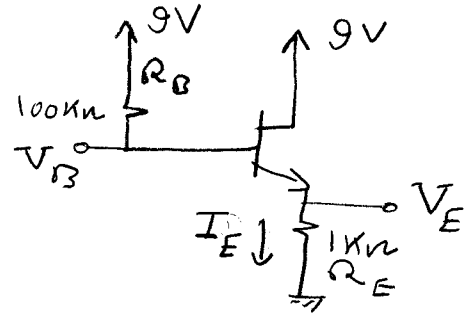
$$I_E = 5.54 \text{ mA} ; V_E = 5.54 \text{ V} ; V_B = 6.24 \text{ V}$$



* A.C Analysis:

All c's short; d.c sources zero

$$R_{in} = \frac{V_b}{i_i} = R_B || (1+\beta)(r_e + R'_L)$$

$$\frac{V_o}{V_{sig}} = \frac{V_o}{V_b} * \frac{V_b}{V_{sig}} = \frac{R'_L}{R'_L + r_e} * \frac{R_{in}}{R_{in} + R_{sig}}$$

for $\beta = \beta_{min} = 40$

$$r_e = \frac{V_T}{I_C} = \frac{25 \text{ mV}}{0.98 * I_E} = 10.6 \Omega$$

$$R_{in} = 17.3 \text{ k}\Omega$$

$$\frac{V_o}{V_{sig}} = 0.62 \text{ V/V}$$

for $\beta = \beta_{max} = 200$

$$r_e = \frac{V_T}{I_C} = \frac{25 \text{ mV}}{0.98 * 5.54 \text{ mA}} = 4.6 \Omega$$

$$R_{in} = 50.35 \text{ k}\Omega$$

$$\frac{V_o}{V_{sig}} = 0.83 \text{ V/V}$$

