



CSC 220: Computer Organization

Unit 10 Arithmetic-Logic Units

Prepared by:

Md Saiful Islam, PhD

Department of Computer Science
College of Computer and Information Sciences

Overview

- Arithmetic Unit Design
 - Primitive gates base implementation
 - MUX-based implementation
- Logic Unit Design
- Arithmetic-logic Unit Design
- Function Unit Design
 - Combinational Shifter


Chapter-8

M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design Fundamentals**, Global (5th) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124

Arithmetic Unit Design

Designing a simple 4-bit AU

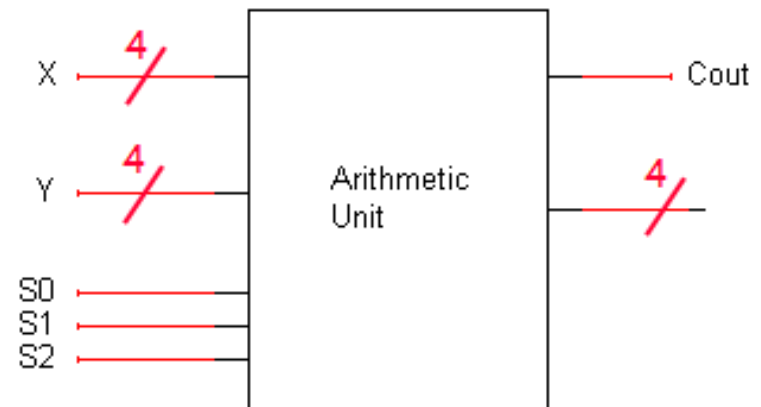
- 8 arithmetic operations
- Inputs:
 - X (4 bits)
 - Y (4 bits)
 - S (3 bits)
- Outputs:
 - G (4 bits)
 - C_{out} (final carry)
- The / and 4 on a line indicate that it's actually *four* lines



S_2	S_1	S_0	Operation
0	0	0	$G = X$
0	0	1	$G = X + 1$
0	1	0	$G = X + Y$
0	1	1	$G = X + Y + 1$
1	0	0	$G = X + Y'$
1	0	1	$G = X + Y' + 1$
1	1	0	$G = X - 1$
1	1	1	$G = X$

The four-bit parallel adder

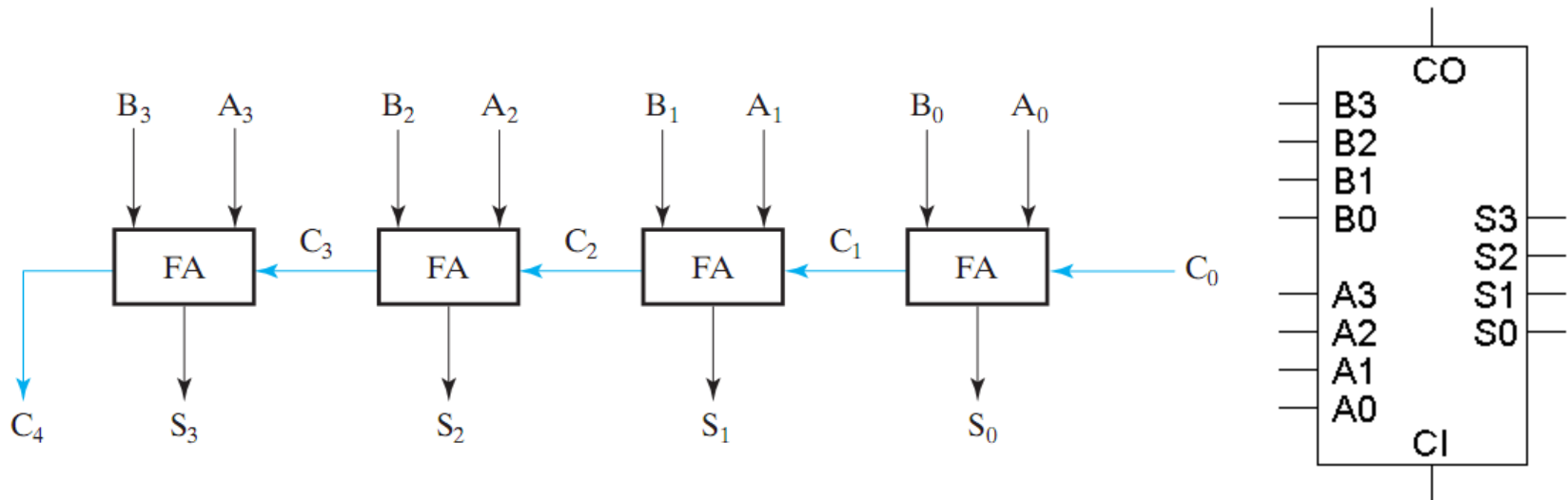
- The basic four-bit adder *always* computes $S = A + B + CI$.



- But by changing what goes into the adder inputs A , B and CI , we can change the adder output S .
- This is also what we did to build the combined adder-subtractor circuit.


The adder-subtractor

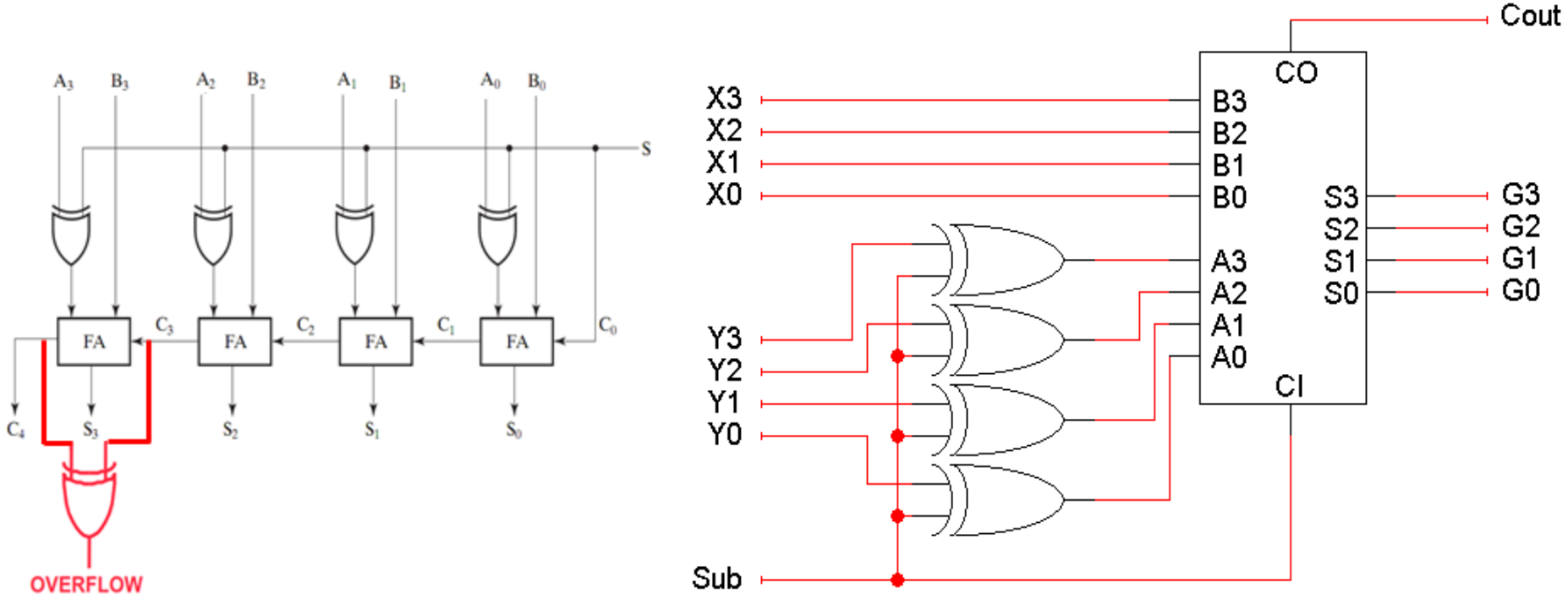- Here the signal **Sub** and some **XOR** gates alter the adder inputs.
 - When **Sub = 0**, the adder inputs **A, B, CI** are **Y, X, 0**, so the adder produces **G = X + Y + 0**, or just **X + Y**.
 - When **Sub = 1**, the adder inputs are **Y', X** and **1**, so the adder output is **G = X + Y' + 1**, or the two's complement operation **X - Y**.




The multi-talented adder

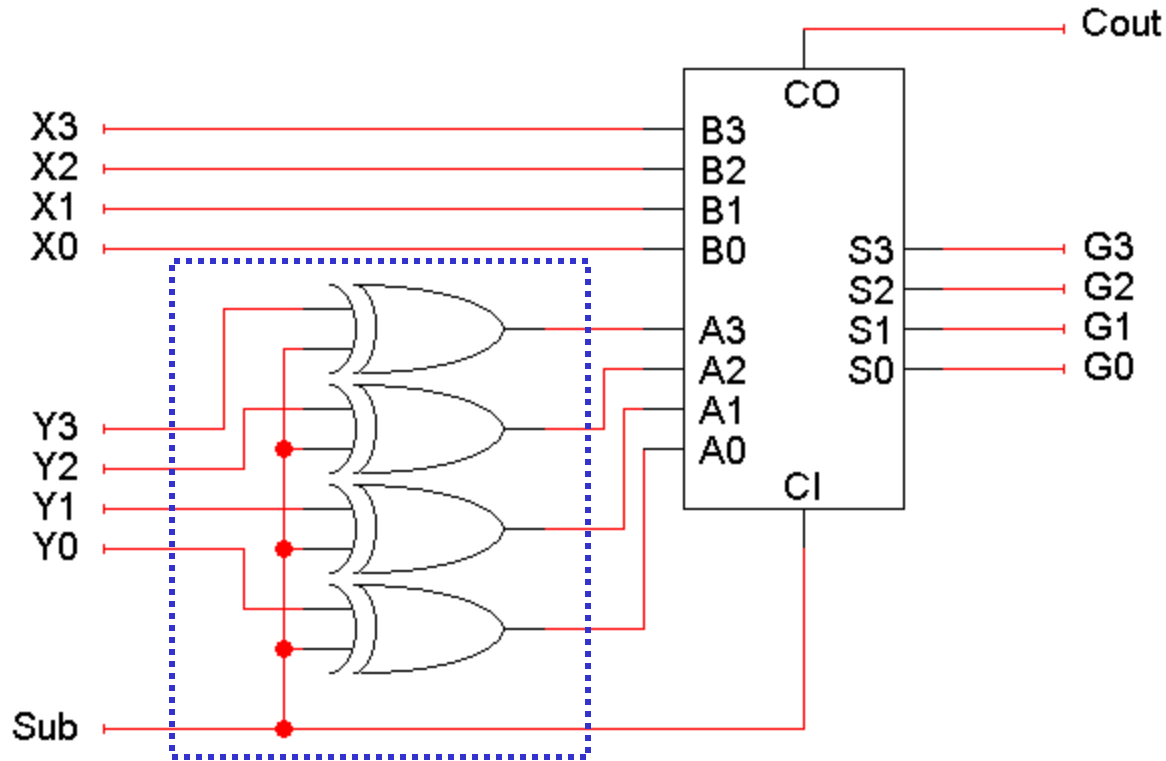- So we have one adder performing **two separate functions**.
- “Sub” acts like a **function select input** which determines whether the circuit performs addition or subtraction.
- “Sub” modifies the adder’s inputs **A and CI**.



Modifying the adder inputs

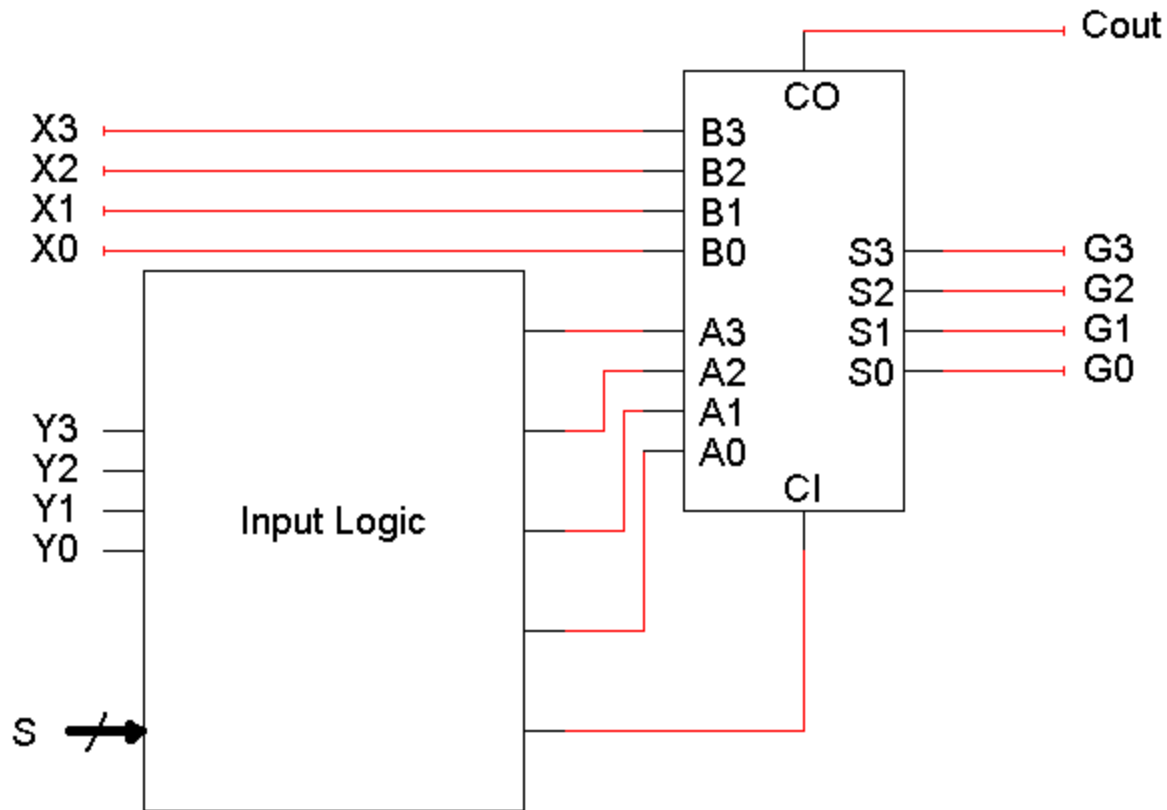- By following the same approach, we can use an adder to compute *other* functions as well.
- We just have to figure out which functions we want, and then put the right circuitry into the “Input Logic” box .



Some more possible functions

- We already saw how to set adder inputs A , B and CI to compute either $X + Y$ or $X - Y$.
- How can we produce the increment function $G = X + 1$?

One way: Set $A = 0000$, $B = X$, and $CI = 1$


- How about decrement: $G = X - 1$?

$A = 1111$ (-1), $B = X$, $CI = 0$

- How about transfer: $G = X$?
(This can be useful.)

$A = 0000$, $B = X$, $CI = 0$

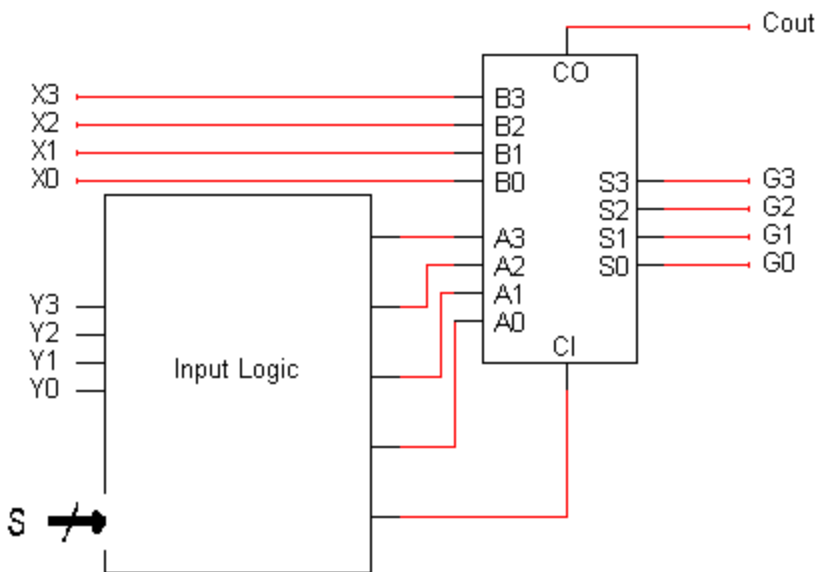This is almost the same as the increment function!



The role of CI

- The transfer and increment operations have the same A and B inputs, and differ only in the CI input.
- In general we can get **additional functions** (not all of them useful) by using both **CI = 0** and **CI = 1**.
- Another example:
 - Two's-complement subtraction is obtained by setting $A = Y'$, $B = X$, and $CI = 1$, so $G = X + Y' + 1$.
 - If we keep $A = Y'$ and $B = X$, but set CI to 0, we get $G = X + Y'$. This turns out to be a **ones' complement subtraction** operation.


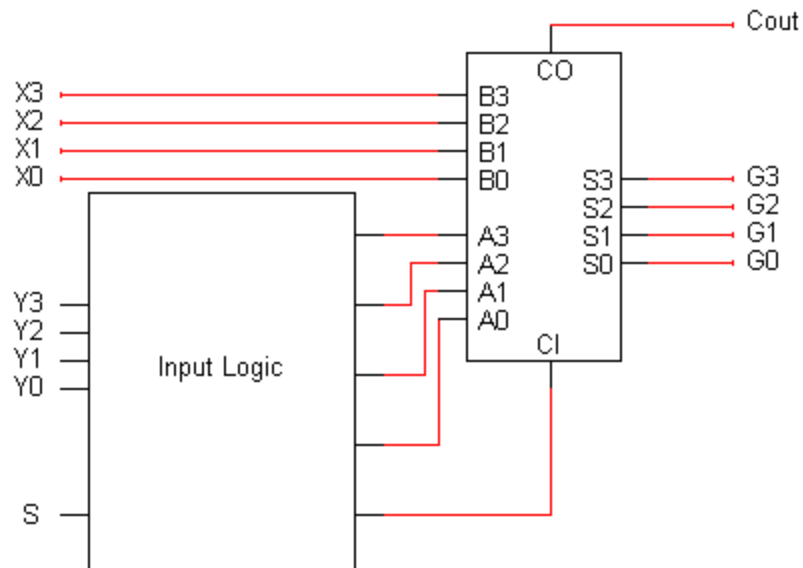


Table of arithmetic functions

- Here are some of the different possible arithmetic operations.
- We'll need some way to specify which function we're interested in, so we've *randomly assigned* a selection code to each operation.

S_2	S_1	S_0	Arithmetic operation	
0	0	0	X	(transfer)
0	0	1	$X + 1$	(increment)
0	1	0	$X + Y$	(add)
0	1	1	$X + Y + 1$	
1	0	0	$X + Y'$	(1C subtraction)
1	0	1	$X + Y' + 1$	(2C subtraction)
1	1	0	$X - 1$	(decrement)
1	1	1	X	(transfer)

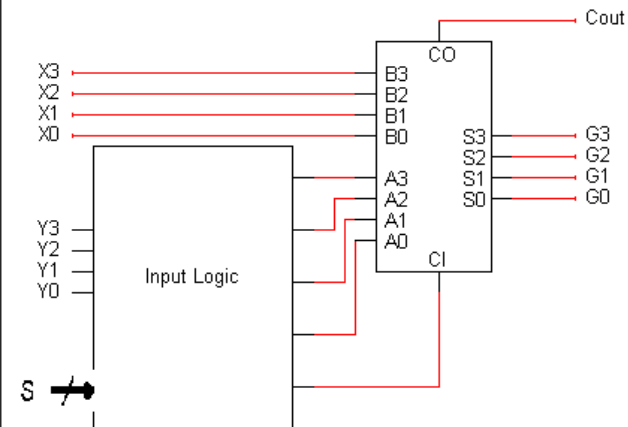


Mapping the table to an adder

- This second table shows what the adder's inputs should be for each of our eight desired arithmetic operations.

Selection code			Desired arithmetic operation $G(A + B + CI)$	Required adder inputs		
S_2	S_1	S_0		A	B	CI
0	0	0	X (transfer)	0000	X	0
0	0	1	$X + 1$ (increment)	0000	X	1
0	1	0	$X + Y$ (add)	Y	X	0
0	1	1	$X + Y + 1$	Y	X	1
1	0	0	$X + Y'$ (1C subtraction)	Y'	X	0
1	0	1	$X + Y' + 1$ (2C subtraction)	Y'	X	1
1	1	0	$X - 1$ (decrement)	1111	X	0
1	1	1	X (transfer)	1111	X	1

- Adder input CI is always the same as selection code bit S_0 .
- B is always set to X.
- A depends only on S_2 and S_1 .

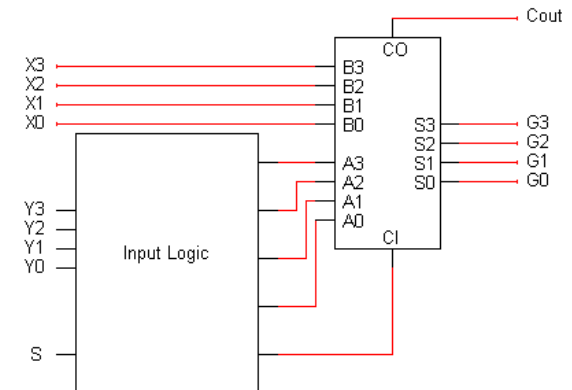
- These equations depend on both the desired operations and the assignment of selection codes.



Building the input logic

- All we need to do is **compute the adder input A**, given the arithmetic unit input Y and the function select code S (actually just S_2 and S_1).
- Here is an abbreviated truth table:

S_2	S_1	A
0	0	0000
0	1	Y
1	0	Y'
1	1	1111

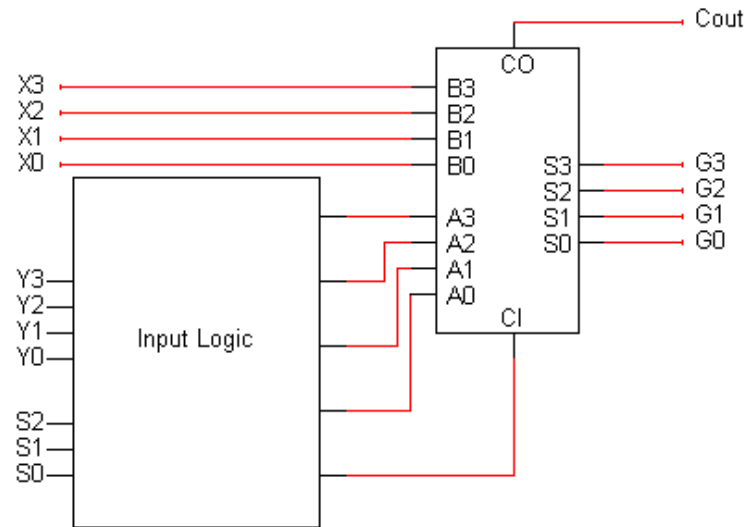


- We want to pick one of these four possible values for A, depending on S_2 and S_1 .

Primitive gate-based input logic

- We could build this **circuit using primitive gates**.
- If we want to use K-maps for simplification, then we should first **expand out the abbreviated truth table**.
 - The **Y** that appears in the output column (**A**) is actually an input.
 - We make that explicit in the table on the right.
- Remember **A and Y are each 4 bits long!**

S_2	S_1	A
0	0	0000
0	1	Y
1	0	Y'
1	1	1111

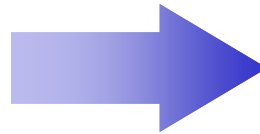

inputs			output
S_2	S_1	Y_i	A_i
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



Primitive gate implementation

- From the truth table, we can find an MSP:

		S_1		
	0	0	1	0
S_2	1	0	1	1
		Y_i		

$$A_i = S_2 Y_i' + S_1 Y_i$$

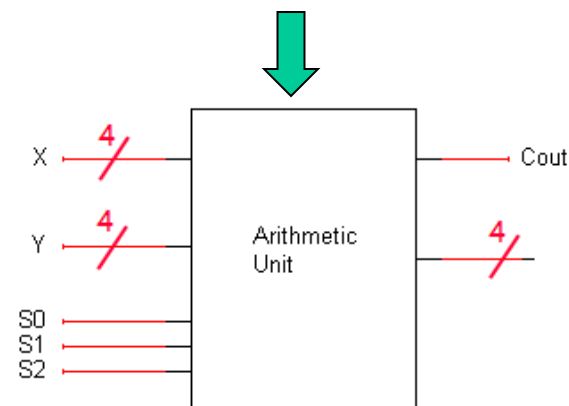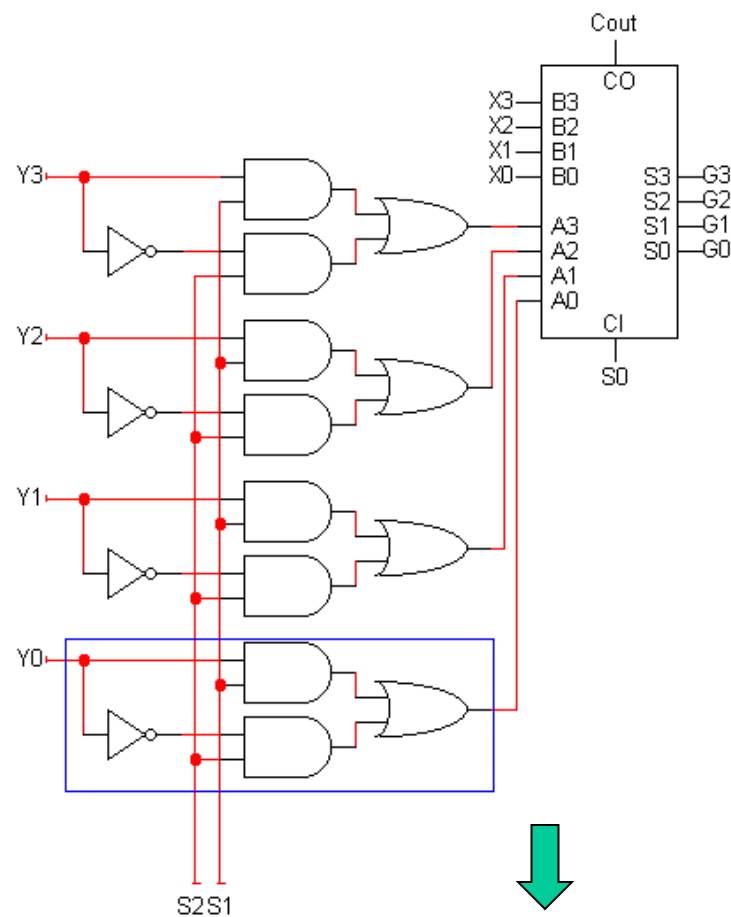- Again, we have to repeat this once for each bit Y_3 - Y_0 , connecting to the adder inputs A_3 - A_0 .
- This completes our arithmetic unit.




Multiplexer-based implementation

Alternative Implementation using 4 bit adder circuit and multiplexers


Selection code			Desired arithmetic operation $G(X + Y + CI)$	Required adder inputs		
S_2	S_1	S_0		Y	X	CI
0	0	0	A (transfer)	0000	A	0
0	0	1	A + 1 (increment)	0000	A	1
0	1	0	A + B (add)	B	A	0
0	1	1	A + B + 1	B	A	1
1	0	0	A + B' (1C subtraction)	B'	A	0
1	0	1	A + B' + 1 (2C subtraction)	B'	A	1
1	1	0	A - 1 (decrement)	1111	A	0
1	1	1	A (transfer)	1111	A	1



S_2	S_1	Y
0	0	0000
0	1	B
1	0	B'
1	1	1111

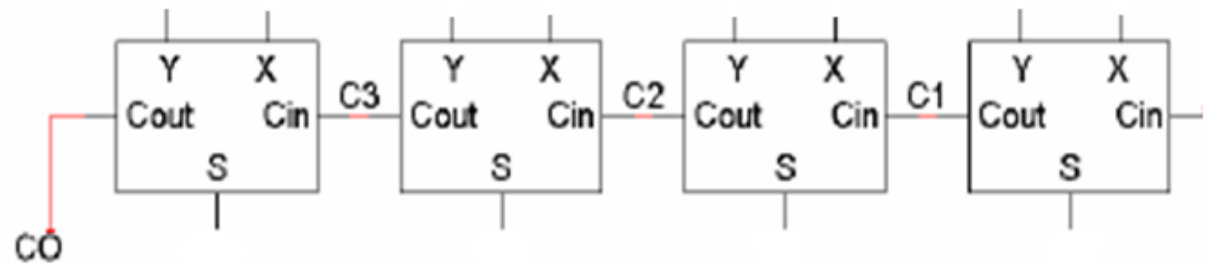


Multiplexer-based implementation

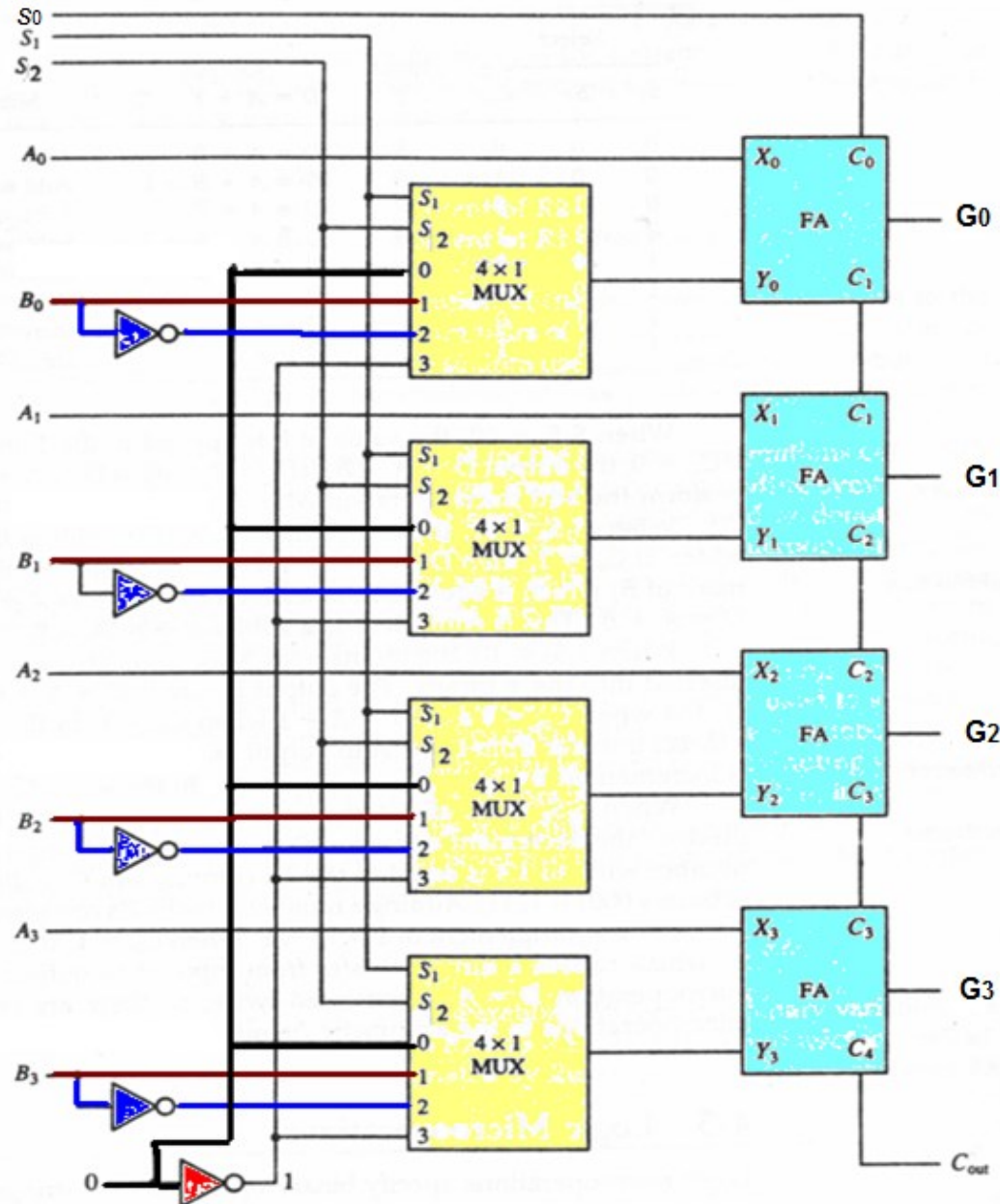

S ₂	S ₁	Y
0	0	0000
0	1	B
1	0	B'
1	1	1111

Logic Unit Design

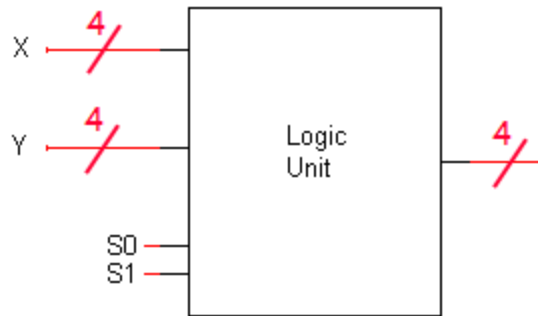- Most computers also support logical operations like AND, OR, XOR and NOT, but extended to multi-bit **words** instead of just single bits.



- **Inputs:**
 - X (4 bits)
 - Y (4 bits)
 - S (2 bits)
- **Outputs:**
 - G (4 bits)

- **Bitwise operations:** To apply a logical operation to two words X and Y, apply the operation on each pair of bits X_i and Y_i :

$$\begin{array}{r} \text{AND} \quad 1 \ 0 \ 1 \ 1 \\ \quad 1 \ 1 \ 1 \ 0 \\ \hline \quad 1 \ 0 \ 1 \ 0 \end{array}$$

$$\begin{array}{r} \text{OR} \quad 1 \ 0 \ 1 \ 1 \\ \quad 1 \ 1 \ 1 \ 0 \\ \hline \quad 1 \ 1 \ 1 \ 1 \end{array}$$

$$\begin{array}{r} \text{XOR} \quad 1 \ 0 \ 1 \ 1 \\ \quad 1 \ 1 \ 1 \ 0 \\ \hline \quad 0 \ 1 \ 0 \ 1 \end{array}$$


- Single operand logical operation: “complementing” all the bits in a number.

$$\begin{array}{r} \text{NOT} \quad 1 \ 0 \ 1 \ 1 \\ \hline \quad 0 \ 1 \ 0 \ 0 \end{array}$$

Defining a logic unit




- A logic unit supports different logical functions on two multi-bit inputs **X** and **Y**, producing an output **G**.
- This abbreviated table shows four possible functions and assigns a selection code **S** to each.

S_1	S_0	Output
0	0	$G_i = X_i Y_i$
0	1	$G_i = X_i + Y_i$
1	0	$G_i = X_i \oplus Y_i$
1	1	$G_i = X_i'$


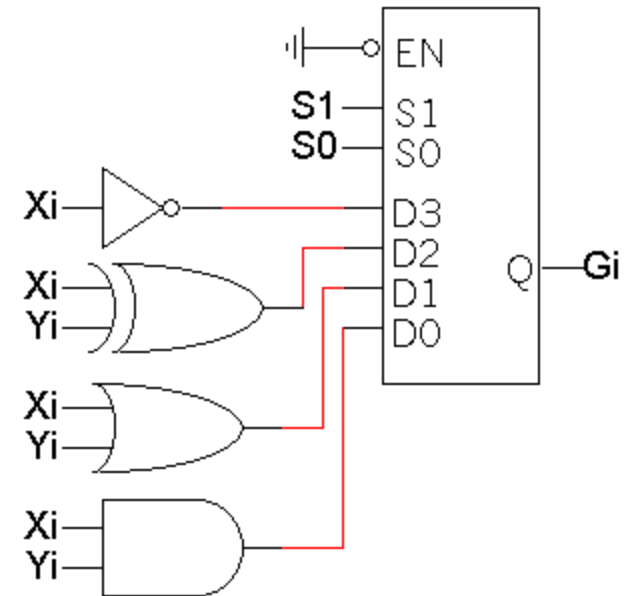


- We'll just use multiplexers and some primitive gates to implement this.
- Again, we need one multiplexer for *each bit* of **X** and **Y**.

Our simple logic unit

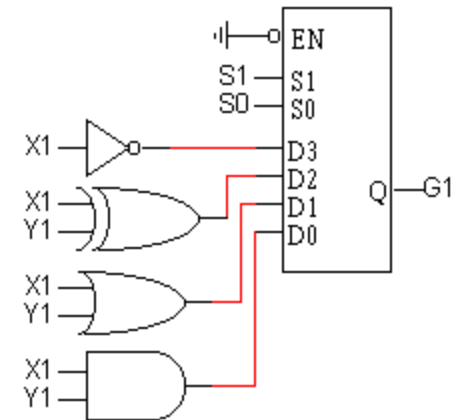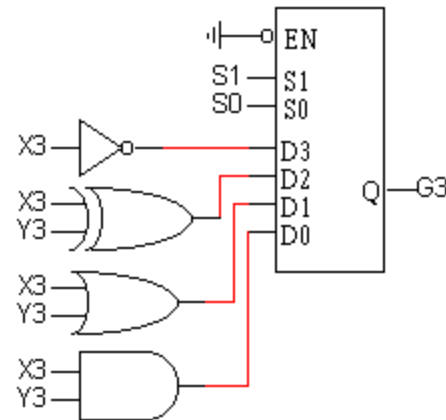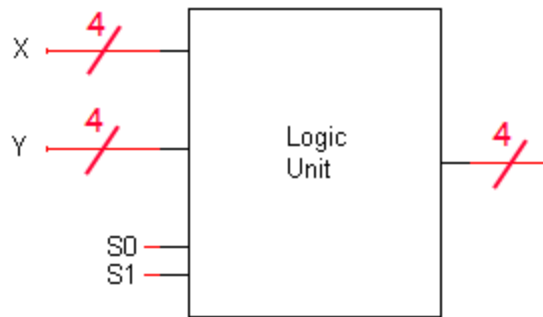


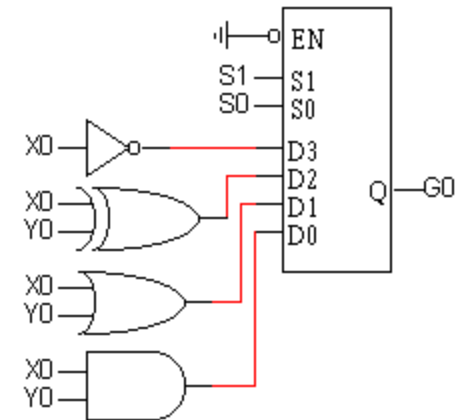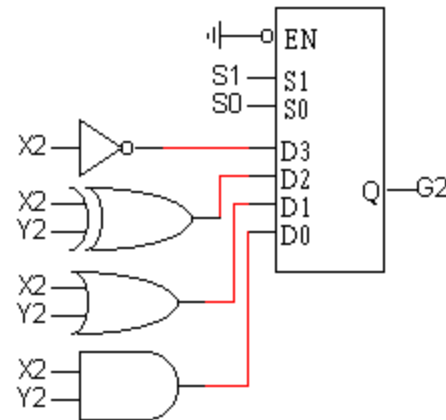- **Inputs:**
 - X (4 bits)
 - Y (4 bits)
 - S (2 bits)
- **Outputs:**
 - G (4 bits)



The arithmetic and logic units

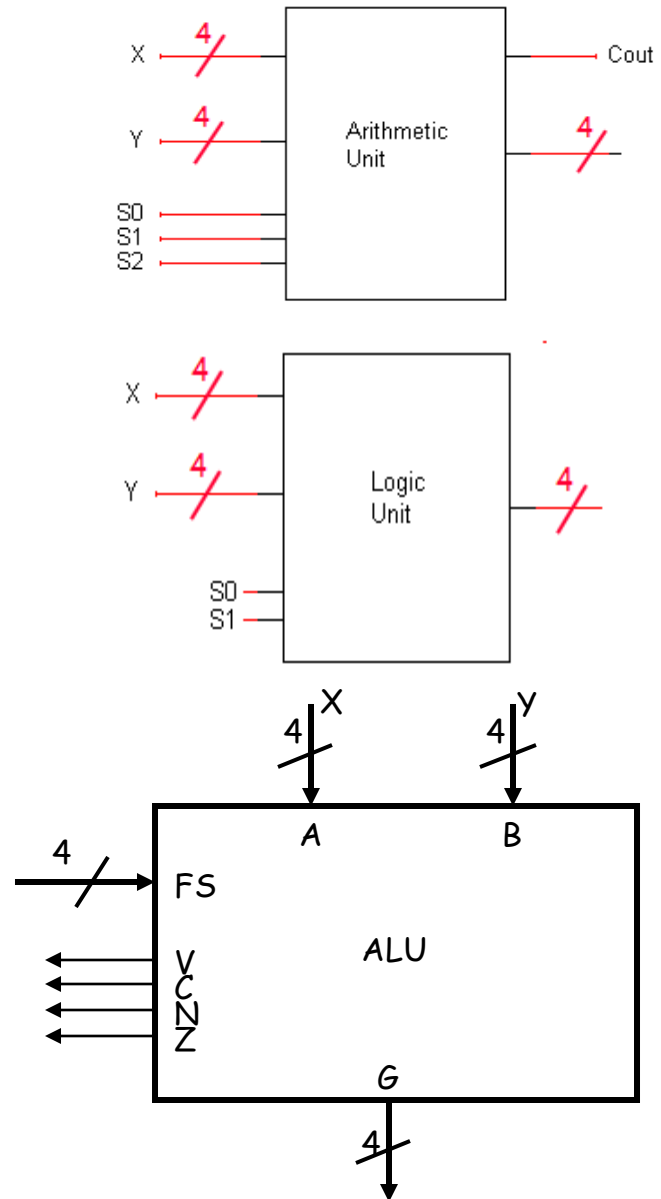- Now we have two pieces of the puzzle:
 - An arithmetic unit that can compute eight functions on 4-bit inputs.
 - A logic unit that can perform four functions on 4-bit inputs.
- We can combine these together into a single circuit, an arithmetic-logic unit (ALU).




Our ALU function table

- This table shows a sample function table for an ALU.
- All of the arithmetic operations have $S_3=0$, and all of the logical operations have $S_3=1$.
- These are the same functions we saw when we built our arithmetic and logic units a few minutes ago.
- Since our ALU only has 4 logical operations, we don't need S_2 . The operation done by the logic unit depends only on S_1 and S_0 .

S_3	S_2	S_1	S_0	Operation
0	0	0	0	$G = X$
0	0	0	1	$G = X + 1$
0	0	1	0	$G = X + Y$
0	0	1	1	$G = X + Y + 1$
0	1	0	0	$G = X + Y'$
0	1	0	1	$G = X + Y' + 1$
0	1	1	0	$G = X - 1$
0	1	1	1	$G = X$
1	x	0	0	$G = X \text{ and } Y$
1	x	0	1	$G = X \text{ or } Y$
1	x	1	0	$G = X \oplus Y$
1	x	1	1	$G = X'$

A complete ALU circuit

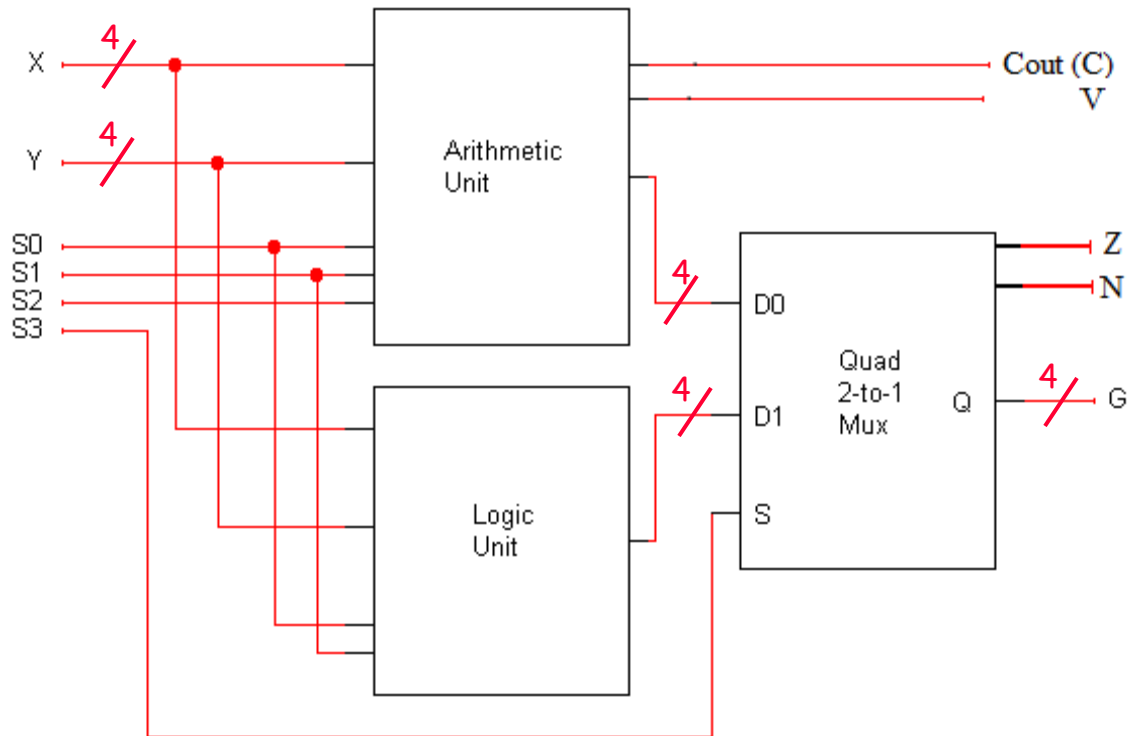

G is the final ALU output.

- When $S3 = 0$, the final output comes from the arithmetic unit.
- When $S3 = 1$, the output comes from the logic unit.


Status bits: Additional outputs

- C_{out} (C)
- Over-flow (V)
- Zero (Z)
- Negative (N)

- The arithmetic and logic units share the select inputs $S1$ and $S0$, but only the arithmetic unit uses $S2$.
- **Both** the arithmetic unit and the logic unit are “active” and produce outputs.
 - The mux determines whether the final result comes from the arithmetic or logic unit.
 - The output of the other one is effectively ignored.
- **Our hardware scheme may seem like wasted effort, but it’s not really.**
 - “Deactivating” one or the other wouldn’t save that much time.
 - We have to build hardware for both units anyway, so we might as well run them together.

The all-important ALU

- We'll use the following general block symbol for the ALU.
 - **A** and **B** are two n -bit numeric inputs.
 - **FS** is an m -bit function select code, which picks one of 2^m functions.
 - The n -bit result is called **G**.
 - Several **status bits** provide more information about the output **G**:
 - **V = 1** in case of signed overflow.
 - **C** is the carry out.
 - **N = 1** if the result is negative.
 - **Z = 1** if the result is 0.

 


S_3	S_2	S_1	S_0	Operation
0	0	0	0	$G = X$
0	0	0	1	$G = X + 1$
0	0	1	0	$G = X + Y$
0	0	1	1	$G = X + Y + 1$
0	1	0	0	$G = X + Y'$
0	1	0	1	$G = X + Y' + 1$
0	1	1	0	$G = X - 1$
0	1	1	1	$G = X$
1	x	0	0	$G = X \text{ and } Y$
1	x	0	1	$G = X \text{ or } Y$
1	x	1	0	$G = X \oplus Y$
1	x	1	1	$G = X'$

Combinational Shifter

- **Bidirectional shift register with parallel load**
 - Disadvantage: 3 clock pulses required
 - Ex: $R1 \leftarrow sr R2$
- **Combinational Shifter**
 - Transfer from a source to destination register
 - One clock cycle
- **Operations:**
 - Transfer
 - Shift Left,
 - Shift Right

4-Bit Basic Left/Right Shifter

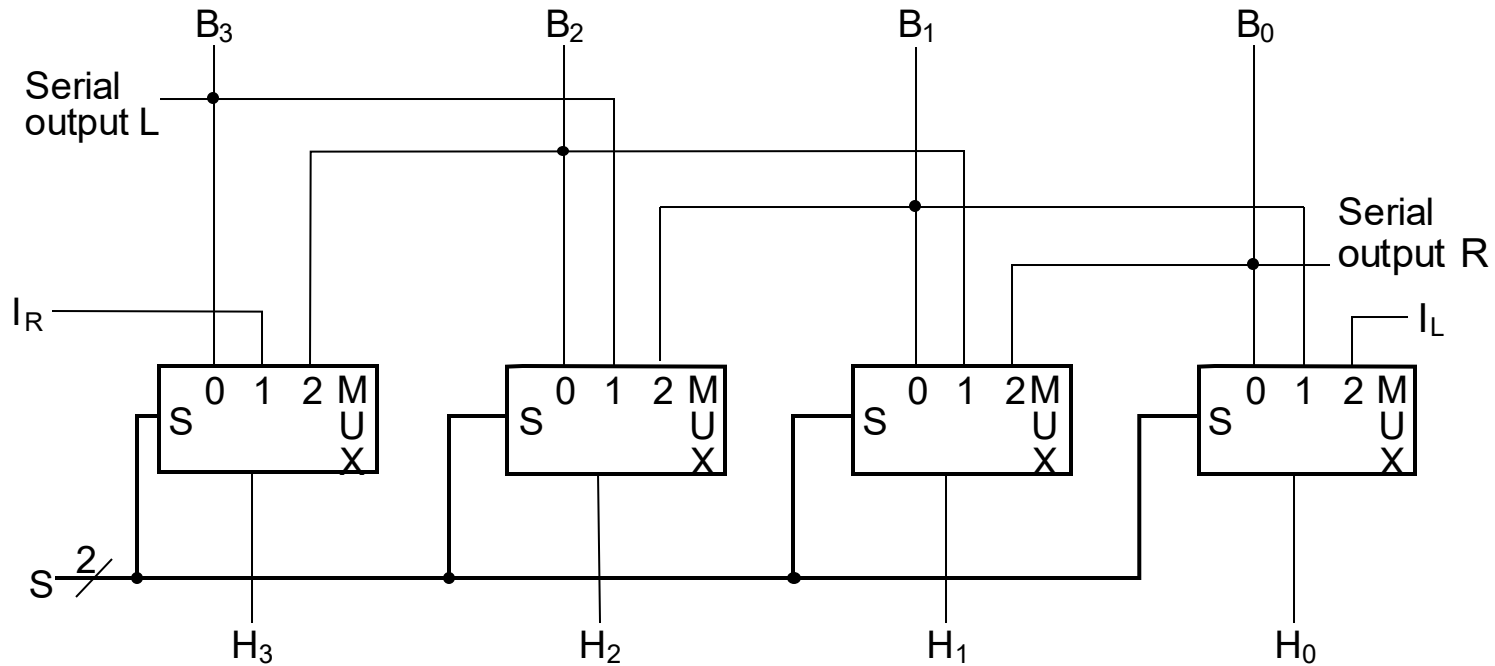



- **Serial Inputs:**
 - I_R for right shift
 - I_L for left shift
- Logic Shift (**zero**) will be used
- Many options depending on instruction set
- **Shift Functions:**
 - (S1, S0) = 00 Pass B unchanged
 - 01 Right shift
 - 10 Left shift
 - 11 Unused
- **Serial Outputs** (we will ignore)
 - R for right shift (Same as MSB input)
 - L for left shift (Same as LSB input)

Function Unit Design

Function Unit = ALU + Shifter

- The function select code **FS** is 4 bits long, but there are only **15 different functions** here.

FS	Operation
0000	$F = A$
0001	$F = A + 1$
0010	$F = A + B$
0011	$F = A + B + 1$
0100	$F = A + B'$
0101	$F = A + B' + 1$
0110	$F = A - 1$
0111	$F = A$
1000	$F = A \wedge B$ (AND)
1001	$F = A \vee B$ (OR)
1010	$F = A \oplus B$ (XOR)
1011	$F = A'$
1100	$F = B$
1101	$F = sr B$ (shift right)
1110	$F = sl B$ (shift left)

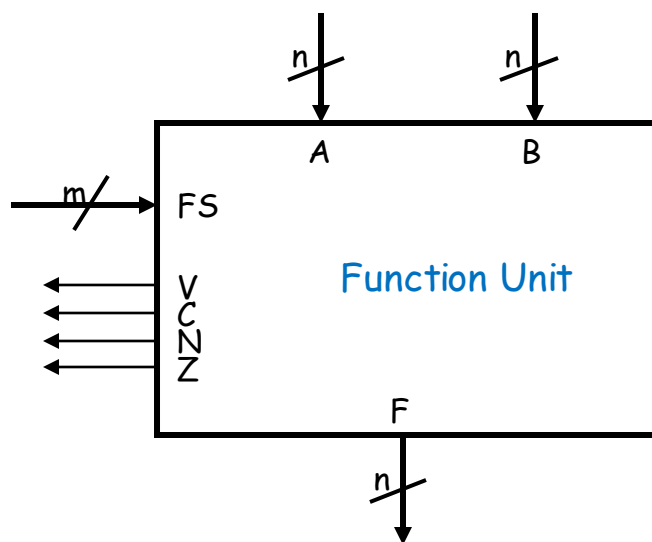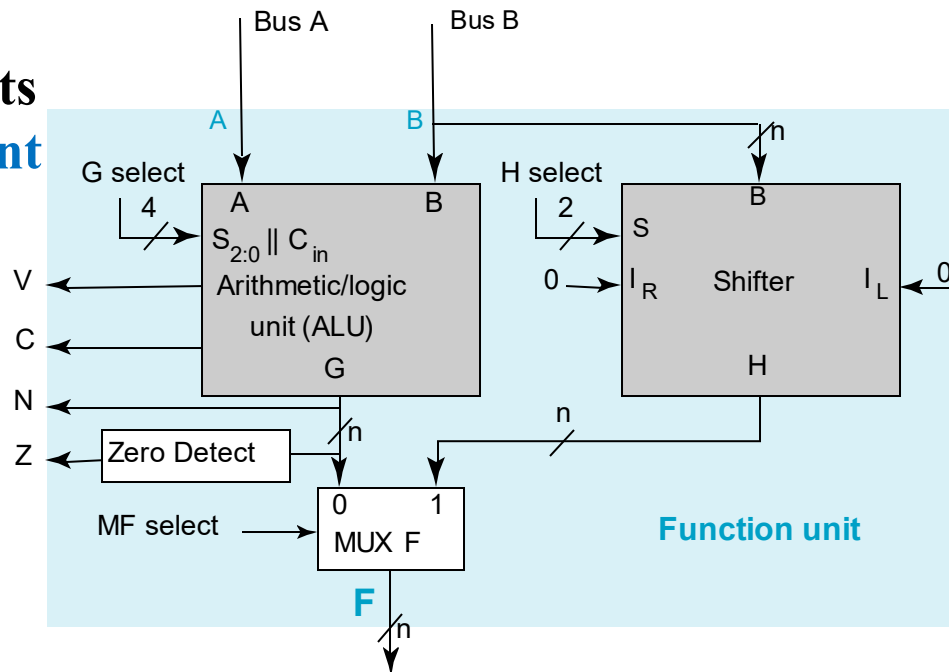

Definition of Function Unit Select (FS) Codes

FS(3:0)	MF Select	G Select(3:0)	H Select(3:0)	Micr operation
0000	0	0000	XX	$F \leftarrow A$
0001	0	0001	XX	$F \leftarrow A + 1$
0010	0	0010	XX	$F \leftarrow A + B$
0011	0	0011	XX	$F \leftarrow A + B + 1$
0100	0	0100	XX	$F \leftarrow A + \overline{B}$
0101	0	0101	XX	$F \leftarrow A + \overline{B} + 1$
0110	0	0110	XX	$F \leftarrow A - 1$
0111	0	0111	XX	$F \leftarrow A$
1000	0	1X00	XX	$F \leftarrow A \wedge B$
1001	0	1X01	XX	$F \leftarrow A \vee B$
1010	0	1X10	XX	$F \leftarrow A \oplus B$
1011	0	1X11	XX	$F \leftarrow \overline{A}$
1100	1	XXXX	00	$F \leftarrow B$
1101	1	XXXX	01	$F \leftarrow sr B$
1110	1	XXXX	10	$F \leftarrow sl B$

Boolean

Equations:

$$MF = F_3 F_2$$

$$G_i = F_i$$

$$H_i = F_i$$