



# CSC 220: Computer Organization

## Unit 2 Digital Circuit Design

Prepared by:  
Md Saiful Islam, PhD

**Department of Computer Science**  
**College of Computer and Information Sciences**

# Overview

- Digital Circuit Design
  - Logic Gates
  - Logic Functions
  - Standard Forms (SOP/POS)
- Universal Gates (NAND/NOR)
- XOR and XNOR Gates
- Logical Equivalence
- Logic Chips

## Chapter-2

M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design Fundamentals**, Global (5<sup>th</sup>) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124

---



# Digital Circuit

- ▶ **Digital Circuit** (hardware) manipulate binary information

---

- ▶ **Input-output:** one or more binary values
- ▶ Hardware consists of a few simple building blocks called *logic gates*
- ▶ **Logic gate:** a electronic device the operates on one or more input signals and produce an output.
  - ▶ **Basic Logic gates:** AND, OR, NOT, ...
  - ▶ **Additional gates:** NAND, NOR, XOR, XNOR...
- ▶ **Logic gates are built using transistors**
  - ▶ NOT gate can be implemented by a single transistor
  - ▶ AND-OR gate requires 3 transistors
- ▶ **Transistors are the fundamental devices**
  - ▶ Pentium consists of 3 million transistors
  - ▶ Compaq Alpha consists of 9 million transistors
  - ▶ Now we can build chips with more than 100 million transistors



# Logic Gates

## ▶ Basic gates


- ▶ **AND**
- ▶ **OR**
- ▶ **NOT**

## ▶ Functionality can be expressed by a truth table

- ▶ A truth table lists output for each possible input combination

 
## ▶ Precedence

- ▶ NOT > AND > OR
- ▶  $F = A \bar{B} + \bar{A} B$   
 $= (A (\bar{B})) + ((\bar{A}) B)$




AND gate

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

 

OR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

 

NOT gate

A	F
0	1
1	0

Logic symbol


Truth table



# Logic Gates ...

 
## ▶ Additional useful gates

- ▶ NAND
  - ▶ NOR
  - ▶ XOR
  - ▶ XNOR
- ▶ NAND = AND + NOT
  - ▶ NOR = OR + NOT
  - ▶ NAND and NOR gates require only 2 transistors
    - ▶ AND and OR need 3 transistors!
  - ▶ XOR implements exclusive-OR function
  - ▶ XNOR is complement of XOR



NAND gate

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 

NOR gate

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0



XOR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Logic symbol

Truth table

# Logic Functions

- ▶ A Boolean function consists of
  - ▶ Binary variables
  - ▶ Constants 0, 1
  - ▶ Logic operators: AND ( $\cdot$ ), OR ( $+$ ), NOT ( $-$ ), ...
- ▶ A function with  $N$  input variables
  - ▶ With  $N$  logical variables, we can define  $2^N$  combination of inputs
  - ▶ A **single-output function** relates the output (0/1) to inputs
  - ▶ Multiple-output Boolean function
    - ▶ More than one outputs
    - ▶ Each output (0/1) is related to same inputs

# Logic Functions ...

---

## ▶ Designing a Logic Circuit

- ▶ A truth table is used to represent a logic function
- ▶ Logical expressions can be obtained from truth table
- ▶ Logical expressions can be transfer to logic diagram of the circuit

## ▶ Example:

- ▶ Majority function
    - ▶ Output is one whenever majority of inputs is 1
    - ▶ We use 3-input majority function
- 



# Logic Functions ...

## Truth Table:


3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1
 
## ▶ Logical expression form

$$F = A'BC + AB'C + ABC' + ABC$$

$$= AB + BC + AC \text{ (after simplification)}$$





# Standard Forms

---

## Standard Forms Boolean Expressions

- Sum-of-Products (SOP)
    - Derived from the Truth table for a function by considering those rows for which  $F = 1$ .
    - The logical sum (OR) of product (AND) terms.
    - Realized using an AND-OR circuit.
  - Product-of-Sums (POS)
    - Derived from the Truth table for a function by considering those rows for which  $F = 0$ .
    - The logical product (AND) of sum (OR) terms.
    - Realized using an OR-AND circuit.
- 




## Sum of products expressions

- There are many equivalent ways to write a function, but some forms turn out to be more useful than others.
- A **sum of products** or **SOP** expression consists of:
  - One or more terms *summed* (OR'ed) together.
  - Each of those terms is a *product of literals*.

$$f(x, y, z) = y' + x'yz' + xz$$

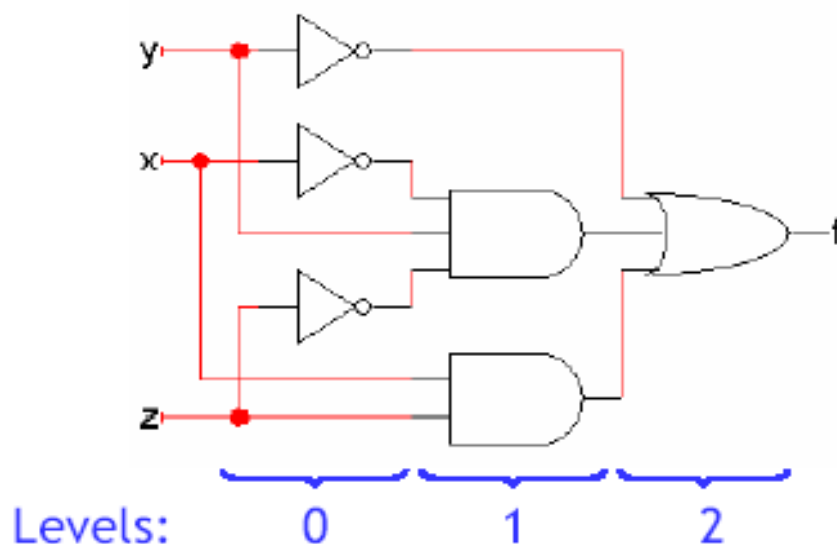- Sum of products expressions can be implemented with **two-level circuits**.



# Minterms

- A **minterm** is a special product of literals, in which each input variable appears exactly once.
- A function with  $n$  input variables has  $2^n$  possible minterms.
- For instance, a three-variable function  $f(x,y,z)$  has 8 possible minterms:

$$\begin{array}{cccc}
 x'y'z' & x'y'z & x'yz' & x'yz \\
 xy'z' & xy'z & xyz' & xyz
 \end{array}$$

- Each minterm is true for exactly one combination of inputs.

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

## Sum of minterms expressions

- A **sum of minterms** is a special kind of sum of products.
- Every function can be written as a *unique* sum of minterms expression.
- A truth table for a function can be rewritten as a sum of minterms just by finding the table rows where the function output is 1.

x	y	z	$C(x,y,z)$	$C'(x,y,z)$
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$\begin{aligned}C &= x'yz + xy'z + xyz' + xyz \\ &= m_3 + m_5 + m_6 + m_7 \\ &= \Sigma m(3,5,6,7)\end{aligned}$$

$$\begin{aligned}C' &= x'y'z' + x'y'z + x'yz' + xy'z' \\ &= m_0 + m_1 + m_2 + m_4 \\ &= \Sigma m(0,1,2,4)\end{aligned}$$

$C'$  contains all the minterms *not* in  $C$ , and vice versa.

# Sum-of-Products

- Any function F can be represented by a sum of minterms, where each minterm is ANDed with the corresponding value of the output for F.

- $F = \sum (m_i \cdot f_i)$

Denotes the logical  
sum operation

- where  $m_i$  is a minterm
    - and  $f_i$  is the corresponding functional output

- Only the minterms for which  $f_i = 1$  appear in the expression for function F.

- $F = \sum (m_i) = \sum m(i)$  ← shorthand notation

- Sum of minterms are a.k.a. Canonical Sum-of-Products
- Synthesis process
  - Determine the Canonical Sum-of-Products
  - Use Boolean Algebra (and K-maps) to find an optimal, functionally equivalent, expression.




## Product of sums expressions

- As you might expect, we can work with the duals of these ideas too.
- A **product of sums** or **POS** consists of:
  - One or more terms *multiplied* (AND'ed) together.
  - Each of those terms is a *sum of literals*.

$$g(x, y, z) = y'(x' + y + z')(x + z)$$

 - Products of sums can also be implemented with **two-level circuits**.



# Maxterms

- A **maxterm** is a *sum* of literals where each input variable appears once.
- A function with  $n$  input variables has  $2^n$  possible maxterms.
- For instance, a function with three variables  $x$ ,  $y$  and  $z$  has 8 possible maxterms:

$$\begin{array}{cccc}
 x + y + z & x + y + z' & x + y' + z & x + y' + z' \\
 x' + y + z & x' + y + z' & x' + y' + z & x' + y' + z'
 \end{array}$$

- Each maxterm is *false* for exactly one combination of inputs.

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

## Product of maxterms expressions

- Every function can also be written as a unique **product of maxterms**.
- A truth table for a function can be rewritten as a product of maxterms just by finding the table rows where the function output is 0.

x	y	z	$C(x,y,z)$	$C'(x,y,z)$
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$\begin{aligned}
 C &= (x + y + z)(x + y + z') \\
 &\quad (x + y' + z)(x' + y + z) \\
 &= M_0 M_1 M_2 M_4 \\
 &= \prod M(0,1,2,4) \quad \text{When the o/p is Zero} \\
 &= \sum m(3,5,6,7) \quad \text{When the o/p is 1}
 \end{aligned}$$

$$\begin{aligned}
 C' &= (x + y' + z')(x' + y + z') \\
 &\quad (x' + y' + z)(x' + y' + z') \\
 &= M_3 M_5 M_6 M_7 \\
 &= \prod M(3,5,6,7)
 \end{aligned}$$

$C'$  contains all the maxterms *not* in  $C$ , and vice versa.



# Product-of-Sums

- Any function  $F$  can be represented by a product of Maxterms, where each Maxterm is ANDed with the *complement* of the corresponding value of the output for  $F$ .

- $F = \prod (M_i \cdot f'_i)$

- where  $M_i$  is a Maxterm

Denotes the logical product operation

- and  $f'_i$  is the complement of the corresponding functional output

- Only the Maxterms for which  $f_i = 0$  appear in the expression for function  $F$ .

- $F = \prod (M_i) = \prod M(i)$  ← shorthand notation

- The Canonical Product-of-Sums for function  $F$  is the Product-of-Sums expression in which each sum term is a Maxterm.

- Synthesis process

- Determine the Canonical Product-of-Sums


- Use Boolean Algebra (and K-maps) to find an optimal, functionally equivalent, expression.




# Universal Gates

- ▶ NAND and NOR gates are called universal gates
- 


- ▶ Proving NAND gate is universal

 

AND gate

 

NOT gate

 


OR gate




# Universal Gates...


- ▶ Proving NOR gate is universal

 

OR gate

 

NOT gate

 


AND gate




# XOR and XNOR Gates

## The XOR Gate

$A$   
 $B$

 

$A$   
 $B$

 

The **XOR** gate produces a HIGH output only when the inputs are at opposite logic levels. The truth table is

Inputs		Output
$A$	$B$	$X$
0	0	0
0	1	1
1	0	1
1	1	0


The **XOR** operation is written as  $X = \bar{A}B + A\bar{B}$ .

Alternatively, it can be written with a circled plus sign between the variables as  $X = A \oplus B$ .


# XOR and XNOR Gates ...

## The XOR Gate


*A*  
*B*

 

*A*  
*B*

 


Example waveforms:

 

Notice that the XOR gate will produce a HIGH only when exactly one input is HIGH.

# XOR and XNOR Gates ...

The **XNOR** Gate


 


The **XNOR** gate produces a HIGH output only when the inputs are at the same logic level. The truth table is


Inputs		Output
$A$	$B$	$X$
0	0	1
0	1	0
1	0	0
1	1	1

The **XNOR** operation can be shown as  $X = AB + \bar{A}\bar{B}$ .

# The XNOR Gate

  

Example waveforms:

 


Notice that the XNOR gate will produce a HIGH when both inputs are the same. This makes it useful for comparison functions.


# Logical Equivalence

- ▶ When two circuits implement same logic function

 
**Example:** All three circuits implement  $F = A B$  function



(a)

 

(b)

 


(c)


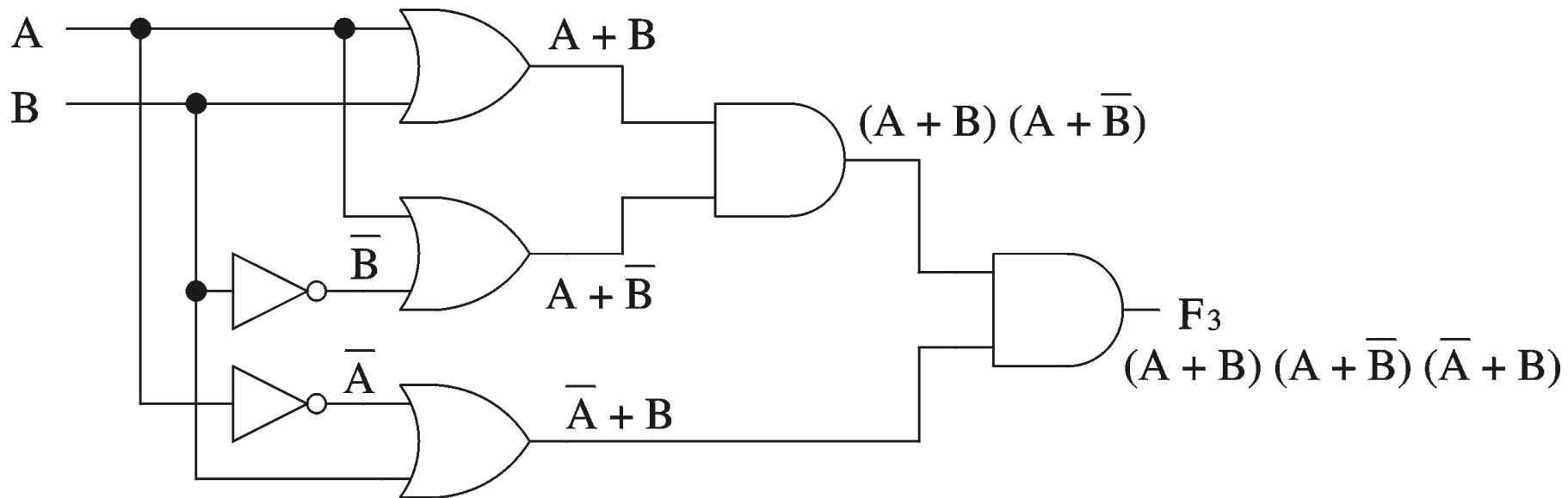
# Logical Equivalence ...

- ▶ **Proving logical equivalence:**
- ▶ **Derivation of logical expression from a circuit**
  - ▶ Trace from the input to output
  - ▶ Write down intermediate logical expressions along the path



# Logical Equivalence ...


- ▶ Build the truth table relating inputs to the output for each circuit
- ▶ If each function give the same output, they are logically equivalent

A	B	$F1 = A B$	$F3 = (A + B) (\overline{A} + B) (A + \overline{B})$
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

## ▶ Exercise:

- ▶ Show that  $X \oplus Y$  is logically equivalent to  $X'Y + XY'$


# Logic Chips

 

7400

7408


7432

 

7404

7486

7430

 

7420

7430

## ▶ Integration levels

- ▶ SSI (small scale integration)
  - ▶ Introduced in late 1960s
  - ▶ 1-10 gates (previous examples)
- ▶ MSI (medium scale integration)
  - ▶ Introduced in late 1960s
  - ▶ 10-100 gates
- ▶ LSI (large scale integration)
  - ▶ Introduced in early 1970s
  - ▶ 100-10,000 gates
- ▶ VLSI (very large scale integration)
  - ▶ Introduced in late 1970s
  - ▶ More than 10,000 gates

