



CSC 220: Computer Organization

Unit 3

Simplification of Logic Function

Prepared by:

Md Saiful Islam, PhD

Department of Computer Science

College of Computer and Information Sciences

Overview

- Minimal Sum of Product (MSP)
 - K-Map
 - Simplification Procedure
- Don't Care Condition
- Four Variable K-Map

Chapter-2


M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design Fundamentals**, Global (5th) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124

Minimal sums of products

- When used properly, Karnaugh maps can reduce expressions to a **minimal sum of products**, or **MSP**, form.
 - There are a minimal number of product terms.
 - Each product has a minimal number of literals.
- For example, both expressions below (from the last lecture) are sums of products, but only the right one is a *minimal* sum of products.

$$x'y' + yz + x'y = x' + yz$$

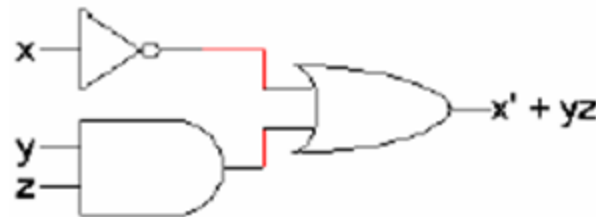- Minimal sum of products expressions lead to minimal two-level circuits.



- A minimal sum of products might not be “minimal” by other definitions! For example, the MSP $xy + xz$ can be reduced to $x(y + z)$, which has fewer literals and operators—but it is no longer a sum of products.

Simplification with K-Map

- Kmaps provide an easy graphical method of simplifying Boolean expressions.
- A Kmap is a matrix consisting of the outputs of the minterms of a Boolean function.
- In this section, we will discussed 2- 3- and 4-input Kmaps.
- This method can be extended to any number of inputs through the use of multiple tables.

Organizing the minterms

- Recall that an n -variable function has up to 2^n minterms, one for each possible input combination.
- A function with inputs x , y and z includes up to eight minterms, as shown below.

x	y	z	Minterm
0	0	0	$x'y'z'$ (m_0)
0	0	1	$x'y'z$ (m_1)
0	1	0	$x'yz'$ (m_2)
0	1	1	$x'yz$ (m_3)
1	0	0	$xy'z'$ (m_4)
1	0	1	$xy'z$ (m_5)
1	1	0	xyz' (m_6)
1	1	1	xyz (m_7)

- We'll rearrange these minterms into a **Karnaugh map**, or **K-map**.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$xy'z'$	$xy'z$	xyz	xyz'

- You can show either the actual minterms or just the minterm numbers.
- Notice the minterms are almost, but not quite, in numeric order.

Reducing two minterms

- In this layout, any two adjacent minterms contain at least one common literal. This is useful in simplifying the sum of those two minterms.
- For instance, the minterms $x'y'z'$ and $x'y'z$ both contain x' and y' , and we can use Boolean algebra to show that their sum is $x'y'$.

$x'y'z'$	$x'y'z$	$x'y z$	$x'y z'$
$x y'z'$	$x y'z$	$x y z$	$x y z'$

$$\begin{aligned}
 x'y'z' + x'y'z &= x'y'(z' + z) \\
 &= x'y' \cdot 1 \\
 &= x'y'
 \end{aligned}$$

- You can also “wrap around” the sides of the K-map—minterms in the first and fourth columns are considered to be next to each other.

$x'y'z'$	$x'y'z$	$x'y z$	$x'y z'$
$x y'z'$	$x y'z$	$x y z$	$x y z'$

$$\begin{aligned}
 x y'z' + x y z' &= xz'(y' + y) \\
 &= xz' \cdot 1 \\
 &= xz'
 \end{aligned}$$

Reducing four minterms

- Similarly, rectangular groups of four minterms can be reduced as well. You can think of them as two adjacent groups of two minterms each.

$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$xy'z'$	$xy'z$	xyz	xyz'

- These four green minterms all have the literal y in common. Guess what happens when you simplify their sum?

$$\begin{aligned}
 x'yz + x'yz' + xyz + xyz' &= y(x'z + x'z' + xz + xz') \\
 &= y(x'(z + z') + x(z + z')) \\
 &= y(x' + x) \\
 &= y
 \end{aligned}$$

Reducible groups

- Only rectangular groups of minterms, where the number of minterms is a power of two, can be reduced to a single product term.
 - Non-rectangular groups may not even contain a common literal.

$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$xy'z'$	$xy'z$	xyz	xyz'

- Groups of other sizes cannot be simplified to just one product term.

$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$xy'z'$	$xy'z$	xyz	xyz'

The pattern behind the K-map

- The literal x occurs in the bottom four minterms, while the literal x' appears in the top four minterms.
- The literal y shows up on the right side, and y' appears on the left.
- The literal z occurs in the middle four squares, while z' occurs in the first and fourth columns.

x'	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
x	$xy'z'$	$xy'z$	xyz	xyz'

	y'		y
$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$xy'z'$	$xy'z$	xyz	xyz'

$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$xy'z'$	$xy'z$	xyz	xyz'
z'		z	z'


Filling in the K-map

- Since our labels help us find the correct position of minterms in a K-map, writing the minterms themselves is redundant and repetitive.
- We usually just put a 1 in the K-map squares that correspond to the function minterms, and 0 in the other squares.
- For example, you can quickly fill in a K-map from a truth table by copying the function outputs to the proper squares of the map.

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0

1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Example 1

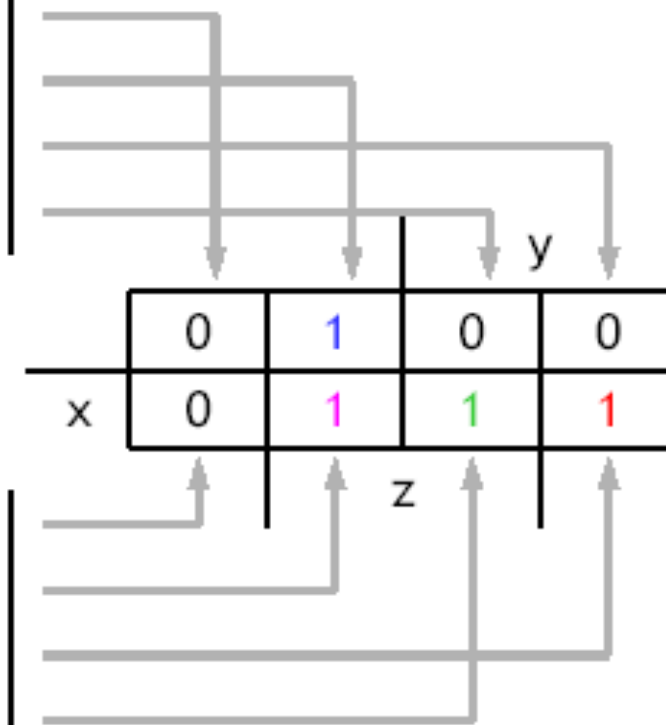

$$f(x,y,z) = x'y'z + xy'z + xyz' + xyz$$

Example 2

Four steps in K-map simplifications

1. Start with a sum of minterms or truth table.

$$x'y'z' + x'y'z + xyz + xyz'$$

2. Plot the minterms on a Karnaugh map.

		y	
		1	1
x		0	0
		z	
		1	1

3. Find rectangular groups of minterms whose sizes are powers of two. Be sure to include all the minterms in at least one group!

		y	
		1	1
x		0	0
		z	
		1	1

4. Reduce each group to one product term.

$$x'y' + xy$$

The tricky part

- The tricky part is finding the best groups of minterms.
 - Each group represents one product term, so *making as few groups as possible* will result in a minimal number of products.
 - *Making each group as large as possible* corresponds to combining more minterms, and will result in a minimal number of literals.
- Which groups would you form in the following example map?

Example 3

			y	
	0	0	1	1
x	1	1	1	1
			z	

Minimizing the number of groups

- The following two possibilities include too many groups, and would result in more product terms than necessary.

			y	
	0	0	1	1
x	1	1	1	1
	z			

			y	
	0	0	1	1
x	1	1	1	1
	z			

- We can put all six minterms into just two groups. Two ways of doing this are shown below.

			y	
	0	0	1	1
x	1	1	1	1
	z			

			y	
	0	0	1	1
x	1	1	1	1
	z			

Solutions for practice K-map 1

- Here is the K-map for $f(x,y,z) = m_1 + m_3 + m_5 + m_6$, with all groups shown.
 - The magenta and green groups overlap, which makes each of them as large as possible.
 - Minterm m_6 is in a group all by its lonesome.

		y			
		0	1	1	0
x	0	0	1	0	1
			z		

Example 4

MSP

Minimal Sum of Product

- The final MSP here is $x'z + y'z + xyz'$.

Don't care conditions

- There are times when we don't care what a function outputs—some input combinations might never occur, or some outputs may have no effect.
- We can express these situations with **don't care conditions**, denoted with **X** in truth table rows.
- An expression for this function has two parts.
 - One part includes the function's minterms.
 - Another describes the don't care conditions.

$$f(x,y,z) = m_3, \quad d(x,y,z) = m_2 + m_4 + m_5$$

- Circuits *always* output 0 or 1; there is no value called "X". Instead, the Xs just indicate cases where both 0 or 1 would be acceptable outputs.

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	0
0	1	0	X
0	1	1	1
1	0	0	X
1	0	1	X
1	1	0	0
1	1	1	0

Example 5

Don't care simplifications

- In a K-map we can treat each don't care as 0 or 1. Different selections can produce different results.

			y	
	0	0	1	X
x	X	X	0	0
			z	

Example 5

- In this example we can use the don't care conditions to our advantage.
 - It's best to treat the bottom two Xs as 0s. If either of them were 1, we'd end up with an extra, unnecessary term.
 - On the other hand, interpreting the top X as 1 results in a larger group containing m_3 .
- The resulting MSP is $x'y$.

Four-variable Karnaugh maps

- We can do four-variable Karnaugh maps too!
- A four-variable function $f(w,x,y,z)$ has sixteen possible minterms. They can be arranged so that adjacent minterms have common literals.
 - You can wrap around the sides *and* the top and bottom.
 - Again the minterms are almost, but not quite, in numeric order.

		y		
	w'x'y'z'	w'x'y'z	w'x'yz	w'x'yz'
	w'xy'z'	w'xy'z	w'xyz	w'xyz'
w	wxy'z'	wxy'z	wxyz	wxyz'
	wx'y'z'	wx'y'z	wx'yz	wx'yz'
		z		
				x

		y		
wx	m ₀	m ₁	m ₃	m ₂
	m ₄	m ₅	m ₇	m ₆
w	m ₁₂	m ₁₃	m ₁₅	m ₁₄
	m ₈	m ₉	m ₁₁	m ₁₀
		z		
				x

Four-variable example

- Let's say we want to simplify $m_0 + m_2 + m_5 + m_8 + m_{10} + m_{13}$

		y		
	m_0	m_1	m_3	m_2
	m_4	m_5	m_7	m_6
w	m_{12}	m_{13}	m_{15}	m_{14}
	m_8	m_9	m_{11}	m_{10}
		z		

		y		
	1	0	0	1
	0	1	0	0
w	0	1	0	0
	1	0	0	1
		z		

Example 6

- The following groups result in the minimal sum of products $x'z' + xy'z$.

		y		
	1	0	0	1
	0	1	0	0
w	0	1	0	0
	1	0	0	1
		z		

Prime implicants


- Finding the best groups is even more difficult in larger K-maps.
- One good approach to deriving an MSP is to first find the largest possible groupings of minterms.
 - These groups correspond to **prime implicant** terms.
 - The final MSP will contain a subset of the prime implicants.
- Here is an example K-map with prime implicants marked.

		y			
		1	1	0	0
		1	1	0	0
w		0	1	1	0
		0	0	1	1
			z		
				x	

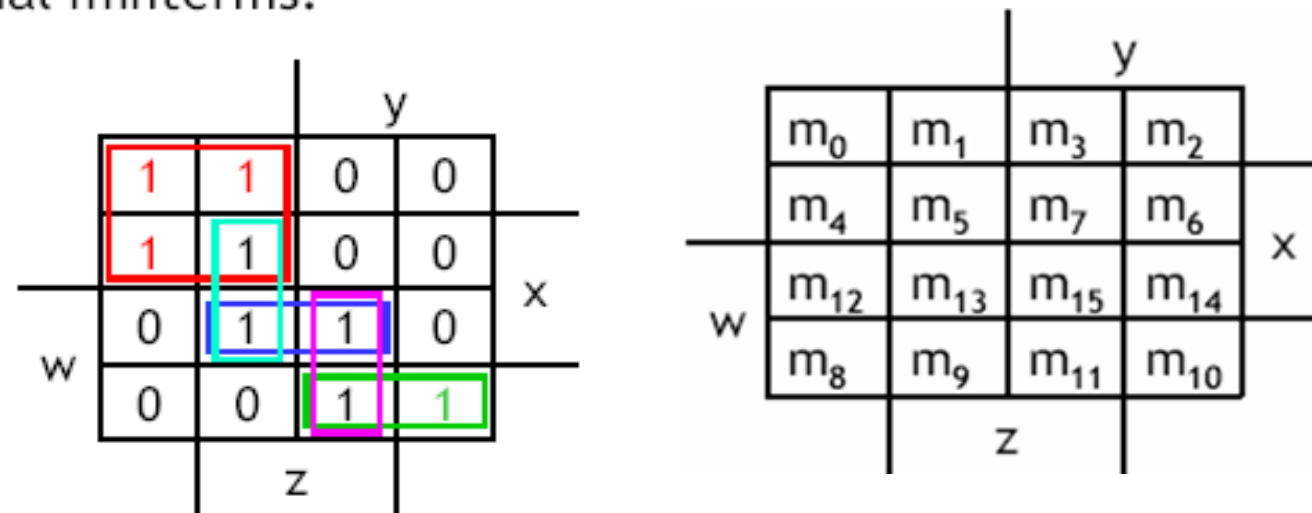Example 7

Essential prime implicants


- If any minterm belongs to only one group, then that group represents an **essential prime implicant**.
- Essential prime implicants *must* appear in the final MSP, which has to include all of the original minterms.



- This example has two essential prime implicants.
 - The red group ($w'y$) is essential, since m_0 , m_1 and m_4 are not in any other group.
 - The green group ($wx'y$) is essential because of m_{10} .

Covering the other minterms

- Finally, pick as few other prime implicants as necessary to ensure that all of the original minterms are included.

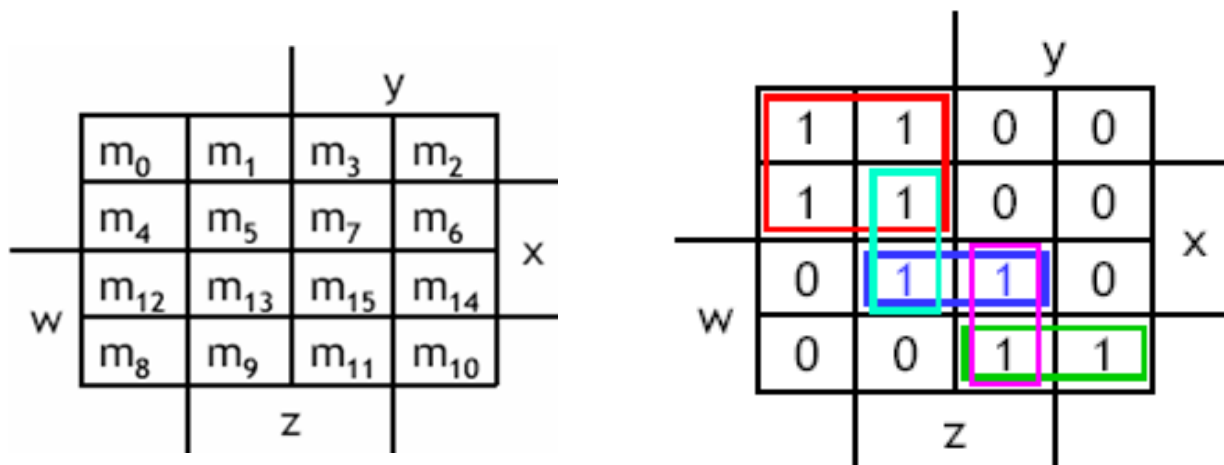


Example 7

- After choosing the red and green rectangles in our example, there are just two minterms remaining, m₁₃ and m₁₅.
 - They are both included in the blue prime implicant, wxz.
 - The resulting MSP is $w'y' + wxz + wx'y$.
- The magenta and sky blue groups are not needed, since their minterms are already included by the other three prime implicants.

Solutions for practice K-map 2

- Simplify the following K-map.

Example 8

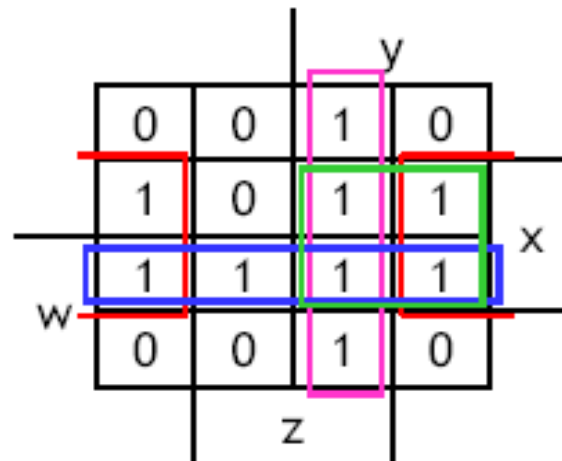


- All prime implicants are circled.
- The essential prime implicants are xz' , wx and yz .
- The MSP is $xz' + wx + yz$. (Including the group xy would be redundant.)

Practice K-map 3

- Find a minimal sum of products for the following.

$$f(w,x,y,z) = \sum m(0,2,4,5,8,14,15), \quad d(w,x,y,z) = \sum m(7,10,13)$$

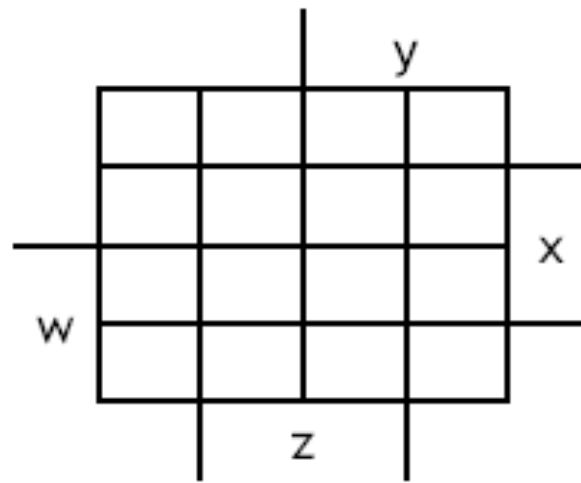

Example 9

Solutions for practice K-map 3

- Find a minimal sum of products for the following.

$$f(w,x,y,z) = \sum m(0,2,4,5,8,14,15), \quad d(w,x,y,z) = \sum m(7,10,13)$$

			y			
			1	0	0	1
		1	1	X	0	
		0	X	1	1	X
w		1	0	0	0	X
			z			

Example 9

- All prime implicants are circled. We can treat Xs as 1s if we want, so the red group includes two Xs, and the light blue group includes one X.
- The *only* essential prime implicant is $x'z'$. The red group is not essential because the two minterms in it also appear in other groups.
- The MSP is $x'z' + wxy + w'xy'$. It turns out the red group is redundant; we can cover all of the minterms in the map without it.

Practice K-map 2

- Simplify the following K-map.

Example 8

			y	
	0	0	1	0
	1	0	1	1
w	1	1	1	1
	0	0	1	0
		z		

Summary

Recapping the rules of Kmap simplification:

- Groupings can contain only 1s; no 0s.
- Groups can be formed only at right angles; diagonal groups are not allowed.
- The number of 1s in a group must be a power of 2 – even if it contains a single 1.
- The groups must be made as large as possible.
- Groups can overlap and wrap around the sides of the Kmap.
- Use don't care conditions when you can.