

Solution to HW Problems

Chapter 28

104 Phys

Prof. Nasser S. Alzayed

6. (a) Find the equivalent resistance between points a and b in Figure P28.6. (b) A potential difference of 34.0 V is applied between points a and b . Calculate the current in each resistor.

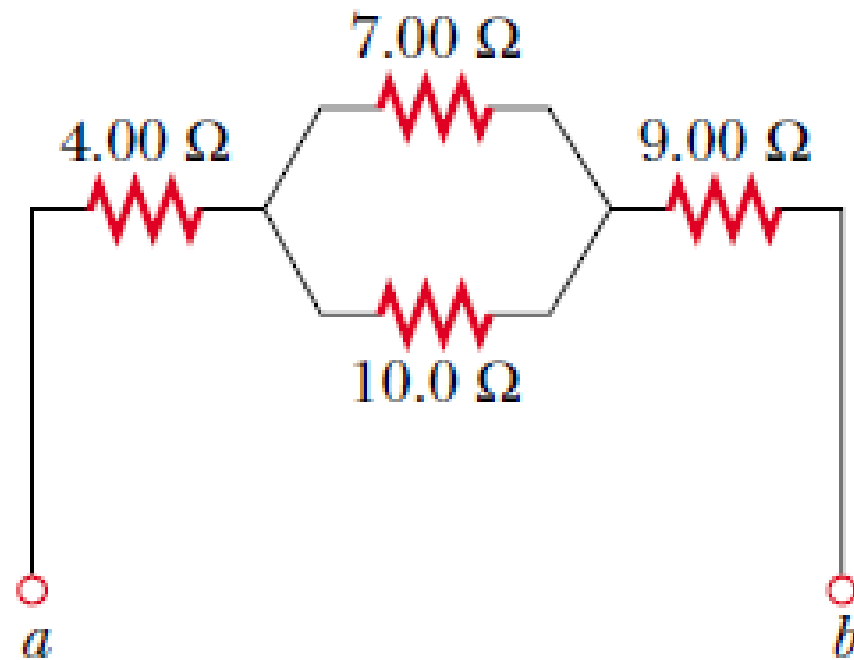


Figure P28.6


p 6/28:

step #1: ① 7 and 10 Ω in //

$$\rightarrow R_{\text{①}} = \left[\frac{1}{7} + \frac{1}{10} \right]^{-1} = 4.12 \Omega$$

step #2: ① + ② \Rightarrow
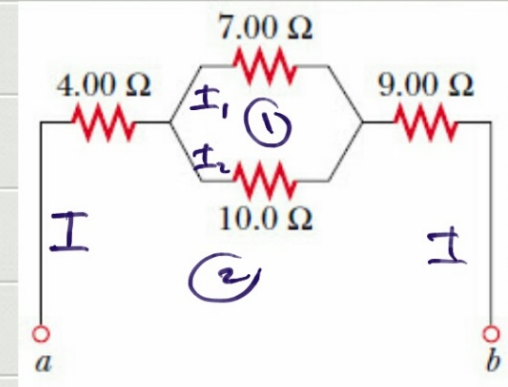
$$R_{\text{eq}} = 4 + 4.12 + 9 = 17.12 \Omega \neq$$



$$b) \because V = IR \rightarrow I = \frac{34}{17.12} = 1.99 \text{ A.}$$

$$\therefore I_{4\Omega} = I_{9\Omega} = 1.99 \text{ A.}$$

$$\text{for 7 and 10 } \Omega: \because R_{\text{①}} = 4.12 \Omega \therefore V = IR \rightarrow V_{\text{①}} = 1.99 \times 4.12 = 8.2 \text{ V}$$

$$\therefore I_7 = \frac{8.2}{7} = 1.17 \text{ A} \quad \text{and} \quad I_{10} = \frac{8.2}{10} = 0.82 \text{ A} \quad \neq$$

12. Using only three resistors— $2.00\ \Omega$, $3.00\ \Omega$, and $4.00\ \Omega$ —find 17 resistance values that may be obtained by various combinations of one or more resistors. Tabulate the combinations in order of increasing resistance.

P 12/28:

1 st . in series only	2 nd in // only	3 rd in // only
① $2\ \Omega$ only	⑧ $\frac{1}{2}$ only	⑮ $\frac{1}{2+3} + \frac{1}{4}$
② $3\ \Omega$ only	⑨ $\frac{1}{3}$ only	⑯ $\frac{1}{2+4} + \frac{1}{3}$
③ $4\ \Omega$ only	⑩ $\frac{1}{4}$ only	⑰ $\frac{1}{3+4} + \frac{1}{2}$
④ $2+3$	⑪ $\frac{1}{2} + \frac{1}{3}$	
⑤ $2+4$	⑫ $\frac{1}{2} + \frac{1}{4}$	
⑥ $3+4$	⑬ $\frac{1}{3} + \frac{1}{4}$	
⑦ $2+3+4$	⑭ $\frac{1}{2} + \frac{1}{3} + \frac{1}{4}$	



21.



Determine the current in each branch of the circuit shown in Figure P28.21.

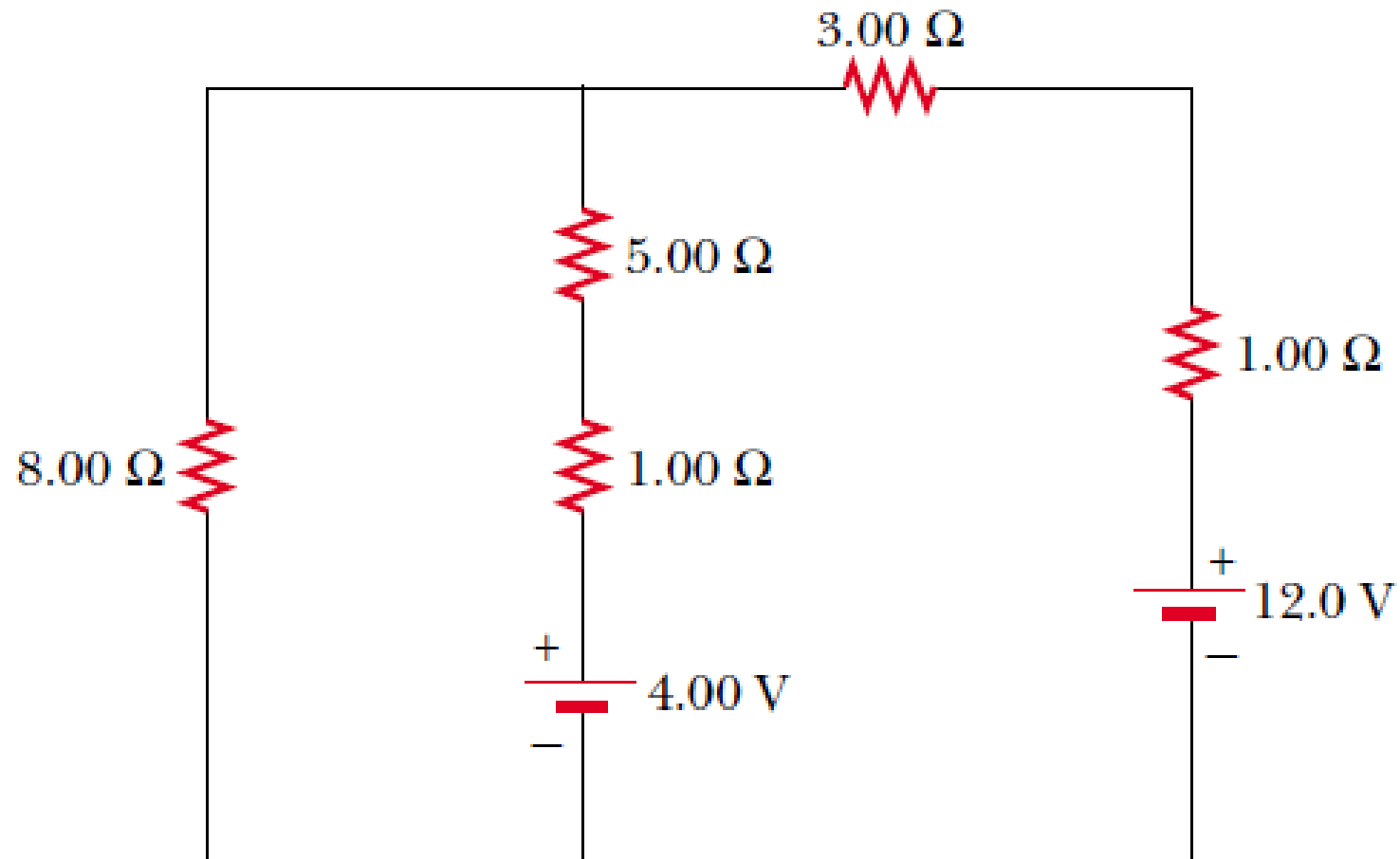



Figure P28.21 Problems 21, 22, and 23.

P. 21/28:

$$\textcircled{1} \rightarrow +4 - I_1 - 5I_1 - 8I_2 = 0 \quad \text{---} \textcircled{1}$$

$$\textcircled{2} \rightarrow +4 - I_1 - 5I_1 - 3I_3 - I_3 - 12 = 0 \quad \text{---} \textcircled{2}$$
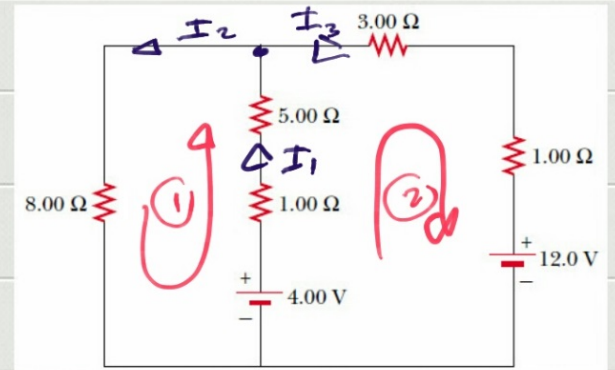
$$\Sigma I = 0 \rightarrow I_1 - I_2 - I_3 = 0 \quad \text{---} \textcircled{3}$$



Arrange equations:

$$\rightarrow +4 - 6I_1 - 8I_2 + 0 = 0 \quad \textcircled{1}$$

$$-8 - 6I_1 + 0 - 4I_3 = 0 \quad \textcircled{2}$$

$$0 + I_1 - I_2 - I_3 = 0 \quad \textcircled{3}$$

$$\textcircled{1} - \textcircled{2}: 12 + 0 - 8I_2 + 4I_3 = 0 \quad \textcircled{4}$$

$$\textcircled{1} + 6 \times \textcircled{3}: 4 + 0 - 14I_2 - 6I_3 = 0 \quad \textcircled{5}$$

$$\textcircled{4} \rightarrow 3 + 0 - 2I_2 + I_3 = 0 \quad \textcircled{6}$$

$$\textcircled{5} \rightarrow 2 + 0 - 7I_2 - 3I_3 = 0 \quad \textcircled{7}$$

$$3 \times \textcircled{6} + \textcircled{7}: 11 - 13I_2 = 0$$

$$\rightarrow I_2 = \frac{11}{13} = 0.846 \text{ A} \quad \text{---} \textcircled{8}$$

$\textcircled{8}$ in $\textcircled{6} \Rightarrow$

$$3 - 2 \times \frac{11}{13} = -I_3 \rightarrow I_3 = -1.3 \text{ A} \quad \textcircled{9}$$

$\textcircled{8} + \textcircled{9}$ in $\textcircled{3}:$

$$I_1 = 0.846 - 1.3$$

$$= 0.462 \text{ A}$$

note: $I_3 = 1.3 \text{ A}$ but

التي هي في العنصر الثالث