

Name:

ID Number:

Question One: How can we connect the ammeter and voltmeter in the circuit? And show me the connection as an example?

Question Two: Write down I_x and V_1 as expression in E , R and I ?
(*Hint:* Use a current and voltage divider rule)

