

Exp.6: Clipping Circuits

1- Objectives:

- To become familiar with the function and operation of clippers.

2- Circuit elements:

- Function generator.
- Oscilloscope.
- Silicon & Germanium diode.
- Resistor 2.2 K Ω .
- DC. Power supply unit (1.5 V).

3- Procedure:

Part 1: Parallel Clippers

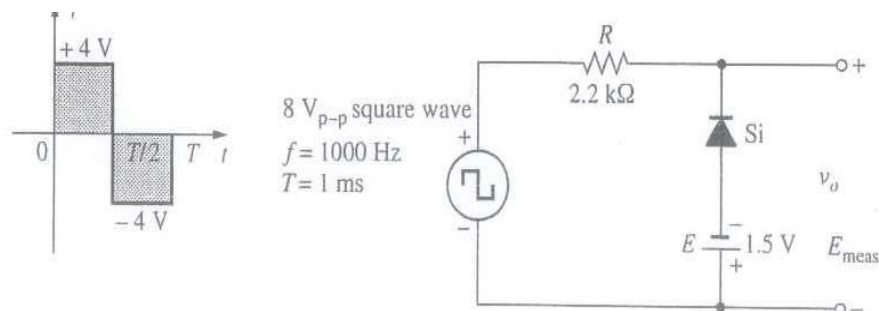


Fig 1

1- Connect the circuit as shown in figure 1. Note that the input is an $8 V_{p-p}$ square wave at a frequency of 1000 Hz.

2- Calculate the voltage V_o when the applied square wave is $+4 V$.


(Calculated) $V_o = \underline{\hspace{2cm}}$

3- Repeat (2) when the applied square wave is $-4 V$.


(Calculated) $V_o = \underline{\hspace{2cm}}$

4- Sketch the expected waveform for V_o .

Calculated:

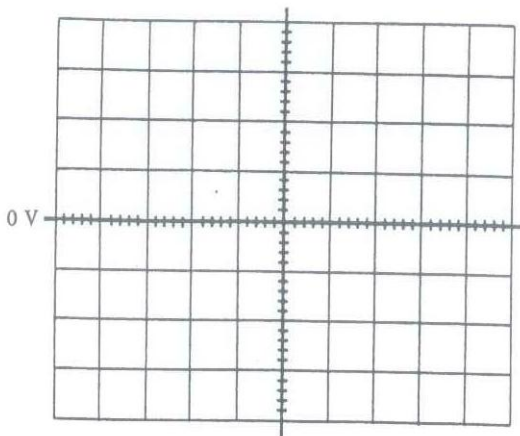

Measured:

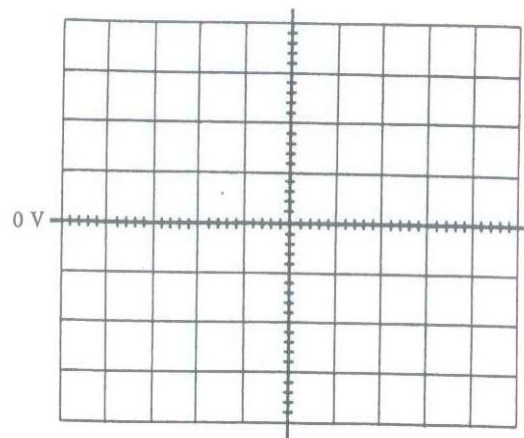

5- Compare with the predicted results.

6- Reverse the battery of fig 1, and calculate the level of V_o when $V_o = +4 V$.

(Calculated) $V_o = \underline{\hspace{2cm}}$


7- Repeat (6) when the applied square wave is -4 V.

(Calculated) $V_o =$ _____


8- Sketch the expected waveform for V_o .

9- Compare with the predicted results.

Calculated:

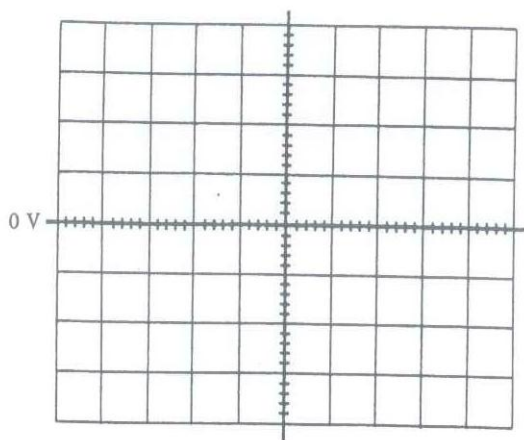

Measured:

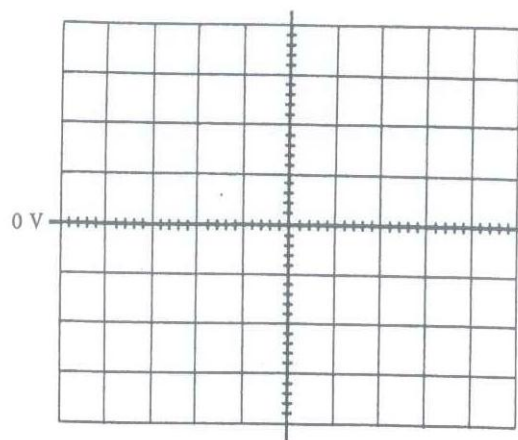

Part 2: Parallel Clippers (continued)

1- Connect the circuit as shown in figure 2. Note that the input is a $4 V_{p-p}$ square wave at a frequency of 1000 Hz.

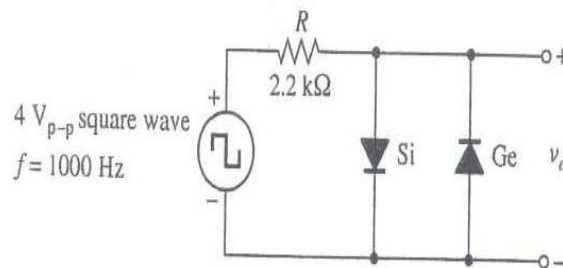


Fig 2

2- Calculate the voltage V_o when the applied square wave is +2 V.

(Calculated) $V_o = \underline{\hspace{2cm}}$


3- Repeat (2) when the applied square wave is -2 V.

(Calculated) $V_o = \underline{\hspace{2cm}}$


4- Sketch the expected waveform for V_o .

5- Compare with the predicted results.

Calculated:

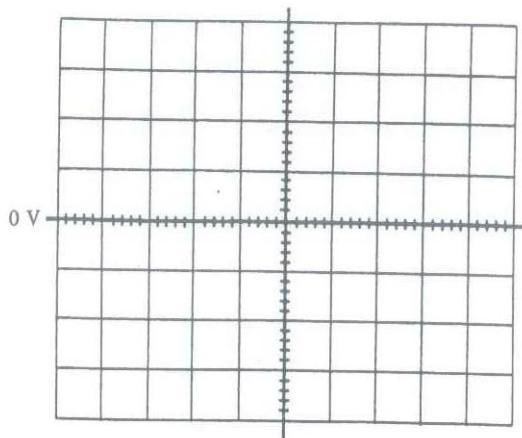

Measured:

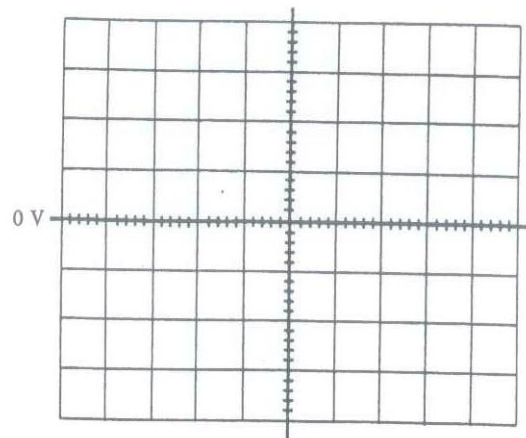

Part 3: Series Clippers

- 1- Connect the circuit as shown in figure 3. Note that the input is an $8\text{ V}_{\text{p-p}}$ square wave at a frequency of 1000 Hz .

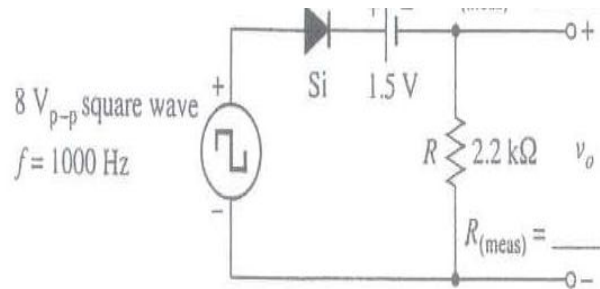


Fig 3

- 2- Calculate the voltage V_o when the applied square wave is $+4\text{ V}$.

(Calculated) $V_o = \underline{\hspace{2cm}}$

- 3- Repeat (2) when the applied square wave is -4 V .

(Calculated) $V_o = \underline{\hspace{2cm}}$

- 4- Sketch the expected waveform for V_o .

- 5- Compare with the predicted results.

- 6- Reverse the battery of fig 1, and calculate the level of V_o when $V_o = +4\text{ V}$.

(Calculated) $V_o = \underline{\hspace{2cm}}$


- 7- Repeat (6) when the applied square wave is -4 V .

(Calculated) $V_o = \underline{\hspace{2cm}}$

8- Sketch the expected waveform for V_o .

9- Compare with the predicted results.

Calculated:

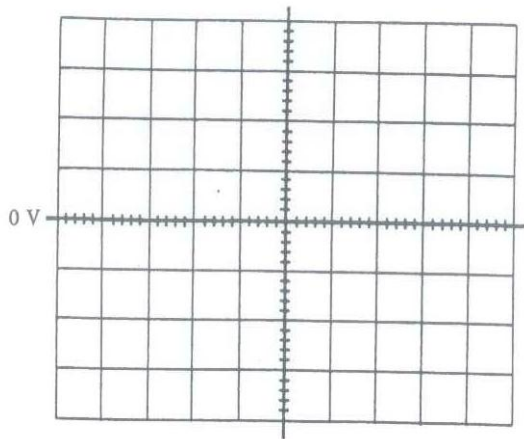

Measured:

