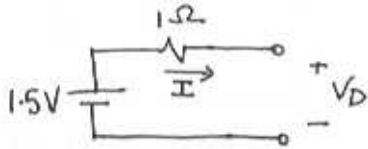


## CHAPTER 3 - PROBLEMS

3.1



The diode can be reverse-biased and thus no current would flow, or forward-biased where current would flow.

(a) Reverse biased  $I = 0A$   $V_D = 1.5V$

(b) Forward biased  $I = 1.5A$   $V_D = 0V$

3.2

(a) Diode is conducting and thus has a 0V drop across it. Consequently

$$V = \underline{-3V}$$

$$I = \frac{3 - (-3)}{10k\Omega} = \underline{0.6mA}$$

(b) Diode is cut off.

$$V = \underline{3V} \quad I = \underline{0A}$$

(c) Diode is conducting

$$V = \underline{3V}$$


$$I = \frac{3 - (-3)}{10k\Omega} = \underline{0.6mA}$$

(d) Diode is cut off.


$$V = \underline{-3V} \quad I = \underline{0A}$$

3.3

(a)

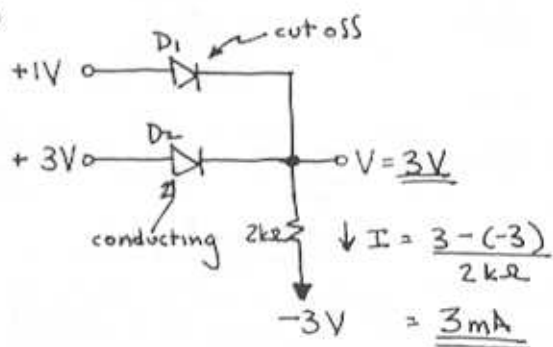


(b)

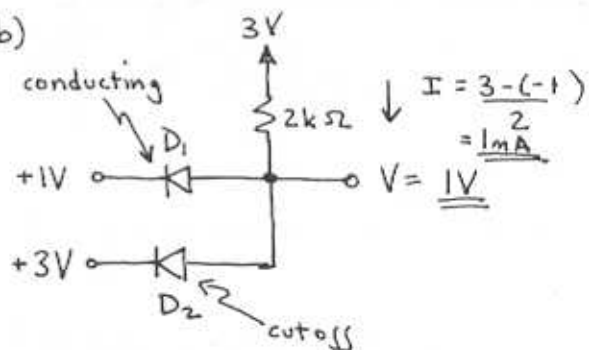

3.4


(a)

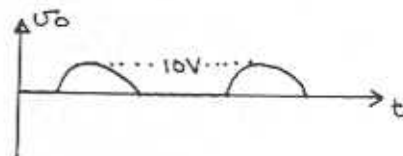

$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{0V}$$

$$f = \underline{1kHz}$$

# CHAPTER 3 PROBLEMS

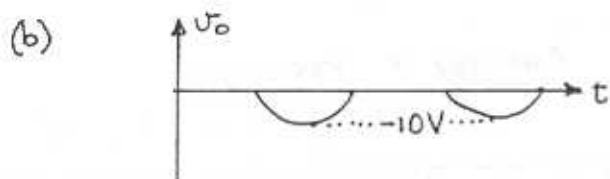


$$V_{p+} = \underline{0V} \quad V_{p-} = \underline{-10V}$$

$$f = 1\text{kHz}$$




$$V_o = \underline{0V}$$

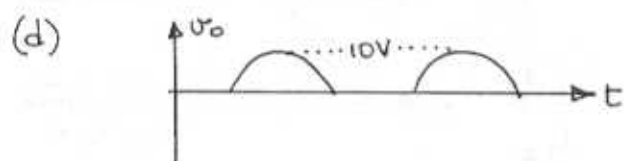Neither  $D_1$  nor  $D_2$  conducts so there is no output.




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{0V} \quad f = 1\text{kHz}$$

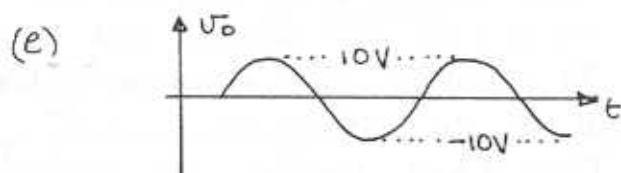Both  $D_1$  and  $D_2$  conduct when  $V_i > 0$




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{-10V} \quad f = 1\text{kHz}$$

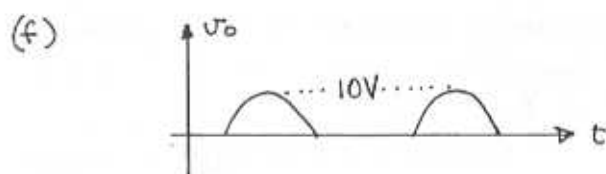$D_1$  conducts when  $V_i > 0$  and  $D_2$  conducts when  $V_i < 0$ . Thus the output follows the input.




$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{0V} \quad f = 1\text{kHz}$$

$D_1$  is cutoff when  $V_i < 0$

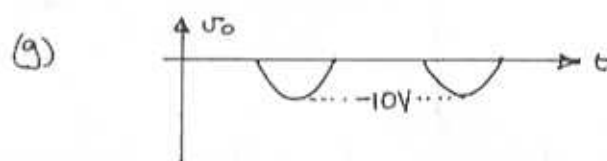


$$V_{p+} = \underline{0V} \quad V_{p-} = \underline{-10V} \quad f = 1\text{kHz}$$

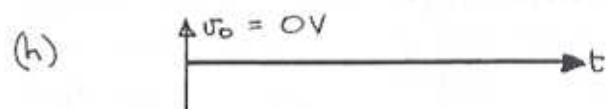$D_1$  shorts to ground when  $V_i > 0$  and is cut off when  $V_i < 0$  whereby the output follows  $V_i$ .



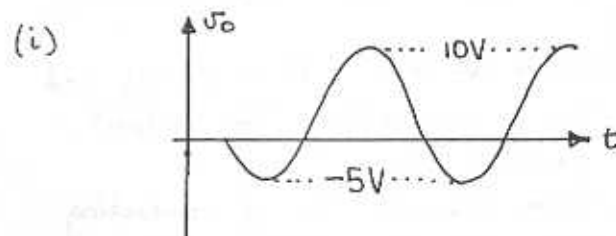$V_o = \underline{0V}$  ~ The output is always shorted to ground as  $D_1$  conducts when  $V_i > 0$  and  $D_2$  conducts when  $V_i < 0$ .



$$V_{p+} = \underline{10V} \quad V_{p-} = \underline{-5V} \quad f = 1\text{kHz}$$

-When  $V_i > 0$ ,  $D_1$  is cutoff and  $V_o$  follows  $V_i$ .


# CHAPTER 3 PROBLEMS

3.5

-When  $V_i < 0$ ,  $D_1$  is conducting and the circuit becomes a voltage divider where the negative peak is

$$\frac{1k\Omega}{1k\Omega + 1k\Omega} \cdot -10V = -5V$$

(j)

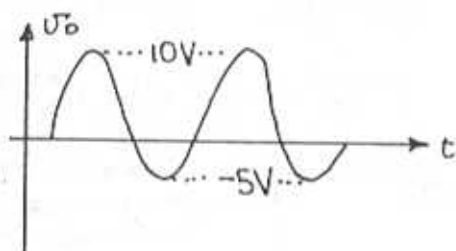


$$V_{p+} = 10V \quad V_{p-} = -5V \quad f = 1kHz$$

-When  $V_i > 0$ , the output follows the input as  $D_1$  is conducting.

-When  $V_i < 0$ ,  $D_1$  is cutoff and the circuit becomes a voltage divider.

(k)


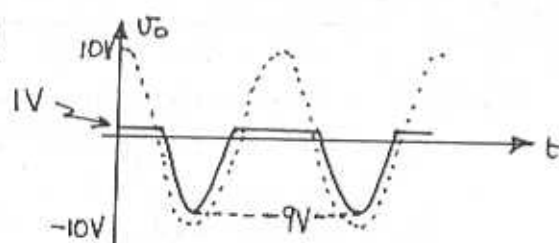


$$V_{p+} = 1V \quad V_{p-} = -9V \quad f = 1kHz$$

-When  $V_i > 0$ ,  $D_1$  is cutoff and  $D_2$  is conducting. The output becomes 1V.

-When  $V_i < 0$ ,  $D_1$  is conducting and  $D_2$  is cutoff. The output becomes:-

$$V_o = V_i + 1V$$

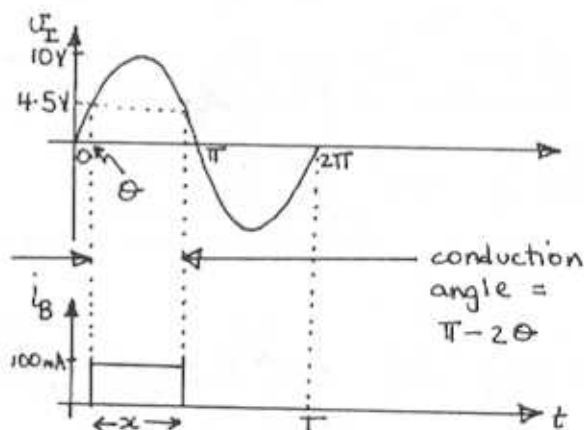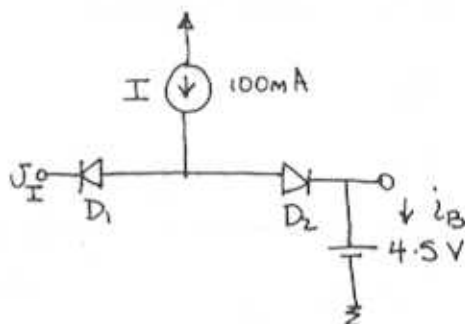

-When  $V_i < 4.5V$   $D_1$  conducts and  $D_2$  is cutoff so  $i_B = 0A$ . For  $V_i > 4.5V$   $D_2$  conducts and  $D_1$  is cutoff thus disconnecting the input  $V_i$ . All of the current then flows through the battery.

$$10 \sin \theta = 4.5V$$

$$\theta = \sin^{-1}(4.5/10)$$

$$\text{conduction angle} = \pi - 2\theta$$

Fraction of cycle that  $i_B = 100mA$  is given by:-

$$x = \frac{\pi - 2\theta}{2\pi} = 0.35$$

$$\begin{aligned}
 i_{B \text{ avg}} &= \frac{1}{T} \int i_B dt \\
 &= \frac{1}{T} [100 \cdot 0.35T] \\
 &= \underline{\underline{35 \text{ mA}}}
 \end{aligned}$$

If  $V_x$  is reduced by 10% the peak value of  $i_B$  remains the same

$$i_{B \text{ peak}} = \underline{\underline{100 \text{ mA}}}$$

but the fraction of the cycle for conduction changes

$$\begin{aligned}
 x &= \frac{\pi - 2\theta}{2\pi} = \frac{\pi - 2 \sin^{-1}(4.5/9)}{2\pi} \\
 &= \underline{\underline{\frac{1}{3}}}
 \end{aligned}$$

Thus:

$$\begin{aligned}
 i_{B \text{ avg}} &= \frac{1}{T} [100 \cdot \frac{T}{3}] \\
 &= \underline{\underline{33.3 \text{ mA}}}
 \end{aligned}$$

3.6

| A | B | x | y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |

$$x = \underline{\underline{AB}}$$

$$y = \underline{\underline{A+B}}$$

### CHAPTER 3 PROBLEMS

-x and y are the same for

$$A=B$$

-x and y are opposite if  $A \neq B$

3.7

$$\frac{5-0}{R} \leq 0.1 \text{ mA}$$

$$R \geq 5/0.1 = \underline{\underline{50 \text{ k}\Omega}}$$

3.8


The maximum input current occurs when one input is low and the other two are high.

$$\frac{5-0}{R} \leq 0.1 \text{ mA}$$


$$R \geq \underline{\underline{50 \text{ k}\Omega}}$$

3.9

(a)

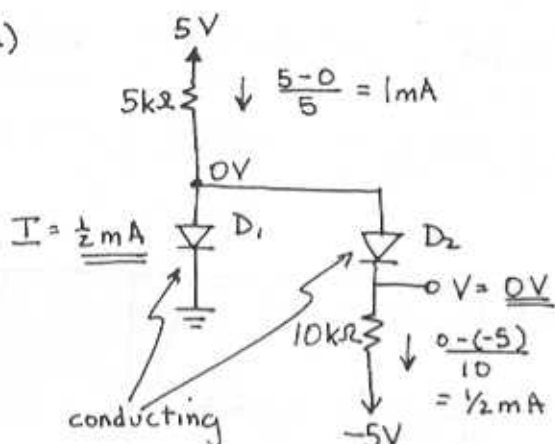

(b)

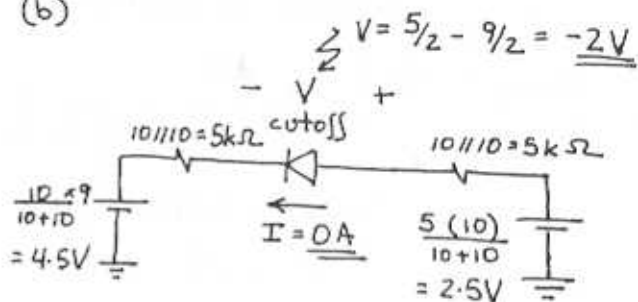


3.11

$$R \geq \frac{120\sqrt{2}}{50} \geq \underline{\underline{3.4 \text{ k}\Omega}}$$


The largest reverse voltage appearing across the diode is equal to the peak input voltage

$$120\sqrt{2} = \underline{\underline{169.7 \text{ V}}}$$

3.12

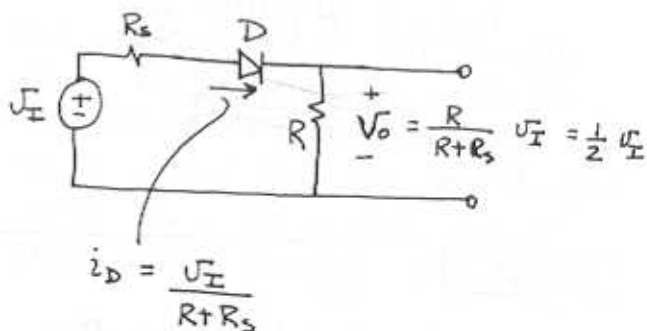


D starts to conduct when  $V_I > 0$

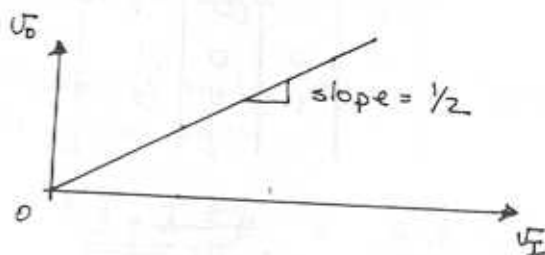

3.10


(a)

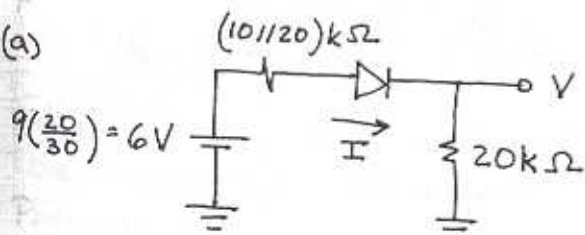

$$I = \frac{6}{(10||20) + 20} = \underline{\underline{0.225 \text{ mA}}}$$

$$V = \frac{20}{(10||20) + 20} \times 6 = \underline{\underline{4.5 \text{ V}}}$$

3.13

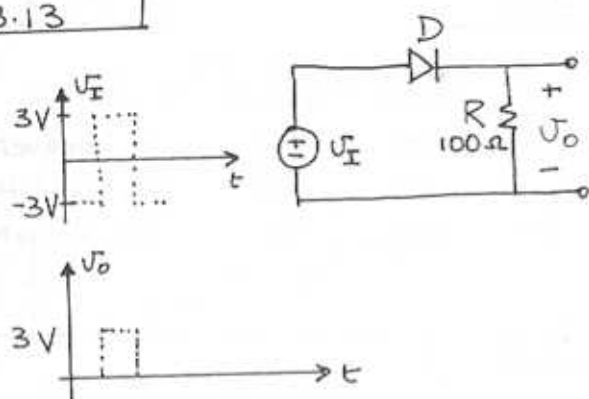

$$V_{O, \text{peak}} = 3V$$


$$V_{O, \text{avg}} = \frac{1}{T} \int V_O dt = \frac{1}{T} \left[ 3 \frac{T}{2} \right] = \underline{\underline{3/2 V}}$$

$$i_{D, \text{peak}} = 3/100 = \underline{\underline{30 \text{ mA}}}$$

$$i_{D, \text{avg}} = \frac{3/2}{100} = \underline{\underline{15 \text{ mA}}}$$

The maximum reverse diode voltage is 3V

3.14

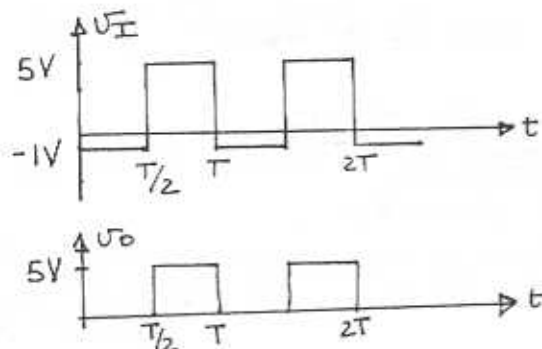

$$V_{O, \text{peak}} = \underline{\underline{5V}}$$



$$V_{O, \text{avg}} = \underline{\underline{2.5V}}$$

$$i_{D, \text{peak}} = \frac{V_{O, \text{peak}}}{100} = \underline{\underline{50 \text{ mA}}}$$

$$i_{D, \text{avg}} = i_{D, \text{peak}}/2 = \underline{\underline{25 \text{ mA}}}$$

maximum reverse voltage = 1V

3.15

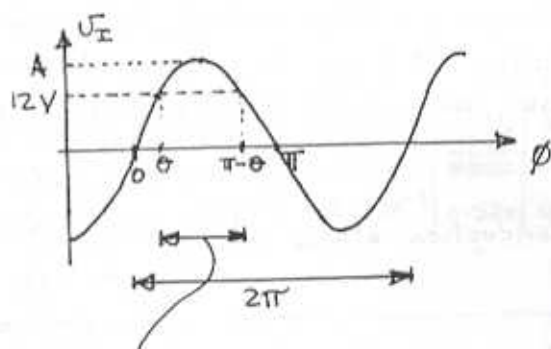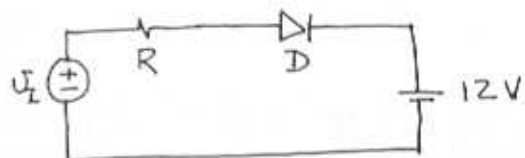

conduction occurs

$$V_I = A \sin \theta = 12 \sim \text{conduction across } D \text{ occurs}$$

For a conduction angle \$(\pi - 2\theta)\$ that is 20% of a cycle

$$\frac{\pi - 2\theta}{2\pi} = \frac{1}{5}$$

$$\theta = 0.3\pi$$

$$A = 12/\sin \theta = 14.83V$$

$$\circ \circ \text{ Peak-to-peak sine wave voltage} = 2A = \underline{\underline{29.67V}}$$

Given the average diode current to be

$$\frac{1}{2\pi} \int_0^{2\pi} \frac{A \sin \phi - 12}{R} d\phi = 100 \text{ mA}$$

$$\frac{1}{2\pi} \left[ \frac{-14.83 \cos \phi - 12 \phi}{R} \right]_{\phi=0.3\pi}^{\phi=0.7\pi} = 0.1$$

$$R = \underline{\underline{3.75 \Omega}}$$

$$\text{Peak diode current} = \frac{A-12}{R} = \underline{\underline{0.75A}}$$

$$\text{Peak reverse voltage} = A+12 = \underline{\underline{26.83V}}$$

For resistors specified to only one significant digit and peak-to-peak voltage to the nearest volt then choose  $A = 15$  so the peak-to-peak sine wave voltage = 30V and  $R = \underline{\underline{3 \Omega}}$

$$\begin{aligned} \text{Conduction starts at } v_E = A \sin \theta &= 12 \\ 15 \sin \theta &= 12 \\ \theta &= 0.93 \text{ rad} \end{aligned}$$

Conduction stops at  $\pi - \theta$

$$\begin{aligned} \therefore \text{Fraction of cycle that current flows is } &\frac{\pi - 2\theta}{2\pi} \times 100 = 20.5 \\ &\approx \underline{\underline{20\%}} \end{aligned}$$

Average diode current =

$$\frac{1}{2\pi} \left[ \frac{-15 \cos \phi - 12 \phi}{3} \right]_{\phi=0.93}^{2.21} = \underline{\underline{136 \text{ mA}}}$$

Peak diode current

$$= \frac{15-12}{3} = \underline{\underline{1A}}$$

Peak reverse voltage =

$$A + 12 = \underline{\underline{27V}}$$

3.16

| V   | RED | GREEN |                           |
|-----|-----|-------|---------------------------|
| 3V  | ON  | OFF   | - D <sub>1</sub> conducts |
| 0   | OFF | OFF   | - No current flows        |
| -3V | OFF | ON    | - D <sub>2</sub> conducts |

3.17

$$V_T = kT/q \quad \text{where } k = 1.38 \times 10^{-23} \text{ J/K}$$

$$T = 273 + x^\circ \text{C}$$

$$q = 1.60 \times 10^{-19} \text{ C}$$

| $x [^\circ \text{C}]$ | $V_T [\text{mV}]$ |
|-----------------------|-------------------|
| -40                   | 20                |
| 0                     | 23.5              |
| 40                    | 27                |
| 150                   | 36.5              |

$$\begin{aligned} \text{for } V_T &= 25 \text{ mV} \\ T &= \underline{\underline{16.8^\circ \text{C}}} \end{aligned}$$

3.18

$$i = I_s e^{v/2 \times 0.025}$$

$$\therefore 1000 I_s = I_s e^{v/0.05}$$

$$v = \underline{\underline{0.345V}}$$

at  $v = 0.7V$

$$i = I_s e^{0.7/0.05} = \underline{\underline{1.2 \times 10^6 I_s}}$$

3.19

$$i_1 = I_s e^{0.7/V_T} = 10^{-3}$$

$$i_2 = I_s e^{0.5/V_T}$$

$$\frac{i_2}{i_1} = \frac{i_2}{10^{-3}} = e^{\frac{0.5-0.7}{0.025}}$$

$$i_2 = \underline{\underline{0.335 \mu A}}$$

3.20

$$i = I_s e^{V/nV_T} = I_s e^{0.7/0.025} = 5(10^{-3})$$

$$I_s = 5(10^{-3}) e^{-0.7/0.025} = \underline{\underline{3.46 \times 10^{-15} A}}$$

| V     | i             |
|-------|---------------|
| 0.71V | 7.46 mA       |
| 0.8V  | 273.21 mA     |
| 0.69V | 3.35 mA       |
| 0.6V  | 91.65 $\mu A$ |

$$\text{Let } i_1 = I_s e^{V_1/0.025}$$

$$i_2 = 10i_1 = I_s e^{V_2/0.025}$$

$$\frac{i_2}{i_1} = 10 = e^{\frac{V_2 - V_1}{0.025}}$$

$$\therefore \Delta V = V_2 - V_1 = \underline{\underline{57.56 mV}}$$

3.21

To calculate  $I_s$  use

$$I_s = I e^{-V/nV_T} = I e^{-V/n \times 0.025}$$

To calculate the voltage at 1% of the measured current use

$$i_2 = 0.01 i_1 \quad \text{so,}$$

$$\frac{i_2}{i_1} = 0.01 = e^{\frac{V_2 - V_1}{nV_T}}$$

$$V_2 = V_1 + nV_T \ln 0.01$$

$$= V + n(0.025) \ln(0.01)$$

| V     | I          | $n=1$<br>[A]           | $I_s$<br>$n=2$<br>[A]  | V<br>$n=1$<br>[V] | V<br>$n=2$<br>[V] |
|-------|------------|------------------------|------------------------|-------------------|-------------------|
| 0.7   | 1 A        | $6.91 \times 10^{-13}$ | $8.32 \times 10^{-7}$  | 0.585             | 0.470             |
| 0.650 | 1 mA       | $5.11 \times 10^{-15}$ | $2.26 \times 10^{-9}$  | 0.535             | 0.420             |
| 0.650 | 10 $\mu A$ | $5.11 \times 10^{-17}$ | $2.26 \times 10^{-11}$ | 0.535             | 0.420             |
| 0.7   | 10 mA      | $6.91 \times 10^{-15}$ | $8.32 \times 10^{-9}$  | 0.584             | 0.470             |

3.22

$$\text{Let } I_1 = I_s e^{V_1/nV_T} \quad \text{and}$$

$$I_2 = I_s e^{V_2/nV_T} = I_1/10$$

Calculate  $n$  by :-

$$\frac{I_2}{I_1} = e^{\frac{V_2 - V_1}{nV_T}}$$

$$n = \frac{1}{V_T} \left[ \frac{V_2 - V_1}{\ln I_2/I_1} \right] = \frac{1}{0.025} \left[ \frac{V_2 - V_1}{\ln 0.1} \right]$$

Calculate  $I_s$  by :-

$$I_s = I_1 e^{-V_1/nV_T}$$

Calculate the diode voltage at  $10I_1$

$$\text{by :- } V_3 = nV_T \ln \frac{10I_1}{I_s}$$


| $I$        | $V_1$<br>[V] | $V_2$<br>[V] | $n$   | $I_s$<br>[A]           | $V_3$<br>[V] |
|------------|--------------|--------------|-------|------------------------|--------------|
| 10mA       | 0.7          | 0.6          | 1.737 | $10^{-9}$              | 0.8          |
| 1mA        | 0.7          | 0.6          | 1.737 | $10^{-10}$             | 0.8          |
| 10A        | 0.8          | 0.7          | 1.737 | $10^{-7}$              | 0.9          |
| 1mA        | 0.7          | 0.58         | 2.085 | $1.47 \times 10^{-9}$  | 0.82         |
| 10 $\mu$ A | 0.7          | 0.64         | 1.042 | $2.15 \times 10^{-17}$ | 0.7          |

3.23

The voltage across each diode is  $V_0/3$

$$I = I_s e^{\frac{V_0/3}{nV_T}} = 10^{-14} e^{\frac{2/3}{0.025}}$$
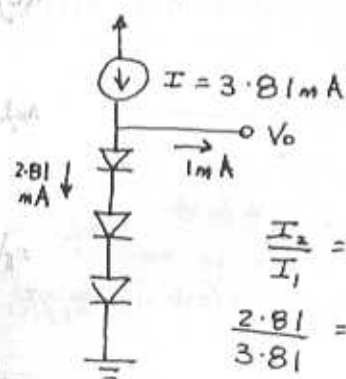
$$= \underline{\underline{3.81 \text{ mA}}}$$




$$\frac{I_2}{I_1} = e^{\frac{(V_2 - V_1)/3}{0.025}}$$

$$\frac{2.81}{3.81} = e^{\frac{(V_2 - 2)/3}{0.025}}$$

$$\Delta V = V_2 - 2 = \underline{\underline{-22.8 \text{ mV}}}$$

3.24

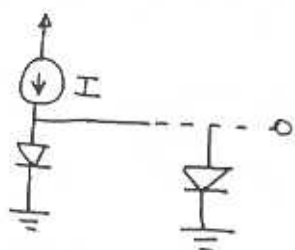

With one diode the current

through it is

$$I = I_s e^{V_1/nV_T}$$

With two diodes in parallel, the current splits between each diode so that the diodes each has half the current


$$\frac{I}{2} = I_s e^{V_2/nV_T}$$

$$\therefore \frac{I/2}{I} = e^{\frac{V_2 - V_1}{nV_T}}$$

The change in voltage is

$$\Delta V = V_2 - V_1 = nV_T \ln\left(\frac{1}{2}\right) = \underline{\underline{-17.3 \text{ mV}}}$$

3.25

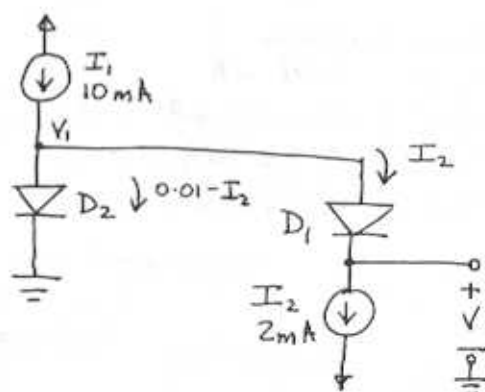

The current through  $D_1$  is

$$10 I_s e^{\frac{V_1 - V}{nV_T}} = I_2 \quad \textcircled{A}$$

The current through  $D_2$  is

$$I_s e^{\frac{V_1}{nV_T}} = 0.01 - I_2$$

$$I_s = (0.01 - I_2) e^{\frac{-V_1}{nV_T}} \quad \textcircled{B}$$

$\textcircled{B} \rightarrow \textcircled{A}$

$$10(0.01 - I_2) e^{\frac{-V_1}{nV_T}} = I_2$$

$$V = -V_T \ln\left(\frac{I_2}{10(0.01 - I_2)}\right)$$

$$= 0.025 \ln\left(\frac{2}{10(8)}\right) = \underline{\underline{92.2 \text{ mV}}}$$

For  $V = 50 \text{ mV}$


$$-V_T \ln\left(\frac{I_2}{10(10 - I_2)}\right) = 50 \times 10^{-3}$$

$$I_2 = 10(10 - I_2) e^{-2}$$

$$I_2(1 + 10e^{-2}) = 100e^{-2}$$

$$I_2 = \underline{\underline{5.75 \text{ mA}}}$$

3.26

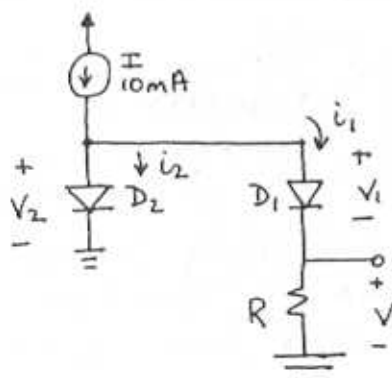

Given for each diode  $\frac{0.7}{n} \times 0.025$

$$i = I_s e^{\frac{V}{nV_T}} \Rightarrow 10 \times 10^{-3} = I_s e^{\frac{0.7}{n} \times 0.025} \quad (1)$$

$$100 \times 10^{-3} = I_s e^{\frac{0.8}{n} \times 0.025} \quad (2)$$

②/①  $10 = e^{\frac{0.1}{n} \times 0.025}$

$$n = 1.737$$

$$V = V_2 - V_1 = nV_T \ln\left(\frac{i_2}{i_1}\right) = 80 \text{ mV}$$

$$1.737 (25 \times 10^{-3}) \ln\left(\frac{0.01 - i_1}{i_1}\right) = 80$$

$$i_1 = 1.4 \text{ mA}$$

$$R = 80 / i_1 = 80 / 1.4 = \underline{\underline{57.1 \Omega}}$$

3.27

At a constant temperature, the diode voltage drop changes with current according to

$$\Delta V = V_T \ln\left(\frac{I_2}{I_1}\right)$$

where

$$V_T = \frac{kT}{q} = \frac{1.38 \times 10^{-23} (273 + \text{Temp. } ^\circ\text{C})}{1.6 \times 10^{-19}}$$

thus:

| TEMP ( $^\circ\text{C}$ ) | 0    | 50   | 75 | 100  | -50  |
|---------------------------|------|------|----|------|------|
| $V_T$ (mV)                | 23.5 | 27.9 | 30 | 32.2 | 19.2 |


At a constant current, the diode voltage drop changes with temperature according to

$$\Delta V = -2 (\text{mV}) \times \text{TEMPERATURE CHANGE } (^\circ\text{C})$$

thus:

- (a) 620 mV at  $10 \mu\text{A}$  and  $0^\circ\text{C}$   
 728 mV at  $1 \text{ mA}$  and  $0^\circ\text{C}$   
 678 mV at  $1 \text{ mA}$  and  $25^\circ\text{C}$


3.28

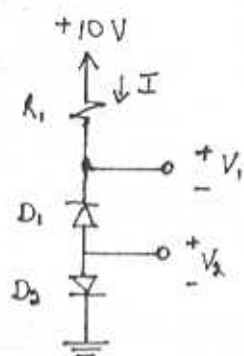At  $20^\circ\text{C}$ :

$$V_{R1} = V_2 = 520 \text{ mV}$$

$$R_1 = 520 \text{ k}\Omega$$

$$I = \frac{520 \text{ mV}}{520 \text{ k}\Omega} = 1 \mu\text{A}$$

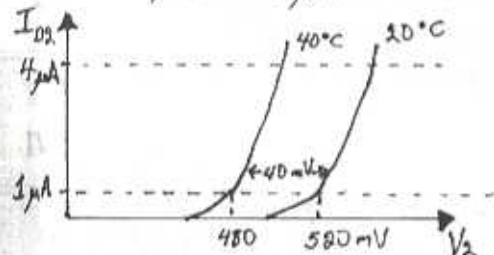At  $40^\circ\text{C}$ ,  $I = 4 \mu\text{A}$ 

$$V_2 = 480 + 2.3 \times 1 \times 25 \log 4$$

$$= 514.6 \text{ mV}$$

$$V_{R1} = 4 \mu\text{A} \times 520 \text{ k}\Omega = \underline{\underline{2.08 \text{ V}}}$$

At  $0^\circ\text{C}$ ,  $I = \frac{1}{4} \mu\text{A}$ 

$$V_2 = 560 - 2.3 \times 1 \times 25 \log 4$$

$$= \underline{\underline{525.4 \text{ mV}}}$$

$$V_{R1} = \frac{1}{4} \times 520 = \underline{\underline{0.13 \text{ V}}}$$

3.29

The voltage drop =  $700 - 580 = 120 \text{ mV}$   
 Since the diode voltage decreases by approximately  $2 \text{ mV}$  for every  $1^\circ\text{C}$  increase in temperature, the junction temperature must have increased by

$$\frac{120}{2} = \underline{\underline{60^\circ\text{C}}}$$

Power being dissipated =

$$580 \times 10^{-3} \times 15 = \underline{\underline{8.7 \text{ W}}}$$

Thermal Resistance = temperature rise / watt

$$= 60 / 8.7 = \underline{\underline{6.9^\circ\text{C/W}}}$$

3.30

$$i = I_s e^{V/nV_T}$$

$$10 = I_s e^{0.8/2(0.025)}$$

$$I_s = 1.12 \times 10^{-6} \text{ A}$$

For current varying between  $i_1 = 0.5 \text{ mA}$  to  $i_2 = 1.5 \text{ mA}$ , the voltage varies from

$$V_1 = 2(0.025) \ln \left( \frac{0.5 \times 10^{-3}}{1.12 \times 10^{-6}} \right) = \underline{\underline{0.305 \text{ V}}}$$

to:

$$V_2 = 2(0.025) \ln \left( \frac{1.5 \times 10^{-3}}{1.12 \times 10^{-6}} \right) = \underline{\underline{0.360 \text{ V}}}$$

∴ The voltage decreases by approximately  $2 \text{ mV}$  for every  $1^\circ\text{C}$  increase in temperature, the voltage may vary by  $\pm 50 \text{ mV}$  for the  $\pm 25^\circ\text{C}$  temperature variation.

3.31

$$i = I_s e^{V/nV_T}$$

$$\frac{I_{s2}}{I_{s1}} = \frac{1}{0.1 \times 10^{-3}} = 10^4$$

For identical currents

$$I_{s1} e^{V_1/nV_T} = I_{s2} e^{V_2/nV_T}$$

$$e^{\frac{V_1 - V_2}{nV_T}} = 10^4$$

$$V_1 - V_2 = nV_T \ln 10^4$$

$$= 26 \times 10^{-3} \ln 10^4$$

$$= \underline{+0.23V}$$


I.E. THE VOLTAGE DIFFERENCE BETWEEN THE TWO DIODES IS +0.23V INDEPENDENT OF THE CURRENT.

HOWEVER, SINCE THE TWO CURRENTS CAN VARY BY A FACTOR OF 3 (0.5 mA TO 1.5 mA) THE DIFFERENCE VOLTAGE WILL BE:

$$0.23V \pm nV_T \ln 3 = 0.23V \pm 2.75 \text{ mV}$$

SINCE TEMPERATURE CHANGE AFFECTS BOTH DIODES SIMILARLY THE DIFFERENCE VOLTAGE REMAINS CONSTANT.

3.32

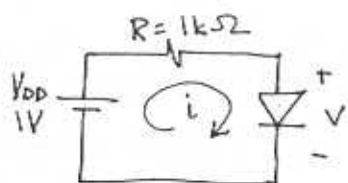


$$i = 10^{-15} e^{V/V_T}$$

where  $n=1$

$$V = 0.7V \quad i = 1.45 \text{ mA}$$

$$V = 0.6V \quad i = 0.026 \text{ mA}$$

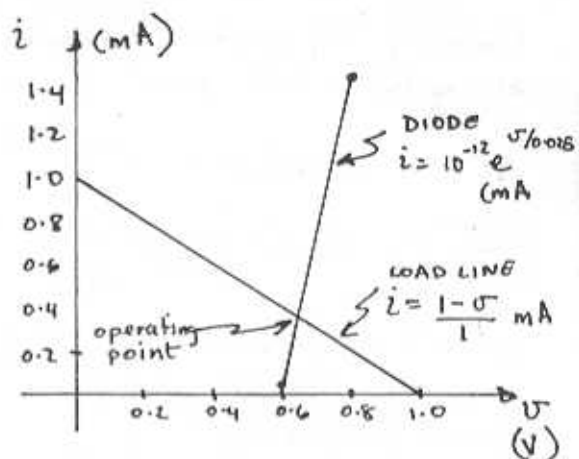A sketch of the graphical construction to determine the operating point is shown below.



From the above sketch we see that the operating point must lie between  $V = 0.6$  and  $0.7V$  and  $i = 0.3$  to  $0.4 \text{ mA}$ . To find the point more accurately an enlarged graph is plotted.


$$\text{For } i = 0.3 \text{ mA} = 10^{-12} e^{V/0.025} \Rightarrow V = 660.7 \text{ mV}$$

$$\text{For } i = 0.4 \text{ mA} = 10^{-12} e^{V/0.025} \Rightarrow V = 667.9 \text{ mV}$$

For the load line:

$$V = 660 \text{ mV} \Rightarrow i = 0.34 \text{ mA}$$
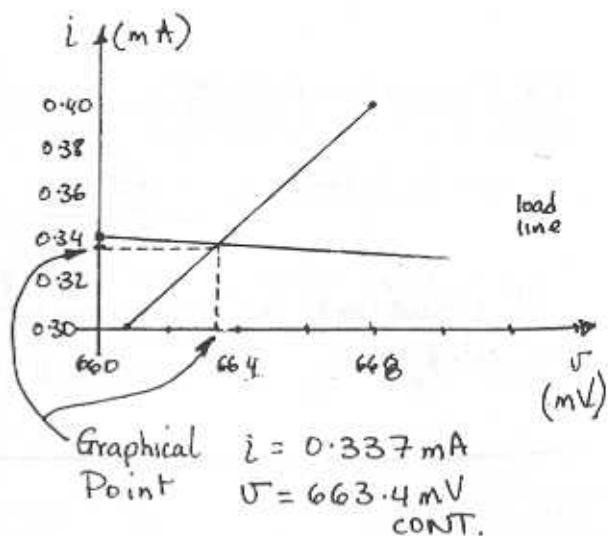
$$V = 670 \text{ mV} \Rightarrow i = 0.33 \text{ mA}$$



Comparing the graphical results to the exponential model gives:


$$\text{At } i = 0.337 \text{ mA} = 10^{-12} e^{v/0.025}$$

$$\Rightarrow v = 663.6 \text{ mV}$$

which is only  $(663.6 - 663.4) = 0.2 \text{ mV}$  greater than the value found graphically!

3.33

Iterative Analysis:

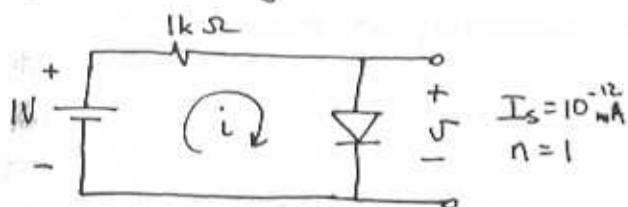

$$\#1 \quad v = 0.7 \text{ V} \quad i = \frac{1 - 0.7}{1} = 0.3 \text{ mA}$$

$$\#2 \quad v = 0.25 \ln \left( \frac{0.3}{10^{-12}} \right) = 0.6607 \text{ V}$$


$$i = \frac{1 - 0.6607}{1} = 0.3393 \text{ mA}$$

$$\#3 \quad v = 0.25 \ln \left( \frac{0.3393}{10^{-12}} \right) = 0.6638 \text{ V}$$

$$i = \frac{1 - 0.6638}{1} = 0.3362$$

$\infty$  i did not change by much stop here.

3.34

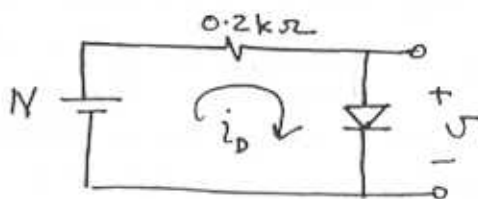

$$(a) \quad i_D = \frac{1 - 0.7}{0.2} = 1.5 \text{ mA}$$

(b) Iterative Analysis given  $v_D = 0.7 \text{ V}$  at  $i_D = 1 \text{ mA}$

$$\#1 \quad v = 0.7 \text{ V} \quad i_D = \frac{1 - 0.7}{0.2} = 1.5 \text{ mA}$$

$$\#2 \quad \because i = I_s e^{v/nV_T} \quad n=2$$

$$\frac{i_2}{i_1} = e^{\frac{v_2 - v_1}{0.05}}$$

$$\text{thus } v_2 = v_1 + 0.05 \ln i_2/i_1$$

$$\therefore \text{ for } i = 1.5 \text{ mA}$$

$$v = 0.7 + 0.05 \ln \frac{1.5}{1} \quad \& \quad i_D = \frac{1 - 0.720}{0.2} = 1.4 \text{ mA}$$

$$= 0.720 \text{ V}$$

#3

$$v = 0.720 + 0.05 \ln \left( \frac{1.4}{1.5} \right) \quad \& \quad i_D = \frac{1 - 0.716}{0.2} = 1.42 \text{ mA}$$


$$= 0.716 \text{ V}$$

#4

$$v = 0.716 + 0.05 \ln \left( \frac{1.42}{1.4} \right) \quad \& \quad i_D = 1.42 \text{ mA}$$

$$= 0.716 \text{ V}$$

3.35

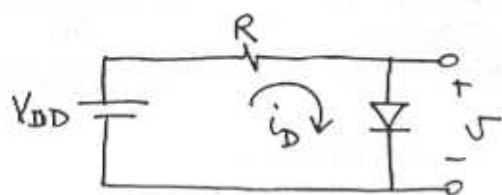

Derivation of iterative equation

$$i_D = I_s e^{V/V_T}$$

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{V_2 - V_1}{nV_T}}$$

$$V_2 = V_1 + nV_T \ln\left(\frac{i_{D2}}{i_{D1}}\right)$$

$$= V_1 + \Delta V \log\left(\frac{i_{D2}}{i_{D1}}\right)$$

(a)  $V = 0.7 \text{ V}$   $i_D = \frac{10 - 0.7}{9.3} = 1 \text{ mA}$

(b)  $V = 0.7 \text{ V}$   $i_D = \frac{3 - 0.7}{2.3} = 1 \text{ mA}$

~ for both these cases the diode is rated at 1mA for 0.7V so stop.

(c)  $V_{DD} = 2 \text{ V}$   $R = 2 \text{ k}\Omega$

#1  $V = 0.7 \text{ V}$   $i_D = \frac{2 - 0.7}{2} = 0.65 \text{ mA}$

#2  $V = 0.7 + 0.1 \log\left(\frac{0.650}{i_D}\right) = 0.581 \text{ V}$

$$i_D = \frac{2 - 0.581}{2} = 0.709 \text{ mA}$$

#3  $V = 0.581 + 0.1 \log\left(\frac{0.709}{0.650}\right)$

$$= 0.584 \text{ V}$$

$$i_D = \frac{2 - 0.584}{2} = 0.708 \text{ mA}$$

(d)  $V_{DD} = 2 \text{ V}$   $R = 2 \text{ k}\Omega$

#1  $V = 0.7 \text{ V}$   $i_D = \frac{2 - 0.7}{2}$

$$= 0.650 \text{ mA}$$

#2.

$$V = 0.7 + 0.1 \log\left(\frac{0.650}{i_D}\right) \quad i_D = \frac{2 - 0.681}{2}$$

$$= 0.681 \text{ V} \quad = 0.659 \text{ mA}$$

#3

$$V = 0.681 + 0.1 \log\left(\frac{0.659}{i_D}\right) \quad i_D = \frac{2 - 0.682}{2}$$

$$= 0.682 \text{ V} \quad = 0.659 \text{ mA}$$

(e)  $V_{DD} = 1 \text{ V}$   $R = 0.3 \text{ k}\Omega$

#1  $V = 0.7 \text{ V}$   $i_D = \frac{1 - 0.7}{0.3} = 1 \text{ mA}$

#2

$$V = 0.7 + 0.1 \log\left(\frac{1}{i_D}\right) \quad i_D = \frac{1 - 0.6}{0.3} = 1.333 \text{ mA}$$

$$= 0.6 \text{ V}$$

#3

$$V = 0.6 + 0.1 \log\left(\frac{1.333}{i_D}\right) \quad i_D = \frac{1 - 0.612}{0.3} = 1.293 \text{ mA}$$

$$= 0.612 \text{ V}$$

#4

$$V = 0.612 + 0.1 \log\left(\frac{1.293}{i_D}\right) \quad i_D = \frac{1 - 0.611}{0.3} = 1.297 \text{ mA}$$

$$= 0.611 \text{ V}$$

#5

$$V = 0.611 + 0.1 \log\left(\frac{1.297}{i_D}\right) \quad i_D = 1.297 \text{ mA}$$

$$= 0.611 \text{ V}$$

(f)  $V_{DD} = 1 \text{ V}$   $R = 0.3 \text{ k}\Omega$

#1  $V = 0.7 \text{ V}$   $i_D = \frac{1 - 0.7}{0.3} = 1 \text{ mA}$

CONST.

#2  

$$V = 0.7 + 0.06 \log \frac{1}{10} \quad i_D = \frac{1 - 0.640}{0.3}$$

$$= 0.640 \text{ V} \quad = 1.2 \text{ mA}$$

#3  

$$V = 0.6 + 0.06 \log \frac{1.2}{1} \quad i_D = \frac{1 - 0.645}{0.3}$$

$$= 0.645 \text{ V} \quad = 1.183 \text{ mA}$$

#4  

$$V = 0.6 + 0.06 \log \frac{1.183}{1.2} \quad i_D = 1.183 \text{ mA}$$

$$= 0.645 \text{ V}$$

(9)  $V_{DD} = 1\text{V} \quad R = 0.3 \text{ k}\Omega$

#1  $V = 0.7 \quad i_D = \frac{1 - 0.7}{0.3} = 1 \text{ mA}$

#2  

$$V = 0.7 + 0.12 \log \frac{1}{10} \quad i_D = \frac{1 - 0.580}{0.3}$$

$$= 0.580 \text{ V} \quad = 1.381 \text{ mA}$$

#3  

$$V = 0.580 + 0.12 \log \frac{1.381}{1} \quad i_D = \frac{1 - 0.597}{0.3}$$

$$= 0.597 \text{ V} \quad = 1.343 \text{ mA}$$

#4  

$$V = 0.597 + 0.12 \log \frac{1.343}{1.381} \quad i_D = \frac{1 - 0.596}{0.3}$$

$$= 0.596 \text{ V} \quad = 1.347 \text{ mA}$$

#5  

$$V = 0.596 + 0.12 \log \frac{1.347}{1.343} \quad i_D = 1.347 \text{ mA}$$

$$= 0.596 \text{ V}$$

(h)  $V_{DD} = 0.5 \text{ V} \quad R = 30 \text{ k}\Omega$

#1 let  $V = 0.4 \text{ V} \quad i_D = \frac{0.5 - 0.4}{30}$   

$$= 3.333 \mu\text{A}$$

#2  

$$V = 0.7 + 0.1 \log \frac{3.333 \times 10^{-3}}{10} \quad i_D = \frac{0.5 - 0.352}{30}$$

$$= 0.352 \text{ V} \quad = 4.933 \mu\text{A}$$

#3  

$$V = 0.352 + 0.1 \log \frac{4.933}{3.333} \quad i_D = \frac{0.5 - 0.369}{30}$$

$$= 0.369 \text{ V} \quad = 4.367 \mu\text{A}$$

#4  

$$V = 0.369 + 0.1 \log \frac{4.367}{4.933} \quad i_D = \frac{0.5 - 0.364}{30}$$

$$= 0.364 \text{ V} \quad = 4.533 \mu\text{A}$$

#5  

$$V = 0.364 + 0.1 \log \left( \frac{4.533}{4.367} \right) \quad i_D = \frac{0.5 - 0.366}{30}$$

$$= 0.366 \text{ V} \quad = 4.467 \mu\text{A}$$

#6  

$$V = 0.366 + 0.1 \log \frac{4.467}{4.533} \quad i_D = \frac{0.5 - 0.365}{30}$$


$$= 0.365 \text{ V} \quad = 4.5 \mu\text{A}$$

#7  

$$V = 0.365 + 0.1 \log \frac{4.5}{4.467}$$

$$= 0.365 \text{ V} \quad i_D = 4.5 \mu\text{A}$$

3.36

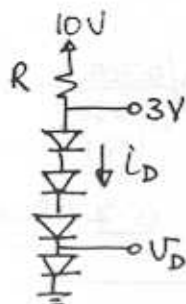

$$V_D = \frac{3}{4} = 0.75 \text{ V}$$

$$i_D = I_s e^{V_D / nV_T}$$

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{V_{D2} - V_{D1}}{nV_T}}$$


CONST.

$$\begin{aligned} \therefore i_D = i_{D2} = i_{D1} e^{\frac{V_{D2} - V_{D1}}{nV_T}} \\ = 1 \times e^{\frac{0.75 - 0.7}{1 \times 0.025}} \\ = 7.389 \text{ mA} \end{aligned}$$

$$\therefore R = \frac{10 - 3}{i_D} = \frac{10 - 3}{7.389} = \underline{\underline{0.947 \text{ k}\Omega}}$$

3.37

Piecewise linear model:

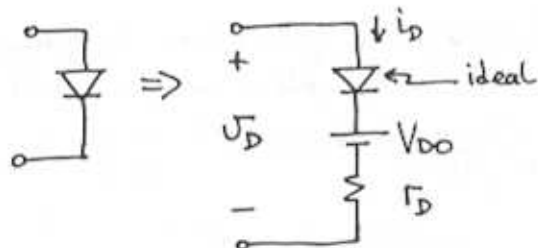

Given  $n=2$ ,  $V_D = 0.7 \text{ V}$ ,  $i_D = 1 \text{ mA}$

The current through the diode is given by:

$$i_D = \frac{V_D - V_{D0}}{R_D} \quad \sim \text{need to find the parameters } V_{D0} \text{ and } R_D$$

Using the exponential model to find the diode voltage at  $10 \text{ mA}$

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{V_{D2} - V_{D1}}{nV_T}}$$

$$\begin{aligned} V_{D2} &= nV_T \ln\left(\frac{i_{D2}}{i_{D1}}\right) = 0.05 \ln\left(\frac{10}{1}\right) \\ &= 0.815 \text{ V} \end{aligned}$$

FINDING  $V_{D0}$  &  $R_D$  using the given facts:

$$i_D = \frac{0.7 - V_{D0}}{R_D} = 1 \text{ mA} \quad (1)$$

$$i_D = \frac{0.815 - V_{D0}}{R_D} = 10 \text{ mA} \quad (2)$$

$$\frac{(2)}{(1)} \Rightarrow \frac{0.815 - V_{D0}}{0.7 - V_{D0}} = 10$$

$$V_{D0} = \underline{\underline{0.687 \text{ V}}}$$

$$R_D = \frac{0.7 - V_{D0}}{1} = \underline{\underline{12.8 \Omega}}$$

Using the piecewise linear model

$$i_D = \frac{V_D - 0.687}{12.8} \Rightarrow V_D = 0.687 + 12.8 i_D$$

Using the exponential model

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{V_{D2} - 0.7}{0.05}} \Rightarrow V_D = 0.7 + 0.05 \ln\left(\frac{i_{D2}}{1}\right)$$

| $i_D$<br>(mA) | PIECEWISE<br>LINEAR<br>$V_D$ (V) | EXPONENTIAL<br>$V_D$ (V) | Error<br>(mV) |
|---------------|----------------------------------|--------------------------|---------------|
| 0.5           | 0.693                            | 0.655                    | 28            |
| 5             | 0.751                            | 0.780                    | -29.5         |
| 14            | 0.866                            | 0.832                    | 34            |

3.38

Looking at the copy of Fig 3.12 below, we see at

$$i_D = 1 \text{ mA} \rightarrow V_D = 0.7 \text{ V}$$

$$i_D = 10 \text{ mA} \rightarrow V_D = 0.8 \text{ V}$$


$$\therefore \text{slope} = \frac{1}{R_D} = \frac{10 - 1}{0.8 - 0.7} = 90 \frac{\text{mA}}{\text{V}}$$

$$\therefore R_D = \frac{1}{90 \times 10^{-3}} = \underline{\underline{11.15 \Omega}}$$

To find  $V_{D0}$ :

$$I_D = \frac{V_D - V_{D0}}{r_D}$$
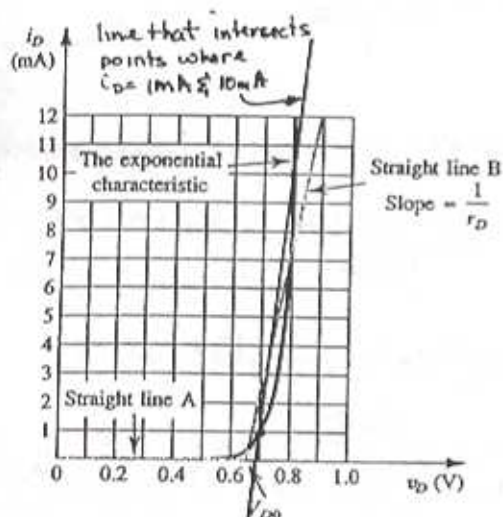
$$10^{-3} = \frac{0.7 - V_{D0}}{11.1} \Rightarrow V_{D0} = \underline{\underline{0.689V}}$$



(a) The load line intersects the exponential model at:

$$V_D = \underline{\underline{0.73V}} \quad I_D = \underline{\underline{1.7mA}}$$

(b) The load line intersects the straight-line model at

$$V_D = \underline{\underline{0.7V}} \quad I_D = \underline{\underline{2mA}}$$

3.40

Calculating the parameters  $r_D$  &  $V_{D0}$  for the battery plus resistor model


$$I_D = I_S e^{V_D / nV_T} \quad n=1$$

$$\text{For } I_D = 0.1 I_D$$

$$V_{D2} = 0.7 + 0.025 \ln(0.1) = \underline{\underline{0.642V}}$$

$$\text{For } I_D = 10 I_D$$
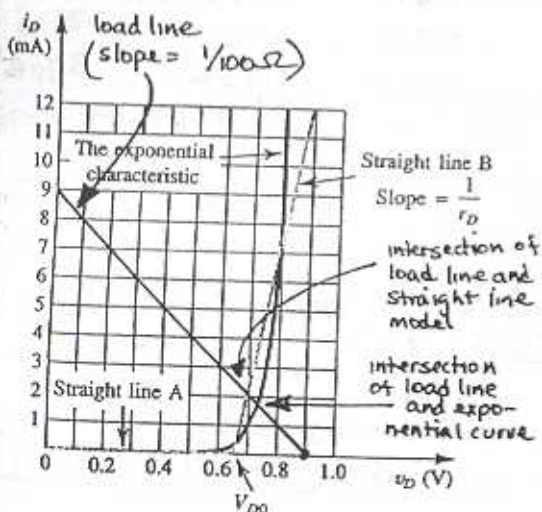
$$V_{D3} = 0.7 + 0.025 \ln(10) = \underline{\underline{0.758V}}$$



Note that since the specifications for all of the diodes are given for 0.7V, the end voltages are the same as the voltage change for relative currents are independent to  $I_D$  &  $I_S$ .

$$\circ \circ \quad V_{D2} = V_{D0} + I_{D2} r_D \quad (1)$$

$$V_{D3} = V_{D0} + I_{D3} r_D \quad (2)$$

$$(2) \rightarrow (1)$$

$$V_{D3} - V_{D2} = (I_{D3} - I_{D2}) r_D$$

CONT.

$$0.758 - 0.642 = (0.1 I_D - 0.1 I_D) r_D$$

$$0.166 = 9.9 I_D r_D$$

$$r_D = \frac{0.0117}{I_D} \quad (3)$$

$$\text{for (a) } I_D = 1 \text{ mA} \quad r_D = \frac{0.0117}{1} = 11.7 \Omega$$

$$(b) I_D = 1 \text{ A} \quad r_D = \frac{0.0117}{1} = 0.0117 \Omega$$

$$(c) I_D = 10 \mu\text{A} \quad r_D = \frac{0.0117}{10 \mu\text{A}} = 1.17 \text{ k}\Omega$$

(3)  $\rightarrow$  (1)

$$0.642 = V_{D0} + 0.1 I_D \times \frac{0.0117}{I_D}$$

$$= V_{D0} + 0.00117$$

$$V_{D0} = 0.641 \text{ V} \quad \leftarrow \text{same for all diodes}$$

3.41

Since for a current of 10 mA, the diode voltage is 0.8 V, this would be a suitable choice for the constant-voltage-drop model.

3.42

Constant Voltage drop Model:

$$\text{Using } V_D = 0.7 \text{ V} \Rightarrow I_{D1} = \frac{V - 0.7}{R}$$

$$\text{Using } V_D = 0.6 \text{ V} \Rightarrow I_{D2} = \frac{V - 0.6}{R}$$

For the difference in currents to vary by only 1%  $\Rightarrow$

$$I_{D2} = 1.01 I_{D1}$$

$$V - 0.6 = 1.01 (V - 0.7)$$

$$V = 1.0 \text{ V}$$

$$\text{For } V = 2 \text{ V} \quad R = 1 \text{ k}\Omega$$

$$\text{At } V_D = 0.7 \text{ V} \quad I_{D1} = \frac{2 - 0.7}{1} = 1.3 \text{ mA}$$


$$V_D = 0.6 \text{ V} \quad I_{D2} = \frac{2 - 0.6}{1} = 1.4 \text{ mA}$$

$$\frac{I_{D2}}{I_{D1}} = \frac{1.4}{1.3} = 1.08$$

Thus the percentage difference is 8%

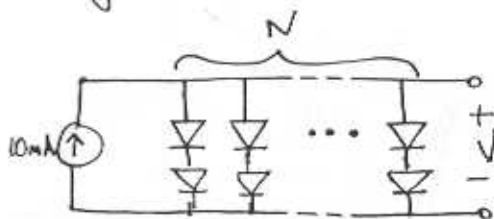3.43

Since  $2 V_D = 1.4 \text{ V}$  is close to the required  $1.25 \text{ V}$ , use  $N$  parallel pairs of diodes to split the current evenly.




$$V = 2 \left[ 0.7 + 0.1 \log \frac{10/N}{20} \right] = 1.25 \text{ V}$$

$$N = 2.8 \Rightarrow \text{Use } \underline{\underline{3 \text{ sets of diodes}}}$$

$$V = 2 \left( 0.7 + 0.1 \log \frac{10/3}{20} \right) = \underline{\underline{1.244 \text{ V}}}$$

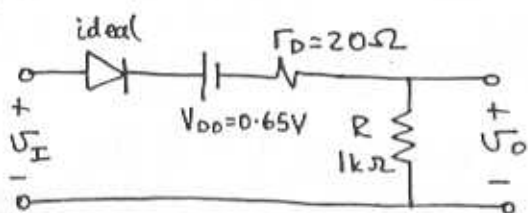3.44

Piecewise linear model in a half-wave rectifier.





$$U_O = \frac{U_I - V_{D0}}{R_D + R} R, \text{ for } U_I \gg V_{D0}$$

$$\text{Thus, } U_O = 0.98(U_I - 0.65) \text{ for } U_I \gg 0.65$$



$$U_O = 0 \text{ for } U_I < 0.65V$$

Sketch of transfer characteristic :-

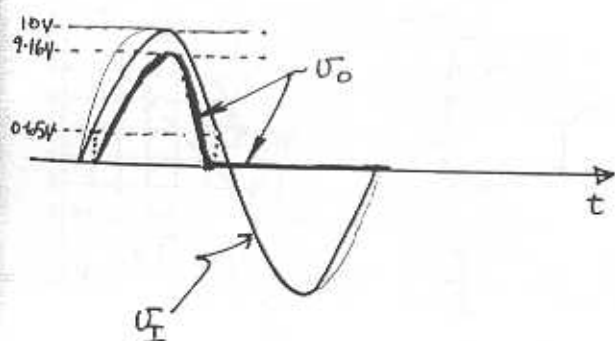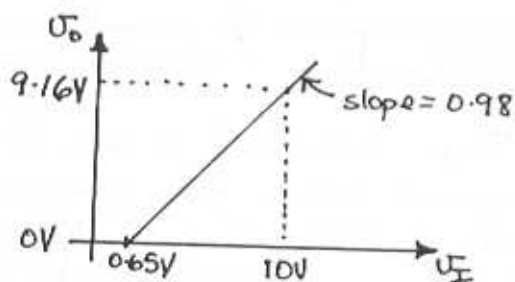

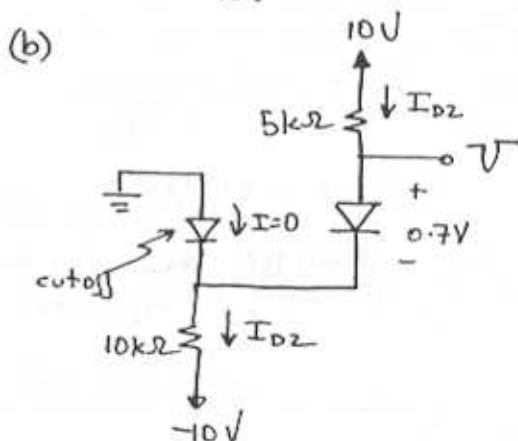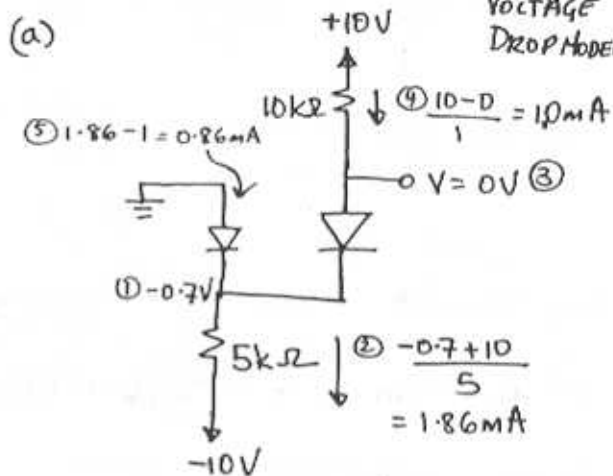3.45


Refer to example 3-2 ~ CONSTANT VOLTAGE DROP MODEL






$$I_{D2} = \frac{10 - (-10) - 0.7}{15} = 1.29mA$$



$$V = -10 + 1.29(10) + 0.7 = \underline{\underline{3.6V}}$$

3.46


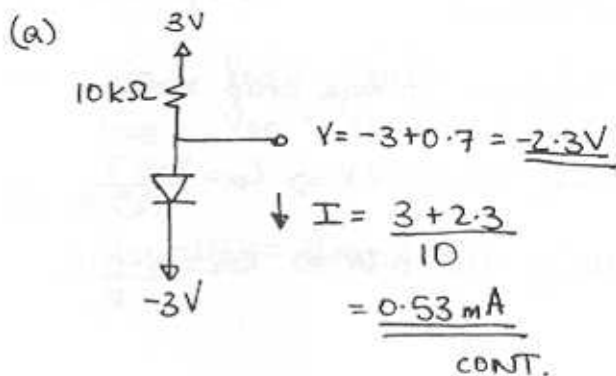


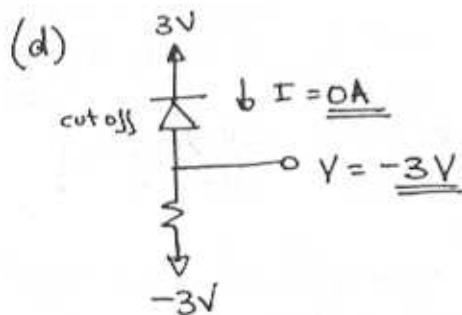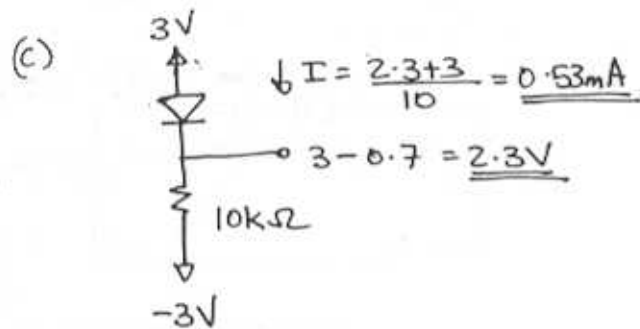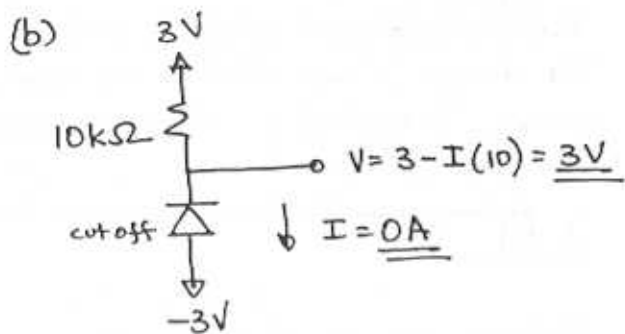


3.47

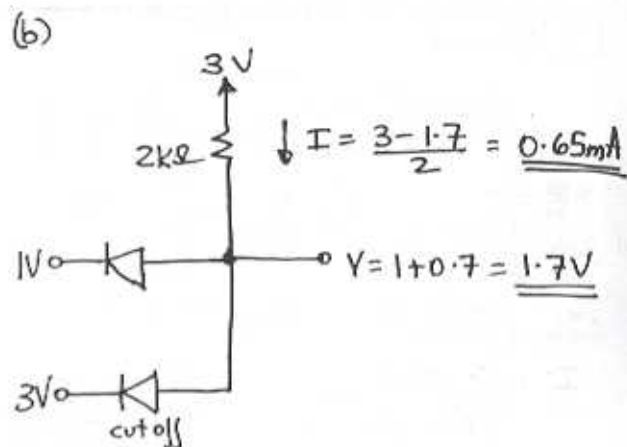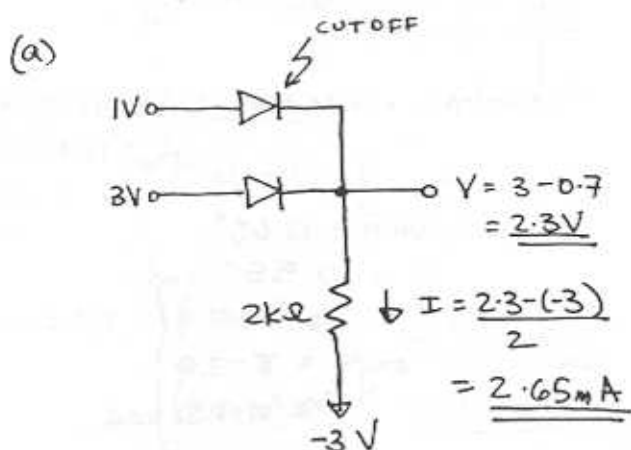

3.48

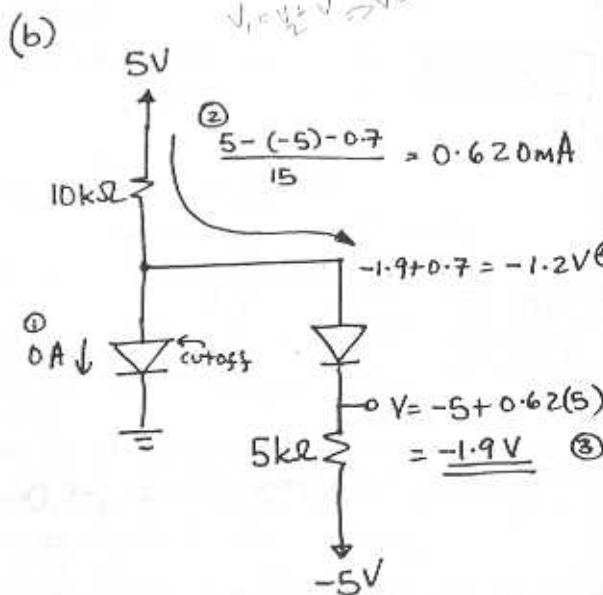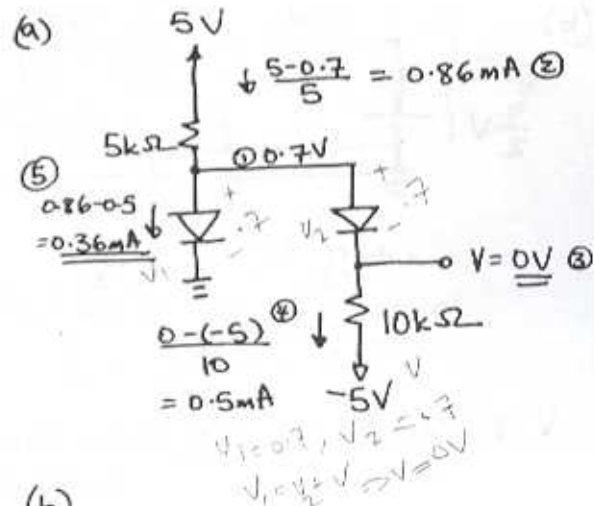


3.49

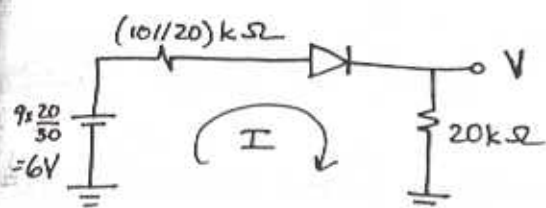

$$I = \frac{6 - 0.7}{(10||20) + 20} = \underline{0.199 \text{ mA}}$$

$$V = 20I = \underline{3.98 \text{ V}}$$

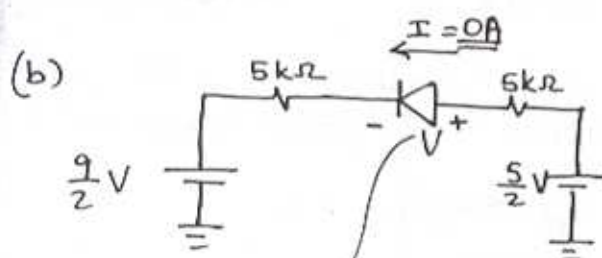


cutoff  $\therefore \frac{5}{2} < \frac{9}{2}$

$$\therefore I = \underline{0 \text{ A}}$$

$$V = \frac{9}{2} - \frac{5}{2} = \underline{-2 \text{ V}}$$

3.50

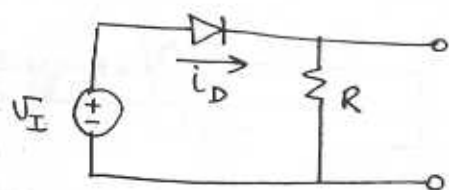


$$i_{D, \text{peak}} = \frac{V_{I, \text{peak}} - 0.7}{R} \leq 50$$

$$R \gg \frac{120\sqrt{2} - 0.7}{50} = \underline{3.38 \text{ k}\Omega}$$

Reverse voltage =  $120\sqrt{2} = 169.7 \text{ V}$ .  
The design is essentially the same since the supply voltage  $\gg 0.7 \text{ V}$


3.51

Battery plus resistance model

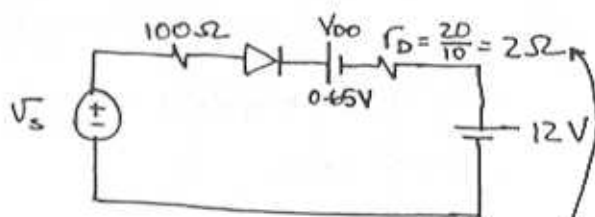

since the diode has 10x the area  $r_D$  is  $1/10$  as big.
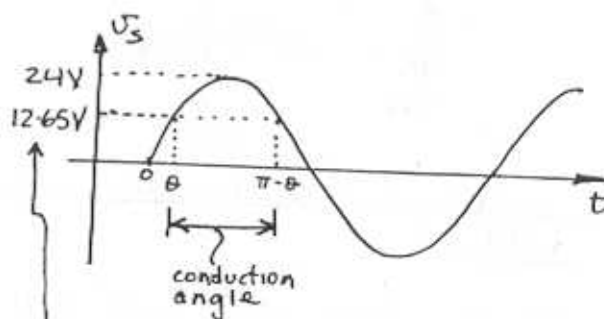
$$i_D = I_S e^{V/nV_T} = \frac{V_S - V_{D0} - 12}{100 + 2}$$



Conduction starts when  $V_S > 12 + V_{D0}$   
 $V_S > 12.65 \text{ V}$

$$\therefore 24 \sin \theta = 12.65^\circ$$

$$\theta = 0.555 \text{ rad}$$

$$\text{Conduction angle} = \pi - 2\theta$$

$$= 2.031 \text{ rad.}$$

$$\text{Fraction of cycle for conduction} = \frac{2.031}{2\pi} = \underline{0.323}$$

CONT.

$$i_{D, \text{peak}} = \frac{24 - 12.65}{100 + 2} = \underline{\underline{0.111 \text{ A}}}$$

Maximum reverse voltage occurs across the diode when  $V_s$  is at its negative peak and is equal to:

$$24 + 12 = \underline{\underline{36 \text{ V}}}$$

3.52

Using the exponential model

$$i_D = I_s e^{DV/nV_T}$$

FOR A +10mV CHANGE

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{\Delta V/nV_T}{0.025}} = e^{0.01/n(0.025)}$$

$$= \begin{cases} 1.492 & \sim n=1 \\ 1.221 & \sim n=2 \end{cases}$$

$$\% \text{ CHANGE} = \frac{i_{D2} - i_{D1}}{i_{D1}} \times 100$$

$$= \begin{cases} (1.492 - 1) \times 100 = \underline{\underline{+49.2\%}} & n=1 \\ (1.221 - 1) \times 100 = \underline{\underline{22.1\%}} & n=2 \end{cases}$$

FOR A -10mV CHANGE

$$\frac{i_{D2}}{i_{D1}} = 10^{-0.01/n(0.025)} = \begin{cases} 0.670 & n=1 \\ 0.819 & n=2 \end{cases}$$


$$\% \text{ CHANGE} = \begin{cases} (0.670 - 1) \times 100 = \underline{\underline{-33\%}} & n=1 \\ (0.819 - 1) \times 100 = \underline{\underline{-18\%}} & n=2 \end{cases}$$

For a current change limited to  $\pm 10\%$

$$\frac{i_{D2}}{i_{D1}} = e^{\frac{\Delta V/n \times 0.025}{0.025}} = 0.9 \text{ to } 1.1$$

$$\Delta V = \begin{cases} -2.634 \text{ mV to } 2.383 \text{ mV} & n=1 \\ -5.268 \text{ mV to } 4.766 \text{ mV} & n=2 \end{cases}$$

3.53

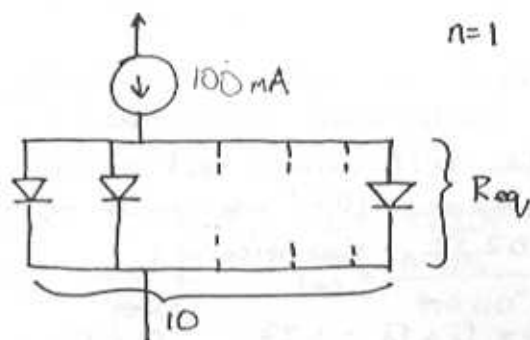

Each diode has the current

$$i_D = \frac{0.1}{10} = 0.01 \text{ A}$$

Each diode has a small-signal resistance

$$r_d = \frac{nV_T}{I_D} = \frac{0.025}{0.01} = \underline{\underline{2.5 \Omega}}$$

$$R_{eq} = r_d/10 = \underline{\underline{0.25 \Omega}}$$

For one diode conducting 0.1 A

$$r_d = nV_T/0.1 = \frac{0.025}{0.1} = \underline{\underline{0.25 \Omega}}$$

This is the same as  $R_{eq}$ . We can think of the parallel connection as equivalent to a single diode having 10 times the junction area of each diode. This large diode

is fed with  $10\times$  the current (or  $0.1A$ ) and this exhibits the same small-signal resistance as 10 parallel smaller diodes.

Now consider the series resistance of  $0.2\Omega$  to connect a diode.  
For the parallel combination above:

$$R_{eq} = \frac{1}{10} (0.2 + 2.5) = 0.27\Omega$$


To have an equivalent resistance, the single diode conducting all of the  $0.1A$  would need a series resistance  $10\times$  as small or  $0.02\Omega$ . Specifically:

$$r_{out} = r_s + r_d = 0.27$$

$$= r_s + \frac{nV_T}{I_D} = 0.27$$

$$= r_s + 0.25 = 0.27$$
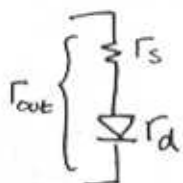
$$r_s = 0.27 - 0.25 = \underline{\underline{0.02\Omega}}$$



$$r_d = \frac{nV_T}{I}$$

$$n=2$$

Now:

$$V_o = V_s \frac{r_d}{r_d + R_s}$$

$$= V_s \frac{\frac{nV_T}{I}}{\frac{nV_T}{I} + R_s} = V_s \frac{nV_T}{nV_T + IR_s}$$

Q.E.D.

$$V_o = 10mV \frac{0.05}{0.05 + 10^3 I}$$

$$= \begin{cases} 0.476 mV & \sim I = 1mA \\ 3.333 mV & \sim I = 0.1mA \\ 9.804 mV & \sim I = 1\mu A \end{cases}$$

$$\text{For } V_o = \frac{1}{2} V_s = V_s \times \frac{0.05}{0.05 + 10^3 I}$$

$$I = \underline{\underline{50\mu A}}$$

3.55

$R_s = 10k\Omega$ ,  $n=1$ , a  $1mA$  diode

$$V_o/V_i = \frac{0.025}{0.025 + R_s I}$$


$$= \frac{0.025}{0.025 + 10^4 I} \quad (1)$$

For the current change limited to  $\pm 10\%$  of  $I$  & using the exponential model we get

$$\frac{i_{D2}}{i_{D1}} = e^{\Delta V/nV_T} = 0.9 \text{ to } 1.1$$

CONT.

3.54

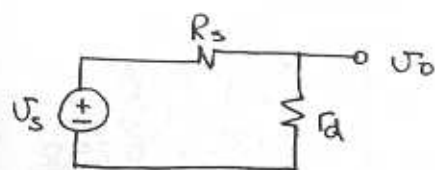

SMALL  
SIGNAL  
EQUIVALENT  
CIRCUIT

To find the small-signal response,  $V_o$ , open the dc current source  $I$ , and short the capacitors  $C_1$  and  $C_2$ . Also replace the diode with its small signal resistance:

$$\Delta V = \underline{\underline{-2.63 \text{ mV to } 2.38 \text{ mV}}}$$


This is the amount the output will vary for a 10% change in diode current. Divide this by the specific gains given in the problem to find the limit on the input signal.

$$\Delta V_s = \frac{\Delta V_o}{V_o/V_i}$$

$$= \frac{-2.63 \text{ mV}}{\Delta V_o/V_i} \text{ to } \frac{2.38 \text{ mV}}{V_o/V_i} \text{ (2)}$$

| $V_o/V_i$ | $I_{\text{use}} \text{ (mA)} \text{ (1)}$ | $V_s \text{ (using (2)) (mV)}$ |
|-----------|-------------------------------------------|--------------------------------|
| 0.5       | 0.0025                                    | 5.26 to 4.76                   |
| 0.1       | 0.0225                                    | 26.3 to 23.8                   |
| 0.01      | 0.25                                      | 263 to 238                     |
| 0.001     | 2.5                                       | 2630 to 2380                   |

3.56

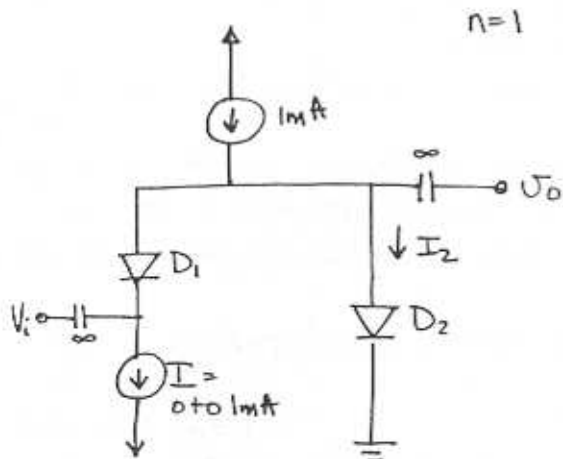

small signal model when  $D_1$  &  $D_2$  are conducting



(a)  $I = 0 \mu\text{A}$

$D_1$  - cutoff  $\Rightarrow \frac{V_o}{V_i} = 0 \text{ V/V}$   
 $I_2 = 1 \text{ mA}$

(b)  $I = 1 \mu\text{A}$   $I_2 = 999 \mu\text{A}$

$$r_{d1} = \frac{nV_T}{I} \quad r_{d2} = \frac{0.025}{999 \times 10^{-6}}$$

$$= \frac{0.025}{I} \quad = 25.025 \Omega$$

$$= 25 \Omega$$

$$\frac{V_o}{V_i} = \frac{r_{d2}}{r_{d1} + r_{d2}} = \underline{\underline{0.001 \text{ V/V}}}$$

(c)  $I = 10 \mu\text{A}$   $I_2 = 990 \mu\text{A}$

$$r_{d1} = \frac{0.025}{10 \times 10^{-6}} \quad r_{d2} = \frac{0.025}{990 \times 10^{-6}}$$

$$= 2.5 \text{ k}\Omega \quad = 25.25 \Omega$$

$$V_o/V_i = \underline{\underline{0.01 \text{ V/V}}}$$

(d)  $I = 100 \mu\text{A}$

$I_2 = 900 \mu\text{A}$

$$r_{d1} = \frac{0.025}{100 \times 10^{-6}} \quad r_{d2} = \frac{0.025}{900 \times 10^{-6}}$$

$$= 250 \Omega \quad = 27.78 \Omega$$

$$\frac{V_o}{V_i} = \underline{\underline{0.1 \text{ V/V}}}$$

(e)  $I = 500 \mu\text{A}$

$I_2 = 500 \mu\text{A}$

$$r_{d1} = r_{d2} = \frac{0.025}{500 \times 10^{-6}} = 50 \Omega$$

$$\frac{V_o}{V_i} = \underline{\underline{\frac{1}{2} \text{ V/V}}}$$

(f)  $I = 600 \mu\text{A}$

$I_2 = 400 \mu\text{A}$

$$r_{d1} = \frac{0.025}{600 \times 10^{-6}} \quad r_{d2} = \frac{0.025}{400 \times 10^{-6}}$$

$$= 41.67 \Omega \quad = 62.5 \Omega$$

IF THE BIAS CURRENT IN EACH  
DIODE IS  $\geq 10 \mu A$ , THE DIODE RESISTANCE  
WILL BE  $\leq 2.5 k\Omega$ . TO LIMIT THE  
CURRENT SIGNAL TO A MAXIMUM OF 10%,  
BIAS, THE CURRENT SIGNAL MUST BE  
 $1 \mu A$ . THUS, THE SIGNAL VOLTAGE ACROSS  
A "STARVED" DIODE WILL BE  
10 mV WHICH IS APPROXIMATELY THE  
LEVEL TO WHICH THE INPUT SIGNAL  
VOLTAGE SHOULD BE LIMITED.


3.57

$$(a) \frac{v_o}{v_i} = \frac{R}{R + (2r_d // 2r_d)}$$

$$= \frac{R}{R + r_d}$$

WHERE  $r_d = \frac{V_T}{I/2} = \frac{2V_T}{I}$

$$= \frac{0.05V}{I}$$

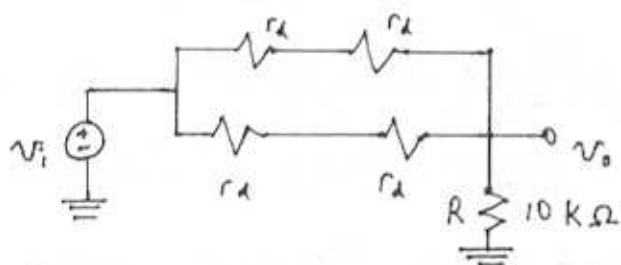

| $I$ (mA)  | $v_o/v_i$ (V/V) |
|-----------|-----------------|
| 0         | 0               |
| $10^{-3}$ | 0.167           |
| 0.01      | 0.667           |
| 0.1       | 0.952           |
| 1.0       | 0.995           |
| 10        | 0.9995          |

(b) IF THE SIGNAL CURRENT IS TO BE LIMITED TO  $\pm 10I$ , THE CHANGE IN DIODE VOLTAGE  $\Delta v_D$  CAN BE FOUND FROM

$$\frac{i_D}{I} = e^{\Delta v_D / nV_T} = 0.9 \text{ TO } 1.1$$

THUS, FOR  $n=1$


$$\Delta v_D = -2.63 \text{ mV TO } +2.38 \text{ mV}$$

OR APPROXIMATELY  $\pm 2.5 \text{ mV}$

CONT.

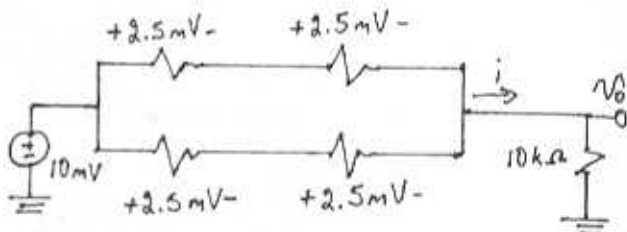3.57 CONT.

(b CONT.) FOR THE DIODE CURRENT TO REMAIN WITHIN  $\pm 10\%$  OF THEIR dc BIAS CURRENTS, THE SIGNAL VOLTAGE ACROSS EACH DIODE MUST BE LIMITED TO  $2.5 \text{ mV}$ . NOW, IF  $v_{i\text{PEAK}} = 10 \text{ mV}$  WE CAN OBTAIN THE FOLLOWING SITUATION



WE SEE THAT  $v_o = 5 \text{ mV}$  AND

$$i = \frac{5 \text{ mV}}{10 \text{ k}\Omega} = 0.5 \mu\text{A}$$

THUS, EACH DIODE IS CARRYING A CURRENT SIGNAL OF  $0.25 \text{ mA}$ . FOR THIS TO BE AT MOST  $10\%$  OF THE dc CURRENT, THE dc CURRENT IN EACH DIODE MUST BE AT LEAST  $2.5 \mu\text{A}$ . IT FOLLOWS THAT THE MINIMUM VALUE OF  $I$  MUST BE  $5 \mu\text{A}$ .

(c) FOR  $I = 1 \text{ mA}$ ,  $I_D = 0.5 \text{ mA}$ , AND FOR MAXIMUM SIGNAL OF  $10\%$ ,  $I_D = 0.05 \text{ mA}$ . THUS  $i_D = 2i_d = 0.1 \text{ mA}$  AND THE CORRESPONDING MAXIMUM  $v_o$  IS  $0.1 \text{ mA} \times 10 \text{ k}\Omega = 1 \text{ V}$ .


THE CORRESPONDING PEAK INPUT CAN BE FOUND BY DIVIDING  $v_o$  BY THE TRANSMISSION FACTOR OF  $0.995$ , THUS

$$v_{i\text{MAX}} = \frac{1 \text{ V}}{0.995} = \underline{\underline{1.005 \text{ V}}}$$

SEE FIGURE.


EACH DIODE HAS  $r_d = 50 \Omega$

3.57 CONT.

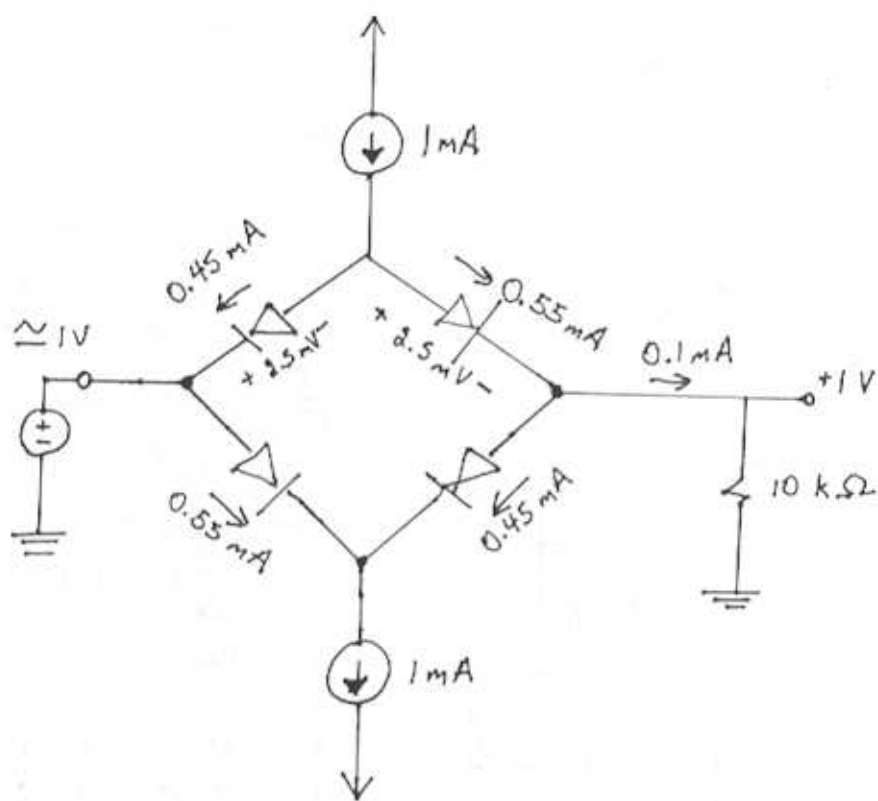

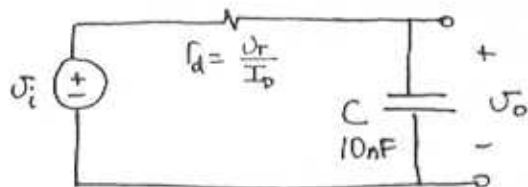3.58

Opening the current source we get the following small-signal circuit:  
( $n=1$ )



$$\frac{V_o}{V_i} = \frac{1/sC}{1/sC + r_d} = \frac{1}{1 + sC r_d}$$

$$\text{Phase Shift} = -\tan^{-1}\left(\frac{\omega C r_d}{1}\right)$$

$$= -\tan^{-1}\left(2\pi \cdot 10^5 \times 10 \times 10^{-9} \times 0.025/I\right)$$

For a phase shift of  $-45^\circ$  we have


$$2\pi \cdot 10^5 \times 10 \times 10^{-9} \times \frac{0.025}{I} = 1$$

$$I = \underline{157 \mu A}$$

Range of phase shift for  $I = 15.7 \mu A$  to  $1570 \mu A$  is :

$$\underline{-84.3^\circ \text{ to } -5.71^\circ}$$

3.59

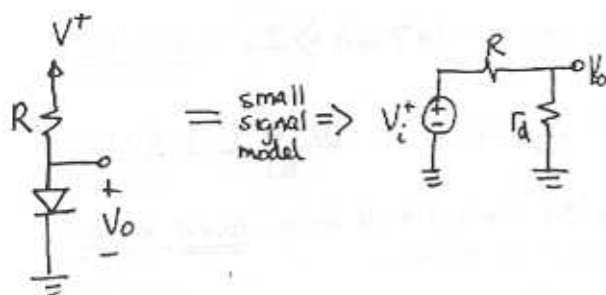

CONT.

$$\begin{aligned}
 (a) \quad \frac{\Delta V_o}{\Delta V^+} &= \frac{r_d}{r_d + R} = \frac{nV_T/I}{nV_T/I + R} \\
 &= \frac{nV_T}{nV_T + IR} \quad \text{where at no load} \\
 &\quad I = \frac{V^+ - 0.7}{R} \\
 &= \frac{nV_T}{nV_T + V^+ - 0.7} \quad \text{Q.E.D.}
 \end{aligned}$$

$$\Delta V_o = -I_L (R \parallel r_d)$$

$$\frac{\Delta V_o}{I_L} = -\frac{1}{\frac{1}{R} + \frac{1}{r_d}} \quad \text{Q.E.D.}$$

$$(b) \text{ Given at DC } I_D = \frac{V^+ - 0.7}{R}$$

$$\text{Also } r_d = \frac{nV_T}{I_D}$$

We have:

$$\frac{\Delta V_o}{I_L} = -\frac{1}{\frac{1}{R} + \frac{1}{r_d}}$$

$$= -\frac{1}{\frac{I_D}{V^+ - 0.7} + \frac{I_D}{nV_T}}$$

$$= -\frac{nV_T}{I_D} \frac{1}{1 + \frac{nV_T}{V^+ - 0.7}}$$

$$= -\frac{nV_T}{I_D} \frac{V^+ - 0.7}{V^+ - 0.7 + nV_T} \quad \text{Q.E.D.}$$

(b) For  $m$  diodes in series use

$$I = \frac{V^+ - m \times 0.7}{R}$$

Thus:

$$\frac{\Delta V_o}{\Delta V^+} = \frac{m r_d}{m r_d + R} = \frac{m(nV_T)}{m(nV_T) + IR}$$


$$= \frac{m(nV_T)}{m(nV_T) + V^+ - 0.7m}$$

(c) Line Regulation for  $V^+ = 10V$ ,  $n=2$

$$i) m=1 \quad \frac{\Delta V_o}{\Delta V^+} = \underline{\underline{5.35 \text{ mV/V}}}$$

$$ii) m=3 \quad \frac{\Delta V_o}{\Delta V^+} = \underline{\underline{18.63 \text{ mV/V}}}$$

3.60

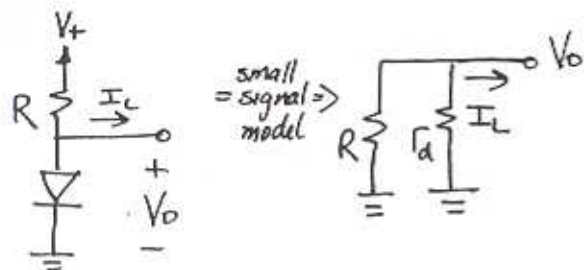

$$I_D \gg 9.947 \text{ mA} \Rightarrow I_D = \underline{\underline{10 \text{ mA}}}$$

$$R = \frac{V^+ - 0.7}{I_D} = \frac{10 - 0.7}{10} = \underline{\underline{930 \Omega}}$$

Thus the diode should be a 10mA diode.

(c) For  $m$  diodes

$$I_D = \frac{V^+ - 0.7m}{R} \quad \& \quad r_d = \frac{m(nV_T)}{I_D}$$

CONST.

$$\frac{\Delta V_o}{I_L} = \frac{-1}{\frac{1}{R} + \frac{1}{Q}}$$


$$= \frac{-1}{\frac{I_D}{V^+ - 0.7m} + \frac{I_D}{mnV_T}}$$

$$= -\frac{mnV_T}{I_D} \frac{1}{\frac{mnV_T}{V^+ - 0.7m} + 1}$$

$$= \underline{\underline{-\frac{mnV_T}{I_D} \frac{V^+ - 0.7m}{V^+ - 0.7m + mnV_T}}}$$

3.61

3.62

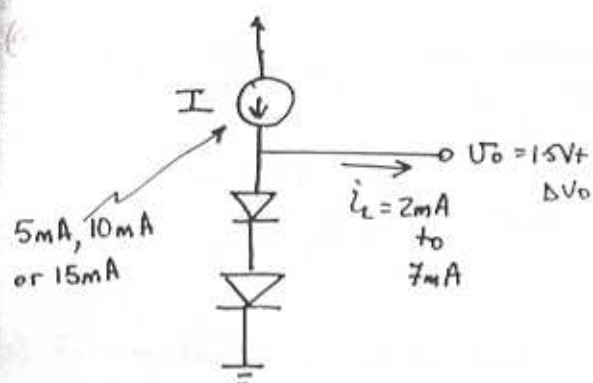

For a load current of 2 to 7 mA,  $I$  must be greater than 7 mA. Thus the 5 mA source would not do.

We are left to choose between the 10 and 15 mA sources. The 15 mA source provides lower load regulation because the diodes will have more current flowing through them at all times. This is shown below:

Load Regulation if  $I = 10$  mA

$$\text{use } \frac{I_{D2}}{I_{D1}} = e^{\frac{\Delta V}{2 \times n V_T}} \quad \text{2 diodes}$$

$$\text{so } e^{\frac{\Delta V}{0.05 \times 2}} = \frac{3}{10} \text{ to } \frac{8}{10}$$

$$\Delta V_O = -120 \text{ mV to } -22.3 \text{ mV}$$

∴ The peak to peak ripple is  $-120 - (-22.3) \approx -100 \text{ mV}$

$$\text{Load Regulation} = \frac{\Delta V_O}{I_L} = \frac{-100}{5}$$

$$= -20 \frac{\text{mV}}{\text{mA}}$$

Load Regulation for  $I = 15$  mA.


Here the current through the diodes change from 8 to 13 mA corresponding to

$$\Delta V_O = 0.1 \ln(8/13) = -49 \text{ mV}$$

$$\text{Load Regulation} = \frac{-49}{5} \approx -10 \frac{\text{mV}}{\text{mA}}$$

The obvious disadvantage of using the 15 mA supply is the requirement of higher current and higher power dissipation.

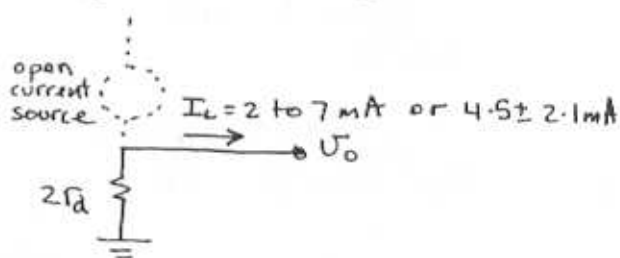Alternate solution of Line Regulation using the small signal model



$$\text{Load Regulation} = \frac{\Delta V_O}{I_L} = -2r_d = -\frac{2nV_T}{I_D}$$

Where the bias current  $I_D = 10 - 4.5$  for the 10 mA source.


$$\Rightarrow \frac{\Delta V_O}{I_L} = \frac{-2 \times 2 \times 0.025}{10 - 4.5} = -18.2 \frac{\text{mV}}{\text{mA}}$$

For 15 mA source  $I_D = 15 - 4.5$

$$\frac{\Delta V_O}{\Delta I_L} = \frac{-0.1}{15 - 4.5} = -9.5 \frac{\text{mV}}{\text{mA}}$$

CONT.

Sketch of output:-

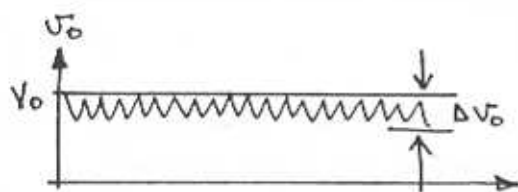

3.63

3.64

$$\begin{aligned} (a) \quad V_z &= V_{z0} + r_z I_{zT} \\ 10 &= 9.6 + r_z \times 50 \times 10^{-3} \\ r_z &= \underline{8 \Omega} \end{aligned}$$

Power rating:

$$\begin{aligned} V_z &= V_{z0} + r_z \times 2I_{zT} \\ &= 9.6 + 8 \times 100 \times 10^{-3} \\ &= 10.4 \text{ V} \end{aligned}$$

$$P = 10.4 \times 100 \times 10^{-3} = \underline{1.04 \text{ W}}$$

$$\begin{aligned} (b) \quad V_z &= V_{z0} + r_z I_{zT} \\ 9.1 &= V_{z0} + 30 \times 10 \times 10^{-3} \\ V_{z0} &= \underline{8.8 \text{ V}} \end{aligned}$$

$$\begin{aligned} V_z &= 8.8 + 30 \times 20 \times 10^{-3} = 9.4 \text{ V} \\ P &= 9.4 \times 20 \times 10^{-3} = \underline{188 \text{ mW}} \end{aligned}$$

$$\begin{aligned} (c) \quad 6.8 &= 6.6 + 2 \times I_{zT} \\ I_{zT} &= \underline{100 \text{ mA}} \end{aligned}$$

$$\begin{aligned} V_z &= 6.6 + 2 \times 200 \times 10^{-3} = 7 \text{ V} \\ P &= 7 \times 200 \times 10^{-3} = \underline{1.4 \text{ W}} \end{aligned}$$

$$\begin{aligned} (d) \quad 18 &= 17.2 + r_z \times 5 \times 10^{-3} \\ r_z &= \underline{160 \Omega} \end{aligned}$$

$$\begin{aligned} V_z &= 17.2 + 160 \times 10 \times 10^{-3} = 18.8 \text{ V} \\ P &= 18.8 \times 10 \times 10^{-3} = \underline{188 \text{ mW}} \end{aligned}$$

$$\begin{aligned} (e) \quad 7.6 &= V_{z0} + 1.5 \times 200 \times 10^{-3} \\ V_{z0} &= \underline{7.2 \text{ V}} \end{aligned}$$

$$\begin{aligned} V_z &= 7.2 + 1.5 \times 400 \times 10^{-3} = 7.8 \text{ V} \\ P &= 7.8 \times 400 \times 10^{-3} = \underline{3.12 \text{ W}} \end{aligned}$$

3.65

(a) Three 6.8 V zeners provide  $3 \times 6.8 = 20.4 \text{ V}$  with  $3 \times 10 = 30 \Omega$  resistance. Neglecting  $R$ , we have


$$\text{Load Regulation} = \underline{-30 \text{ mV/mA}}$$

(b) For 5.1 V zeners we use 4 diodes to provide 20.4 V with  $4 \times 30 = 120 \Omega$  resistance.

$$\text{Load regulation} = \underline{-120 \text{ mV/mA}}$$

3.66

Small signal model for line regulation:

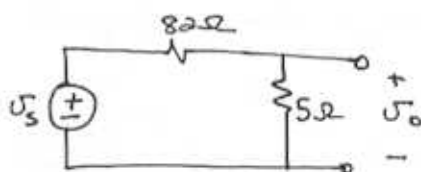

$$\frac{\Delta V_o}{\Delta V_s} = \frac{5}{5 + 82}$$

$$\Delta V_o = \frac{5}{87} \times \Delta V_s$$

$$= \frac{5}{87} \times 1.3$$

$$= \underline{74.7 \text{ mV}}$$

3.67

$$V_Z = V_{Z0} + r_Z I_{ZT}$$

$$9.1 = V_{Z0} + 5 \times 28 \times 10^{-3}$$

$$V_{Z0} = 8.96V$$

$$V_Z = V_{Z0} + 5I_Z = 8.96 + 5I_Z$$

$$\text{For } I_Z = 10\text{mA} \quad V_Z = \underline{\underline{9.01V}}$$

$$\text{For } I_Z = 100\text{mA} \quad V_Z = \underline{\underline{9.46V}}$$

3.68

$$r_z = 30 \Omega$$

$$I_{ZK} = 0.5 \text{ mA}$$

$$V_Z = 7.5 \text{ V}$$

$$I_Z = 12 \text{ mA}$$

$$7.5 = V_{Z0} + 12 \times 30 \times 10^{-3}$$

$$\Rightarrow V_{Z0} = 7.14 \text{ V}$$


$$I_Z = \frac{7.5}{1.2} = 6.25 \text{ mA}$$

SELECT  $I = 10 \text{ mA}$

SO THAT  $I_Z = 3.7 \text{ mA}$

WHICH IS  $> I_{ZK}$
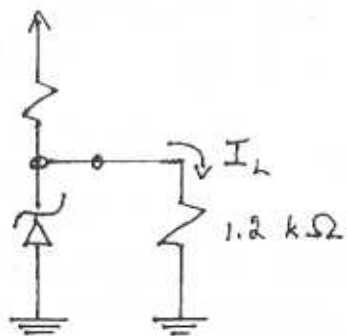
$$R = \frac{10 - 7.5}{10} = \underline{\underline{250 \Omega}}$$



For  $\Delta V^+ = \pm 1 \text{ V}$



$$\Delta V_o = \pm 1 \times \frac{1.2 // 0.03}{0.250 + (1.2 // 0.03)}$$

$$= \pm 0.1 \text{ V}$$

THUS  $V_o = +7.4 \text{ V TO } +7.6 \text{ V}$   
WITH  $V^+ = 11 \text{ V}$  AND  $I_L = 0$

$$V_o = V_{Z0} + \frac{11 - V_o}{0.25} \times 0.03$$
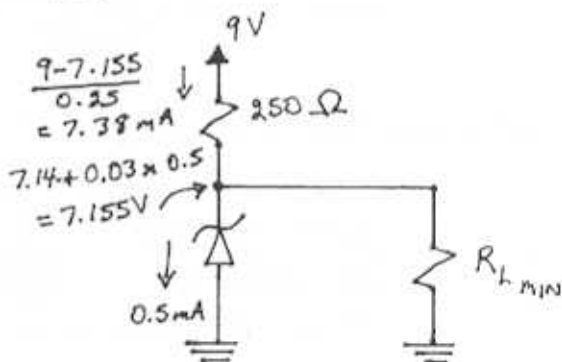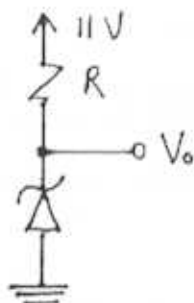
$$\Rightarrow V_o = \underline{\underline{7.55 \text{ V}}}$$



$$R_{L \min} = \frac{7.155}{7.38 - 0.5}$$

$$= \underline{\underline{1.04 \text{ k}\Omega}}$$

$$\therefore R = \frac{9 - 0.68}{20} = \underline{\underline{110\Omega}}$$

$$\begin{aligned} \text{Line Regulation} &= \frac{\Delta V_o}{\Delta V_s} = \frac{r_z}{r_z + R} \\ &= \frac{5}{5 + 110} \\ &= \underline{\underline{43.5 \frac{mV}{V}}} \end{aligned}$$

SECOND DESIGN ~ limited current from 9V supply


$$I_z = 0.25 \text{ mA}$$

$$\begin{aligned} V_z &= V_{zk} \approx V_{zo} - \text{calculate } V_{zo} \text{ from} \\ V_z &= V_{zo} + r_z I_{zT} \\ 6.8 &= V_{zo} + 5 \times 0.02 \\ V_{zo} &= 6.7 \text{ V} \end{aligned}$$

$$\therefore R = \frac{9 - 6.7}{0.25} = \underline{\underline{9.2 \text{ k}\Omega}}$$

$$\begin{aligned} \text{Line Regulation} &= \frac{\Delta V_o}{\Delta V_s} = \frac{750}{750 + 9200} \\ &= \underline{\underline{75.4 \frac{mV}{V}}} \end{aligned}$$

3.69

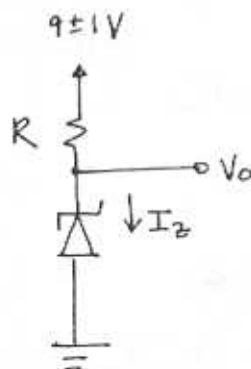


Given Parameters  
 $V_z = 6.8 \text{ V}$ ,  $r_z = 5\Omega$ ,  
 $I_z = 20 \text{ mA}$

By knee  
 $I_{zk} = 0.25 \text{ mA}$   
 $r_z = 750\Omega$

FIRST DESIGN - 9V supply can easily supply current

Let  $I_z = 20 \text{ mA}$  ~ well above knee

3.70

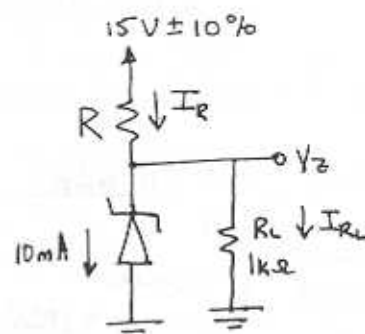

$$\begin{aligned} V_z &= V_{zo} + r_z I_z \\ 9.1 &= V_{zo} + 30(0.009) \\ V_{zo} &= \underline{\underline{8.83 \text{ V}}} \end{aligned}$$

CONT.

$$V_z = 8.83 + 30(0.01) = 9.13 \text{ V}$$

$$I_{R_L} = 9.13 / 1 \text{ k}\Omega = 9.13 \text{ mA}$$

$$I_R = 10 + 9.13 = \underline{19.13 \text{ mA}}$$

$$\therefore R = \frac{15 - 9.13}{19.13} = 306.8 \Omega$$

$$\approx \underline{300 \Omega}$$

$$V_z = 8.83 + 30 \left( \frac{15 - V_z}{300} - \frac{V_z}{1000} \right)$$

$$= 10.33 - V_z/10 - 3/100 V_z$$

$$V_z = 9.14 \text{ V}$$

$$V_z = 8.83 + 30 \left( \frac{15 \pm 1.5 - V_z}{300} - \frac{V_z}{1000} \right)$$

$$= \frac{1}{1.13} [8.83 + 15 \pm 0.15] = 9.14 \pm 0.13 \text{ V}$$

$\pm 0.13 \text{ V}$  variation in output voltage  
Halving the load current  $\approx R_L$  doubling

$$V_z = 8.83 + 30 \left( \frac{15 - V_z}{300} - \frac{V_z}{2000} \right)$$

$$= \frac{10.33}{1.115} = 9.26 \text{ V}$$


$\therefore 9.26 - 9.14 = 0.12 \text{ V}$  increase in output voltage.

At the edge of the breakdown region

$$V_z \approx V_{z0} = 8.83 \text{ V} \quad I_{zK} = 0.3 \text{ mA}$$

$$R_L = \frac{8.83}{\frac{13.5 - 8.83}{300} - 0.0003}$$

$$= \underline{578 \Omega}$$

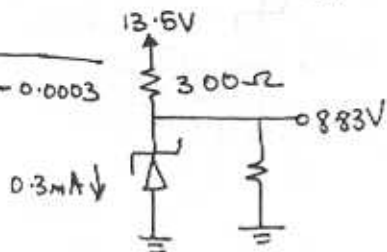

lowest output voltage = 8.83 V

$$\text{Line Regulation} = \frac{r_z}{R + r_z} = \frac{30}{300 + 30}$$

$$= 90 \frac{\text{mV}}{\text{V}}$$

$$\text{Load Regulation} = - (r_z \parallel R) = -29.1 \frac{\text{mV}}{\text{mA}}$$

3.71

$$(a) V_{zT} = V_{z0} + r_z I_{zT}$$

$$10 = V_{z0} + 7(0.025)$$


$$\Rightarrow V_{z0} = \underline{9.825 \text{ V}}$$

(b) The minimum zener current of 5mA occurs when  $I_L = 20 \text{ mA}$  and  $V_S$  is at its minimum of  $20(1 - 0.25) = 15 \text{ V}$ . See the circuit below:

$$R \leq \frac{15 - (V_{z0} + r_z I_z)}{20 + 5}$$

$$\leq \frac{15 - (9.825 + 7(0.005))}{25}$$

$$\leq 205.6 \Omega$$

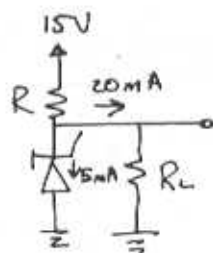

$\therefore$  Use  $R = \underline{205 \Omega}$

$$(c) \text{Line Regulation} = \frac{7}{205 + 7} = 33 \frac{\text{mV}}{\text{V}}$$


$$\pm 25\% \text{ change in } V_S \approx \pm 5 \text{ V}$$

$$V_o \text{ changes by } \pm 5 \times 33 = \pm 165 \text{ mV}$$

$$\text{corresponding to } \frac{\pm 165}{10} \times 100 = \pm 1.65\%$$

CONT.

3.75

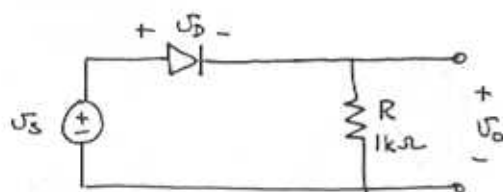

$$i_D = I_S e^{V_D / nV_T}$$


$$\frac{i_D}{1mA} = e^{\frac{V_D - 0.7}{nV_T}}$$

$$V_D - 0.7 = nV_T \ln(i_D / 10^{-3}) = 0.1 \log\left(\frac{i_D}{10^{-3}}\right)$$


$$V_D = 0.7 + 0.1 \log\left(\frac{V_o}{R}\right) \quad R = 1k\Omega$$

$$= 0.7 + 0.1 \log\left(\frac{V_o}{1}\right)$$

| $V_o (V)$ | $V_D (V)$ | $V_s = V_D + V_o (V)$ |
|-----------|-----------|-----------------------|
| 0.10      | 0.6       | 0.7                   |
| 0.5       | 0.67      | 1.17                  |
| 1         | 0.7       | 1.7                   |
| 2         | 0.73      | 2.73                  |
| 5         | 0.77      | 5.77                  |
| 10        | 0.8       | 10.8                  |

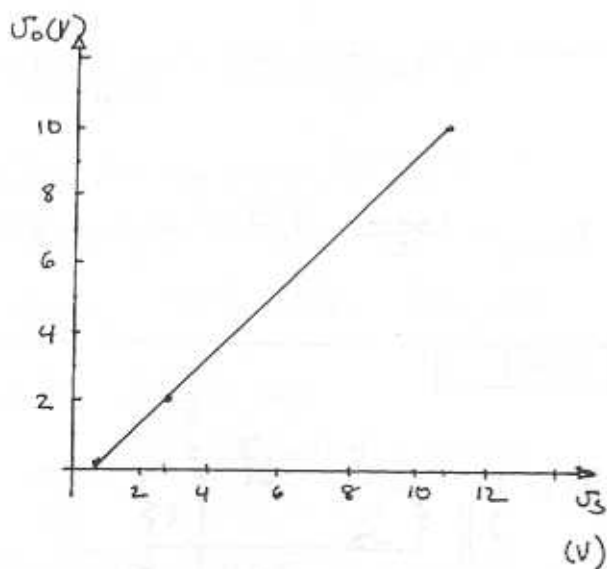

3.76

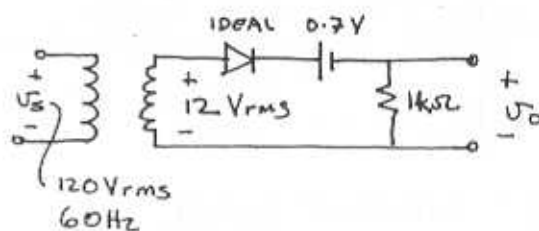

$$\hat{V}_o = 12\sqrt{2} - 0.7 = \underline{16.27V}$$

Conduction begins at

$$V_s = 12\sqrt{2} \sin \theta = 0.7$$

$$\theta = \sin^{-1}\left(\frac{0.7}{12\sqrt{2}}\right)$$

$$= 0.0412 \text{ rad}$$

Conduction ends at  $\pi - \theta$ 

$$\therefore \text{Conduction angle} = \pi - 2\theta = \underline{3.06 \text{ rad}}$$

The diode conducts for


$$\frac{3.06}{2\pi} \times 100 = \underline{48.7\%} \text{ of the cycle}$$

$$V_{o, \text{avg}} = \frac{1}{2\pi} \int_{\theta}^{\pi-\theta} 12\sqrt{2} \sin \phi - 0.7 d\phi$$


$$= \underline{5.06V}$$

$$i_{D, \text{avg}} = \frac{V_{o, \text{avg}}}{R} = \underline{5.06mA}$$

3.77

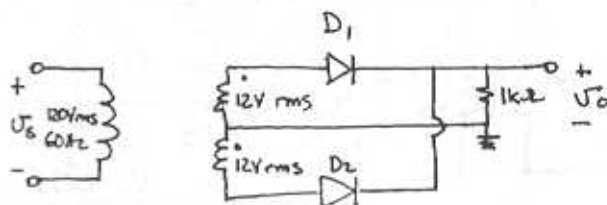

CONST.

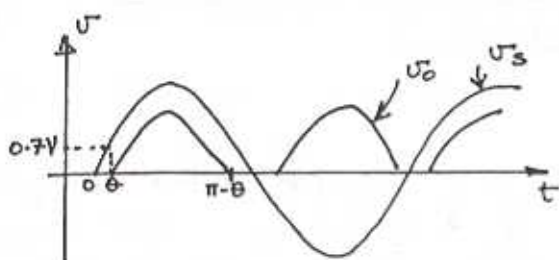

$$\hat{U}_o = 12\sqrt{2} - V_{D0} = \underline{16.27V}$$

Conduction starts at  $\theta = \sin^{-1} \frac{0.7}{12\sqrt{2}}$   
 $= 0.0412 \text{ rad}$

and ends at  $\pi - \theta$ . Conduction angle  
 $= \pi - 2\theta = 3.06 \text{ rad}$  in each half  
 cycle. Thus the fraction of a  
 cycle for which one of the two  
 diodes conduct  $= \frac{2(3.06)}{2\pi} \times 100$   
 $= \underline{97.4\%}$


Note that during 97.4% of the cycle  
 there will be conduction. However  
 each of the two diodes conducts for  
 only half the time, i.e. for  
 48.7% of the cycle.

$$U_{o, \text{avg}} = \frac{1}{\pi} \int_{\theta}^{\pi-\theta} 12\sqrt{2} \sin \phi - 0.7 \, d\phi$$

$$= \underline{10.12V}$$

$$i_{D, \text{avg}} = \frac{10.12}{1k\Omega} = \underline{10.12 \text{ mA}}$$

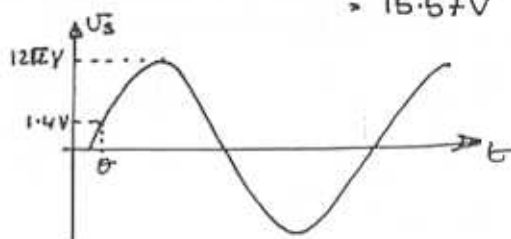Peak voltage across  $R = 12\sqrt{2} - 2V_D$   
 $= 12\sqrt{2} - 1.4$   
 $= 15.57V$



$$\theta = \sin^{-1} \frac{1.4}{12\sqrt{2}} = 0.0826 \text{ rad}$$

Fraction of cycle that  $D_1$  &  $D_2$  conduct  
 is  $\frac{\pi - 2\theta}{2\pi} \times 100 = \underline{47.4\%}$

Note  $D_3$  &  $D_4$  conduct in the other  
 half cycle so that there is  $2(47.4) =$   
 $94.8\%$  conduction interval.

$$U_{o, \text{avg}} = \frac{2}{2\pi} \int_{\theta}^{\pi-\theta} 12\sqrt{2} \sin \phi - 2V_D \, d\phi$$


$$= \frac{1}{\pi} \left[ -12\sqrt{2} \cos \phi - 1.4 \phi \right]_{\theta}^{\pi-\theta}$$

$$= \frac{2(12\sqrt{2} \cos \theta)}{\pi} - \frac{1.4(\pi - 2\theta)}{\pi}$$

$$= \underline{9.44V}$$


$$i_{R, \text{avg}} = \frac{U_{o, \text{avg}}}{R} = \frac{9.44}{1} = 9.44 \text{ mA}$$

3.78

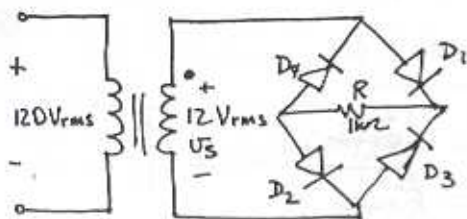

$$V_D = 0.7V$$

3.79

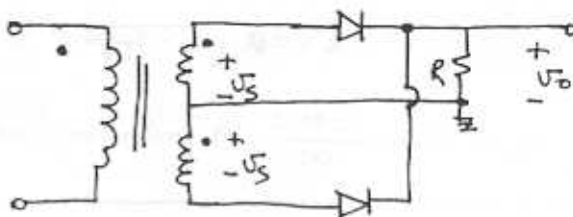

CONT.

For  $V_{D0} \ll V_s$ ,

$$V_{0, \text{avg}} \approx \frac{2}{\pi} V_s - V_{D0}$$

(a) For  $V_{0, \text{avg}} = 10V$

$$10 = \frac{2}{\pi} V_s - 0.7$$

$$\Rightarrow V_s = 16.81V$$

$$\text{Line peak} = 120\sqrt{2}$$

Thus,

$$\text{turns ratio} = \frac{120\sqrt{2}}{16.81} = 10.1:1$$

to each half  
of the secondary

OR 5.05:1 centre tapped

(b) For  $V_{0, \text{avg}} = 100V$

$$V_s = \frac{\pi}{2} (100.7) = 158.2V$$

$$\text{Turns Ratio} = \frac{120\sqrt{2}}{158.2} = 1.07:1 \text{ to each half}$$

OR 0.535:1 centre tapped

3.80

Refer to Fig 3.27.

For  $2V_{D0} \ll V_s$ ,

$$V_{0, \text{avg}} = \frac{2}{\pi} V_s - 2V_{D0} = \frac{2}{\pi} V_s - 1.4$$

(a) For  $V_{0, \text{avg}} = 10V$

$$V_s = \frac{\pi}{2} \times 11.4 = 17.91V$$

$$\text{Turns Ratio} = \frac{120\sqrt{2}}{17.91} = 9.477 \text{ to } 1$$

(b) For  $V_{0, \text{avg}} = 100V$

$$V_s = \frac{\pi}{2} \times 101.4 = 159.3V$$

$$\text{Turns Ratio} = \frac{120\sqrt{2}}{159.3} = 1.065 \text{ to } 1$$

3.81

$$120\sqrt{2} \pm 10\% : 24\sqrt{2} \pm 10\%$$

$$\Rightarrow \text{turns Ratio} = 5:1$$

$$V_s = \frac{24\sqrt{2}}{2} \pm 10\%$$

$$PIV = 2V_{s|_{\text{max}}} - V_{D0}$$


$$= 2 \times \frac{24\sqrt{2}}{2} \times 1.1 - 0.7$$



$$= 36.6V$$

Using a factor of 1.5 for safety we select a diode having a PIV rating of 55V.

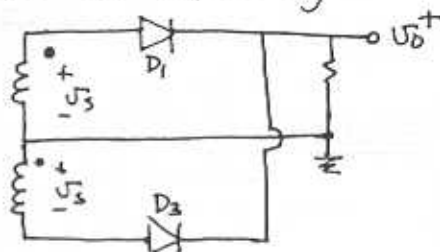3.82

The circuit is a full wave rectifier with centre tapped secondary winding. The circuit can be analyzed by looking at  $V_{0+}$  and  $V_{0-}$  separately.



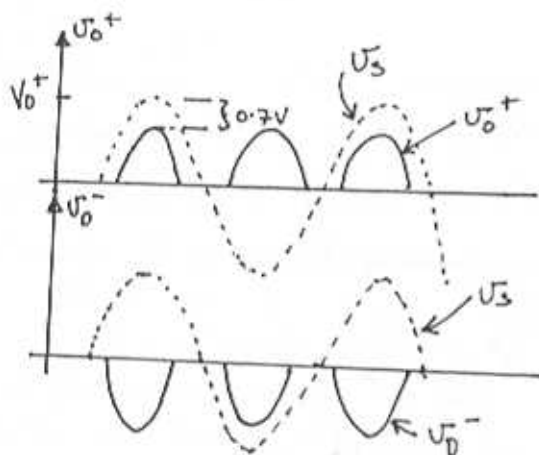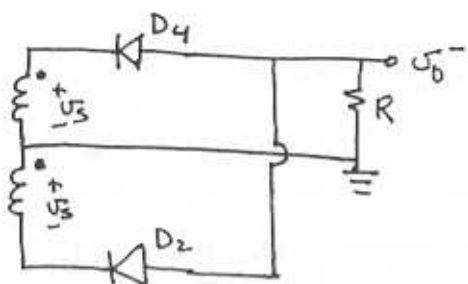

$$V_{D,avg} = \frac{1}{2\pi} \int V_s \sin \phi - 0.7 d\phi = 15$$

$$= \frac{2V_s}{\pi} - 0.7 = 15 \quad \text{assumed } V_s \gg 0.7V$$

$$V_s = \frac{15 + 0.7}{2} \pi = 24.66V$$

Thus voltage across secondary winding  
 $= 2V_s = \underline{49.32V}$

Looking at  $D_4$

$$PIV = V_s - V_o^-$$



$$= V_s + (V_s - 0.7)$$

$$= 2V_s - 0.7$$

$$= \underline{48.6V}$$

If choosing a diode, allow a safety margin of  $1.5PIV = \underline{73V}$

3.83

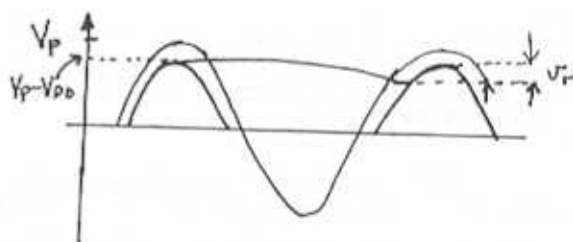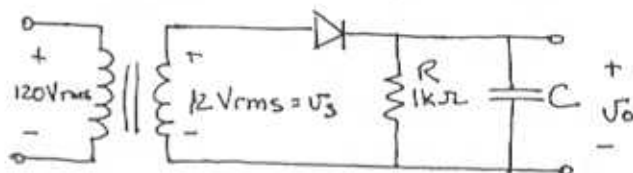

$$(i) V_r \approx (V_p - V_{D0}) \frac{T}{CR} \quad \text{Eq. (3.28)}$$

$$0.1(V_p - V_{D0}) = (V_p - V_{D0}) \frac{T}{CR}$$

$$C = \frac{1}{0.1 \times 60 \times 10^3} = \underline{166.7 \mu F}$$

$$(ii) \text{ For } V_r = 0.01(V_p - V_{D0}) = \frac{(V_p - V_{D0}) T}{CR}$$

$$C = \underline{1667 \mu F}$$

(a)

$$(i) V_{o,avg} = V_p - V_{D0} - \frac{1}{2} V_r$$

$$= 12\sqrt{2} - 0.7 - \frac{1}{2} (12\sqrt{2} - 0.7) 0.1$$

$$= (12\sqrt{2} - 0.7) \left(1 - \frac{0.1}{2}\right)$$

$$= \underline{15.5V}$$

$$(ii) V_{o,avg} = (12\sqrt{2} - 0.7) \left(1 - \frac{0.01}{2}\right)$$

$$= \underline{16.19V}$$

CONT.

(b)

i) Using eq (3.30) we have the conduction angle =

$$\begin{aligned}\omega \Delta t &\approx \sqrt{\frac{2V_r}{V_p - V_{D0}}} \\ &= \sqrt{\frac{2 \times 0.1 (V_p - 0.7)}{(V_p - 0.7)}} \\ &= \sqrt{0.2} \\ &= 0.447 \text{ rad}\end{aligned}$$

∴ Fraction of cycle for conduction =  $\frac{0.447}{2\pi} \times 100$   
 $= 7.1\%$

ii)  $\omega \Delta t \approx \sqrt{\frac{2 \times 0.01 (V_p - 0.7)}{V_p - 0.7}} = 0.141 \text{ rad}$

Fraction of cycle =  $\frac{0.141}{2\pi} \times 100 = 2.25\%$

(c)(i) Use Eq (3.31)

$$\begin{aligned}i_{D, \text{avg}} &= I_L \left( 1 + \pi \sqrt{\frac{2(V_p - V_{D0})}{V_r}} \right) \\ &= \frac{V_{0, \text{avg}}}{R} \left( 1 + \pi \sqrt{\frac{2(V_p - V_{D0})}{0.1(V_p - V_{D0})}} \right) \\ &= \frac{15.5}{10^3} \left( 1 + \pi \sqrt{\frac{2}{0.1}} \right) \\ &= 233 \text{ mA}\end{aligned}$$

ii)  $i_{D, \text{avg}} = \frac{16.19}{10^3} \left( 1 + \pi \sqrt{200} \right)$   
 $= 735 \text{ mA}$

NB Text uses  $I_L \approx V_p/R = \frac{V_p - V_{D0}}{R}$   
 but here we used  $i_{D, \text{avg}} = \frac{V_p - V_{D0} - \frac{1}{2}V_r}{R}$   
 which is more accurate.

(d)i)  $i_{D, \text{peak}} = I_L \left( 1 + 2\pi \sqrt{\frac{2(V_p - V_{D0})}{V_r}} \right)$   
 $= \frac{15.42}{10^3} \left( 1 + 2\pi \sqrt{\frac{2 \times 0.1}{0.1}} \right)$   
 $= 449 \text{ mA}$

ii)  $i_{D, \text{peak}} = \frac{16.19}{10^3} \left( 1 + 2\pi \sqrt{\frac{2}{0.01}} \right)$   
 $= 1455 \text{ mA}$

3.84

i)  $V_r = 0.1(V_p - V_{D0}) = \frac{(V_p - V_{D0})}{2fCR}$

the factor of 2 accounts for discharge occurring only half of the period  $t/2 = \frac{1}{2f}$

$C = \frac{1}{(2fR)0.1} = \frac{1}{2(60)10^3 \times 0.1} = 833 \mu\text{F}$

ii)  $C = \frac{1}{2(60)10^3 \times 0.01} = 833 \mu\text{F}$

(a)i)  $V_0 = V_p - V_{D0} - \frac{1}{2}V_r$   
 $= (V_p - V_{D0}) \left( 1 - \frac{0.1}{2} \right)$   
 $= (16.27) \left( 1 - \frac{0.1}{2} \right)$   
 $= 15.5 \text{ V}$

ii)  $V_0 = (16.27) \left( 1 - \frac{0.01}{2} \right) = 16.19 \text{ V}$

(b)

(i) Fraction of cycle =  $\frac{2\omega \Delta t}{2\pi} \times 100$   
 $= \frac{\sqrt{2V_r/(V_p - V_{D0})}}{\pi} \times 100$   
 $= \frac{1}{\pi} \sqrt{2(0.1)} \times 100 = 14.2\%$

CONST.

$$\text{ii) Fraction of Cycle} = \frac{2\sqrt{2(0.01)}}{2\pi} \times 100$$

$$= \underline{4.5\%}$$

(c) Use eq (3.34)

$$\text{i) } I_{D, \text{avg}} = I_L \left( 1 + \pi \sqrt{\frac{V_p - V_{D0}}{2V_r}} \right)$$

$$= \frac{15.5}{1} \left( 1 + \pi \sqrt{\frac{1}{2(0.1)}} \right) = \underline{124.4 \text{ mA}}$$

$$\text{ii) } I_{D, \text{avg}} = \frac{16.19}{1} \left( 1 + \pi \sqrt{\frac{1}{2(0.01)}} \right) = \underline{376 \text{ mA}}$$

(d) Use eq (3.35)

$$\text{i) } \hat{I}_D = I_L \left( 1 + 2\pi \frac{1}{\sqrt{2(0.1)}} \right) = \underline{233 \text{ mA}}$$

$$\text{ii) } \hat{I}_D = I_L \left( 1 + 2\pi \frac{1}{\sqrt{0.02}} \right) = \underline{735 \text{ mA}}$$

3.85

$$\text{i) } V_r = 0.1(V_p - V_{D0} \times 2) = \frac{V_p - 2V_{D0}}{2fCR}$$

discharge occurs only over  $\frac{1}{2}T = \frac{1}{2f}$

$$C = \frac{(V_p - 2V_{D0})}{(V_p - 2V_{D0})} \frac{1}{2(0.1) f R} = \underline{83.3 \mu\text{F}}$$

$$\text{ii) } C = \frac{1}{2(0.01) f R} = \underline{833 \mu\text{F}}$$

$$\text{(b) Fraction of cycle} = \frac{2\omega \Delta t}{2\pi} \times 100$$

$$= \frac{\sqrt{2(0.1)}}{\pi} \times 100 = \underline{14.2\%}$$

$$\text{ii) Fraction of cycle} = \frac{\sqrt{2(0.01)}}{\pi} \times 100 = \underline{4.5\%}$$

(c) i)

$$I_{D, \text{avg}} = \frac{14.79}{1} \left( 1 + \pi \sqrt{\frac{1}{0.2}} \right) = \underline{119 \text{ mA}}$$


$$\text{ii) } I_{D, \text{avg}} = \frac{15.49}{1} \left( 1 + \pi / \sqrt{0.02} \right) = \underline{356 \text{ mA}}$$

(d)

$$\text{(i) } \hat{I}_D = \frac{14.79}{1} \left( 1 + 2\pi \sqrt{\frac{1}{0.2}} \right) = \underline{223 \text{ mA}}$$

$$\text{(ii) } \hat{I}_D = \frac{15.49}{1} \left( 1 + 2\pi \sqrt{\frac{1}{0.02}} \right) = \underline{704 \text{ mA}}$$

3.86

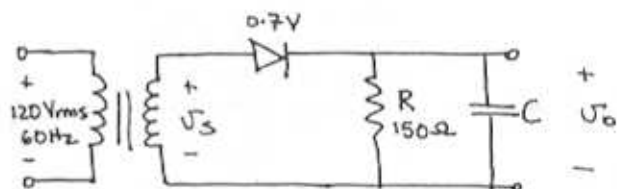

$$V_{o, \text{peak}} = V_p - V_{D0} = 16$$


$$V_p = 16.7 \text{ V}$$

$$V_{\text{rms}} = \frac{16.7}{\sqrt{2}} = 11.8$$

$$\text{(b) } V_r = (V_p - V_{D0}) \frac{1}{CR} \quad \text{Eq (3.28)}$$

$$2 = \frac{16}{60 \times C \times 150}$$

$$C = 889 \mu\text{F}$$

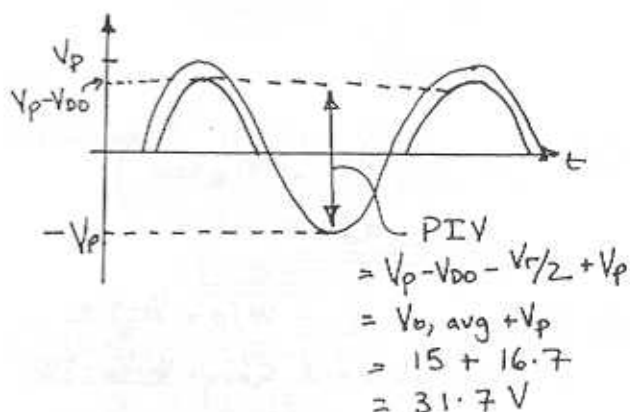

$$\text{For a 50\% safety margin PIV} = 1.5 \times 31.7$$

$$= \underline{47.6 \text{ V}}$$

CONT.


$$(d) \quad i_{D, avg} = I_L \left( 1 + \pi \sqrt{\frac{2(V_p - V_{D0})}{V_r}} \right)$$

using  $I_L = \frac{V_{D0, avg}}{R} = \frac{15}{R}$  we have

$$i_{D, avg} = \frac{15}{150} \left( 1 + \pi \sqrt{\frac{2(16)}{2}} \right) = \underline{1.36A}$$

$$(e) \quad i_{D, peak} = I_L \left( 1 + 2\pi \sqrt{\frac{2(V_p - V_{D0})}{V_r}} \right)$$
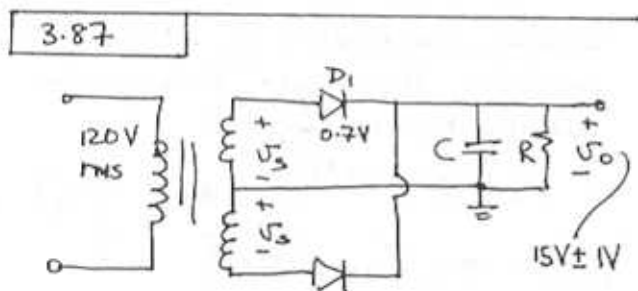
$$= \frac{15}{150} \left( 1 + 2\pi \sqrt{\frac{2(16)}{2}} \right) = \underline{2.61A}$$



$$(a) \quad \hat{U}_o = 16V$$

$$\therefore \hat{U}_s = 16 + V_{D0} = 16.7V$$


RMS Voltage across secondary

$$= \frac{2 \times 16.7}{\sqrt{2}} = \underline{23.6V}$$

$$(b) \text{ Using } E_q. (3.28)$$

$$V_r = \frac{V_p}{2fCR} = \frac{16}{2 \times 60 \times C \times 150} = 2$$

$$C = \underline{444.4 \mu F}$$

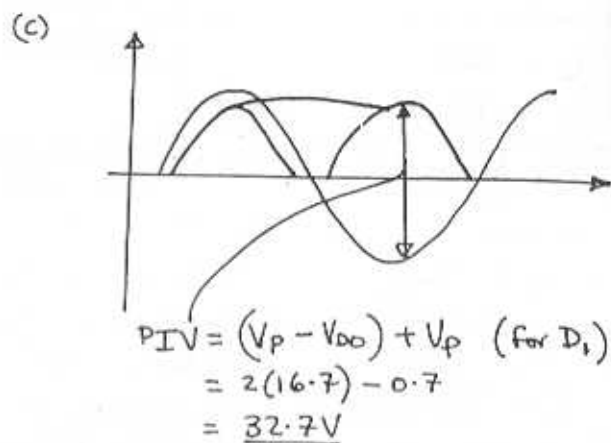

$\therefore$  Using a 50% margin


$$PIV = 1.5(32.7) = \underline{49V}$$

$$(d) \text{ Using } E_q. (3.34)$$

$$i_{D, avg} = I_L \left( 1 + \pi \sqrt{\frac{V_p/2}{V_r}} \right) = \frac{15}{150} \left( 1 + \pi \sqrt{\frac{16}{2 \times 2}} \right) = \underline{0.73A}$$

$$(e) \text{ Using } E_q. (3.35)$$
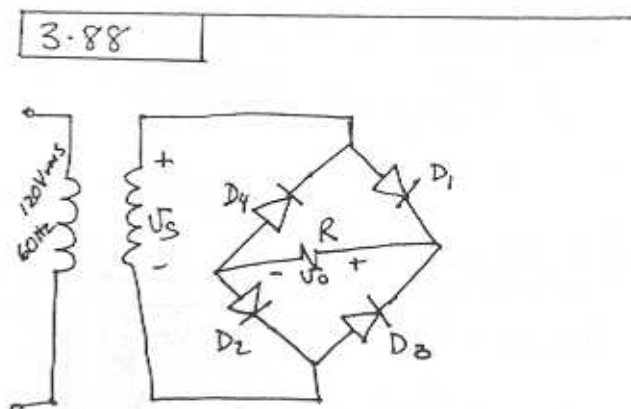
$$i_{D, max} = I_L \left( 1 + 2\pi \sqrt{\frac{V_p/2}{V_r}} \right) = \frac{15}{150} \left( 1 + 2\pi \sqrt{\frac{16}{2 \times 2}} \right) = \underline{1.36A}$$



$$U_o = 15 \pm 1V, R = 150\Omega$$

CONT.

$$\hat{V}_0 = 16V$$

$$\hat{V}_3 = 16 + 2V_{D0} = 17.4V$$


$$\text{RMS Secondary Voltage} = \frac{17.4}{\sqrt{2}} = 12.3V$$

$$(b) V_r = \frac{V_p}{2fCR}$$

$$2 = \frac{16}{2 \times 60 \times C \times 150}$$

$$C = 444.4 \mu F$$

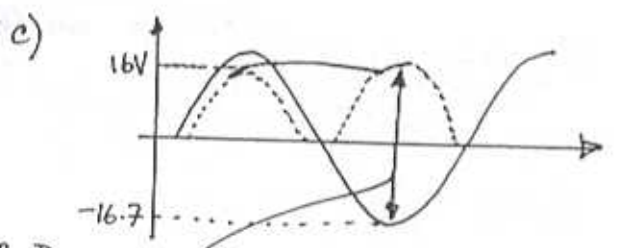note: we got the same value for C as the full wave rectifier as discharge is over the same amt of time  $T/2$  and the peak is the same - 16V.



for  $D_3$

$$PIV = 16 - (-V_{D0})$$

$$= 16 + 0.7$$

$$= 16.7V$$

Allowing a 50% margin =  $16.7 \times 1.5$

$$= 25V$$

(d) Using 3.34

$$i_{D,avg} = I_L \left( 1 + \pi \sqrt{V_p / 2V_r} \right)$$

$$= \frac{15}{150} \left( 1 + \pi \sqrt{16 / 2 \times 2} \right)$$

$$= 0.73A$$



(e) Using (3.35)

$$i_{D,max} = I_L \left( 1 + 2\pi \sqrt{V_p / 2V_r} \right)$$

$$= \frac{15}{150} \left( 1 + 2\pi \sqrt{16 / 2 \times 2} \right)$$

$$= 1.36A$$

3.89

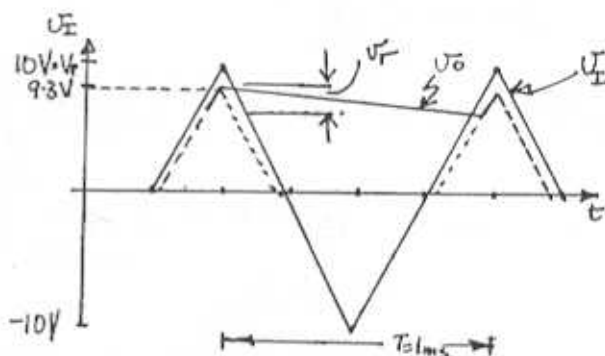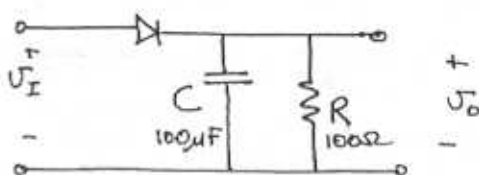

During the diode's off interval, the capacitor discharges through the resistor R according to:

$$V_0 = 9.3 e^{-t/RC} \approx 9.3(1 - T/CR)$$

$$\therefore V_r = 9.3 - 9.3(1 - T/CR)$$

$$= 9.3T/CR$$

$$= \frac{9.3}{fCR}$$


$$= 0.93V$$

NB this is  $E_8(3.38)$

$$V_{0,avg} = V_0 - V_{D0} - \frac{1}{2} V_r$$

$$= 9.3 - \frac{1}{2} 0.93$$

$$= 8.84V$$

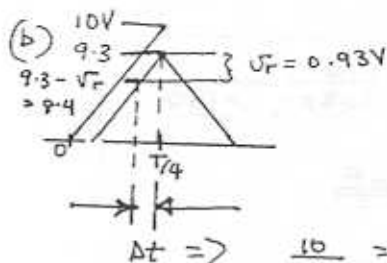

$$\Delta t \Rightarrow$$

$$\frac{10}{T/4} = \frac{0.93}{\Delta t}$$

$$\Delta t = 0.02325T$$

$$= 0.02325 \text{ ms}$$

CONT.

(c)  $\therefore$  Charge gained during conduction = Charge lost during discharge

$$i_{c,avg} \Delta t = C V_r$$

$$i_{c,avg} = \frac{C V_r}{\Delta t} = \frac{100 \times 10^{-6} \times 0.93}{0.02325 \times 10^{-3}}$$

$$= 4.0 \text{ A}$$

$$i_{D,avg} \cong i_{c,avg} + i_{L,avg} \quad \leftarrow \frac{V_{0,avg}}{R}$$

$$\cong 4.0 + \frac{8.84}{100} = \underline{\underline{4.09 \text{ A}}}$$

$$(d) \quad i_{c,max} = C \left. \frac{\delta V_0}{\delta t} \right|_{\text{at onset of conduction}}$$

$$= C \frac{\delta V_r}{\delta t}$$

$$= 100 \times 10^{-6} \times 40 \times 10^3$$

$$= \underline{\underline{4 \text{ A}}}$$

$$i_{D,max} = i_{c,max} + i_{L,max}$$

$$= 4 + V_{0,max}/100$$

$$= 4 + 9.3/100$$

$$= 4.09 \text{ A.}$$

Note that in this case  $i_{D,avg} = i_{D,max}$  owing to the linear input ( $i_c$  is constant and  $i_L$  is approximately constant).

3.90

Refer to Fig P3.82 and let capacitor  $C$  be connected across each of the load resistors  $R$ . The two supplies,  $V_0^+$  and  $V_0^-$  are identical. Each is a full-wave rectifier similar to that based on the centre-tapped transformer circuit. For each supply, the dc output is 15V and the ripple is 1V peak-to-peak. Thus  $V_0 = 15 \pm 0.5 \text{ V}$ . It follows that the peak value of  $V_0$  must be  $15.5 + 0.5 = 16.0 \text{ V}$ .  
 $\therefore$  Voltage across secondary =  $2(16.0) = 32.0 \text{ V}$

$$\text{RMS across secondary} = \frac{32.0}{\sqrt{2}} = \underline{\underline{22.6 \text{ V}_{rms}}}$$

$$\text{Turns Ratio} = \frac{120}{22.6} = 5.24:1$$

Use Eq. (3.35) to find

$$\begin{aligned} i_{D,max} &= I_L \left( 1 + 2\pi \sqrt{V_p / 2V_r} \right) \\ &= 0.2 \left( 1 + 2\pi \sqrt{15.5 / 2} \right) \\ &= \underline{\underline{3.70 \text{ A}}} \end{aligned}$$


$$V_r = \frac{V_p}{2fCR} = 1 \quad \text{Eq. (3.28)}$$

DISCHARGE OCCURS OVER  $T/2 = \frac{1}{2f}$

$$\begin{aligned} \Rightarrow C &= \frac{15.5}{2 \times 60 \times 75} \quad \leftarrow \text{where } 200 \text{ mA} = \frac{15}{R} \\ &= \underline{\underline{1722 \mu\text{F}}} \end{aligned}$$

$$R = \frac{15}{0.2} = 75 \Omega$$

Consider  $D_3$  when looking at PIV

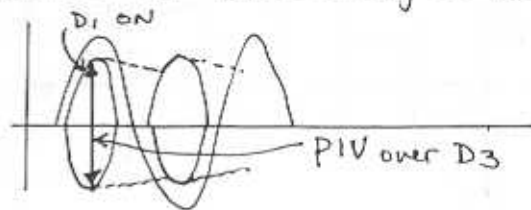

CONT.

$$PIV = \hat{V}_O + \hat{V}_S \\ = 15.5 + 16.2 = 31.7V$$

Allowing for 50% safety margin

$$PIV = 1.5 \times 31.7 = \underline{47.6V}$$

Use Eq (3.34) to find

$$\hat{I}_{D,avg} = I_L \left( 1 + \pi \sqrt{V_P / 2V_r} \right) \\ = 0.2 \left( 1 + \pi \sqrt{15.5/2} \right) \\ = \underline{1.95A}$$

3.91

$$V_O = V_{\pm} (1 + R/R) \\ = 2V_{\pm} \text{ when the diode is conducting.}$$


$$(a) V_{\pm} = +1V \quad V_O = 2V \quad V_A = 1.7V \quad V_- = V_{\pm} = 1V$$

$$b) V_{\pm} = 2V \quad V_O = 4V \quad V_A = 4.7V \quad V_- = 2V$$

$$c) V_{\pm} = -1V \quad V_A = -12V \sim \text{diode is cut off} \\ V_O = 0V \\ V_- = 0V$$

d)
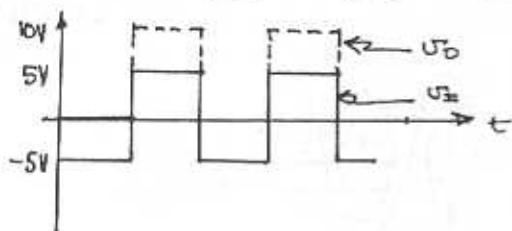
$$V_{\pm} = -2V \quad V_A = -12V \quad V_O = 0V \quad V_- = 0V$$




$$V_{O,avg} = \underline{5V}$$

3.92

$$V_{\pm} > 0 \quad D_1 \text{ conducts } D_2 \text{ cut off}$$

$$V_{\pm} < 0 \quad D_1 \text{ cut off}$$
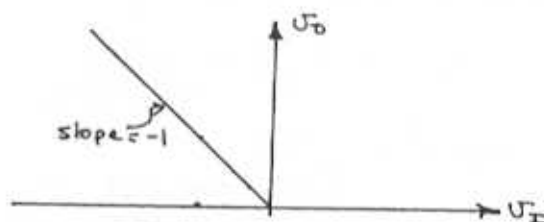
$$D_2 \text{ conducts } \sim \frac{V_O}{V_{\pm}} = -1$$



$$a) V_{\pm} = 1V \quad V_O = 0V$$

$$V_A = -0.7V - \text{keeps } D_2 \text{ off} \\ \text{so no current flows through } R$$

$$\Rightarrow V_- = 0V - \text{virtual gnd as fdbk is closed through } D_1$$

$$(b) V_{\pm} = 2V$$

$$V_O = 0V \\ V_A = -0.7V \\ V_- = 0V$$





$$(c) V_{\pm} = -1V$$

$$V_O = 1V \\ V_A = 1.7V \\ V_- = 0V$$

$\sim$  virtual gnd as negative feedback is closed through R.

$$(d) V_{\pm} = -2V \Rightarrow V_O = 2V \\ V_A = 2.7V \\ V_- = 0V$$

|      |  |
|------|--|
| 3.93 |  |
|------|--|

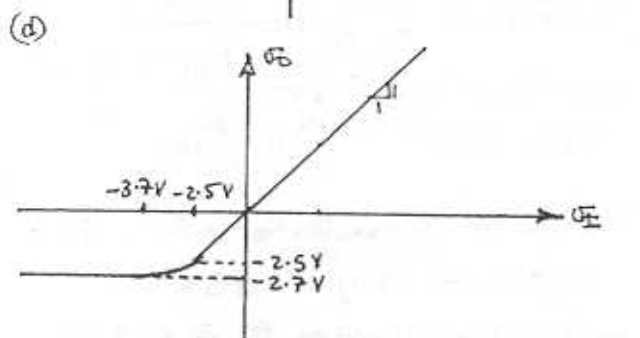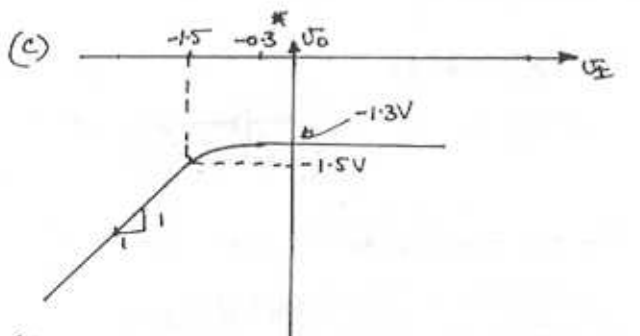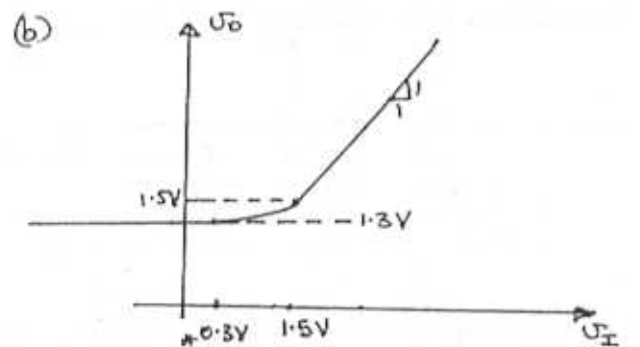
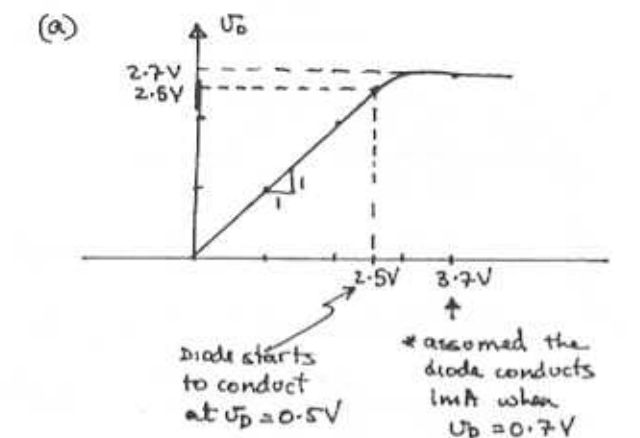


3.94



(a)  $V_E < 2.65V$  ~ the diode is off  
and the circuit reduces to:




With the diode conducting we have:

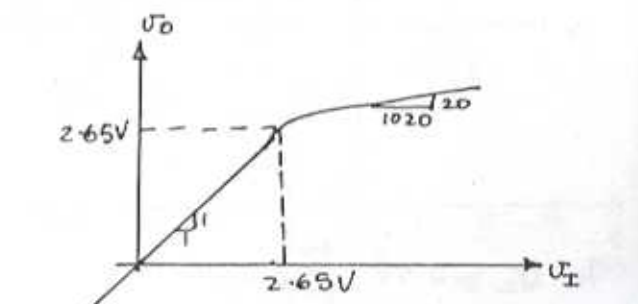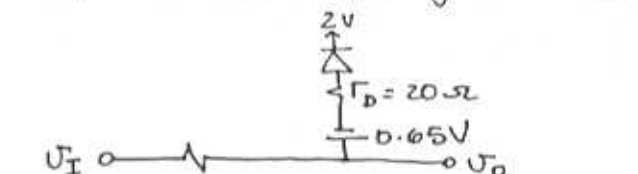


(b) Similarly for (b), (c), (d)

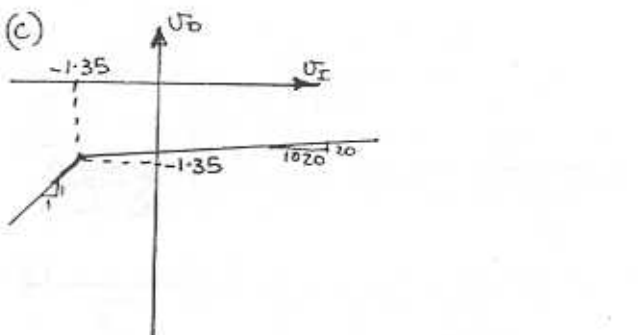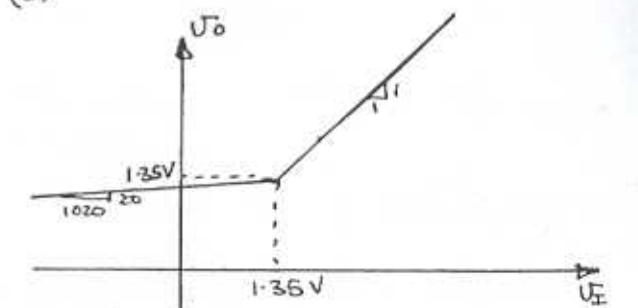


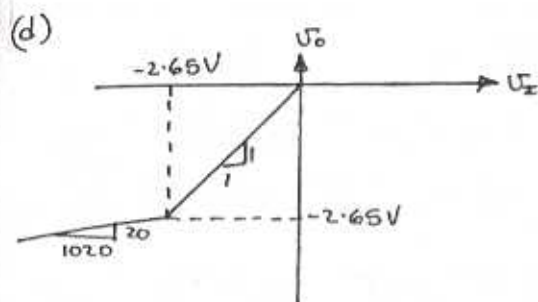



3.95

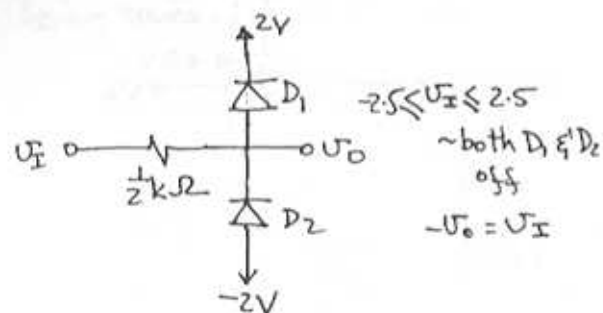

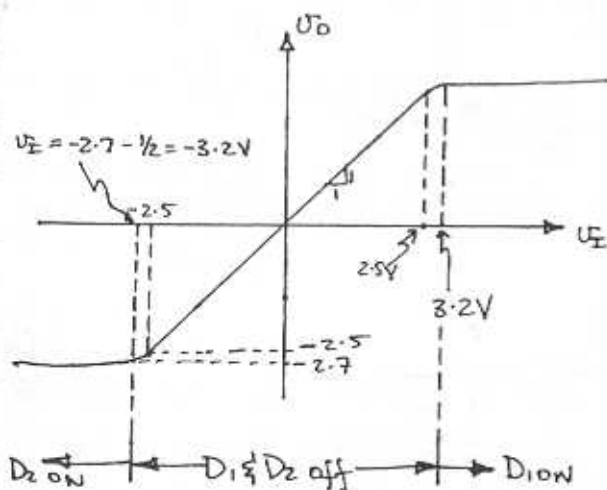For  $U_I \geq 2.5V$   $\sim D_1$  on  
 $U_{D1} = 0.7$  at  $i_{D1} \geq 1mA$   
 $U_O = 2.7V$  at  $U_I = 2.7 + \frac{1}{2} \times 1$   
 $= \underline{\underline{3.2V}}$




3.96

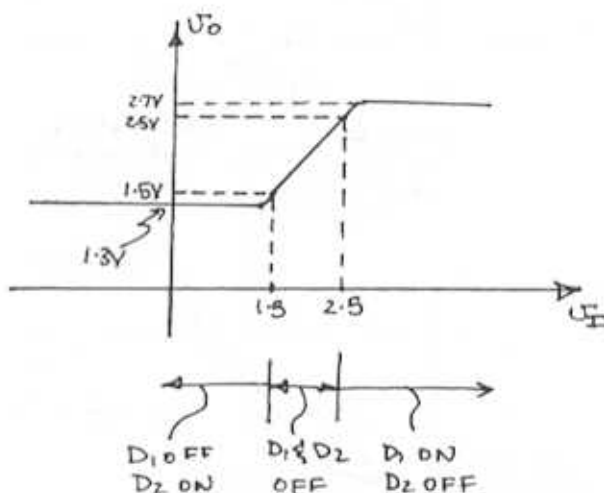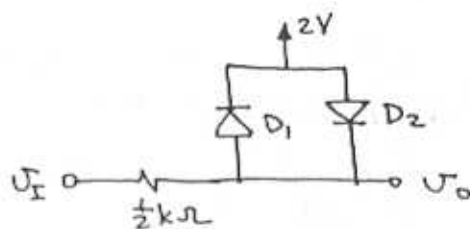


3.97

For each diode

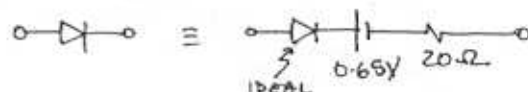

For the Zener diode

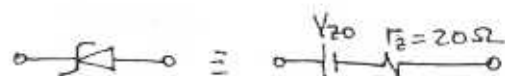

$$8.2 = V_{Z0} + 10 \times 10^{-3} \times 20$$

$$V_{Z0} = 8.0V$$


The limiter thresholds are

$$\pm (2 \times 0.65 + 8.0) = \pm 9.3V$$


For  $U_I > 9.3$  (as well as for  $U_I < -9.3$ )

$$\frac{\partial U_O}{\partial U_I} = \frac{R_{D1} + R_Z + R_{D2}}{1k\Omega + R_{D1} + R_Z + R_{D2}} = \frac{3(20)}{1k\Omega + 3(20)} = 0.057 \frac{V}{V}$$

CONT.

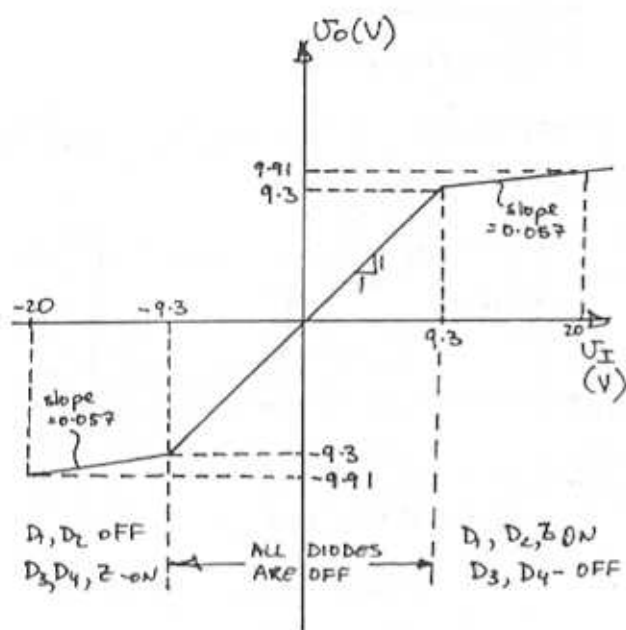

3.98

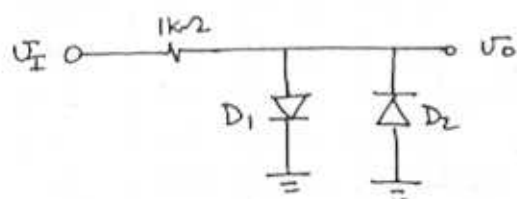

for  $D_1$

Given  $\frac{i_D}{1\text{mA}} = e^{\frac{U_D - 0.7}{nV_T}}$

$$(U_D - 0.7) = nV_{Th}(\frac{i_D}{1\text{mA}})$$

$$= 0.1 \log\left(\frac{i_D}{10^{-3}}\right) \leftarrow \therefore \text{can find } U_D \text{ from } i_D$$

$$\therefore i_D = 10^{-3} \times 10^{\frac{U_D - 0.7}{0.1}}$$


$$= 10^{-3} \times 10^{10(U_D - 0.7)}$$

$$\text{KVL } U_I = U_D + i_D \times 10^3$$

$$= U_D + 10^{10(U_D - 0.7)}$$

for  $D_2$ :  $U_I = U_D - 10^{10(U_D - 0.7)}$

| $U_O (V)$ | $U_I (V)$ |            |
|-----------|-----------|------------|
| 0.5       | 0.510     | } $D_1$ ON |
| 0.6       | 0.7       |            |
| 0.7       | 1.7       |            |
| 0.8       | 10.7      |            |
| 0         | 0         | } $D_2$ ON |
| -0.5      | -0.51     |            |
| -0.6      | -0.7      |            |
| -0.7      | -1.7      |            |
| -0.8      | -10.7     |            |

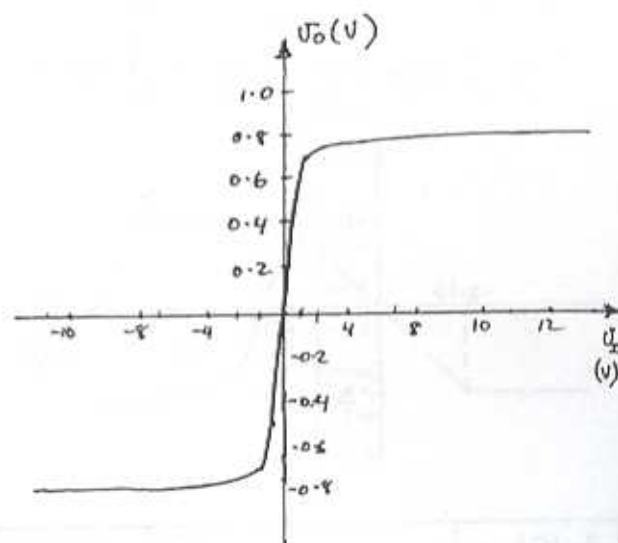


The limiter is fairly hard with a gain


$$K \approx 1$$

$$L_+ \approx \underline{\underline{0.8V}}, \quad L_- \approx \underline{\underline{-0.8V}}$$

3.99

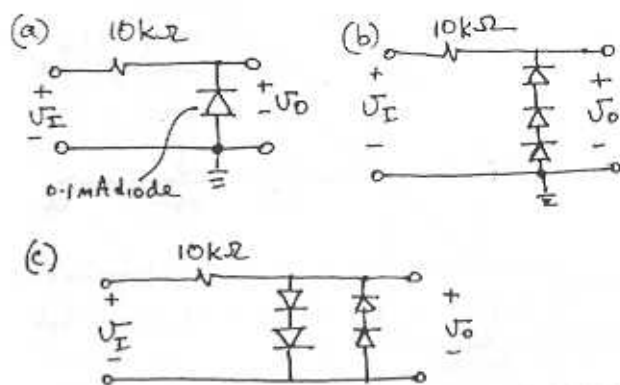


3.100

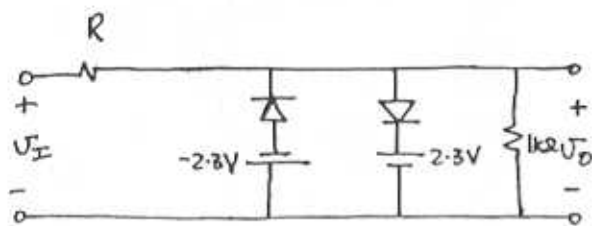

In the limiting region


$$\frac{V_o}{V_I} = \frac{1000}{1000+R} \geq 0.95$$
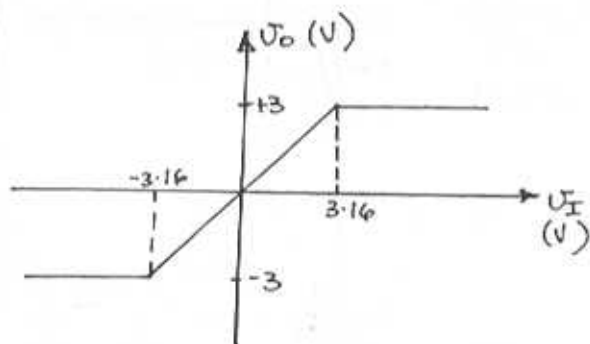
$$R \leq \underline{\underline{52.6\Omega}}$$



$$\frac{0.2}{10 \times 10^{-3}} = 20\Omega \sim$$

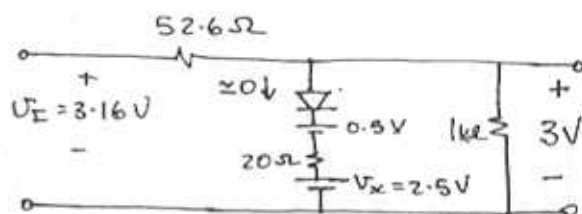At the verge of limiting in the positive direction we have :-



For \$V\_I = 10V\$




$$V_o \approx 3 + 0.28(10 - 3.16) = \underline{\underline{4.9V}}$$

For \$V\_I = -10V\$

$$V_o = \underline{\underline{-4.9V}}$$

3.102

3.101

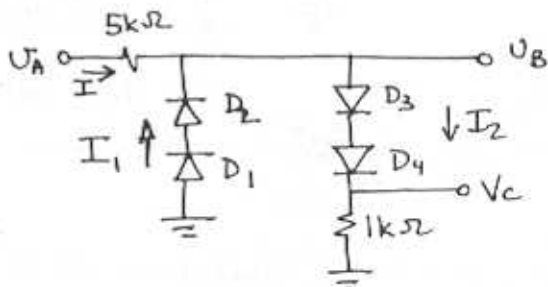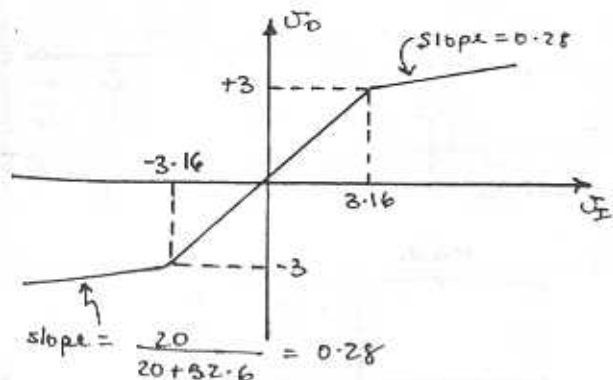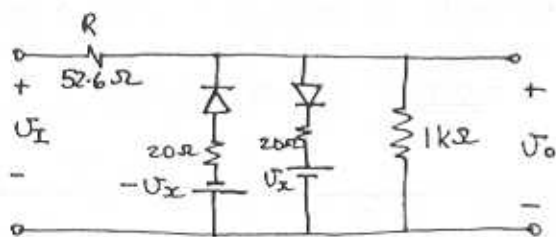

$$V_B = 0.7 + 0.1 \log(I_D/0.1)$$

(a) For \$V\_A &gt; 0\$ \$D\_1, D\_2\$ off \$\Rightarrow I\_1 = 0\$

$$I = I_2 = V_C / 1k\Omega \quad V_A = V_B + I_2 \cdot 5$$

(b) For \$V\_I &lt; 0\$ \$D\_3, D\_4\$ off \$\Rightarrow V\_C = 0\$


$$I = -I_1 \quad V_B = -(V_{D1} + V_{D2})$$

$$V_A = -(V_B + 5I_1)$$

CONT.


(a) List of points for  $V_A > 0$

| $V_C$<br>(V) | $I_Z$<br>(mA) | $V_{D3}, V_{D4}$<br>(V) | $V_B = V_C + V_{D3} + V_{D4}$<br>(V) | $V_A$<br>(V) |
|--------------|---------------|-------------------------|--------------------------------------|--------------|
| 0.0001       | 0.0001        | 0.4                     | 0.8                                  | 0.8          |
| 0.001        | 0.001         | 0.5                     | 1.00                                 | 1.01         |
| 0.01         | 0.1           | 0.6                     | 1.21                                 | 1.24         |
| 0.1          | 0.1           | 0.7                     | 1.50                                 | 1.90         |
| 0.2          | 0.2           | 0.73                    | 1.66                                 | 2.66         |
| 0.3          | 0.3           | 0.75                    | 1.80                                 | 3.30         |
| 0.4          | 0.4           | 0.76                    | 1.92                                 | 3.92         |
| 0.5          | 0.5           | 0.77                    | 2.04                                 | 4.54         |
| 0.6          | 0.6           | 0.78                    | 2.16                                 | 5.16         |

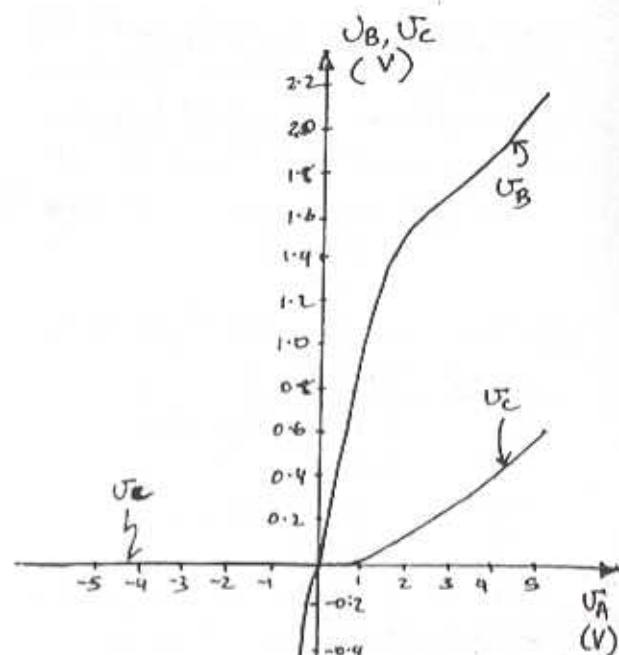


(b) List of Points for  $V_A < 0$

| $I_1$<br>(mA) | $V_{D1}, V_{D2}$<br>(V) | $V_B$<br>(V) | $V_A$<br>(V) |
|---------------|-------------------------|--------------|--------------|
| 0.0001        | 0.4                     | -0.80        | -0.80        |
| 0.001         | 0.5                     | -1.00        | -1.01        |
| 0.01          | 0.6                     | -1.20        | -1.25        |
| 0.10          | 0.7                     | -1.40        | -1.90        |
| 0.20          | 0.73                    | -1.46        | -2.46        |
| 0.30          | 0.75                    | -1.50        | -3.00        |
| 0.40          | 0.76                    | -1.52        | -3.52        |
| 0.50          | 0.77                    | -1.54        | -4.04        |
| 0.60          | 0.78                    | -1.56        | -4.56        |
| 0.70          | 0.785                   | -1.57        | -5.07        |

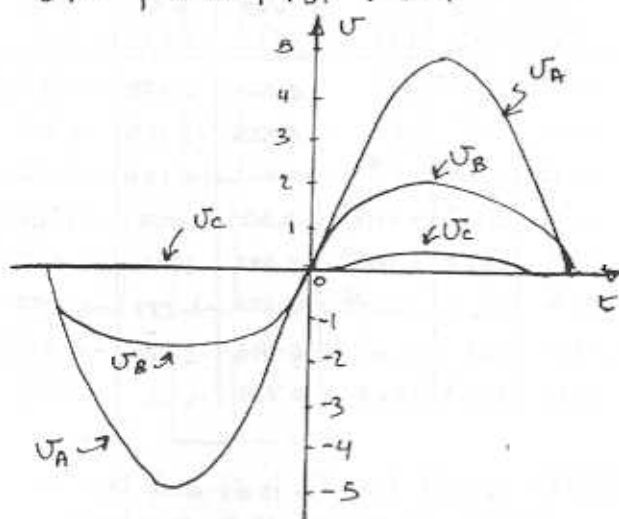

3.103

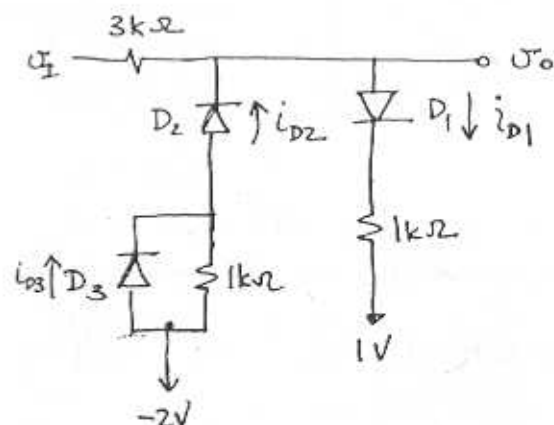

At currents  $i_{D1} > 1\text{mA}$ ,  $V_{D1} \approx 0.7\text{V}$   
 Let  $V_{D1} = 0.71\text{V}$   $V_{IE} > 5.7\text{V}$

CONT.


$$V_o = 1.71 + i_{D1} \times 1k\Omega$$

$$= 1.71 + \left( \frac{V_I - 1.71}{4} \right) \times 1$$

$$= \frac{V_I}{4} + 1.2825 \quad \text{NB slope} = 1/4$$

∴ For  $V_I > 5V$  slope  $V_o/V_I \approx 1/4$

| $V_I (V)$ | $V_o (V)$ |
|-----------|-----------|
| 5.8       | 2.7325    |
| 6.0       | 2.7825    |
| 7.0       | 3.0325    |
| 8.0       | 3.2825    |
| 9.0       | 3.5325    |
| 10.0      | 3.7825    |

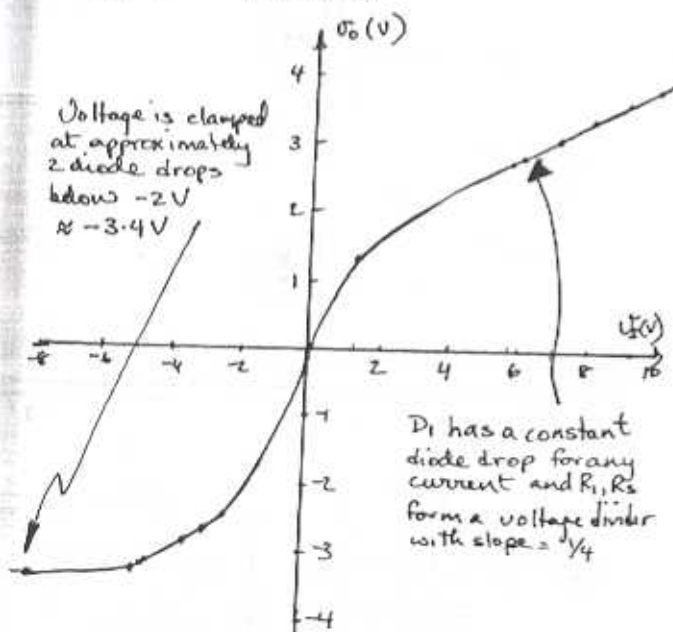

where points for  $-8 \leq V_I \leq 6V$  are calculated as shown below:

$$i_D = 1mA \text{ at } V_D = 0.7V \quad n=1$$

$$i_D = I_S e^{0.7/0.025} = 10^{-3}$$

$$I_S = 6.914 \times 10^{-16} A$$

∴ For Diodes use  $i_D = 6.914 \times 10^{-16} e^{V_D/0.025}$

$D_1$  conducting  $i_{D2} = 0$

| $i_{D1}$<br>(A)      | $V_{D1}$<br>(V) | $V_o$<br>(V) | $V_I = (4k)i_{D1} + V_o + 1$<br>(V) |
|----------------------|-----------------|--------------|-------------------------------------|
| $10^{-6}$            | 0.297           | 1.297        | 1.297                               |
| $10^{-4}$            | 0.527           | 1.528        | 1.5313                              |
| $10^{-5}$            | 0.584           | 1.595        | 1.625                               |
| $10^{-4}$            | 0.64            | 1.742        | 2.042                               |
| $10^{-3}$            | 0.70            | 2.7          | 5.7                                 |
| $0.2 \times 10^{-2}$ | 0.74            | 6.74         | 12.74                               |
| $10^{-2}$            | 0.758           | 11.75        | 41.75                               |

even at small  $i_{D1}$ ,  $V_o > 1V$ ,  $V_o \approx V_I$  since  $i_{D1} \approx 0$

For the  $D_2, D_3$  arm conducting use the following equations:

Note  $V_I < -2.5V$

Starting with a value for  $V_A$  we have

$$V_{D3} = V_A + 2 \quad V_{D3}/0.025 \quad (2)$$

$$i_{D3} = I_S e^{V_{D3}/0.025} \quad (2)$$

$$i_{D2} = i_{D3} + \frac{V_A + 2}{1} \quad (3)$$

$$V_{D2} = 0.025 \ln \left( \frac{i_{D2}}{6.914 \times 10^{-16}} \right) \quad (4)$$

$$V_o = V_A - V_{D2} \quad (5)$$

$$V_I = V_o - i_{D2} \times 3k\Omega \quad (6)$$

| ① $V_A$<br>(V) | ② $i_{D3}$<br>(A)    | ③ $i_{D2}$<br>(A)    | ④ $V_{D2}$<br>(V) | ⑤ $V_o$<br>(V) | ⑥ $V_I$<br>(V) |
|----------------|----------------------|----------------------|-------------------|----------------|----------------|
| -2.001         | $7 \times 10^{-14}$  | $10^{-6}$            | 0.527             | -2.528         | -2.531 (A)     |
| -2.01          | $10^{-15}$           | $10^{-5}$            | 0.585             | -2.595         | -2.625         |
| -2.10          | $3.8 \times 10^{-9}$ | $10^{-4}$            | 0.642             | -2.724         | -3.024         |
| -2.20          | $2 \times 10^{-2}$   | $0.2 \times 10^{-3}$ | 0.659             | -2.859         | -3.459         |
| -2.5           | $33 \mu A$           | $0.5 \times 10^{-3}$ | 0.682             | -3.128         | -4.628 (B)     |
| -2.6           | $18 \mu A$           | $0.6 \times 10^{-3}$ | 0.687             | -3.287         | -5.087         |
| -2.7           | $1mA$                | $1.7 \times 10^{-3}$ | 0.713             | -3.413         | -8.516 (C)     |
| -2.71          | $1.5mA$              | $2.2mA$              | 0.720             | -3.43          | -10            |

(A) for small  $i_{D2}$ ,  $D_3$  is off and  $D_2$  is on  
∴  $i_2$  flows through  $1k\Omega$  resistor


CONT.

(B) 0.5 V drop across  $D_3$  causes  $D_3$  to start to conduct

(C)  $V_A = -2.7V$


The 0.7 voltage across  $D_3$  clamps the voltage across  $R_3$  so that  $D_3$  controls the current  $i_{D2}$

3.104

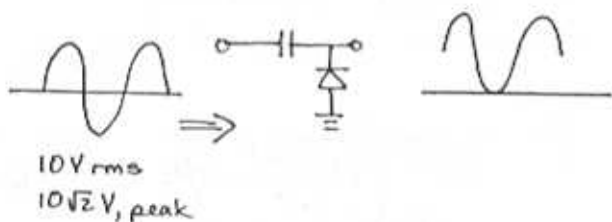

Average (dc) value of output =  $10\sqrt{2}$   
= 14.14V


3.105

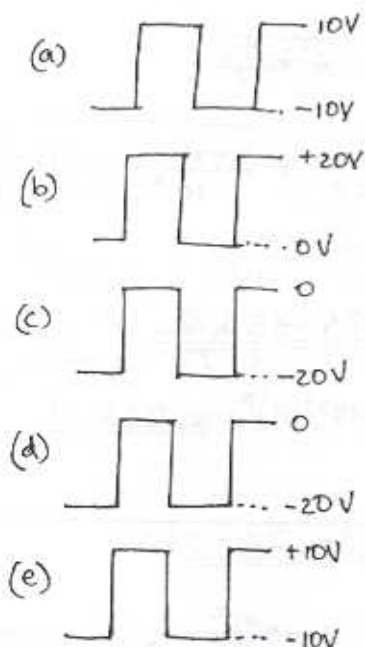

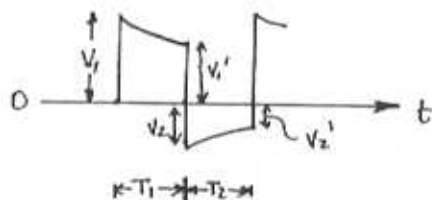(f) Here there are two different time constants involved. To calculate the output levels we shall exaggerate the discharge and charge waveforms.

During  $T_1$   $V_0 = V_1 e^{-t/RC}$

At  $t = T_1 = T$   $V_0 = V_1'$   
=  $V_1 e^{-T/RC}$



where for  $T \ll CR$

$$V_1' \approx V_1 (1 - T/CR) = V_1 (1 - \alpha) \quad \text{where } \alpha \ll 1$$

During the period  $T_2$

$$|V_0| = |V_2| e^{-t/CR/2}$$

at the end of  $T_2$   $t = T$ ,  $V_0 = V_2'$

where  $V_2' = |V_2| e^{-T/CR/2}$

$$\approx |V_2| (1 - \frac{T}{CR/2}) = |V_2| (1 - 2\alpha)$$

$$\text{Now } V_1' + |V_2| = 20 \Rightarrow V_1 + |V_2| - 2\alpha V_1 = 20 \quad (1)$$

$$\text{and } |V_2'| + V_1 = 20 \Rightarrow V_1 + |V_2| - 2\alpha |V_2| = 20 \quad (2)$$

from (1) & (2) we find that


$$V_1 = 2V_2$$

Then using (1) and neglecting  $\alpha V_1$  yields

$$3|V_2| = 20 \Rightarrow |V_2| = \underline{6.67V}$$

$$V_1 = \underline{13.33V}$$


The result is:

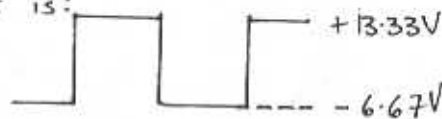

CONT.



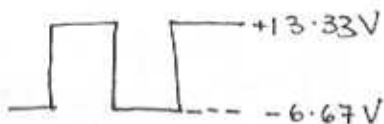(h) Using a method similar to that employed for case (f) above we obtain.



3.106

$$n_i^2 = BT^3 e^{-E_g/kT}$$

$$B = 5.4 \times 10^{31}$$

$$E_g = 1.12 \text{ eV for silicon}$$

$$k = 8.62 \times 10^{-5} \frac{\text{eV}}{\text{K}}$$

Fraction of ionized atoms =  $n_i / 5 \times 10^{22}$ ;  $T = 273 + x^\circ\text{C}$

| T (K) | $n_i$ (carriers/cm <sup>3</sup> ) | Fraction of ionized atoms. |
|-------|-----------------------------------|----------------------------|
| 253   | $2.68 \times 10^5$                | $5.37 \times 10^{-18}$     |
| 273   | $1.53 \times 10^9$                | $3.07 \times 10^{-14}$     |
| 293   | $8.65 \times 10^9$                | $1.73 \times 10^{-13}$     |
| 373   | $1.44 \times 10^{12}$             | $2.89 \times 10^{-11}$     |
| 398   | $4.75 \times 10^{12}$             | $9.51 \times 10^{-11}$     |

3.107

(a) intrinsic silicon

$$\rho = \frac{1}{q(p\mu_p + n\mu_n)}$$

$$= \frac{1}{1.6 \times 10^{-19} (1.5 \times 10^{10} \times 480 + 1.5 \times 10^{10} \times 1350)}$$

$$= 2.28 \times 10^5 \Omega \cdot \text{cm}$$

$$R = \rho L/A = 2.28 \times 10^5 \frac{10 \times 10^{-4}}{3.4 \times 10^{-4}} = 7.6 \times 10^4 \Omega$$

(b)

$$\rho = \frac{1}{q(p\mu_p + n\mu_n)}$$

$$= \frac{1}{(1.6 \times 10^{-19}) \left( \frac{(1.5 \times 10^{10})^2}{10^{16}} \times \frac{1200}{2.5} + 10^{16} \times 1200 \right)}$$

$$= 0.521 \Omega \cdot \text{cm}$$

$$R = \rho \times 10^4 / 3 = 1.74 \text{ k}\Omega$$

(c) n doped  $N_D = n_{no} = 10^{18}$   
 $n_{po} = n_i^2 / n_{no}$

$$\rho = \frac{1}{1.6 \times 10^{-19} \left( \frac{(1.5 \times 10^{10})^2}{10^{18}} \times \frac{1100}{2.5} + 10^{18} \times 1200 \right)}$$

$$= 5.21 \times 10^{-3} \Omega \cdot \text{cm}$$

$$R = \rho \frac{10^4}{3} = 17.4 \Omega$$

(d) P doped  $N_A = p_{po} = 10^{10} / \text{cm}^3$

$$\rho = \frac{1}{q(p\mu_p + n\mu_n)}$$

$$= \frac{1}{1.6 \times 10^{-19} \left( \frac{10^{10} \times 1200}{2.5} + \frac{(1.5 \times 10^{10})^2}{10^{10}} \times 1200 \right)}$$

$$= 2.05 \times 10^4 \Omega \cdot \text{cm}$$

$$R = \rho \frac{10^4}{3} = 68.35 \text{ k}\Omega$$

$$(e) R = 2.8 \times 10^4 / 3 = 0.933 \Omega$$

3.108

$$\rho_{no} = \frac{n_i^2}{N_D} = \frac{(1.5 \times 10^{10})^2}{10^{16}} = 2.25 \times 10^4 / \text{cm}^3$$

CONT.

$$\frac{dP}{dx} = \frac{1000 P_{A0} - P_{A0}}{W}$$

$$\approx \frac{2.25 \times 10^{-1}}{5 \times 10^{-4}}$$

$$J_p = -q D_p \frac{dP}{dx}$$

$$= -1.6 \times 10^{-19} \times 12 \times \frac{-2.25 \times 10^{-1}}{5 \times 10^{-4}}$$

$$= \underline{8.64 \times 10^{-8} \text{ A/cm}^2}$$

3.109

$$V_{\text{drift},p} = \mu_p E$$

$$= 480 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \times \frac{1}{10^{-3}} \frac{\text{V}}{\text{cm}}$$

$$= \underline{4.8 \times 10^5 \text{ cm/s}}$$

$$V_{\text{drift},n} = \mu_n E$$

$$= 1350 \frac{\text{cm}^2}{\text{V}\cdot\text{s}} \times \frac{1}{10^{-3}} \frac{\text{V}}{\text{cm}}$$

$$= \underline{1.35 \times 10^6 \text{ cm/s}}$$

3.110

$$J_{\text{drift}} = q (n \mu_n + p \mu_p) E \quad \text{A/cm}^2$$

$$I_{\text{drift}} = q (n \mu_n + p \mu_p) E \cdot A$$

$$= 1.6 \times 10^{-19} (10^{15} \cdot 1350 + 10^{15} \cdot 480) \times \frac{1}{10^{-3}} \times (5 \times 10^{-8})$$

$$= \underline{15.36 \mu\text{A}}$$

3.111

$$E = \frac{1 \text{ V}}{10 \times 10^{-4}} = \frac{1}{10^{-3}} \frac{\text{V}}{\text{cm}}$$

$$n_{A0} = N_D \quad P_{A0} = \frac{n_i^2}{N_D} \quad \text{assume } P_{A0} \ll n_{A0}$$

$$\therefore J_{\text{drift}} = q (\mu_n n + \mu_p p) E = \frac{10^{-3}}{10^{-8}} \frac{\text{A}}{\text{cm}^2}$$

$$\approx 1.6 \times 10^{-19} (1350 N_D) \frac{1}{10^{-3}} = 10^5$$

$$N_D = 4.6 \times 10^{17} / \text{cm}^3$$

3.112

$$P_{A0} = N_A = 10^{16} / \text{cm}^3 \quad \text{at all temperatures}$$

$$\text{At } 25^\circ\text{C} \approx 300\text{K}$$

$$n_i^2 = B T^3 e^{-E_g/kT}$$

$$= 5.4 \times 10^{31} (300)^3 e^{-1.12/(8.62 \times 10^{-5} (300))}$$

$$= 2.26 \times 10^{20}$$

$$n_{A0} = \frac{n_i^2}{N_A} = \underline{2.26 \times 10^4 / \text{cm}^3}$$

$$\text{At } 125^\circ\text{C} \approx 400\text{K}$$

$$n_i^2 = 5.4 \times 10^{31} (400)^3 e^{-1.12/(8.62 \times 10^{-5} (400))}$$

$$= 2.7 \times 10^{25}$$

$$n_{A0} = \frac{n_i^2}{N_A} = \underline{2.7 \times 10^9 / \text{cm}^3}$$

3.113

| DOPING CONCENTRATION | $\mu_n$<br>$\text{cm}^2/\text{V}\cdot\text{s}$ | $\mu_p$<br>$\text{cm}^2/\text{V}\cdot\text{s}$ | $D_n$<br>$\text{cm}^2/\text{s}$ | $D_p$<br>$\text{cm}^2/\text{s}$ |
|----------------------|------------------------------------------------|------------------------------------------------|---------------------------------|---------------------------------|
| INTRINSIC            | 1350                                           | 480                                            | 34                              | 12                              |
| $10^{16}$            | 1100                                           | 400                                            | 28                              | 10                              |
| $10^{17}$            | 700                                            | 260                                            | 18                              | 6                               |
| $10^{18}$            | 360                                            | 150                                            | 9                               | 4                               |

$$\text{where } D_n = V_T \mu_n = \underline{0.025 \mu\text{m}}$$

$$D_p = V_T \mu_p = \underline{0.025 \mu\text{m}}$$

3.114

$$V_0 = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right) = 0.025 \ln \left( \frac{10^{16} 10^{16}}{10^{10}} \right) \\ = 1.27 \text{ V}$$

$$W_{\text{dep}} = x_n + x_p = \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) V_0} \\ = \sqrt{\frac{2(11.7) 8.85 \times 10^{-14}}{1.6 \times 10^{-19}} \left( \frac{1}{10^{16}} + \frac{1}{10^{16}} \right) 1.27} \\ = 57 \times 10^{-6} \text{ cm} \\ = \underline{0.57 \mu\text{m}}$$

$$\frac{x_n}{x_p} = \frac{N_D}{N_A} \Rightarrow x_n = x_p = \underline{0.28 \mu\text{m}}$$

$$q_J = q_N = q_P = q \frac{N_A N_D}{N_A + N_D} A W_{\text{dep}} \\ = \underline{45.6 \times 10^{-15} \text{ C}}$$

$$C_j = \frac{\epsilon_s A}{W_{\text{dep}}} = \frac{11.7 (8.85 \times 10^{-14}) \times 100 \times 10^{-8}}{0.57 \times 10^{-4}} \\ = \underline{18.2 \text{ fF}}$$

3.115

$$V_0 = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right) = 0.025 \ln \left( \frac{10^{16} 10^{15}}{10^{10}} \right) \\ = 0.633 \text{ V}$$

$$W_{\text{dep}} = x_n + x_p = \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) (V_0 + V_R)}$$

$$W_{\text{dep}} = \sqrt{\frac{2(11.7)(8.85 \times 10^{-14})}{1.6 \times 10^{-19}} \left( \frac{1}{10^{16}} + \frac{1}{10^{15}} \right) (0.633 + 5)} \\ = 2.83 \times 10^{-4} \text{ cm} = \underline{2.83 \mu\text{m}}$$

$$x_n = \frac{N_A}{N_D} x_p = 10 x_p$$

$$\therefore x_p = \frac{2.83}{11} = \underline{0.26 \mu\text{m}}$$

$$x_n = \underline{2.57 \mu\text{m}}$$

$$q_J = q_N = q_P = q \frac{N_A N_D}{N_A + N_D} A W_{\text{dep}} \\ = 1.6 \times 10^{-19} \left( \frac{10^{16} 10^{15}}{10^{16} + 10^{15}} \right) 400 \times 10^{-8} \times 2.83 \times 10^{-4} \\ = \underline{1.65 \times 10^{-13} \text{ C}}$$

$$C_j = \frac{\epsilon_s A}{W_{\text{dep}}} = \frac{11.7 (8.85 \times 10^{-14}) 400 \times 10^{-8}}{2.83 \times 10^{-4}} \\ = 14.6 \times 10^{-15} = \underline{14.6 \text{ fF}}$$

3.116

$$q_J = q_N \times A = 1.6 \times 10^{-19} \times 10^{16} \times 0.1 \times 10^{-4} \times \\ 100 \times 10^{-8} \\ = \underline{16 \text{ fC}}$$

3.117

$$q_J = q \frac{N_A N_D}{N_A + N_D} A W_{\text{dep}} \\ = q \frac{N_A N_D}{N_A + N_D} A \sqrt{\frac{2\epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) (V_0 + V_R)}$$

CONT.

$$\frac{d a_g}{d V_R} = \frac{q}{N_A + N_D} A \times \frac{1}{\sqrt{\frac{2 \epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right) (V_0 + V_R)}} \times \frac{q \epsilon_s}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right)$$

$$= \frac{\epsilon_s A}{W_{dep}}$$

3.118

$$C_j = \frac{C_{j0}}{(1 + V_R/V_0)^m}$$

$$V_R = 1V \quad C_j = \frac{0.6 \text{ pF}}{(1 + 1/0.75)^{1/3}} = 0.45 \text{ pF}$$

$$V_R = 10V \quad C_j = \frac{0.6 \text{ pF}}{(1 + 10/0.75)^{1/3}} = 0.25 \text{ pF}$$

3.119

$$V_Z = 10$$

$$I_D = \frac{1}{2} \left( \frac{0.25}{10} \right) = 12.5 \text{ mA}$$

Since breakdown occurs only half the time, the average breakdown current can be twice the continuous value i.e. it can be 25 mA if the dissipation is limited to half the rated value of 50 mW. If the dissipation is allowed to rise to the rated value.

3.120

$$I_P = A q n_i^2 \left( \frac{D_p}{L_p N_D} \right) (e^{V/V_T} - 1)$$

$$I_n = A q n_i^2 \left( \frac{D_n}{L_n N_A} \right) (e^{V/V_T} - 1)$$

$$\therefore \frac{I_P}{I_n} = \frac{D_p L_n N_A}{D_n L_p N_D} = \frac{10 \times 10 \times 10^{18}}{20 \times 5 \times 10^{18}} = 100$$

$$I = I_P + I_n = 100 I_n + I_n = 1 \text{ mA}$$

$$I_n = 1/101 = 9.9 \mu\text{A}$$

$$I_P = 100(9.9) = 990 \mu\text{A}$$

3.121

$$I_P = A q n_i^2 \frac{D_p}{L_p N_D} (e^{V/V_T} - 1)$$

$$I_n = A q n_i^2 \frac{D_n}{L_n N_A} (e^{V/V_T} - 1)$$

For  $p^+ - n$   $N_A \gg N_D$

$$\therefore I \cong I_P = A q n_i^2 \frac{D_p}{L_p N_D} (e^{V/V_T} - 1)$$

$$I_S \cong A q n_i^2 \frac{D_p}{L_p N_D} = A q n_i^2 \left( \frac{D_p}{\sqrt{D_p \tau_p} N_D} \right)$$

$$= 10^4 (10^{-8}) 1.6 \times 10^{-19} \frac{(1.5 \times 10^{10})^2}{\sqrt{10 \times 0.1 \times 10^{-6}} \times 5 \times 10^{16}}$$

$$= 0.72 \times 10^{-15} \text{ A}$$

CONT.



# Chapter 4 - Problems

4.1

The capacitance per unit area is:  $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$

$$\epsilon_{ox} = 3.45 \times 10^{-11} \text{ F/m}$$

$$t_{ox} = 5 \text{ nm} \Rightarrow C_{ox} = \frac{3.45 \times 10^{-11}}{5 \times 10^{-9}} = 6.9 \text{ fF}/\mu\text{m}^2$$

$$t_{ox} = 40 \text{ nm} \Rightarrow C_{ox} = 0.86 \text{ fF}/\mu\text{m}^2$$

For 1pF capacitance, we require an area A:

$$A = \frac{10^{-12}}{6.9 \times 10^{-15}} = 145 \mu\text{m}^2 \text{ for } t_{ox} = 5 \text{ nm}$$

$$A = \frac{10^{-12}}{0.86 \times 10^{-15}} = 1163 \mu\text{m}^2 \text{ for } t_{ox} = 20 \text{ nm}$$

For a square plate capacitor of 10pF:

$$A = 10 \times 145 = 1450 \mu\text{m}^2 \text{ or } 38 \times 38 \mu\text{m}^2 \text{ square for } t_{ox} = 5 \text{ nm}$$


$$A = 10 \times 1163 = 11630 \mu\text{m}^2 \text{ or } 108 \times 108 \mu\text{m}^2 \text{ square for } t_{ox} = 20 \text{ nm}$$

4.2

Drain current is directly proportional to the width of the channel. Therefore if width is 10 times greater, then  $i_D$  would be 10 times greater as well.

$K = \text{Constant of proportionality} =$
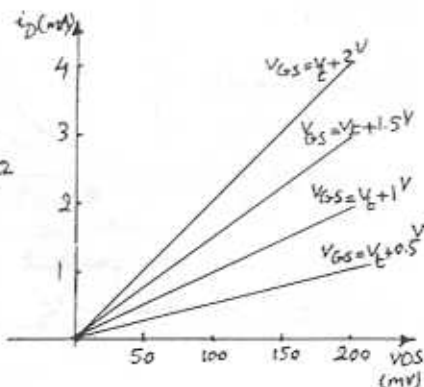
$$\frac{1}{0.5 \times 0.2} = 10 \text{ mA}/V^2$$



$$r_{DS} = \frac{i_D}{V_{DS}} = \frac{1}{0.2} = 5 \text{ k}\Omega \text{ for } V_{OV} = 0.5 \text{ V}$$

$$r_{DS} = 10 \text{ k}\Omega \text{ for } V_{OV} = 1 \text{ V}$$

$$r_{DS} = 15 \text{ k}\Omega \text{ for } V_{OV} = 1.5 \text{ V}$$

$$r_{DS} = 20 \text{ k}\Omega \text{ for } V_{OV} = 2 \text{ V}$$

$$5 \text{ k}\Omega \leq r_{DS} \leq 20 \text{ k}\Omega \text{ for } 0.5 \text{ V} \leq V_{OV} \leq 2 \text{ V}$$

4.3

$$\text{eq. 4.6a: } i_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_T)^2 \quad K'_n = \mu_n C_{ox}$$

for equal drain currents:

$$\mu_n C_{ox} \frac{W_n}{L} = \mu_p C_{ox} \frac{W_p}{L} \Rightarrow \frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} = \frac{1}{0.4} = 2.5$$

4.4

$$\text{for small } V_{DS}: i_D \approx K'_n \frac{W}{L} (V_{GS} - V_T) V_{DS}$$

$$r_{DS} = \frac{V_{DS}}{i_D} = \frac{1}{K'_n \frac{W}{L} (V_{GS} - V_T)} = \frac{1}{50 \times 10^{-6} \times 20 \times (5 - 0.8)}$$

$$r_{DS} = 238 \Omega \quad V_{DS} = r_{DS} \times i_D = 238 \text{ mV}$$

for the same performance of a p-channel device:

$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p} = 2.5 \Rightarrow \frac{W_p}{L} = \frac{W_n}{L} \times 2.5 = 20 \times 2.5$$

$$\Rightarrow \frac{W_p}{L} = 50$$

4.5

$$\text{Eq. 4.5a: } i_D = K'_n \frac{W}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right] \text{ triode region}$$

for small  $V_{DS}$ :

$$i_D \approx K'_n \frac{W}{L} (V_{GS} - V_T) V_{DS}$$

$$r_{DS} = \frac{V_{DS}}{i_D} = \frac{1}{K'_n \frac{W}{L} (V_{GS} - V_T)}$$

for  $r_{DS} = 1 \text{ k}\Omega$ :

$$K'_n = 100 \text{ mA}/V^2: 1000 = \frac{1}{100 \times 10^{-6} \times \frac{W}{L} \times (5 - 0.8)} \Rightarrow W = 2.4 \mu\text{m}$$

4.6

$$\text{a) } C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{3.45 \times 10^{-11}}{15 \times 10^{-9}} = 2.3 \text{ fF}/\mu\text{m}^2$$

$$K'_n = \mu_n C_{ox} = 550 \times 10^{-4} \times 2.3 \times 10^{-3} = 126.5 \text{ mA}/V^2$$

$$\text{b) } i_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_T)^2 = 100 = \frac{1}{2} \times 126.5 \times \frac{16}{0.8} (V_{GS} - 0.7)^2$$

$$V_{GS} - 0.7 = 0.28 \Rightarrow V_{OV} = 0.28 \text{ V}$$

$$V_{GS} = 0.98 \text{ V}$$

$$V_{DSmin} = V_{GS} - V_T = 0.28 \text{ V}$$

$$\text{c) for small } V_{DS} \text{ (triode region)} i_D \approx K'_n \frac{W}{L} V_{OV} V_{DS}$$

Cont.