

$$\text{P 1.8} \quad n = \frac{35 \times 10^{-6} \text{ C/s}}{1.6022 \times 10^{-19} \text{ C/elec}} = 2.18 \times 10^{14} \text{ elec/s}$$

P 1.9 First we use Eq. (1.2) to relate current and charge:

$$i = \frac{dq}{dt} = 24 \cos 4000t$$

$$\text{Therefore, } dq = 24 \cos 4000t \, dt$$

To find the charge, we can integrate both sides of the last equation. Note that we substitute x for q on the left side of the integral, and y for t on the right side of the integral:

$$\int_{q(0)}^{q(t)} dx = 24 \int_0^t \cos 4000y \, dy$$

We solve the integral and make the substitutions for the limits of the integral, remembering that $\sin 0 = 0$:

$$q(t) - q(0) = 24 \left. \frac{\sin 4000y}{4000} \right|_0^t = \frac{24}{4000} \sin 4000t - \frac{24}{4000} \sin 4000(0) = \frac{24}{4000} \sin 4000t$$

But $q(0) = 0$ by hypothesis, i.e., the current passes through its maximum value at $t = 0$, so $q(t) = 6 \times 10^{-3} \sin 4000t \text{ C} = 6 \sin 4000t \text{ mC}$

$$\text{P 1.10} \quad w = qV = (1.6022 \times 10^{-19})(6) = 9.61 \times 10^{-19} = 0.961 \text{ aJ}$$

$$\text{P 1.11} \quad p = (9)(100 \times 10^{-3}) = 0.9 \text{ W}; \quad 5 \text{ hr} \cdot \frac{3600 \text{ s}}{1 \text{ hr}} = 18,000 \text{ s}$$

$$w(t) = \int_0^t p \, dt \quad w(18,000) = \int_0^{18,000} 0.9 \, dt = 0.9(18,000) = 16.2 \text{ kJ}$$

P 1.12 Assume we are standing at box A looking toward box B. Then, using the passive sign convention $p = vi$, since the current i is flowing into the + terminal of the voltage v . Now we just substitute the values for v and i into the equation for power. Remember that if the power is positive, B is absorbing power, so the power must be flowing from A to B. If the power is negative, B is generating power so the power must be flowing from B to A.


$$[\text{a}] \quad p = (120)(5) = 600 \text{ W} \quad 600 \text{ W from A to B}$$

$$[\text{b}] \quad p = (250)(-8) = -2000 \text{ W} \quad 2000 \text{ W from B to A}$$

$$[\text{c}] \quad p = (-150)(16) = -2400 \text{ W} \quad 2400 \text{ W from B to A}$$

$$[\text{d}] \quad p = (-480)(-10) = 4800 \text{ W} \quad 4800 \text{ W from A to B}$$

P 1.13 [a]

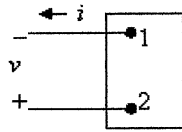

$$p = vi = (40)(-10) = -400 \text{ W}$$

Power is being delivered by the box.


[b] Leaving

[c] Gaining

P 1.14 [a] $p = vi = (-60)(-10) = 600 \text{ W}$, so power is being absorbed by the box.

[b] Entering

[c] Losing

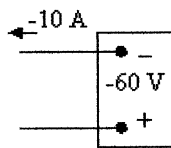

P 1.15 [a] In Car A, the current i is in the direction of the voltage drop across the 12 V battery (the current i flows into the + terminal of the battery of Car A). Therefore using the passive sign convention,

$$p = vi = (30)(12) = 360 \text{ W}.$$

Since the power is positive, the battery in Car A is absorbing power, so Car A must have the "dead" battery.


[b] $w(t) = \int_0^t p dx; \quad 1 \text{ min} = 60 \text{ s}$

$$w(60) = \int_0^{60} 360 dx$$

$$w = 360(60 - 0) = 360(60) = 21,600 \text{ J} = 21.6 \text{ kJ}$$

P 1.16 $p = vi; \quad w = \int_0^t p dx$

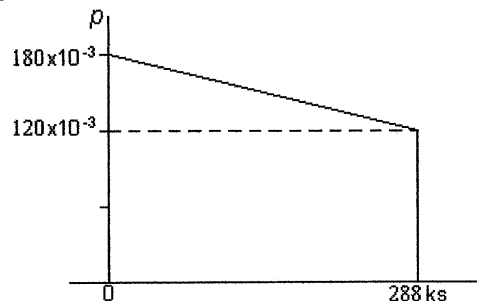Since the energy is the area under the power vs. time plot, let us plot p vs. t .



Note that in constructing the plot above, we used the fact that 80 hr = 288,000 s = 288 ks

$$p(0) = (9)(20 \times 10^{-3}) = 180 \times 10^{-3} \text{ W}$$

$$p(288 \text{ ks}) = (6)(20 \times 10^{-3}) = 120 \times 10^{-3} \text{ W}$$

$$w = (120 \times 10^{-3})(288 \times 10^3) + \frac{1}{2}(180 \times 10^{-3} - 120 \times 10^{-3})(288 \times 10^3) = 43.2 \text{ kJ}$$

P 1.17 [a] $p = vi = 30e^{-500t} - 30e^{-1500t} - 40e^{-1000t} + 50e^{-2000t} - 10e^{-3000t}$
 $p(1 \text{ ms}) = 3.1 \text{ mW}$

[b] $w(t) = \int_0^t (30e^{-500x} - 30e^{-1500x} - 40e^{-1000x} + 50e^{-2000x} - 10e^{-3000x}) dx$
 $= 21.67 - 60e^{-500t} + 20e^{-1500t} + 40e^{-1000t} - 25e^{-2000t} + 3.33e^{-3000t} \mu\text{J}$

$$w(1 \text{ ms}) = 1.24 \mu\text{J}$$

[c] $w_{\text{total}} = 21.67 \mu\text{J}$

P 1.18 [a] $v(10 \text{ ms}) = 400e^{-1} \sin 2 = 133.8 \text{ V}$
 $i(10 \text{ ms}) = 5e^{-1} \sin 2 = 1.67 \text{ A}$
 $p(10 \text{ ms}) = vi = 223.79 \text{ W}$

[b] $p = vi = 2000e^{-200t} \sin^2 200t$
 $= 2000e^{-200t} \left[\frac{1}{2} - \frac{1}{2} \cos 400t \right]$
 $= 1000e^{-200t} - 1000e^{-200t} \cos 400t$
 $w = \int_0^\infty 1000e^{-200t} dt - \int_0^\infty 1000e^{-200t} \cos 400t dt$
 $= 1000 \frac{e^{-200t}}{-200} \Big|_0^\infty - 1000 \left\{ \frac{e^{-200t}}{(200)^2 + (400)^2} [-200 \cos 400t + 400 \sin 400t] \right\} \Big|_0^\infty$
 $= 5 - 1000 \left[\frac{200}{4 \times 10^4 + 16 \times 10^4} \right] = 5 - 1$
 $w = 4 \text{ J}$

P 1.19 [a] $0 \text{ s} \leq t < 4 \text{ s}$:

$$v = 2.5t \text{ V}; \quad i = 1 \mu\text{A}; \quad p = 2.5t \mu\text{W}$$

$4 \text{ s} < t \leq 8 \text{ s}$:

$$v = 10 \text{ V}; \quad i = 0 \text{ A}; \quad p = 0 \text{ W}$$

$8 \text{ s} \leq t < 16 \text{ s}$:

$$v = -2.5t + 30 \text{ V}; \quad i = -1 \mu\text{A}; \quad p = 2.5t - 30 \mu\text{W}$$

$16 \text{ s} < t \leq 20 \text{ s}$:

$$v = -10 \text{ V}; \quad i = 0 \text{ A}; \quad p = 0 \text{ W}$$

$20 \text{ s} \leq t < 36 \text{ s}$:

$$v = t - 30 \text{ V}; \quad i = 0.4 \mu\text{A}; \quad p = 0.4t - 12 \mu\text{W}$$

$36 \text{ s} < t \leq 46 \text{ s}$:


$$v = 6 \text{ V}; \quad i = 0 \text{ A}; \quad p = 0 \text{ W}$$

$46 \text{ s} \leq t < 50 \text{ s}$:

$$v = -1.5t + 75 \text{ V}; \quad i = -0.6 \mu\text{A}; \quad p = 0.9t - 45 \mu\text{W}$$

$t > 50 \text{ s}$:
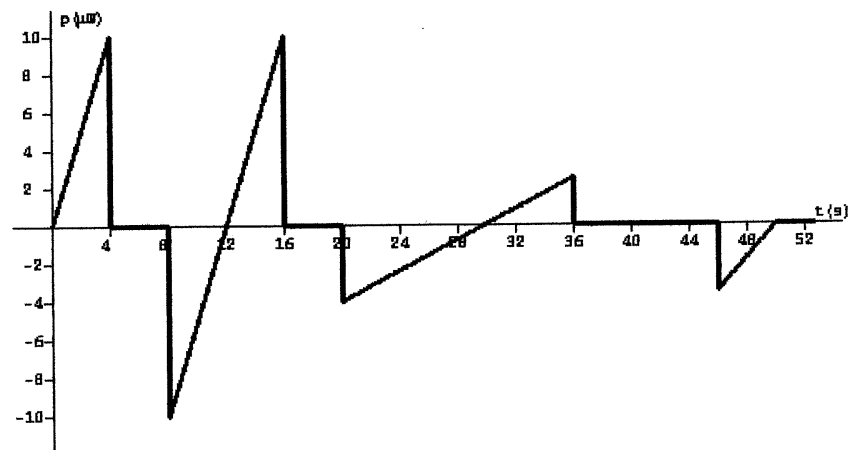
$$v = 0 \text{ V}; \quad i = 0 \text{ A}; \quad p = 0 \text{ W}$$



[b] Calculate the area under the curve from zero up to the desired time:

$$w(4) = \frac{1}{2}(4)(10) = 20 \mu\text{J}$$

$$w(12) = w(4) - \frac{1}{2}(4)(10) = 0 \text{ J}$$

$$w(36) = w(12) + \frac{1}{2}(4)(10) - \frac{1}{2}(10)(4) + \frac{1}{2}(6)(2.4) = 7.2 \mu\text{J}$$

$$w(50) = w(36) - \frac{1}{2}(4)(3.6) = 0 \text{ J}$$

$$\sum P_{\text{del}} = 2000 + 2100 = 4100 \text{ W}$$

$$\sum P_{\text{abs}} = 750 + 500 + 600 + 50 + 1400 + 800 = 4100 \text{ W}$$

Now the power delivered equals the power absorbed and the power balances for the circuit.

$$\text{P 1.28 } p_a = -v_a i_a = -(36)(250 \times 10^{-6}) = -9 \text{ mW}$$

$$p_b = v_b i_b = (44)(-250 \times 10^{-6}) = -11 \text{ mW}$$

$$p_c = v_c i_c = (28)(-250 \times 10^{-6}) = -7 \text{ mW}$$

$$p_d = v_d i_d = (-108)(100 \times 10^{-6}) = -10.8 \text{ mW}$$

$$p_e = v_e i_e = (-32)(150 \times 10^{-6}) = -4.8 \text{ mW}$$

$$p_f = -v_f i_f = -(60)(-350 \times 10^{-6}) = 21 \text{ mW}$$

$$p_g = v_g i_g = (-48)(-200 \times 10^{-6}) = 9.6 \text{ mW}$$

$$p_h = v_h i_h = (80)(-150 \times 10^{-6}) = -12 \text{ mW}$$

$$p_j = -v_j i_j = -(80)(-300 \times 10^{-6}) = 24 \text{ mW}$$

Therefore,

$$\sum P_{\text{abs}} = 21 + 9.6 + 24 = 54.6 \text{ mW}$$

$$\sum P_{\text{del}} = 9 + 11 + 7 + 10.8 + 4.8 + 12 = 54.6 \text{ W}$$

$$\sum P_{\text{abs}} = \sum P_{\text{del}}$$

Thus, the interconnection satisfies the power check

$$\text{P 1.29 } p_a = -v_a i_a = -(1.6)(0.080) = -128 \text{ mW}$$

$$p_b = -v_b i_b = -(2.6)(0.060) = -156 \text{ mW}$$

$$p_c = v_c i_c = (-4.2)(-0.050) = 210 \text{ mW}$$

$$p_d = -v_d i_d = -(1.2)(0.020) = -24 \text{ mW}$$

$$p_e = v_e i_e = (1.8)(0.030) = 54 \text{ mW}$$

$$p_f = -v_f i_f = -(-1.8)(-0.040) = -72 \text{ mW}$$

$$p_g = v_g i_g = (-3.6)(-0.030) = 108 \text{ mW}$$

$$p_h = v_h i_h = (3.2)(-0.020) = -64 \text{ mW}$$

$$p_j = -v_j i_j = -(-2.4)(0.030) = 72 \text{ mW}$$

$$\sum P_{\text{del}} = 128 + 156 + 24 + 72 + 64 = 444 \text{ mW}$$

$$\sum P_{\text{abs}} = 210 + 54 + 108 + 72 = 444 \text{ mW}$$