

Answer All Questions.

Question #1

The switch in Figure (1) has been closed for a long time. At $t=0$, it is opened

- Find I_L for $t < 0$.
- Just after the switch is opened find, $I_L(0^+)$
- Find $I_L(\infty)$
- Derive an expression for $I_L(t)$ for $t > 0$
- Sketch $I_L(t)$ against time.

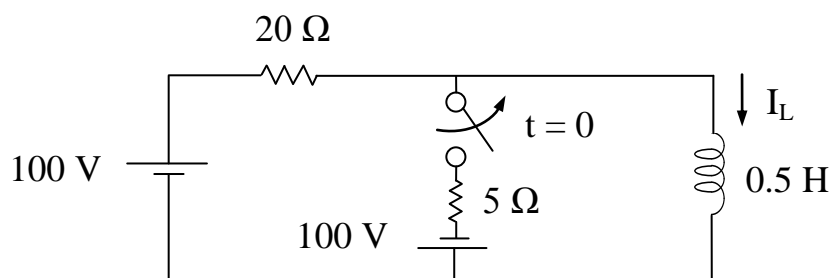


Fig. (1)

Question #2

In the circuit shown in Figure (2), the switch has been closed for a long time. At $t=0$ it is opened. Find $V_C(t)$ for $t > 0$.

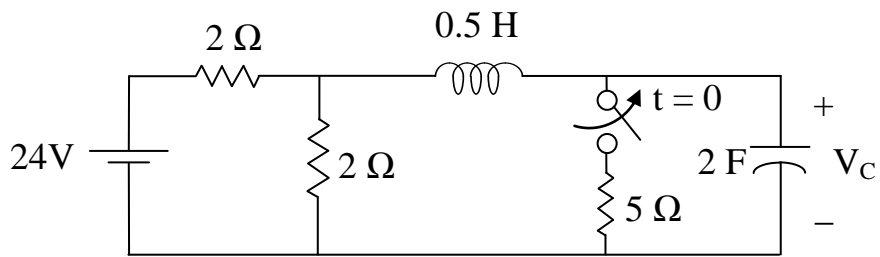


Fig. (2)

Question #3

A) For the circuit shown in Figure (3), find the coupling coefficient and $V(t)$.

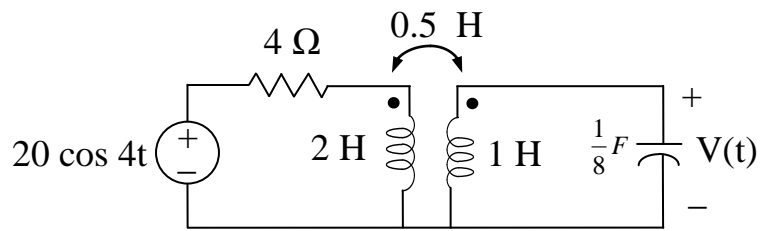


Fig. (3)

B) For the following Laplace transform functions $F(s)$ find the corresponding $f(t)$

i)
$$F(s) = \frac{s + 3}{(s + 1)(s + 2)}$$

ii)
$$F(s) = \frac{4}{(s+2)(s+1)^2}$$

iii)
$$F(s) = \frac{10}{(s+3)(s^2+6s+10)}$$

Question #4

A) An ideal voltage source $V_s = 100 \cos(\omega t)$ V, where ω is variable, is applied to a series *RLC* circuit with $C = 0.25 \mu\text{F}$. At resonance ($\omega = \omega_0$), the circuit current is $I = 1 \cos(\omega_0 t)$ A. When $\omega = 5200$ rad/s, $I = (1/\sqrt{2}) \cos(5200t - 45^\circ)$ A.

Determine:-

- i) R
- ii) L
- iii) Resonant frequency ω_0
- iv) Bandwidth
- v) Quality factor

B) Obtain the transfer function V_o/V_i of the circuit in Figure (4). What type of filter is this circuit? Give its cut-off frequency.

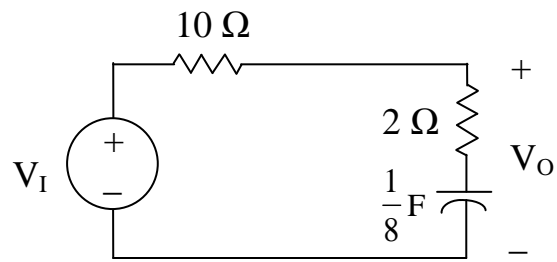


Fig. (4)

Question #5

A) Obtain the Z parameters for the network shown in Figure (4).

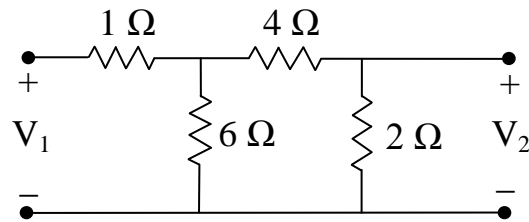


Fig. (5)

B) A two port circuit has the following y parameters

$$y_{11} = 0.5\ \text{S} \qquad y_{12} = y_{21} = -0.4\ \text{S} \qquad y_{22} = 0.6\ \text{S}$$

If a $2\text{-}\Omega$ load resistance is connected to port 2, determine the ratio V_2/V_1 and I_2/I_1 .

C) On the attached graph paper, construct the Bode magnitude plot for

$$H(s) = \frac{40(s+1)}{(s+20)(s+100)}$$