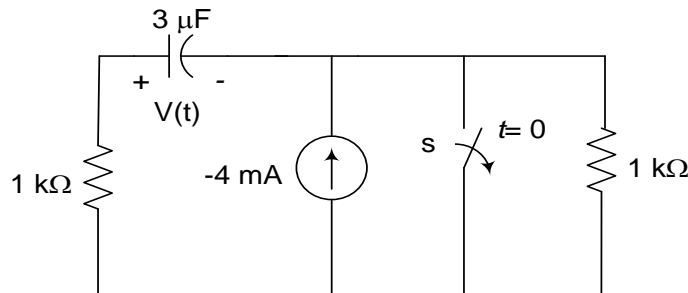


Question #1 [10 marks]

In the circuit shown in Fig.1 the switch has been closed for a long time. At $t = 0$ it is opened. Determine an expression for $v(t)$ for $t \geq 0$ and draw a sketch to show its variation with time.





(Fig.1)

Solution:

With switch closed the current source is shorted and hence $V(0^-) = 0$.

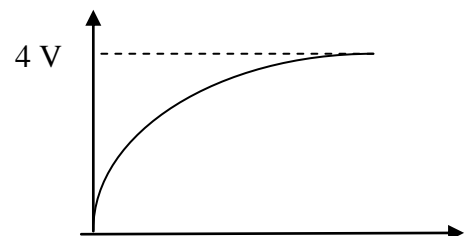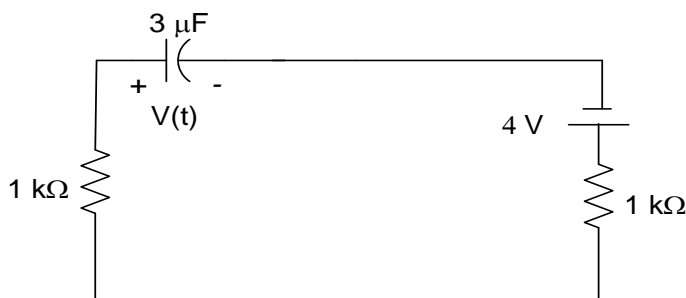With switch S open, converting current source to voltage source $V(\infty) = 4 \text{ V}$.




$$\tau = RC = 6 \times 10^{-3} \text{ S.}$$

$$V(t) = 4 - 4e^{-166.67t}$$

Question #2 [15 marks]

In the circuit shown in Fig.2 both switches have been open for a long time. Switch S_1 is closed first at $t=0$ and then switch S_2 is closed at $t= 4$ seconds later. Both switches remain closed.

- Determine an expression for $i(t)$ for $0 \leq t \leq 4\text{s}$ and for $4\text{s} \leq t \leq \infty$.
- Find the magnitude of current i at $t= 2 \text{ s}$ and $t = 5\text{s}$.
- Draw a sketch to show variation of $i(t)$ with time for $0 \leq t \leq \infty$.

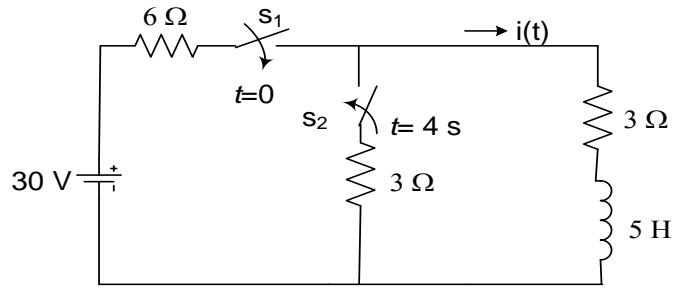

(Fig.2)

Solution:

a) With switch S1 closed,


$I_V = 0, FV = 30/(6+3) = 3.33 \text{ A}$ Therefore $I(t) = 3.33 - 3.33 e^{-t/\tau}$ where $\tau = L/R = 5/9 = 0.55 \text{ S}$.

Therefore the expression for current is

$$i(t) = 3.33 - 3.33 e^{-1.8t} \quad 0 \leq t \leq 4$$

When switch S2 closed at $t=4 \text{ S}$ the value of $i(4)$ is calculated by substituting $t=4 \text{ S}$ in the expression for $i(t)$ to get $i(4) = 3.33 - 3.33e^{-1.8 \times 4} = 3.33 \text{ A}$, (approximately). This will be the initial value when switch S2 is closed at $t=4 \text{ S}$.

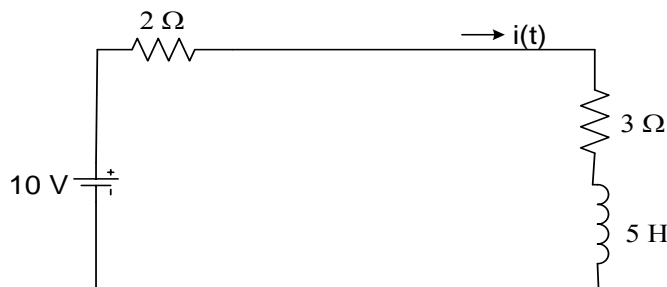By obtaining Thevenin equivalent circuit, the circuit becomes series as shown below




The final value of current is $10/(2+3) = 2 \text{ A}$, and $\tau = 5/5 = 1 \text{ S}$. The expression for current is

$$i(t) = 3.33e^{-(t-4)/\tau} = 3.33e^{-(t-4)} \quad 4 \leq t \leq \infty$$

Notice since 4s of time is already passed we subtract it from t in the expression.

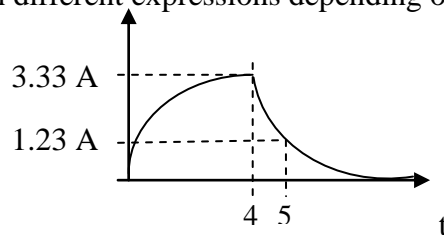
b) At $t=2$, $i = 3.33 - 3.33 e^{-1.8 \times 2} = 3.3 \text{ A}$ and At $t=5$, $i = 3.33 e^{-(5-4)} = 1.23 \text{ A}$

Notice we substitute in different expressions depending on the value of t.



Question # 3 [20 marks]


In the circuit shown (**Fig.3**), switch S has been closed for a long time. At $t=0$, it is opened. Find expression for $i(t)$ and $v(t)$.

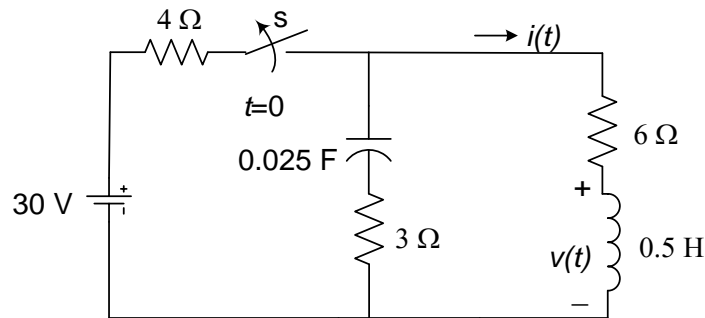

(Fig.3)

Solution:

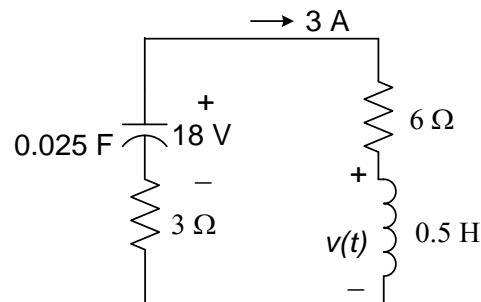With switch S closed for a long time the capacitor is open and fully charged 18 V (6Ω and 4Ω voltage divider). The inductor current will be $30/(4+6) = 3$ A. These will be the initial values when switch is open. When switch is open the circuit is series.



Series circuit with initial conditions

The differential equation for this circuit from $V_R + V_L + V_C = 0$ is:

$$\frac{d^2 I(t)}{d^2 t} + \frac{R}{L} \frac{dI(t)}{dt} + \frac{1}{LC} I(t) = 0$$

$$\frac{d^2 I(t)}{d^2 t} + 18 \frac{dI(t)}{dt} + 180 I(t) = 0$$

$$m^2 + 18m + 180 = 0$$

$$(m + 10)(m + 8) = 0$$

$$m = 10, m = 8$$

Assume solution $I(t) = Ae^{-10t} + Be^{-8t}$

Applying initial conditions,

$$I(0) = 3 = A + B$$

$$\frac{dI(t)}{dt} = -10Ae^{-10t} - 8Be^{-8t} = -10A - 8B \text{ at } t=0.$$

But $\frac{dI(t)}{dt}$ at $t=0$ is equal to $V_L(0)/L$

From the series circuit $V_L(0^+) = 18 - 3 \times 6 - 3 \times 3 = -9V$. Therefore $\frac{dI(t)}{dt} = -9/0.5 = -18$

Therefore $-10A - 8B = -18$

But $A + B = 3$. Therefore $A = -3$ and $B = 6$. Therefore $I(t) = 6e^{-8t} - 3e^{-10t}$

$V(t)$ is across the inductor, therefore $V(t) = L dI(t)/dt = 0.5 \times (-48e^{-8t} + 30e^{-10t})$

$$V(t) = 15e^{-10t} - 24e^{-8t}$$

Check: $V_L(0) = 15 - 24 = -9$