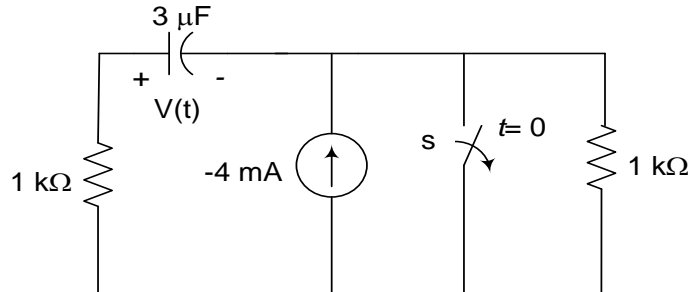


Question #1 [10 marks]

In the circuit shown in Fig.1 the switch has been closed for a long time. At $t = 0$ it is opened. Determine an expression for $v(t)$ for $t \geq 0$ and draw a sketch to show its variation with time.




(Fig.1)

Question #2 [15 marks]

In the circuit shown in Fig.2 both switches have been open for a long time. Switch S_1 is closed first at $t=0$ and then switch S_2 is closed at $t= 4$ seconds later. Both switches remain closed.


- Determine an expression for $i(t)$ for $0 \leq t \leq 4s$ and for $4s \leq t \leq \infty$.
- Find the magnitude of current i at $t= 2$ s and $t = 5s$.
- Draw a sketch to show variation of $i(t)$ with time for $0 \leq t \leq \infty$.

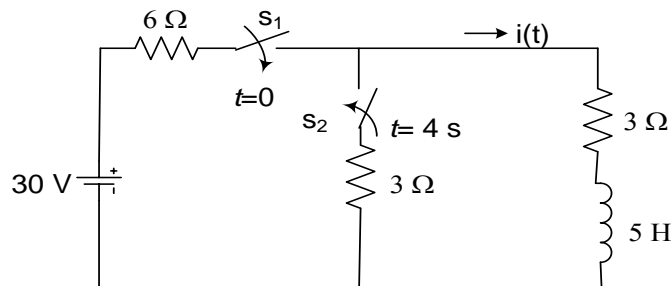

(Fig.2)

Question # 3 [20 marks]

In the circuit shown (Fig.3), switch S has been closed for a long time. At $t=0$, it is opened. Find expression for $i(t)$ and $v(t)$.

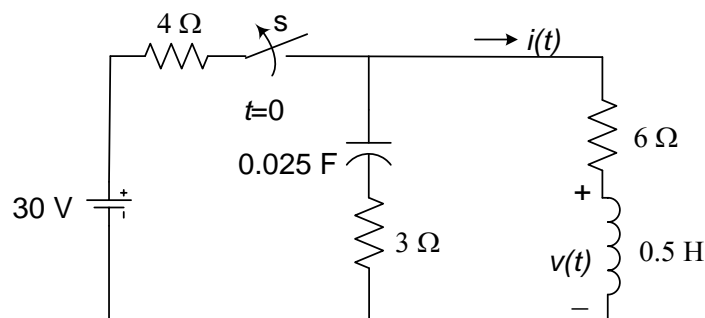

(Fig.3)