

---

## EXERCISES

Q1. Let  $E = (xy)' + x' + y = 1$ . Find  $E^d$ , ( $E^d$  or  $\bar{E}$  is the Duality of  $E$ )

---

Q2. Let  $B$  is a Boolean Algebra and  $x, y \in B$ . Show that  $x + y = xy + xy' + x'y$  is valid.

Q3. Let  $f(x, y, z) = x(y + z') + y'$ . Find  $CSP(f)$  (sum-of-products expansion) and  $CPS(f)$  (product-of-sums expansion) ?

---

Q4. Let  $f(x, y, z) = x'z + yz'$ . Find  $CSP(f)$  (sum-of-products expansion)  
and  $CPS(f)$  (product-of-sums expansion) ?

Q5. Let  $f(x, y, z) = (x' + z)(x + y)$ . Find  $CSP(f)$  (sum-of-products expansion) and  $CPS(f)$  (product-of-sums expansion) ?

Q6. Let  $f(x, y, z) = (x' + y)' (x + y + z)$

- (i) Use NAND gates to construct circuits with this output.
- (ii) Use NOR gates to construct circuits with this output.

Q7. Let  $f(x, y, z) = (x + y)(x' + yz')$

- (i) Find  $CSP(f)$  and  $CPS(f)$ .
- (ii) Find  $MSP(f)$  and  $MPS(f)$ .
- (iii) Construct a minimal circuit using (AND-OR) gates, with  $f(x, y, z)$  output.

Q8. Let  $f(x, y, z) = xy' + xz + y'z' + x'yz'$

- (i) Find the Karnaugh -map for  $f(x, y, z)$  .
- (ii) Find  $MSP(f)$  and  $MPS(f)$  .
- (iii) Construct a minimal circuit using (AND-OR) gates, with  $f(x, y, z)$  output.
- (iv) Use NAND gates to construct circuits with  $f(x, y, z)$  output.
- (v) Use NOR gates to construct circuits with  $f(x, y, z)$  output.

Q9. Let  $g(x, y, z) = xy'z + x'yz + x'y'z' + y'z$

- (i) Find the Karnaugh -map for  $g(x, y, z)$ .
- (ii) Find  $MSP(g)$  and  $MPS(g)$ .
- (iii) Construct a minimal circuit using (AND-OR) gates, with  $g(x, y, z)$  output.
- (iv) Use NAND gates to construct circuits with  $g(x, y, z)$  output.
- (v) Use NOR gates to construct circuits with  $g(x, y, z)$  output.

Q10. Let

	$yz$	$yz'$	$y'z'$	$y'z$
$x$				
$x'$				

Be the Karnaugh -map for  $g(x, y, z)$ .

(i) Find  $MSP(g)$  and  $MPS(g)$ .

(ii) Construct a minimal circuit using (AND-OR) gates, with  $g(x, y, z)$  output.

(iii) Use NAND gates to construct circuits with  $g(x, y, z)$  output.

(iv) Use NOR gates to construct circuits with  $g(x, y, z)$  output.

Q11. Let

	$yz$	$yz'$	$y'z'$	$y'z$
$x$				
$x'$				

Be the Karnaugh -map for  $g(x, y, z)$ .

- (i) Find  $MSP(g)$  and  $MPS(g)$ .
- (ii) Construct a minimal circuit using (AND-OR) gates, with  $g(x, y, z)$  output.
- (iii) Use NAND gates to construct circuits with  $g(x, y, z)$  output.
- (iv) Use NOR gates to construct circuits with  $g(x, y, z)$  output.

Q12. Let

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

Be the Karnaugh -map for  $f(x, y, z)$  .

- (i) Find  $MSP(f)$  and  $MPS(f)$  .
- (ii) Construct a minimal circuit using (AND-OR) gates, with  $f(x, y, z)$  output.
- (iii) Use NAND gates to construct circuits with  $f(x, y, z)$  output.
- (iv) Use NOR gates to construct circuits with  $f(x, y, z)$  output.

Q13. Let

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

Be the Karnaugh -map for  $f(x, y, z)$  .

(i) Find  $MSP(f)$  and  $MPS(f)$  .

(ii) Construct a minimal circuit using (AND-OR) gates, with  $f(x, y, z)$  output.

(iii) Use NAND gates to construct circuits with  $f(x, y, z)$  output.

(iv) Use NOR gates to construct circuits with  $f(x, y, z)$

Q14. Let

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

Be the Karnaugh -map for  $f(x, y, z)$  .

- (i) Find  $MSP(f)$  and  $MPS(f)$  .
- (ii) Construct a minimal circuit using (AND-OR) gates, with  $f(x, y, z)$  output.
- (iii) Use NAND gates to construct circuits with  $f(x, y, z)$  output.
- (iv) Use NOR gates to construct circuits with  $f(x, y, z)$

Q15. Let

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

Be the Karnaugh -map for  $f(x, y, z)$  .

(i) Find  $MSP(f)$  and  $MPS(f)$  .

(ii) Construct a minimal circuit using (AND-OR) gates, with  $f(x, y, z)$  output.



(iii) Use NAND gates to construct circuits with  $f(x, y, z)$  output.

(iv) Use NOR gates to construct circuits with  $f(x, y, z)$

Q16.

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$	1	0	1	1
$xy'$	1	0	0	1
$x'y'$	0	0	0	0
$x'y$	1	1	0	0

Q17.

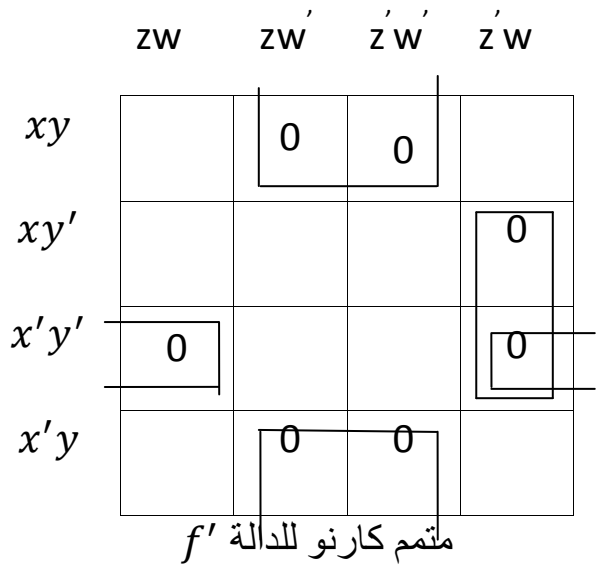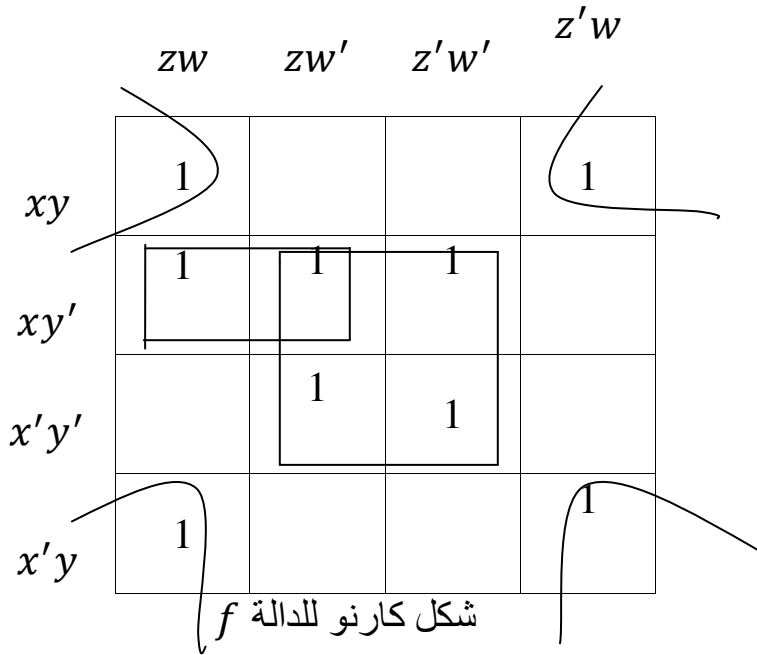

**ASSIGNMENT**

Q1. Find *CSP*(sum-of-products expansion) and *CPS* ( product-of-sums expansion ) for the following Boolean functions

$$1- f(x, y, z) = (x + z)(x' + y)' \quad 2- f(x, y, z) = z(y + x') + y' .$$

$$3- f(x, y, z) = (x + yz)(y + xz') . \quad 4- g(x, y, z) = xy + z .$$

$$5- f(x, y, z) = xy' + z . \quad 6- f(x, y, z) = (x' + y)'(yz')' .$$

$$7- g(x, y, z) = xz + y'z' . \quad 8- f(x, y, z) = 1 \text{ when } x = y .$$

Q2. Let  $h(x, y, z) = xy' + xyz + y'z' + x'yz'$

- (i) Find the Karnaugh -map for  $h(x, y, z)$  .
- (ii) Find  $MSP(h)$  and  $MPS(h)$  .
- (iii) Construct a minimal circuit using AND gates, OR gates, with  $h(x, y, z)$  output.
- (iv) Use NAND gates to construct circuits with  $h(x, y, z)$  output.
- (v) Use NOR gates to construct circuits with  $h(x, y, z)$  output.

Q3. Let  $f(x, y, z) = xy' + xz + yz + x'yz'$

- (i) Find the Karnaugh -map for  $f(x, y, z)$  .
- (ii) Find  $MSP(f)$  and  $MPS(f)$  .
- (iii) Construct a minimal circuit using AND gates, OR gates, with  $f(x, y, z)$  output.
- (iv) Use NAND gates to construct circuits with  $f(x, y, z)$  output.
- (v) Use NOR gates to construct circuits with  $f(x, y, z)$  output.

Q4. Let the Karnaugh -maps for  $f(x, y, z)$  given as bellow from exercise 1-15

- (i) Find  $MSP(f)$  and  $MPS(f)$ .
- (ii) Construct a minimal circuit using (AND-OR) gates, with  $f(x, y, z)$  output.
- (iii) Use NAND gates to construct circuits with  $f(x, y, z)$  output.
- (iv) Use NOR gates to construct circuits with  $f(x, y, z)$  output.

1-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

2-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

3-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

4-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

5-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

6-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

7-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

8-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

9-

$zW$   $zW'$   $z'W'$   $z'W$

$xy$				
$xy'$				
$x'y'$				
$x'y$				

10-

$zW$   $zW'$   $z'W'$   $z'W$

$xy$				
$xy'$				
$x'y'$				
$x'y$				

11-

$zW$   $zW'$   $z'W'$   $z'W$

$xy$				
$xy'$				
$x'y'$				
$x'y$				

12-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

13-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

14-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				

15-

	$zw$	$zw'$	$z'w'$	$z'w$
$xy$				
$xy'$				
$x'y'$				
$x'y$				