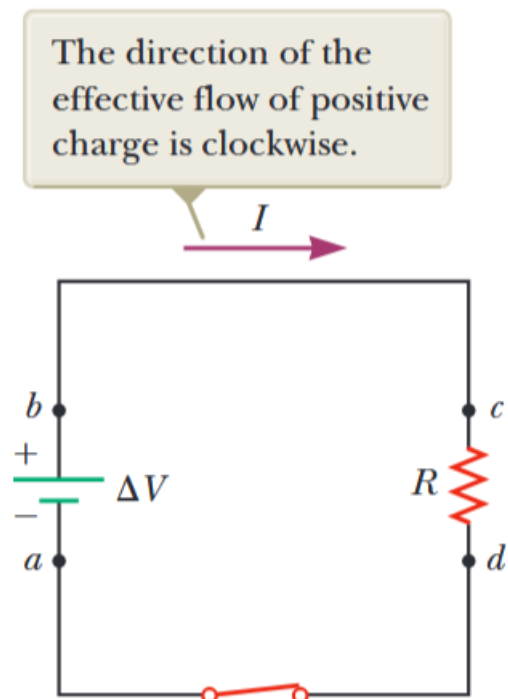


27-6 Electric energy and power:



If a battery is used to establish an electric current in a conductor, the chemical energy stored in the battery is continuously transformed into kinetic energy of the charge carriers.

In the conductor, this kinetic energy is quickly lost as a result of collisions between the charge carriers and the atoms making up the conductor, and this leads to an increase in the temperature of the conductor. In other words, the chemical energy stored in the battery is continuously transformed to internal energy associated with the temperature of the conductor.

Now imagine following a positive quantity of charge Q that is moving clockwise around the circuit (shown up) from point a through the battery and resistor back to point a .

As the charge Q moves from a to b through the battery, its electric potential energy U increases by an amount $(\Delta V \cdot \Delta Q)$ (where ΔV is the potential

difference between b and a), while the chemical potential energy in the battery decreases by the same amount. (Recall that: $\Delta U = q \cdot \Delta V$).

However, as the charge moves from c to d through the resistor, it loses this electric potential energy as it collides with atoms in the resistor, thereby producing internal energy. **If we neglect the resistance of the connecting wires**, no loss in energy occurs for paths bc and da. When the charge arrives at point a, it must have the same electric potential energy (zero) that it had at the start.

Note that because charge cannot build up at any point, the current is the same everywhere in the circuit.

The rate at which the charge Q loses potential energy in going through the resistor is

$$\frac{dU}{dt} = \frac{d}{dt}(q \cdot \Delta v) = \frac{dq}{dt} \Delta v = I \cdot \Delta v \quad (27-9)$$

where I is the current in the circuit. In contrast, the charge regains this energy when it passes through the battery.

Because the rate at which the charge loses energy equals the power delivered to the resistor (which appears as internal energy), we have

$$P = I \cdot \Delta v = I^2 \cdot R = \frac{(\Delta v)^2}{R} \quad (27-9)$$

◆ **Commercial Unit of Energy:**

- **Kilowatt-hour (kWh)** is used for billing electricity in homes.
- **1 kWh = 1000 W × 3600 s = 3.6 × 10⁶ J.**

◆ **Example Calculation:**

A 100W light bulb runs for 5 hours. How much energy does it consume?

$$E=(100\text{W})(5\text{h})=500\text{Wh}=0.5\text{kWh}$$

If electricity costs **\$0.20 per kWh**, the cost of using the bulb is:

$$\text{Cost}=0.5\times 0.20=0.10 \text{ dollars}$$

Example 27-7

An electric heater is constructed by applying a potential difference of 120 V to a Ni-chrome wire that has a total resistance of 8.0Ω . Find the current carried by the wire and the power rating of the heater.

Example 27-9

Estimate the cost of cooking a turkey for 4 h in an oven that operates continuously at 20.0 A and 240 V.