



CSC 220: Computer Organization

Unit 9

Counters & RAM

Prepared by:

Md Saiful Islam, PhD

Updated by:

Isra Al-Turaiki, PhD

Department of Computer Science

College of Computer and Information Sciences

Overview

- Counters:
 - Asynchronous (Ripple) Counters
 - Synchronous Counters
- Introduction to Memory
 - RAM
 - ROM

Chapter-6, 7

M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design**

Fundamentals, Global (5th) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124

Binary Counters

- A *counter* is sequential circuits which "counts" through a specific state sequence.
- A counter that follows the binary number sequence is called a *binary counter*.
- A *n*-bit binary counter
 - consists of *n* flip-flops
 - counts: $0 - (2^n - 1)$
- Example: 2 bit binary counter: $00 \rightarrow 01 \rightarrow 10 \rightarrow 11 \rightarrow 00$.

Binary Counters

- They can count **up**, count **down**, or count through other fixed sequences.
- Categories of Counter
 - **Ripple / asynchronous**: clock pulses are different for flip-flops
 - **Synchronous**: all flip-flops receive the same clock pulse

Ripple Counters

- The LSB is complemented by each count pulse.
- If Q_0 goes from 1 to 0, complement Q_1 .
- If Q_1 goes from 1 to 0, complement Q_2 .
- If Q_2 goes from 1 to 0, complement Q_3 and so on..


Upward Counting Sequence

Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Ripple Counters

- Consists of a series of **complementing** flip-flops (ex. JK).
- The **LSB flip-flop is connected to clock**.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.
- The state change of one flip-flop **triggers the next flip-flop** in line.
- An **n**-bit Asynchronous counter can have 2^n possible counting states
 - **Example:** 3-bit asynchronous counter
has (0-7) states and is called MOD-8 counter

2-bit Ripple Counter (MOD-4)


 


When Q'_0 goes from 0 to 1, Q_1 is complemented.

The LSB Q_0 is complemented with each clock pulse.



J	K	C_{FF1}	Q1	Q0	CLK
			0	0	
1	1		0	1	
1	1		1	0	
1	1		1	1	

2-bit Ripple Counter (MOD-4)

 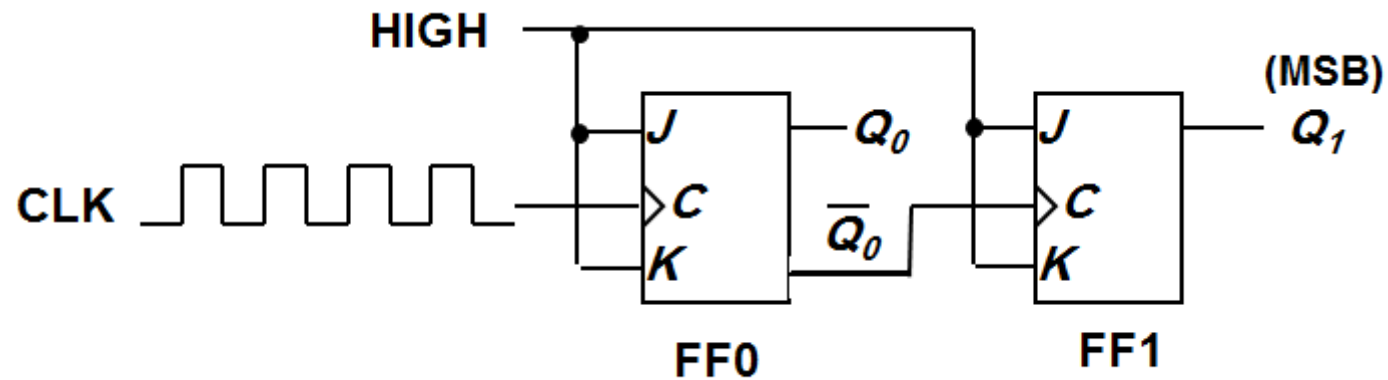

Timing diagram: 00 $\rightarrow$ 01 $\rightarrow$ 10 $\rightarrow$ 11 $\rightarrow$ 00...

2-bit Ripple Counter (MOD-4)

 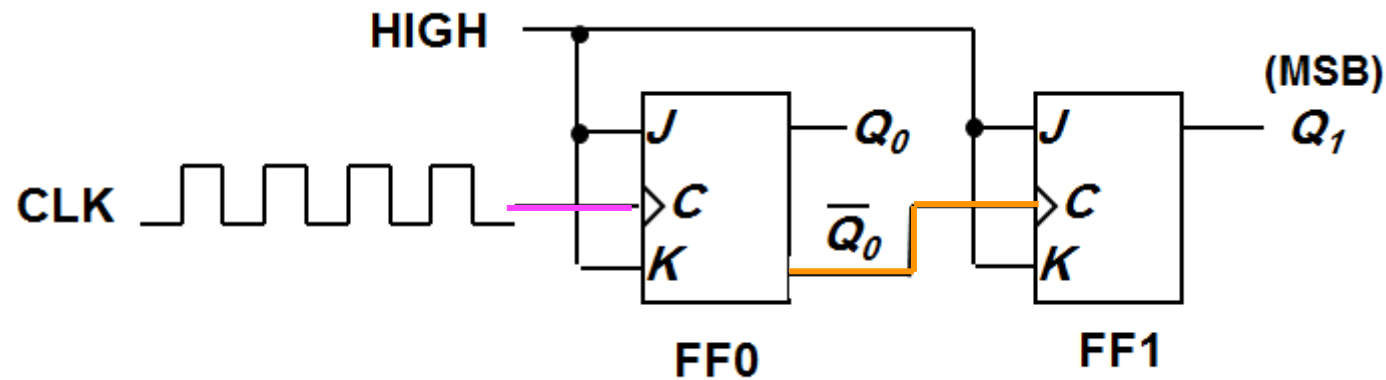



Q_0 will always be complemented on the rising

Q_1 will be complemented on the transition of Q_0 from 0 to 1

Timing diagram: 00 $\rightarrow$ 01 $\rightarrow$ 10 $\rightarrow$ 11 $\rightarrow$ 00...



3-bit Ripple Counter (MOD-8)

Design of a 3-bit ripple binary counter:

  

3-bit Ripple Counter (MOD-8)

Design of a 3-bit ripple binary counter:

  


Q_0 will always be complemented on the rising edge of CLK

Q_1 will be complemented on the transition of Q_0' from 0 to 1


Q_2 will be complemented on the transition of Q_1' from 0 to 1

Up and Down Counters

 - **Up counters:** count upward from zero to a maximum value, **and repeat**




 - **Down counters:** count downward from a maximum value to zero, **and repeat** (decrement by 1)



Asynchronous Counters with MOD no. $< 2^n$

 - Design of an asynchronous MOD-10 counter: counts (0-9)




- MOD-10 counter: known as **decade counter** or **BCD counter**
- Counter with 10 states (modulus-10) in their sequence
- They are commonly used in daily life (e.g.: utility meters, odometers, etc.).

				Q1	
	0 ₀	0 ₁	0 ₃	0 ₂	
	0 ₄	0 ₅	0 ₇	0 ₆	Q2
Q3	X ₁₂	X ₁₃	X ₁₅	X ₁₄	
	0 ₈	0 ₉	X ₁₁	1 ₁₀	
					Q0

Asynchronous Counters with MOD no. $< 2^n$

 
- Exercise: How to construct an asynchronous MOD-5 counter? MOD-7 counter? MOD-12 counter?
- **Question:** The following is a MOD-? counter?




The counter is to be cleared when it reaches the count of $(111100)_2$ so it is MOD-60.

Ripple Counter: Propagation Delays

 - *Propagation delay* is the time required for a change in value of a signal to propagate from input to output.
 - *high-to-low propagation time* t_{PHL}
 - *low-to-high propagation time* t_{PLH}
- If the accumulated delay is greater than the clock pulse, some counter states may be misrepresented!
- Large ripple counters can be slow circuits → synchronous binary counters are favored




Ripple Counter: Propagation Delays

 

Synchronous Counters

 - The **clock** applied to the C inputs of all flip-flops.
- **Count Enable:** If 0, “hold” the state
- 2-input AND gates:
 - provide information to each stage about the state of the prior stages in the counter.
 - AND chain causes complement of a bit if all previous LSB are equal 1.




(a) Logic Diagram-Serial Gating

Synchronous Counters (continued)

	<i>A</i>	<i>B</i>	XOR
Hold	0	0	0
	0	1	1
Complement	1	0	1
<i>t</i>	1	1	0


XOR complements each bit

 

 
(a) Logic Diagram-Serial Gating

Synchronous Counters with MOD no. $< 2^n$

- A synchronous 4-bit binary counter with a synchronous load and an asynchronous clear is used to make a **Modulo 7 counter**
- Use the Load feature to **detect the count "6"** and load in "zero". This gives a count of 0, 1, 2, 3, 4, 5, 6, 0, 1, 2, 3, 4, 5, 6, 0, ...
- Using don't cares for states above 0110, detection of 6 can be done with $\text{Load} = Q_2 Q_1$




Synchronous BCD Counter

 

Synchronous Modulo 6 Counter: 9 to 14

 
- A synchronous, 4-bit binary counter with a synchronous Load is to be used to make a **Modulo 6 counter**.
- Use the Load feature to preset the count to **9** on Reset and detection of count **14**.



- This gives a count of 9, 10, 11, 12, 13, 14, 9, 10, 11, 12, 13, 14, 9, ...

Memory

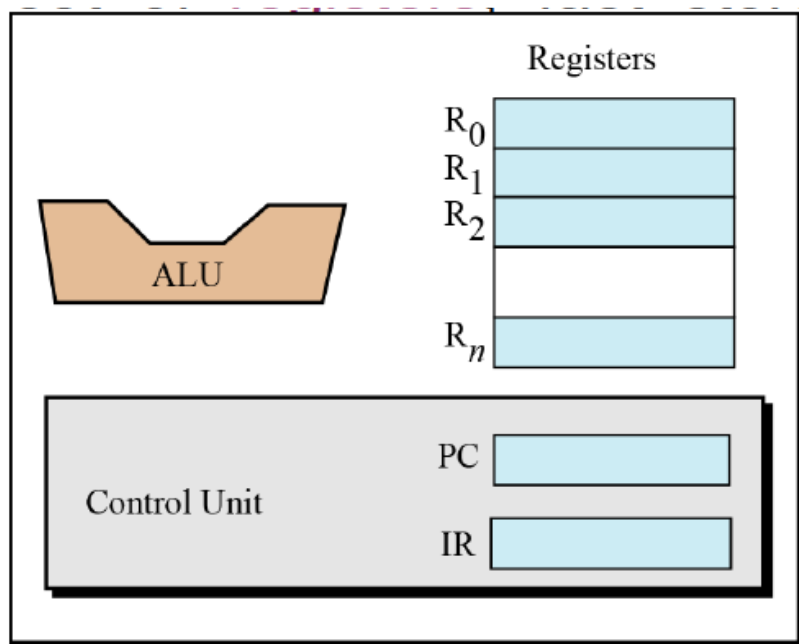
- Memory:
A collection of **storage cells** together with the necessary **circuits to transfer** information to and from them.
- Random Access Memory (RAM):
a memory organized such that data can be transferred to or from any desired location, with the access taking the same time **regardless of the location**.



Memory Definitions

- Typical data elements are:
 - Bit: a single binary digit
 - Byte: a collection of eight bits accessed together
 - Word:
 - is an entity of bits that moves in and out of memory as a unit.
 - It is typically a power of two multiple of bytes (e.g., 1 byte, 2 bytes, 4 bytes, 8 bytes, etc.)

Memory Block Diagram

 

Memory Block Diagram

Communication between a memory and its environment is achieved through:

- n data input lines: since each word is n bits.
- n output lines.
- k address selection lines: to address 2^k words of memory.
- Read and Write are single control lines defining the simplest of memory operations.

Memory Example

- This is a 1024 X 16 Memory

words

word size (bits)

- Number of address lines, $k=10$
- Number of input data lines, $n=16$
- Number of output data lines, $n=16$

<u>Memory Address</u>		<u>Memory Contents</u>
<u>Binary</u>	<u>Decimal</u>	
0000000000	0	10110101 01011100
0000000001	1	10101011 10001001
0000000010	2	00001101 01000110
	⋮	⋮
	⋮	⋮
	⋮	⋮
	⋮	⋮
	⋮	⋮
1111111101	1021	10011101 00010101
1111111110	1022	00001101 00011110
1111111111	1023	11011110 00100100

FIGURE 7-2
Contents of a 1024×16 Memory

Write and Read Operations

- **Read Memory:** an operation that reads a data value stored in memory:
 - Place a valid address on the address lines.
 - Activate the Read input
 - Wait for the read data to become stable.
- **Write Memory:** an operation that writes a data value to memory:
 - Place a valid address on the address lines
 - Apply the data to the data lines.
 - Toggle the memory write control line

Control Inputs to a Memory Chip

- Instead of separate Read and Write control lines, most ICs provide a **Chip Select** that selects the chip to be read from or written to and a **Read/Write** that determines the particular operation.

□ **TABLE 7-1**
Control Inputs to a Memory Chip

Chip Select CS	Read/Write R/ $\overline{W}$	Memory Operation
0	×	None
1	0	Write to selected word
1	1	Read from selected word

Memory Size

- we refer to 2^{10} as K (kilo), 2^{20} as M (mega), 2^{30} as G (giga), and 2^{40} as T (tera)
- Example: a memory of 2^{28} bits


$$2^{28} / 8 = 2^{25} \text{ Bytes}$$

$$2^{25} = 2^5 \times 2^{20} = 32 \text{ MB}$$


Read Only Memory (ROM)

- Characteristics

 - Perform **read** operation only, write operation is not possible
- Information stored in a ROM is made permanent during production and cannot be changed



32 X 8 ROM

 

- Each output of the decoder represents a **memory address**.
- The ROM is programmed with the word 10010011 in memory address 1.

RTL and Memory

□ **TABLE 6-1**
Basic Symbols for Register Transfers

Symbol	Description	Examples
Letters (and numerals)	Denotes a register	$AR, R2, DR, IR$
Parentheses	Denotes a part of a register	$R2(1), R2(7:0), AR(L)$
Arrow	Denotes transfer of data	$R1 \leftarrow R2$
Comma	Separates simultaneous transfers	$R1 \leftarrow R2, R2 \leftarrow R1$
Square brackets	Specifies an address for memory	$DR \leftarrow M[AR]$

- Memory to register transfers are called *read operations*,
- Register to memory transfers are called *write operations*.
- Both require specification of the memory location to be used (which can be done through a special register (AR) or a special bus (Address bus)).

RTL and Memory

- RTL expressions for a **Read** operation, assuming the use of an address registers:

$$\begin{aligned} \text{AR} &\leftarrow \text{address} \\ \text{DR} &\leftarrow \text{M}[\text{AR}] \end{aligned}$$

- RTL expressions for a **Write** operation, assuming use of a data register:

$$\begin{aligned} \text{AR} &\leftarrow \text{address} \\ \text{DR} &\leftarrow \text{value} \\ \text{M}[\text{AR}] &\leftarrow \text{DR} \end{aligned}$$