



## CSC 220: Computer Organization

### Unit 3 Simplification of Logic Function

---

Prepared by:

Md Saiful Islam, PhD

Updated by:

Isra Al-Turaiki, PhD

**Department of Computer Science  
College of Computer and Information Sciences**

# Overview

- Minimal Sum of Product (MSP)
- K-Map Simplification Procedure
  - Two Variable K-Map
  - Three Variable K-Map
  - Four Variable K-Map
- Don't Care Condition
- Examples

## Chapter-2

M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design Fundamentals**, Global (5<sup>th</sup>) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124

# Overview


- Complexity of a logic circuit is directly related to the algebraic expression.
- To obtain the simplest implementation for a given function, use: Karnaugh map, or K-map.
- What is a K-map?
  - a graphical representation of a Boolean function
  - a reorganized version of the truth table
  - lead directly to minimum cost two-level circuits composed of AND and OR gates.

# Minimum Sum-of-Products

**Minimum sum-of-products** is a sum of product terms which has:


- a minimum number of **terms**
- a minimum number of **literals**
- **Why do we care?**
  - corresponds to a minimum two-level gate circuit which has (a) a minimum number of **gates** and (b) a minimum number of **gate inputs**

$$x'y' + yz + x'y = x' + yz$$

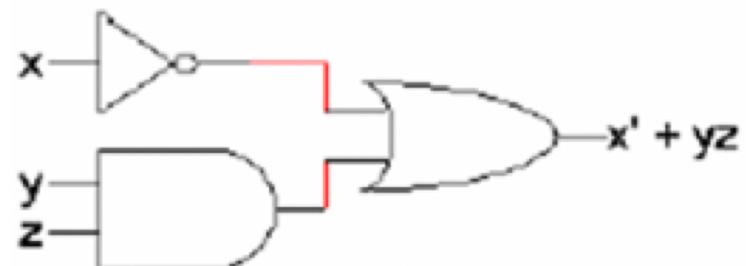
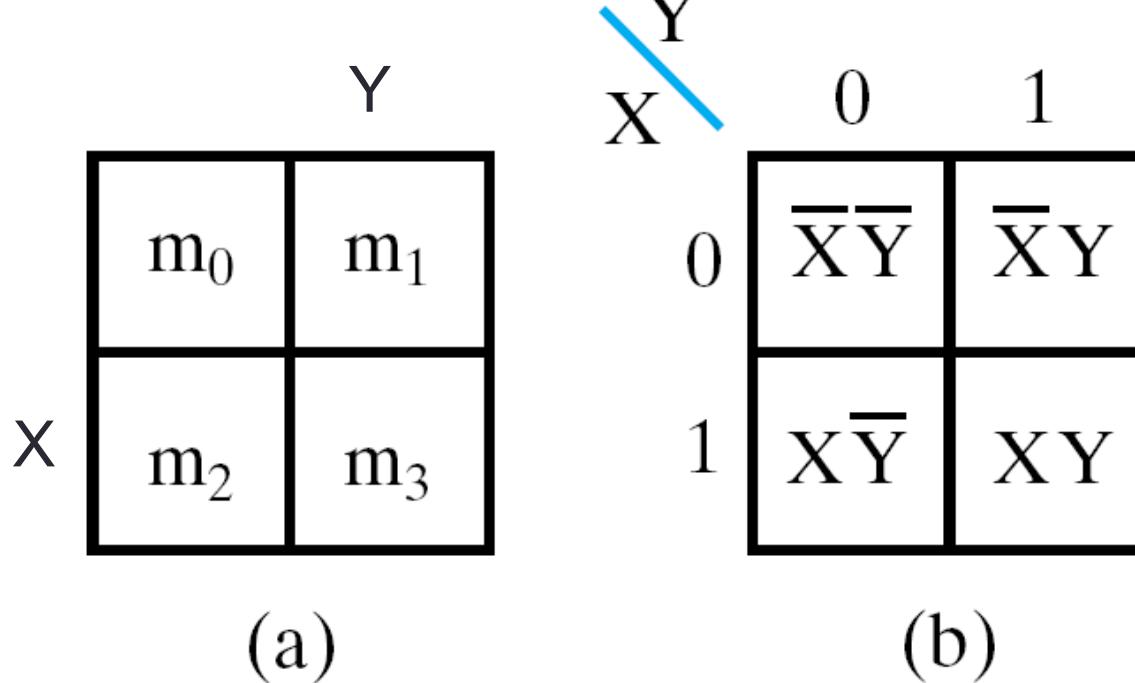
# Two-Variable Maps

- The map is a diagram made up of squares, each **square** representing one **row** of a truth table, or correspondingly, one minterm of a single output function.



Every 2 *adjacent* cells differ in the value of 1 variable only.

# Two-Variable Maps

- Example:

□ TABLE 2-12


Two-Variable Function  $F(A, B)$

A	B	F
0	0	1
0	1	1
1	0	0
1	1	1




Algebraically:
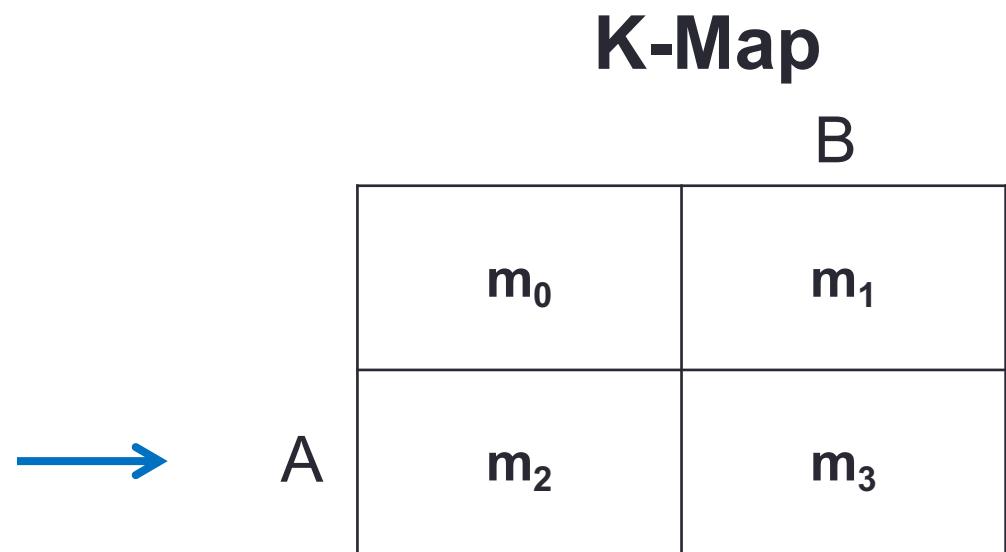
$$\begin{aligned} F &= A'B' + A'B + AB \\ &= A'(B' + B) + AB \\ &= A' + AB \\ &= (A' + A)(A' + B) \\ &= 1 \cdot (A' + B) \\ &= A' + B \end{aligned}$$



A

B

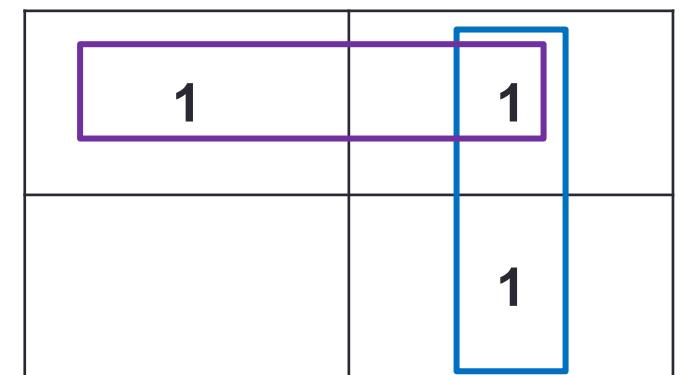



A

B


$$F = \overline{A} + B$$
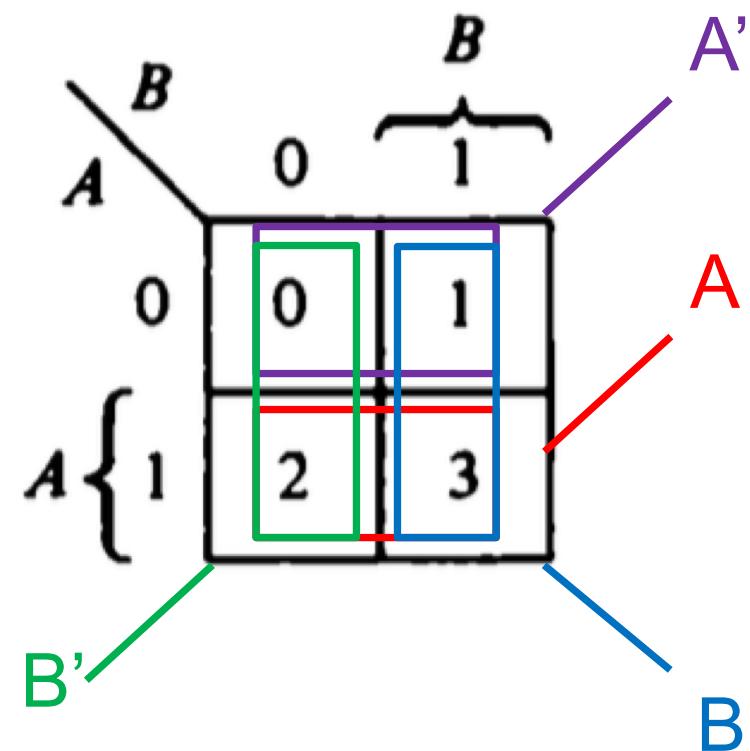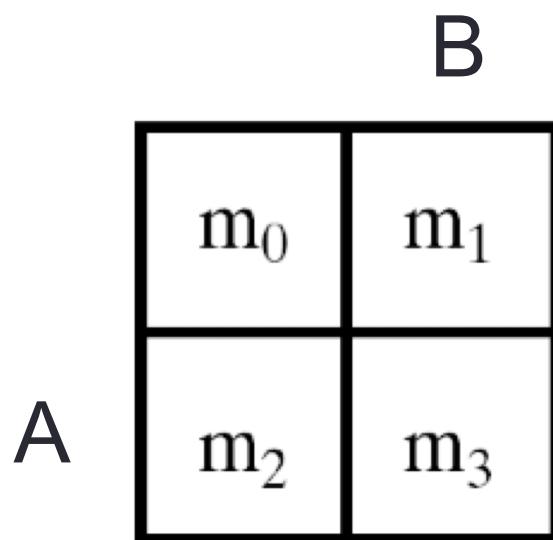
# Two-Variable Maps


- whenever we have two squares sharing edges that are minterms of a function, these squares can be combined to form a product term with one less variable.



# Three-Variable Maps

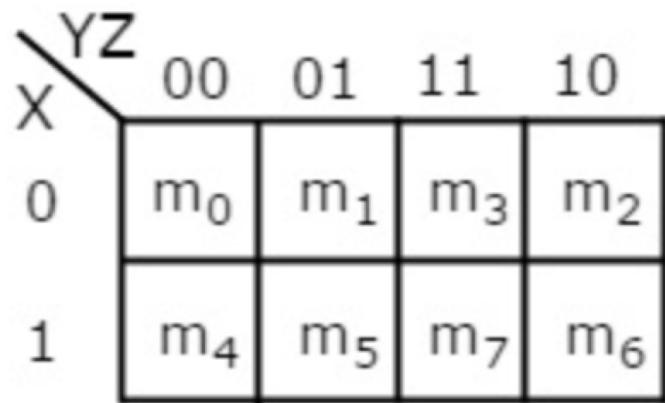

	Y Z	00	01	11	10
X	0	$m_0$	$m_1$	$m_3$	$m_2$
0	1	$m_4$	$m_5$	$m_7$	$m_6$
1					

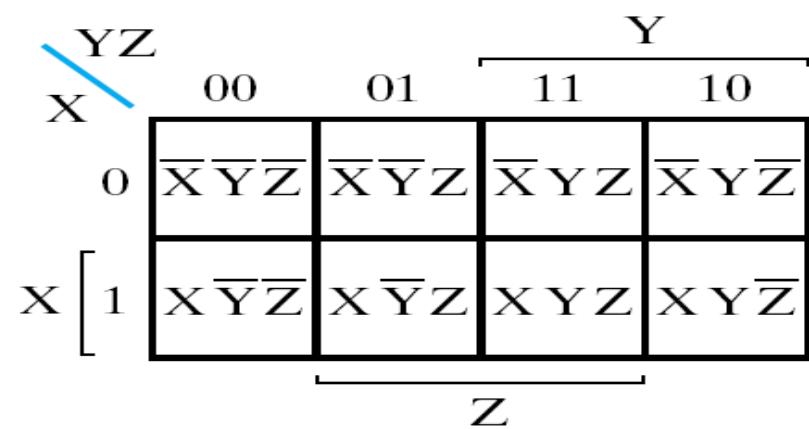

	Y Z	00	01	11	10
X	0	$\bar{X}\bar{Y}\bar{Z}$	$\bar{X}\bar{Y}Z$	$\bar{X}YZ$	$\bar{X}Y\bar{Z}$
0	1	$X\bar{Y}\bar{Z}$	$X\bar{Y}Z$	$XYZ$	$XY\bar{Z}$
1					



Every 2 *adjacent* cells differ in the value of 1 variable only.

# Three-Variable Maps

- **Example:**


Simplify the Boolean function  $F(A, B, C) = \sum m(0, 1, 2, 3, 4, 5)$

## K-Map

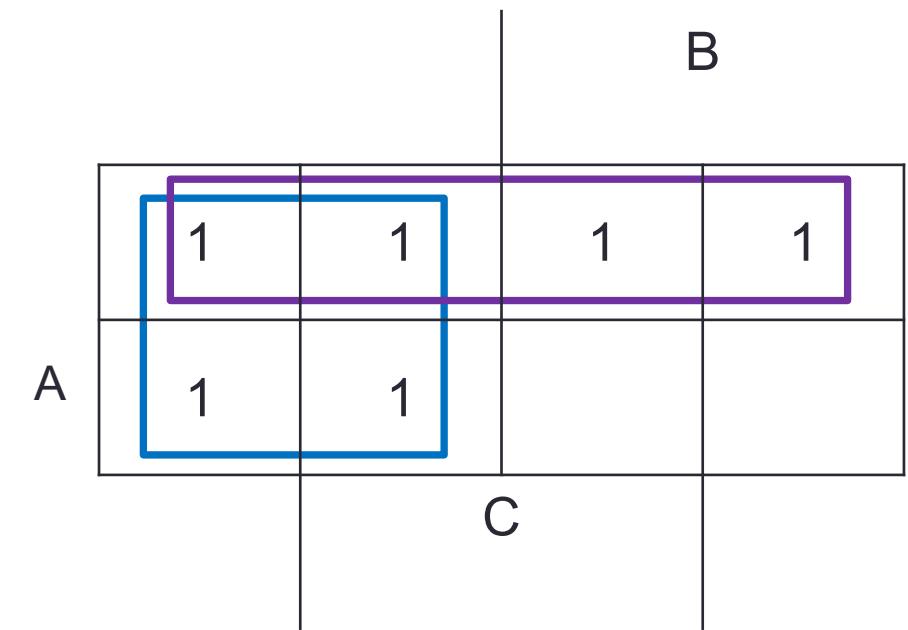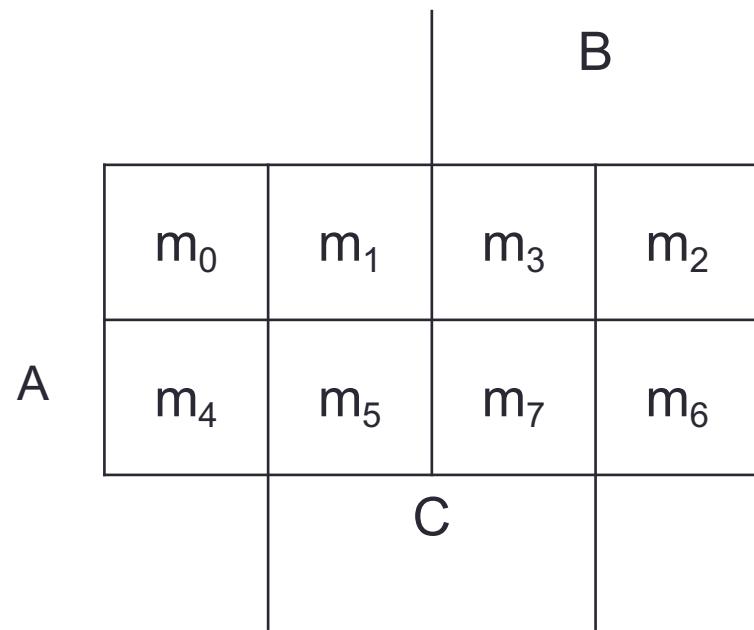

$$F = \overline{A} + \overline{B}$$

# Three-Variable Maps

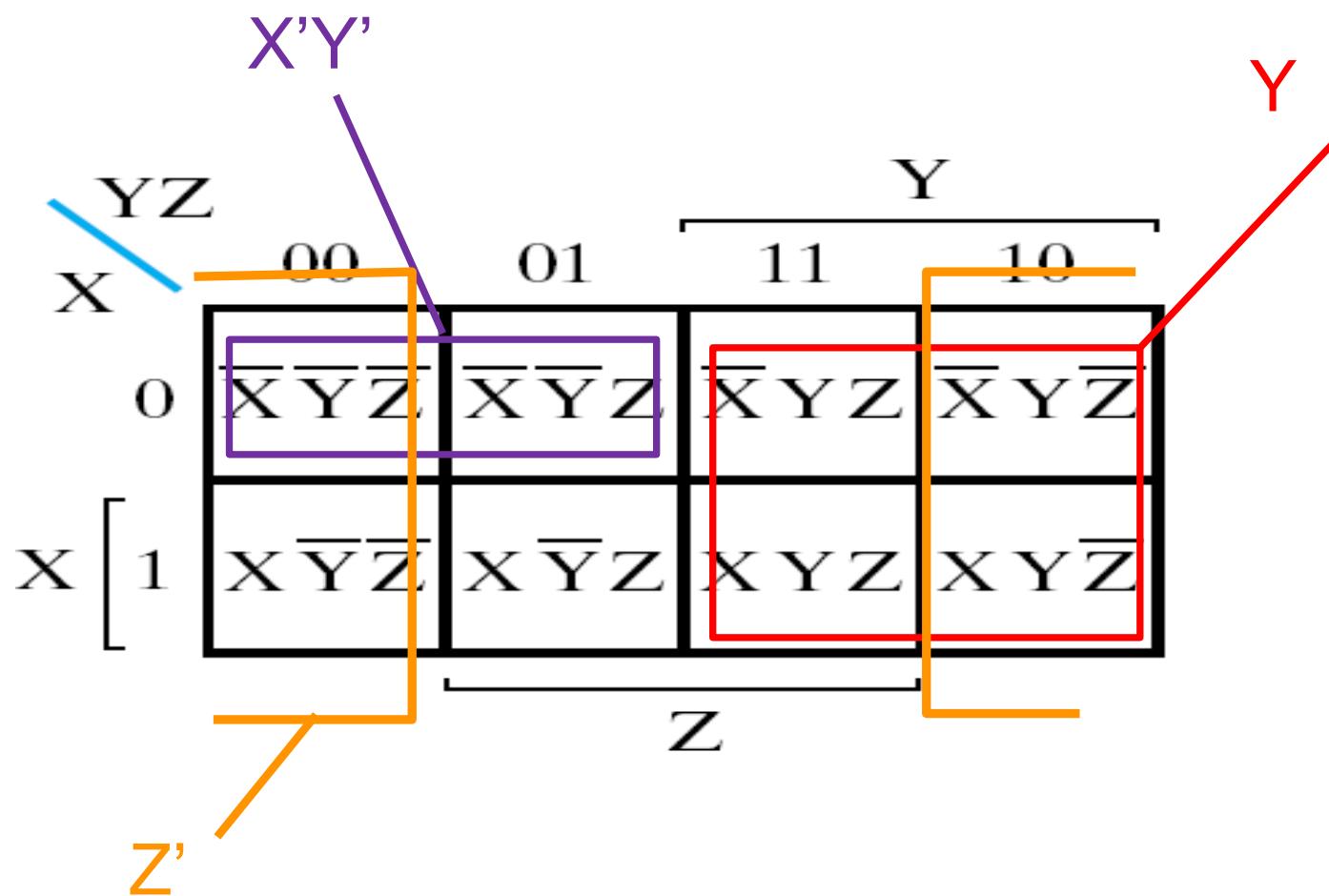



# Combining Squares

Groupings to select product-terms must be:



- Rectangular in shape
- In powers of twos (1, 2, 4, 8, etc.)
- Always select largest possible groupings of minterms (i.e. prime implicants)
- Eliminate redundant groupings
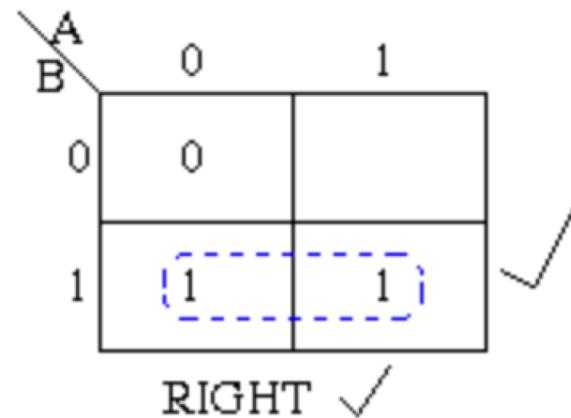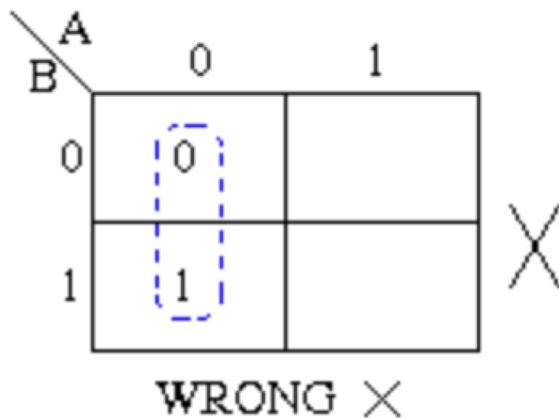
# Combining Squares

- Groups may not include any cell containing a **zero**



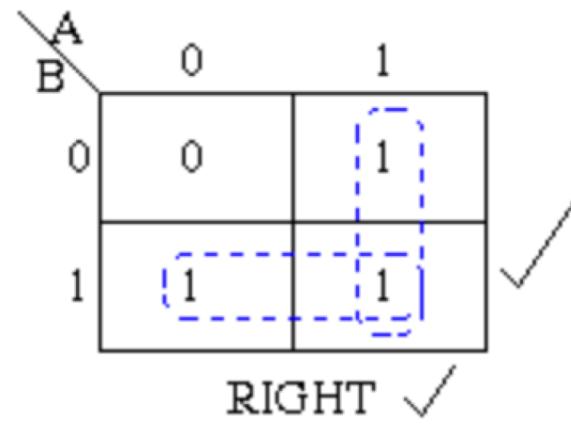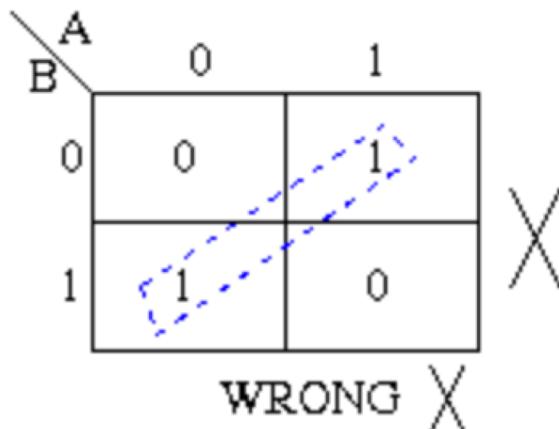- Groups may be horizontal or vertical, but not diagonal.



# Combining Squares

- Groups must contain 1, 2, 4, 8, or in general  $2^n$  cells.

That is if  $n = 1$ , a group will contain two 1's since  $2^1 = 2$ .

If  $n = 2$ , a group will contain four 1's since  $2^2 = 4$ .

	A	0	1
B	0	1	1
	0	0	0
	1	0	0

Group of 2

RIGHT ✓

	AB	00	01	11	10
C	0	0	1	1	1
	1	0	0	0	0

Group of 3

WRONG ✗

	A	0	1
B	0	1	1
	0	1	1
	1	1	1

Group of 4

RIGHT ✓

	AB	00	01	11	10
C	0	1	1	1	1
	1	0	0	0	1

Group of 5

WRONG ✗

# Combining Squares

- Each group should be as large as possible.

AB  
C

	00	01	11	10
0	1	1	1	1
1	0	0	1	1

RIGHT ✓

AB  
C

	00	01	11	10
0	1	1	1	1
1	0	0	1	1

WRONG ✗

(Note that no Boolean laws broken, but not sufficiently minimal)

- Each cell containing a **one** must be in at least one group.

AB  
C

	00	01	11	10
0	0	0	1	1
1	0	0	0	1



Group I

Group II

1 present in at least one group.


# Combining Squares

- Groups may overlap.

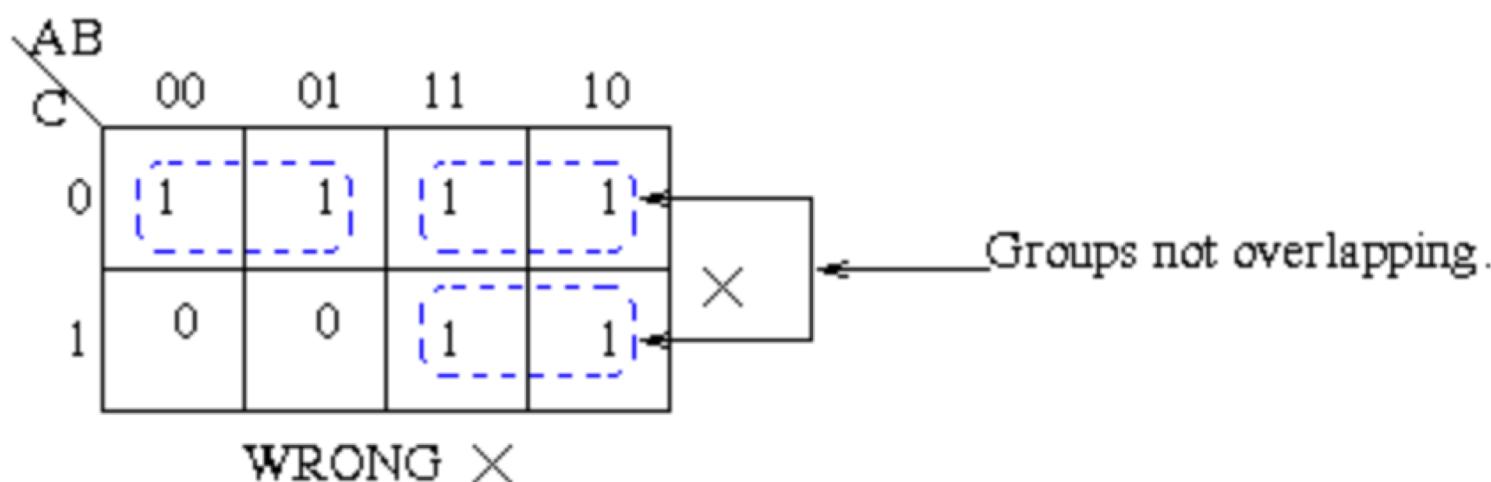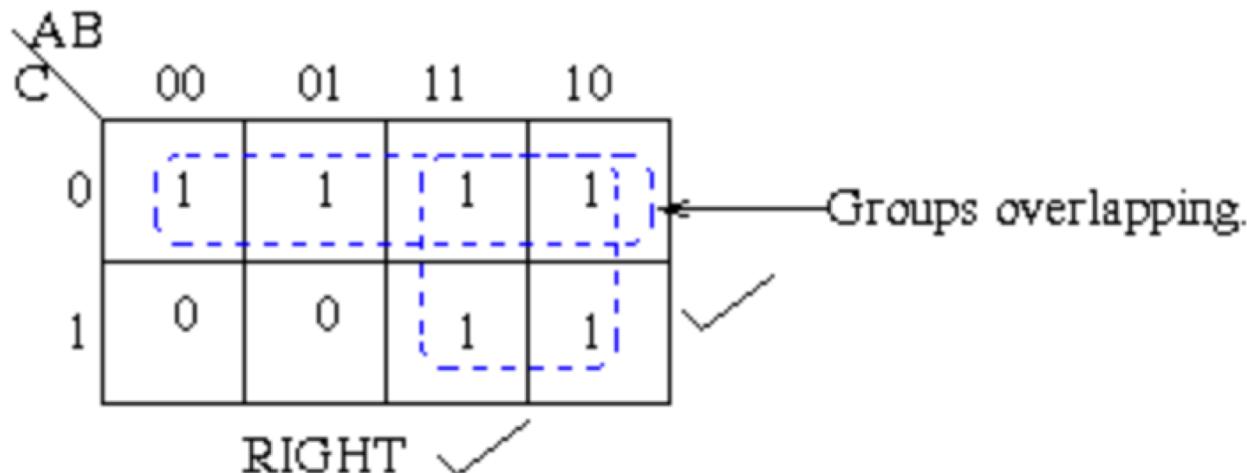
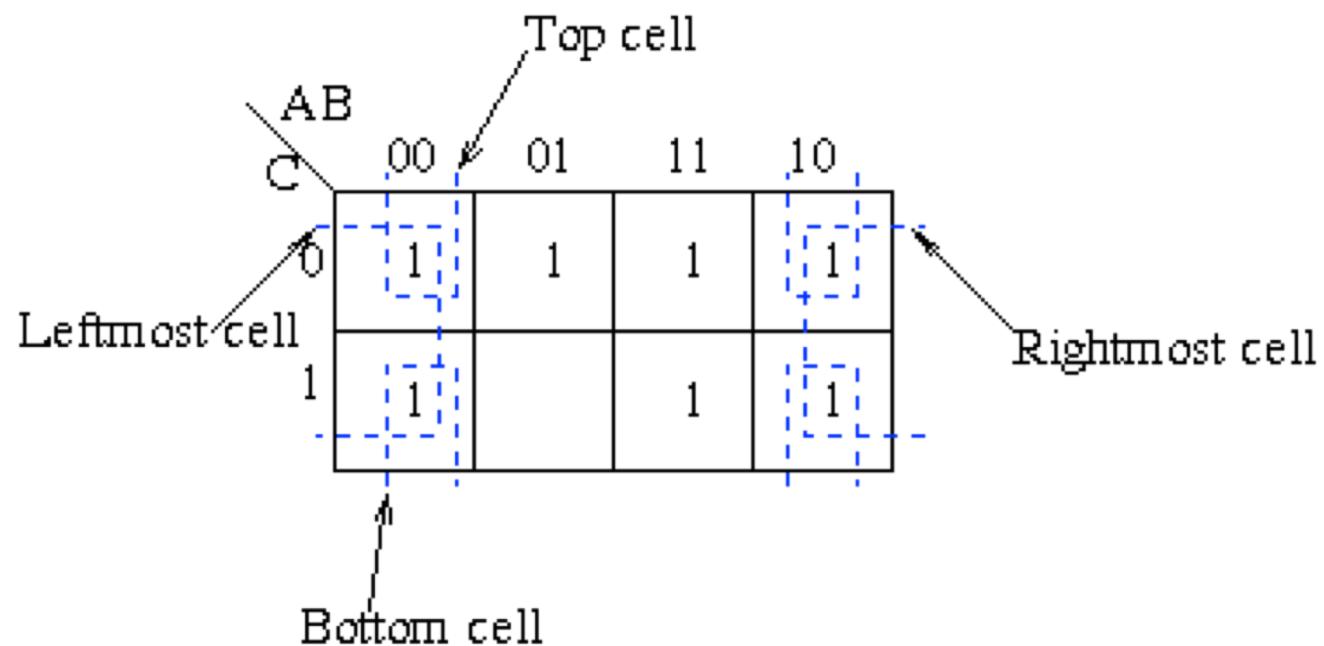
# Combining Squares

- Groups may wrap around the table. The leftmost cell in a row may be grouped with the rightmost cell and the top cell in a column may be grouped with the bottom cell.



# Combining Squares

- There should be as few groups as possible, as long as this does not contradict any of the previous rules.

AB  
C

	00	01	11	10
0	1	1	1	1
1	0	0	1	1

RIGHT ✓

AB  
C

	00	01	11	10
0	1	1	1	1
1	0	0	1	1

WRONG ✗

# Simplification

## Four steps in K-map simplifications

1. Start with a sum of minterms or truth table.

$$x'y'z' + x'y'z + xyz + xyz'$$

2. Plot the minterms on a Karnaugh map.

				y
	1	1	0	0
x	0	0	1	1
			z	

3. Find rectangular groups of minterms whose sizes are powers of two. Be sure to include all the minterms in at least one group!


				y
	1	1	0	0
x	0	0	1	1

4. Reduce each group to one product term.

$$x'y' + xy$$

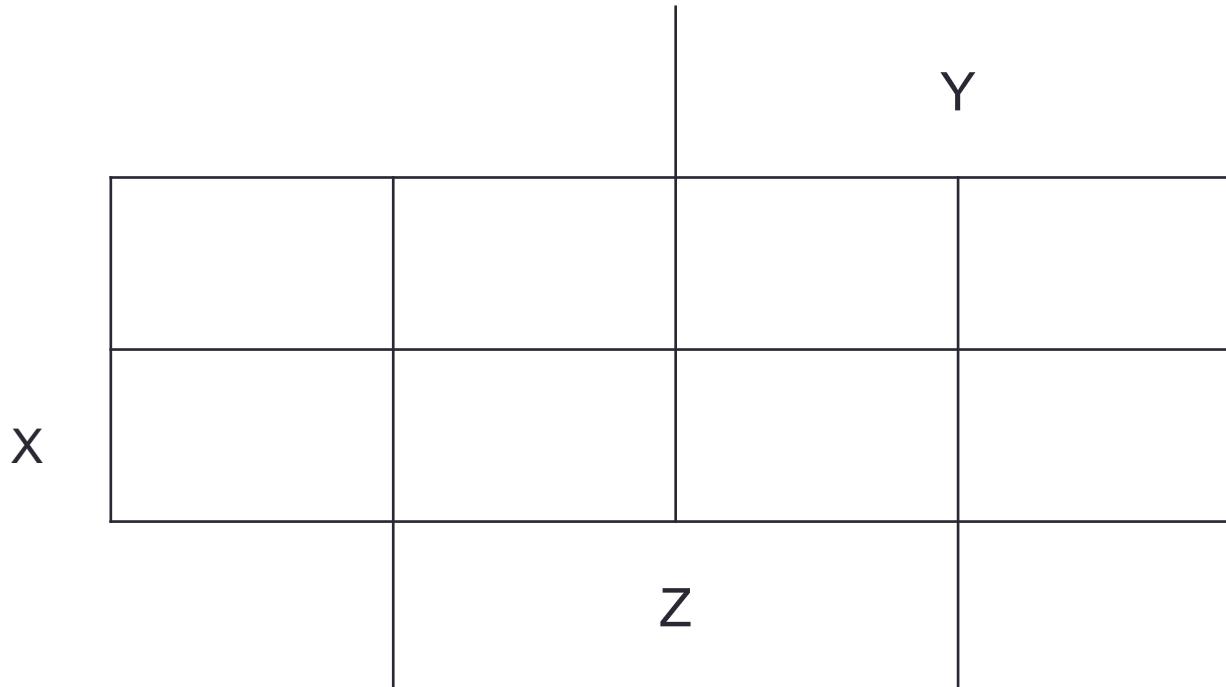
# Example

- Here is the K-map for  $f(x,y,z) = m_1 + \overline{m_3} + m_5 + m_6$ , with all groups shown.
  - The magenta and green groups overlap, which makes each of them as large as possible.
  - Minterm  $m_6$  is in a group all by its lonesome.


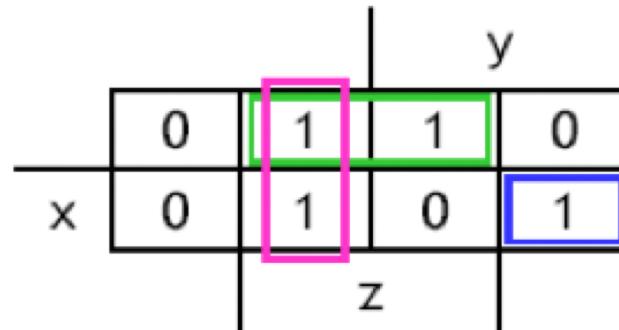
# Example

- Here is the K-map for  $f(x,y,z) = m_1 + m_3 + m_5 + m_6$ , with all groups shown.
  - The magenta and green groups overlap, which makes each of them as large as possible.
  - Minterm  $m_6$  is in a group all by its lonesome.





**MSP**

**Minimal Sum of Product**

- The final MSP here is  $x'z + y'z + xyz'$ .

A

# Four-Variable Maps

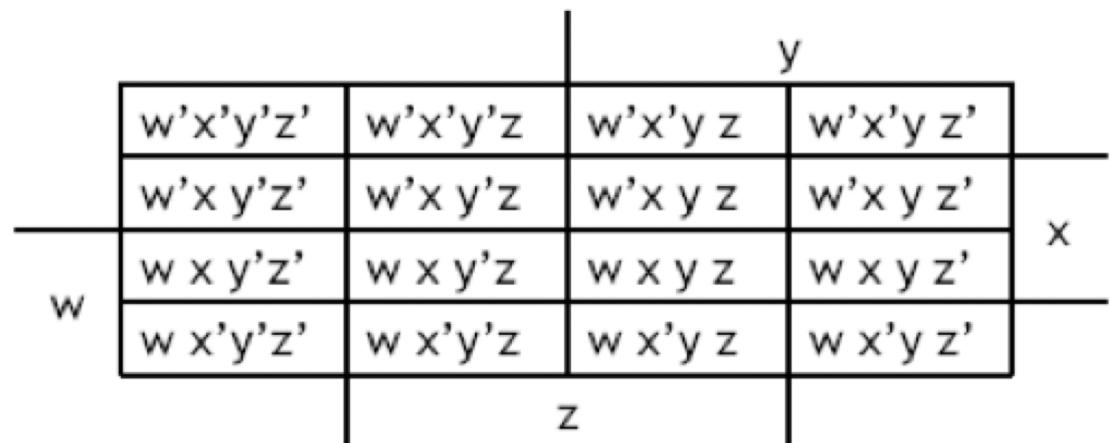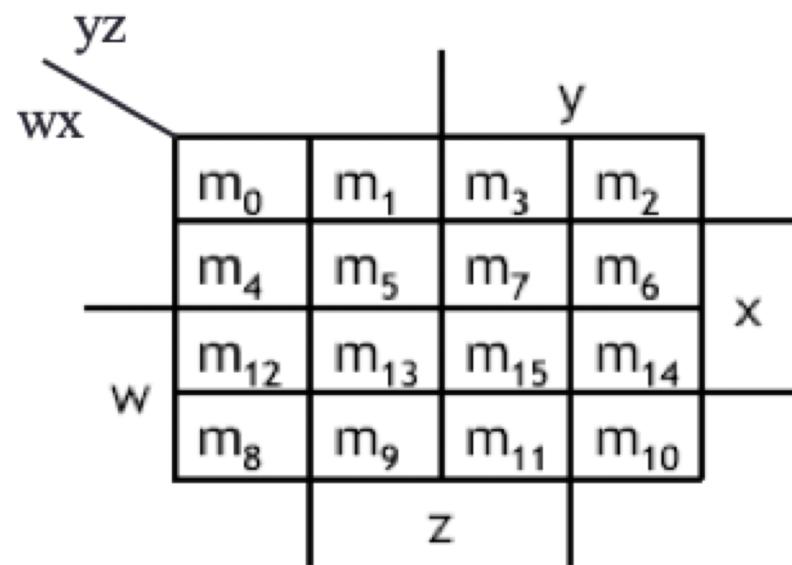

# Four-Variable Maps

- Let's say we want to simplify  $m_0 + m_2 + m_5 + m_8 + m_{10} + m_{13}$

		y		
	$m_0$	$m_1$	$m_3$	$m_2$
	$m_4$	$m_5$	$m_7$	$m_6$
w	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
	$m_8$	$m_9$	$m_{11}$	$m_{10}$
		z		


		y		
	1	0	0	1
	0	1	0	0
w	0	1	0	0
	1	0	0	1
		z		

Example 6

- The following groups result in the minimal sum of products  $x'z' + xy'z$ .

		y		
	1	0	0	1
	0	1	0	0
w	0	1	0	0
	1	0	0	1
		z		

# Four-Variable Maps

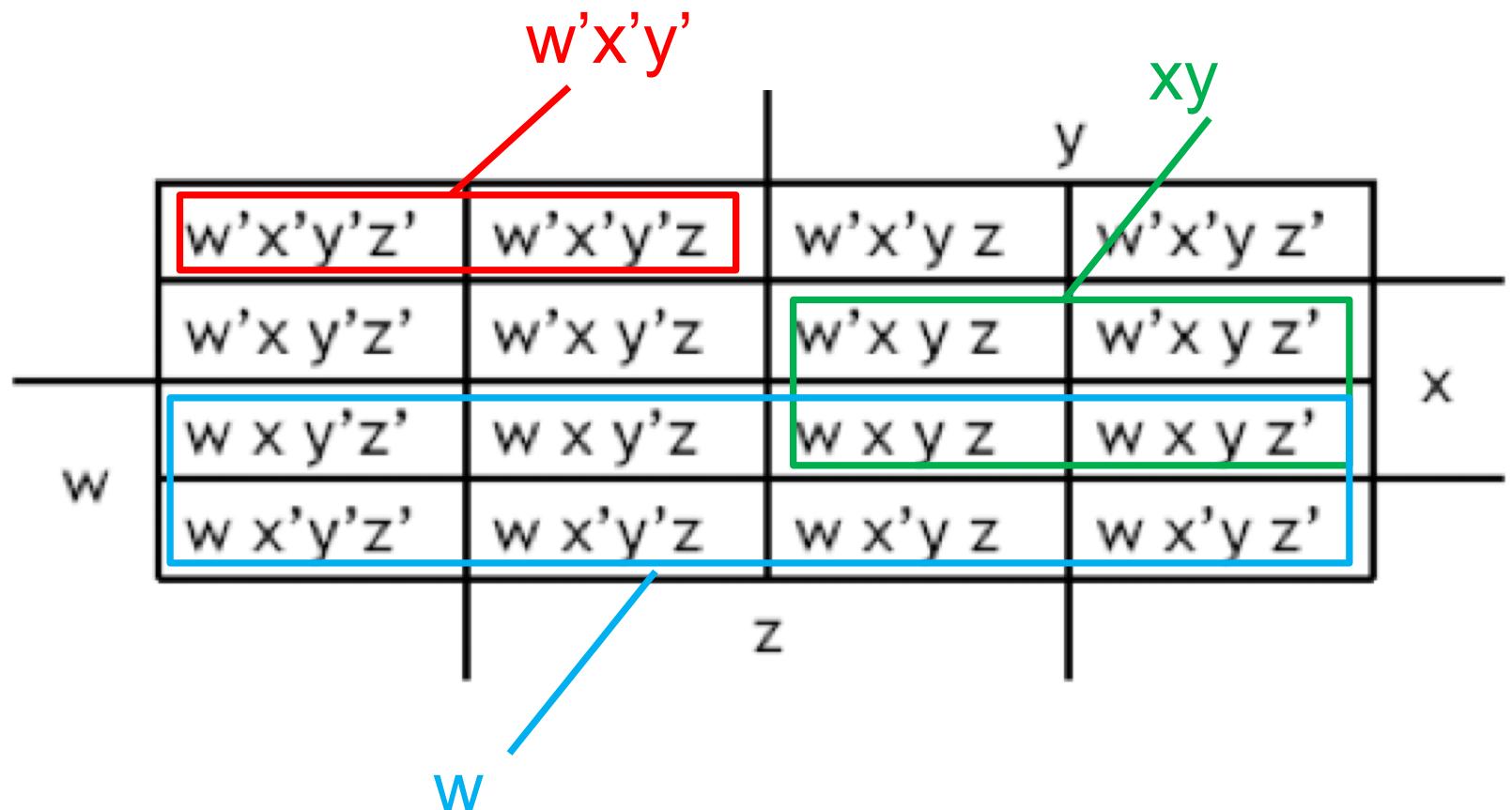


# Map Manipulation

- *Implicant*: A product term that has the value 1 for all minterms of the product term.
  - all rectangles on a map made up of squares containing 1s correspond to implicants.

# Map Manipulation

**Prime Implicant:** is a product term obtained by combining the **maximum** possible number of adjacent squares in the map into a rectangle with the number of squares a power of 2.


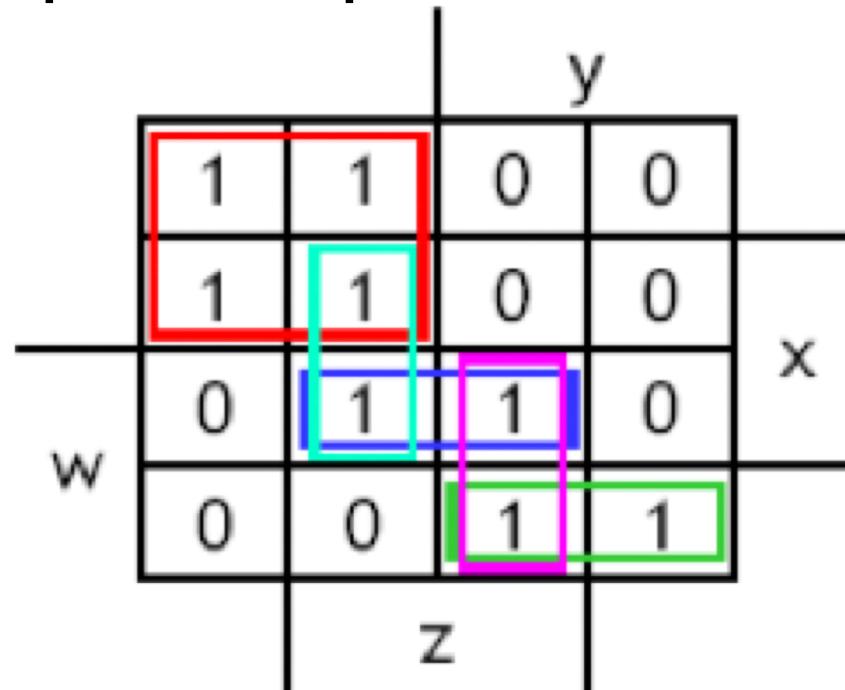
- **Example:** All prime implicants are marked



# Map Manipulation

**Essential Prime Implicant:** If a minterm of a function is included in only one prime implicant.

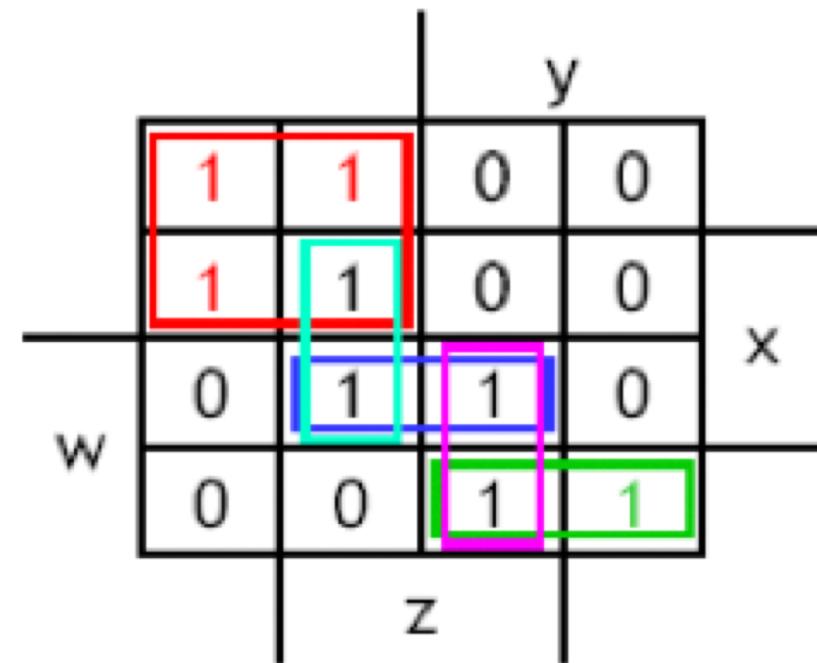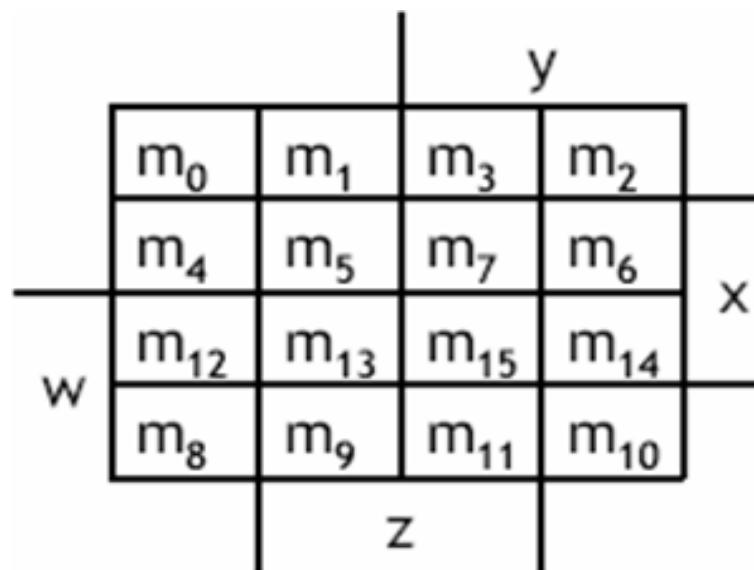- **Example:** red and green groups are essential



# Don't Cares in K-Maps


- There are times when we don't care what a function outputs—some input combinations might never occur, or some outputs may have no effect.
- We can express these situations with **don't care conditions**, denoted with **X** in truth table rows.
- An expression for this function has two parts.
  - One part includes the function's minterms.
  - Another describes the don't care conditions.

$$f(x,y,z) = m_3, \quad d(x,y,z) = m_2 + m_4 + m_5$$


- Circuits *always* output 0 or 1; there is no value called "X". Instead, the Xs just indicate cases where both 0 or 1 would be acceptable outputs.

x	y	z	$f(x,y,z)$
0	0	0	0
0	0	1	0
0	1	0	X
0	1	1	1
1	0	0	X
1	0	1	X
1	1	0	0
1	1	1	0

# Don't Cares in K-Maps

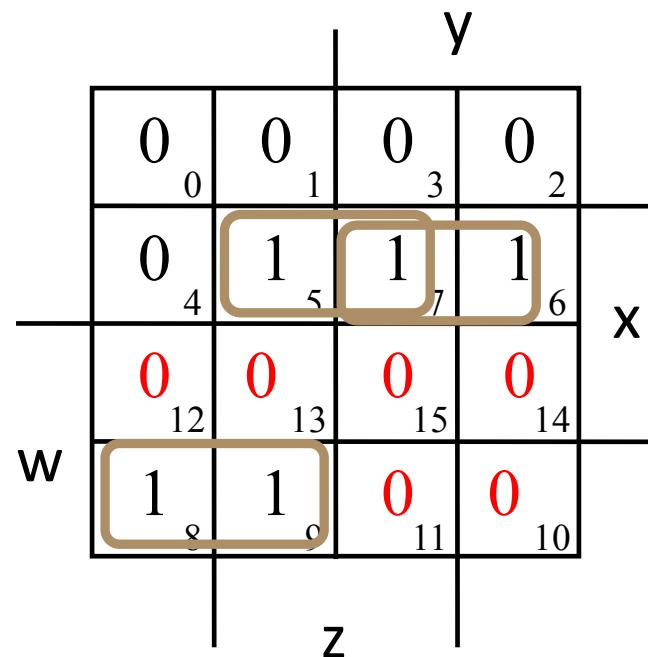

$$F = wx'y' + w'xz + w'xy$$

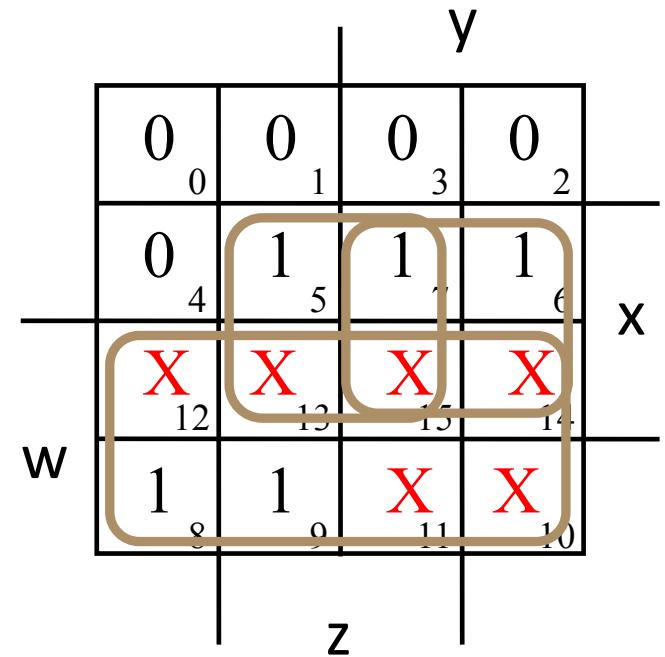



$$F = w + xz + xy$$

## Practice K-map 2

---

- Simplify the following K-map.

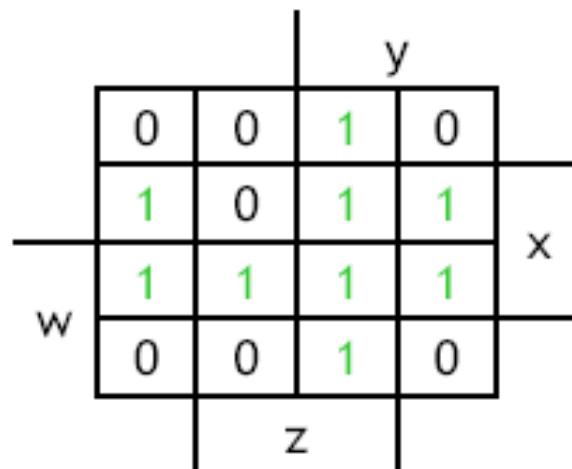


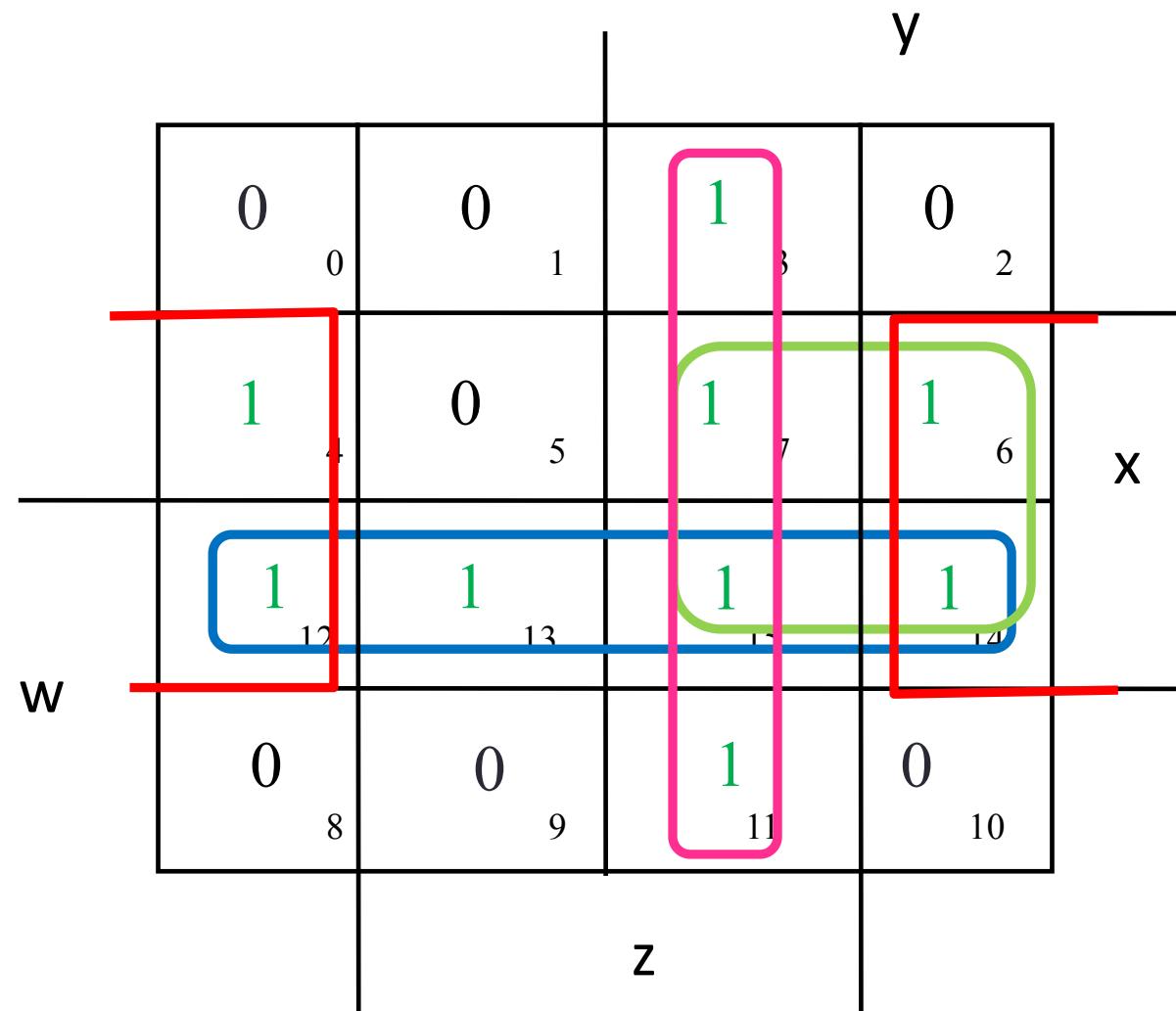

## Solutions for practice K-map 2

---

- Simplify the following K-map.

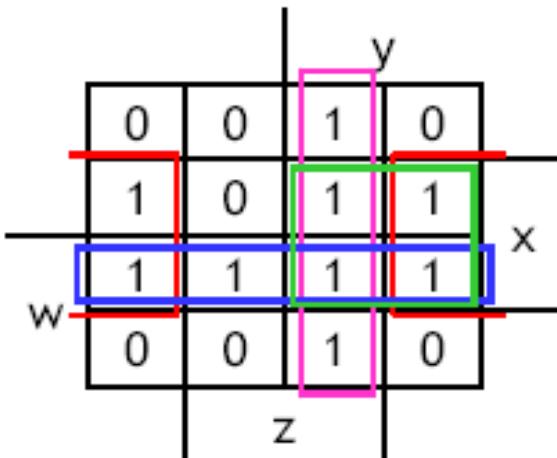


- All prime implicants are circled.
- The essential prime implicants are  $xz'$ ,  $wx$  and  $yz$ .
- The MSP is  $xz' + wx + yz$ . (Including the group  $xy$  would be redundant.)
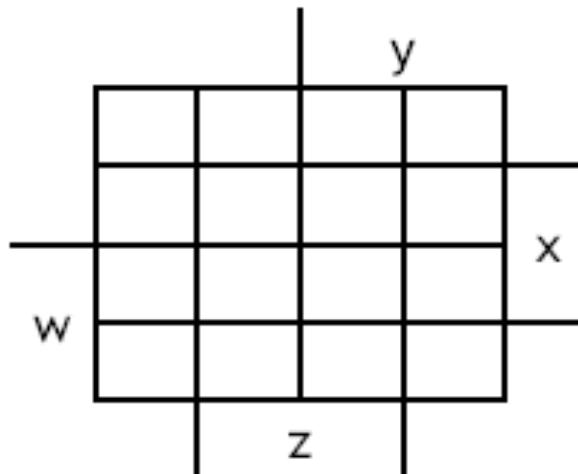
## Practice K-map 3


- Find a minimal sum of products for the following.

$$f(w,x,y,z) = \Sigma m(0,2,4,5,8,14,15), d(w,x,y,z) = \Sigma m(7,10,13)$$



- Find a minimal sum of products for the following.

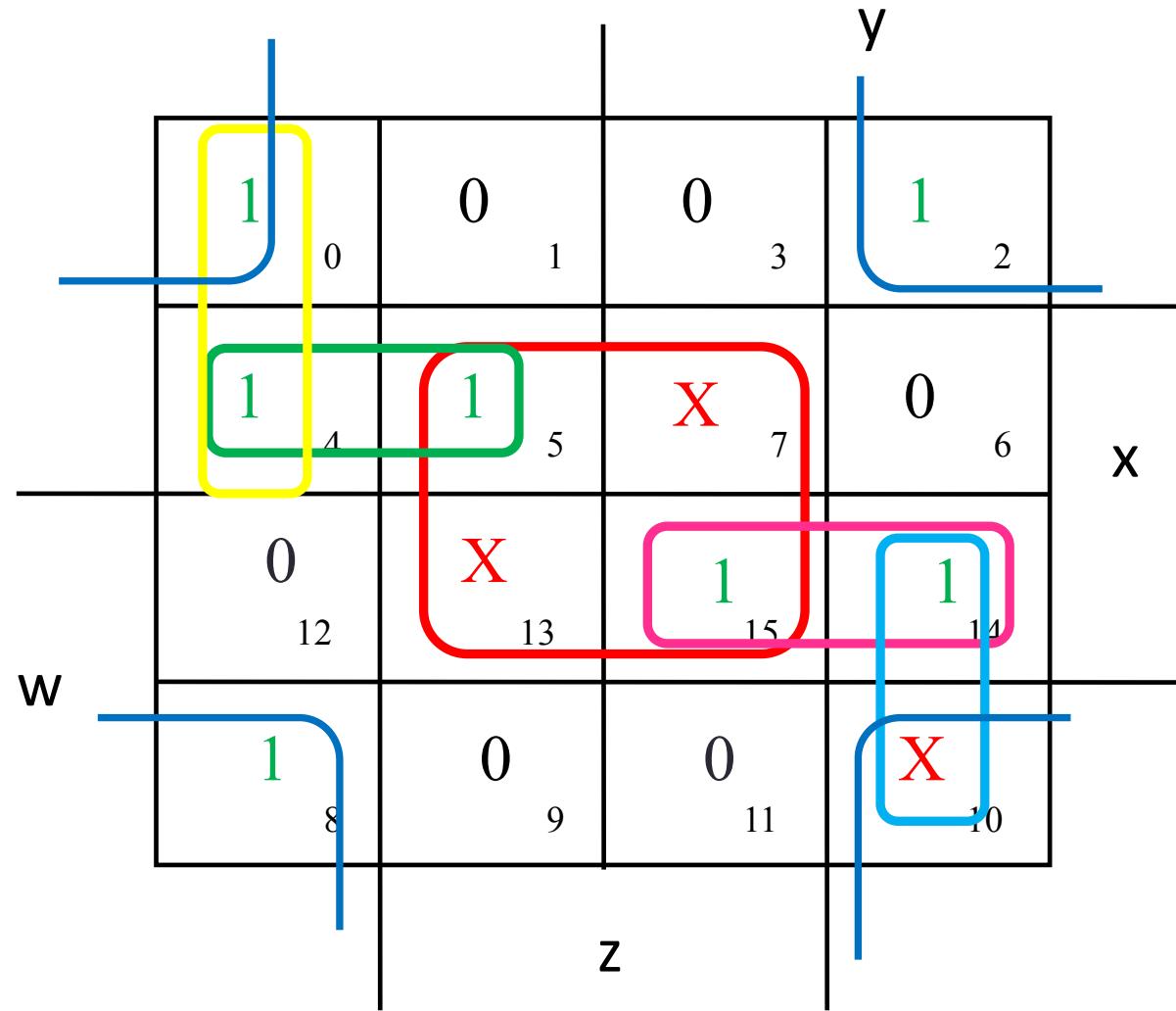
$$f(w,x,y,z) = \Sigma m(0,2,4,5,8,14,15), d(w,x,y,z) = \Sigma m(7,10,13)$$


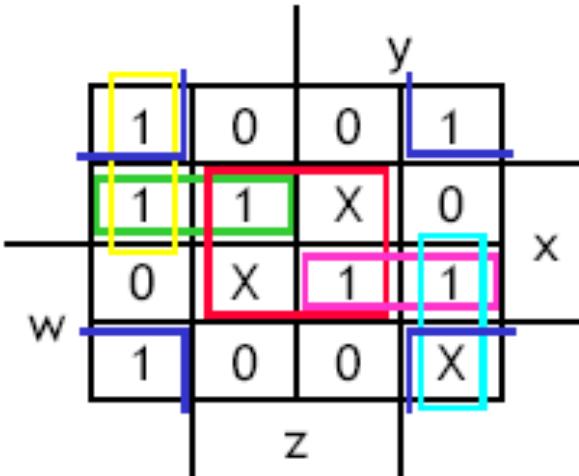
## Solutions for practice K-map 3

- Find a minimal sum of products for the following.

$$f(w,x,y,z) = \Sigma m(0,2,4,5,8,14,15), d(w,x,y,z) = \Sigma m(7,10,13)$$



- All prime implicants are circled. We can treat Xs as 1s if we want, so the red group includes two Xs, and the light blue group includes one X.
- The *only* essential prime implicant is  $x'z'$ . The red group is not essential because the two minterms in it also appear in other groups.
- The MSP is  $x'z' + wxy + w'xy'$ . It turns out the red group is redundant; we can cover all of the minterms in the map without it.