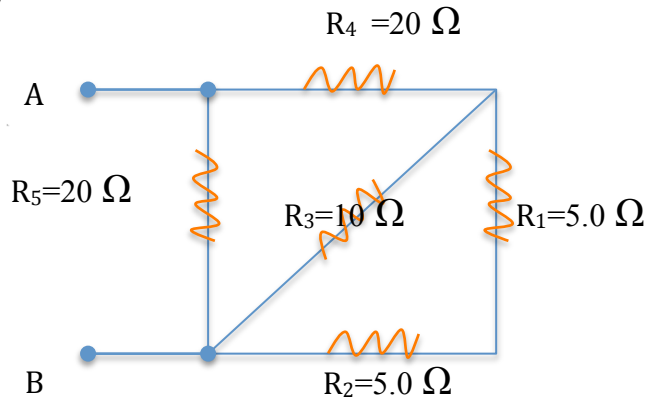



Assignment Solution 3

Questions:

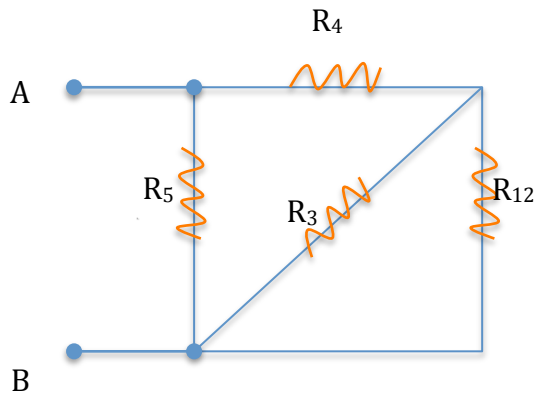1. Calculate the effective resistance between the points A and B in the figure below



$R_1=5\Omega$, $R_2=5\Omega$, $R_3=10\Omega$, $R_4=20\Omega$. $R_5=10\Omega$




R_1 and R_2 are connected in Series, Thus R_{12} is

$$R_{12} = R_1 + R_2 = 10\Omega$$


since R_{12} and R_3 are connected in Parallel, Thus R_{123} is

$$\frac{1}{R_{123}} = \frac{1}{R_{12}} + \frac{1}{R_3} \Rightarrow \frac{1}{R_{123}} = \frac{1}{10} + \frac{1}{10}$$


$$R_{123} = 5\Omega$$

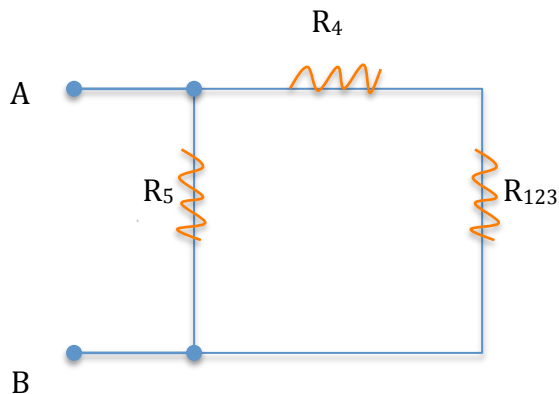

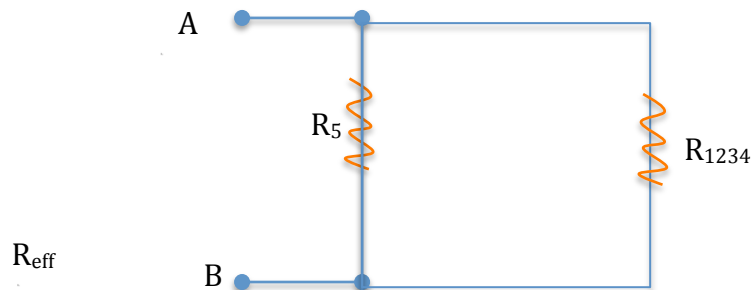R_{123} and R_4 are connected in Series, Thus R_{1234} is
 $R_{1234} = R_{123} + R_4 = 5 + 20 = 25\Omega$



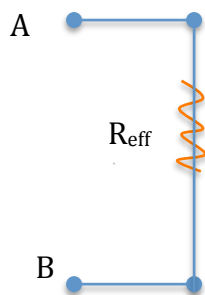since R_{1234} and R_5 are connected in Parallel, Therefore the effective resistance R_{eff} is given by



$$\frac{1}{R_{eff}} = \frac{1}{R_{1234}} + \frac{1}{R_5} \Rightarrow \frac{1}{R_{12345}} = \frac{1}{25} + \frac{1}{10}$$

$$R_{12345} = 7.14\Omega$$

2. A copper wire has a resistance of $25\text{ m}\Omega$ at 20°C . When the wire is carrying a current, heat produced by the current causes the temperature of the wire to increase by 27°C

- Calculate the change in the wire's resistance.
- If its original current was 10.0 mA and the potential difference across wire remains constant, what is its final current? (Given the temperature coefficient of resistivity for copper is $6.80 \times 10^{-3}^\circ\text{C}^{-1}$).

$$\begin{aligned} \text{(a)} \quad R_0 &= 25\text{ m}\Omega \\ T_0 &= 20^\circ\text{C} \quad \Delta T = 27^\circ\text{C} \\ \alpha &= 6.80 \times 10^{-3}^\circ\text{C}^{-1} \end{aligned}$$

By using the equation for R_{123} temperature variation of resistance thus

$$\begin{aligned} R &= R_0(1 + \alpha \Delta T) \Rightarrow R - R_0 = R_0 \alpha \Delta T \\ \Rightarrow \Delta R &= R_0 \alpha \Delta T = 25 \times 10^{-3} \times 6.80 \times 10^{-3} \times (27 - 20) = 1.19 \times 10^{-3} \Omega \end{aligned}$$

(b) $I_0 = 10\text{mA}$

V is constant

By using equation for equation for temperature variation of resistance

$$R = R_0(1 + \alpha \Delta T) \text{ where } R = \frac{V}{I}$$


$$\Rightarrow \frac{V}{I} = \frac{V}{I_0}(1 + \alpha \Delta T) \text{ but}$$

V is constant

$$\Rightarrow \frac{1}{I} = \frac{1}{I_0}(1 + \alpha \Delta T)$$

$$\Rightarrow \frac{1}{I} = \frac{1}{10 \times 10^{-3}}(1 + 6.80 \times 10^{-3} \times 7)$$
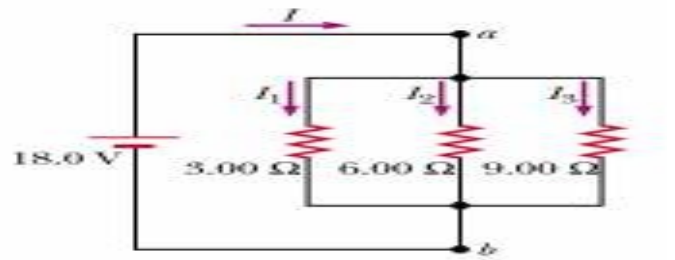
$$\Rightarrow I = 9.54 \times 10^{-3} \text{A}$$



3. Three resistors are connected in parallel as shown in the figure below, A potential difference of 18.0V is maintained between points a and b.

(a). Find the current in each resistor.

(b). Calculate the power delivered to each resistor.

(a) $V=18\text{V}$ $R_1=3\Omega$, $R_2=6\Omega$, $R_3=9\Omega$,

$$I_1 = \frac{V}{R_1} = \frac{18}{3} = 6\text{A}$$

$$I_2 = \frac{V}{R_2} = \frac{18}{6} = 3\text{A}$$

$$I_3 = \frac{V}{R_3} = \frac{18}{9} = 2\text{A}$$

(b)

$$P_1 = I_1^2 R_1 = (6)^2(3) = 108\text{W}$$

$$P_2 = I_2^2 R_2 = (3)^2(6) = 54\text{W}$$

$$P_3 = I_3^2 R_3 = (2)^2(9) = 36\text{W}$$