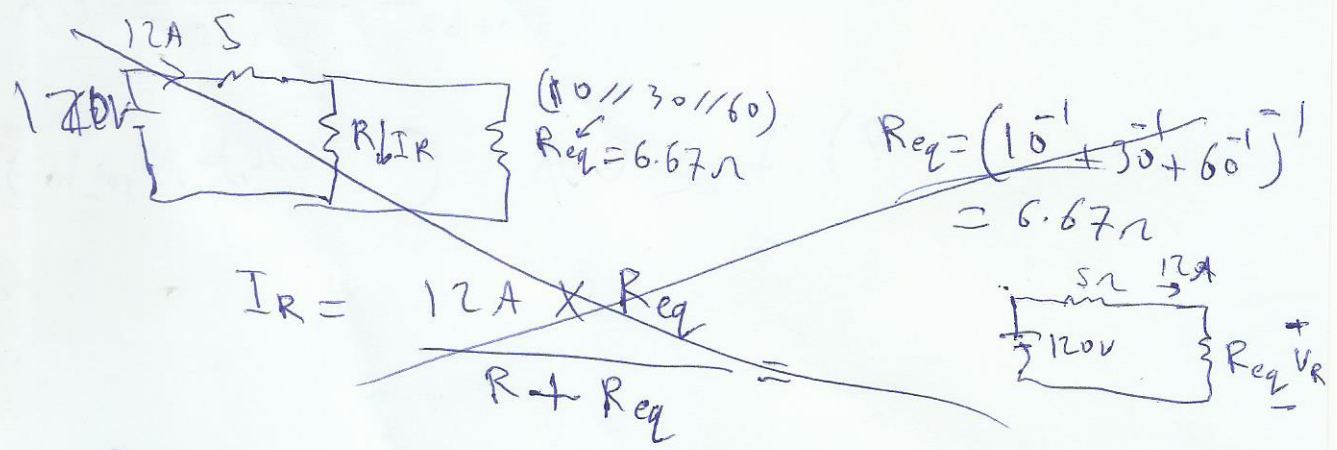


$$P_{60\Omega} = \frac{V_{60}^2}{R_{60}} \rightarrow V_{60} = \sqrt{P_{60} R_{60}} = \sqrt{60(60)} = 60V$$

$$V_{10\Omega} = V_{30\Omega} = V_R = V_{60\Omega} = 60V$$

Kirchof loop: $E = I(5) + V_{10\Omega} = 12 \times 5 + 60 = 120V$

1) $E = 120V$



$$R_{eq} = (10^{-1} + 30^{-1} + 60^{-1} + R^{-1})^{-1} = \frac{V_R}{I} = \frac{60}{12} = 5\Omega$$

~~نفس R موجودة في التيارات~~

2) $R = 20\Omega$; ~~أولها~~

3) $P_{10\Omega} = \frac{V_{10\Omega}^2}{R} = \frac{60^2}{10} = 360W$

Fig. 2: (4-7)



ليست هناك اقل اللولب -> تفصل بين الدائرتين وقيمة التيار فيها (مفتوحاً)


4) $P_{12V} = 0 \text{ W}$

5) $I_1 = -2 \text{ A}$ (current supply اتجاهه عكس)



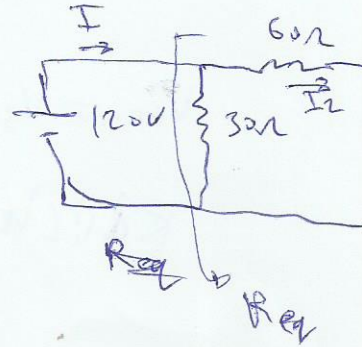6) $I_2 =$

$$R_{eq} = \frac{60 \times 30}{60 + 30} = \frac{60 \times 30}{90} = 2 \Omega$$




$$I = \frac{V}{R_{eq}} = \frac{120}{2} = 60 \text{ A}$$

6) $I_2 = \frac{30 I}{30 + 60} = \frac{30 \times 60}{30 + 60} = 2 \text{ A}$

7) $I_3 = 0 \text{ A}$ (بايبر تيار على 12Ω)

Fig. 3: C8-11)

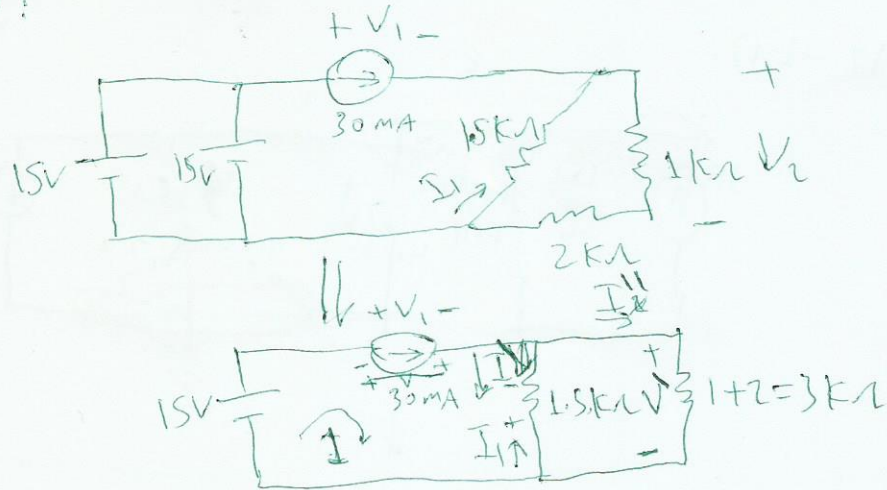

$$8) \quad I_1 = -I' = \frac{-30 \text{ mA} \times 3 \text{ k}\Omega}{1.5 \text{ k}\Omega + 3 \text{ k}\Omega} = -0.02 \text{ A} = \underline{\underline{-20 \text{ mA}}}$$

V. Kirchhoff loop: $15 - V_1 + 1.5 \text{ k}\Omega I_1 = 0$

$$15 = V_1 - 1.5 \text{ k}\Omega I_1$$

$$\rightarrow 9) \quad \rightarrow V_1 = 15 + 1.5 \text{ k}\Omega (-20 \text{ mA}) = \underline{\underline{+45 \text{ V}}}$$



$$10) \quad I'' = 30 \text{ mA} - 20 \text{ mA} = 10 \text{ mA}$$

$$V_2 = 1 \text{ k}\Omega I'' = 1 \text{ k}\Omega \times 10 \text{ mA} = \underline{\underline{10 \text{ V}}}$$


$$11) \quad P_{30 \text{ mA}} = I V_{30 \text{ mA}} = 30 \text{ mA} \times 45 = 450 \text{ mW} = \underline{\underline{0.45 \text{ W}}}$$

$V_{30 \text{ mA}} = -V_1$

Fig. 4) (12-14)

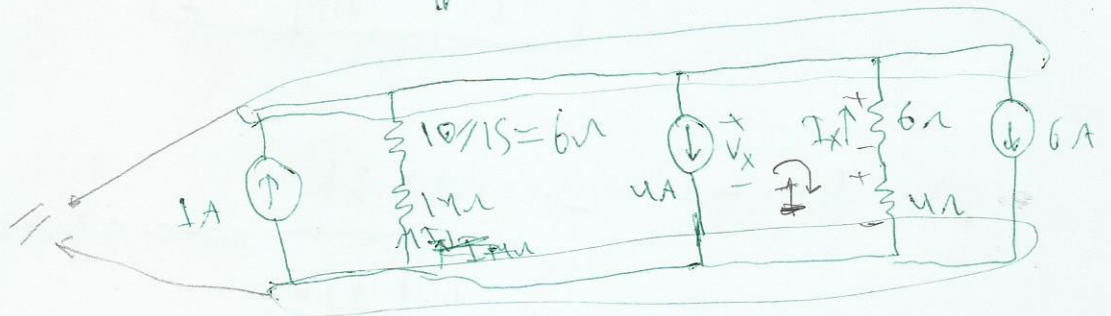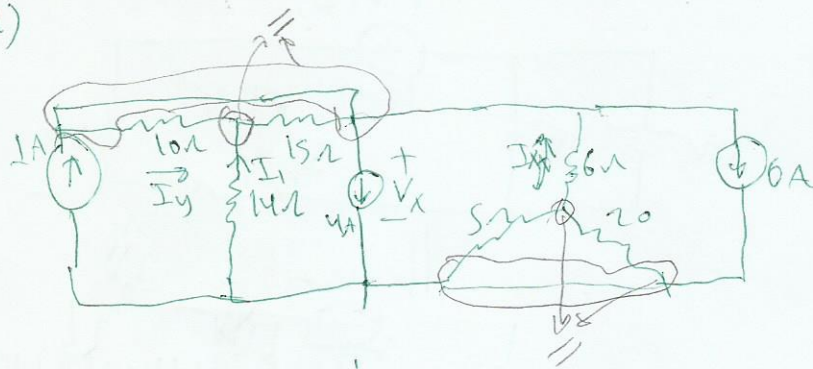

$$1A - 4A - 6A = -9A$$

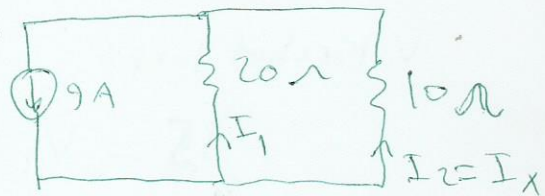

$$I_1 = \frac{9 \times 10}{10 + 20} = 3A, \quad I_x = 9 - 3 = 6A$$


$$\uparrow: \quad V_x = (6\Omega I_x + 4I_x) = 0$$

$$12) \quad V_x = 10I_x = 60V$$

$$13) \quad I_x = 6A$$

$$14) \quad I_d = I_1 \times \frac{15\Omega}{15\Omega + 10\Omega} = 3 \times \frac{15}{25} = 1.8A$$

Fig 5: (15-17)

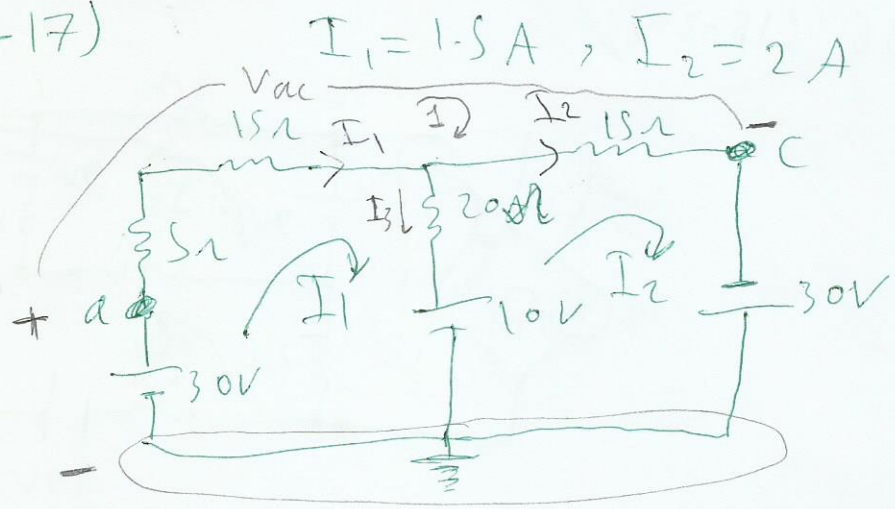

$I_1 = 1.5 \text{ A}, I_2 = 2 \text{ A}$

15. $V_a = V_{a\text{-ground}} = \underline{30 \text{ V}}$

16. $V_{ac} = ?$

by using V. Kir. loop 1:


$$\begin{aligned} V_{ac} &= (5\Omega + 15\Omega)I_1 + 15I_2 \\ &= 20 \times 1.5 + 15 \times 2 \\ &= \underline{60 \text{ V}} \end{aligned}$$

17. $P_{20\Omega} :$

$P = I^2 R$

$$\begin{aligned} P_{20\Omega} &= I_3^2 \times 20 & : I_3 = I_1 \\ &= (-0.5)^2 \times 20 = \underline{5 \text{ W}} & = -0 \end{aligned}$$

Fig 6 : (18-20):

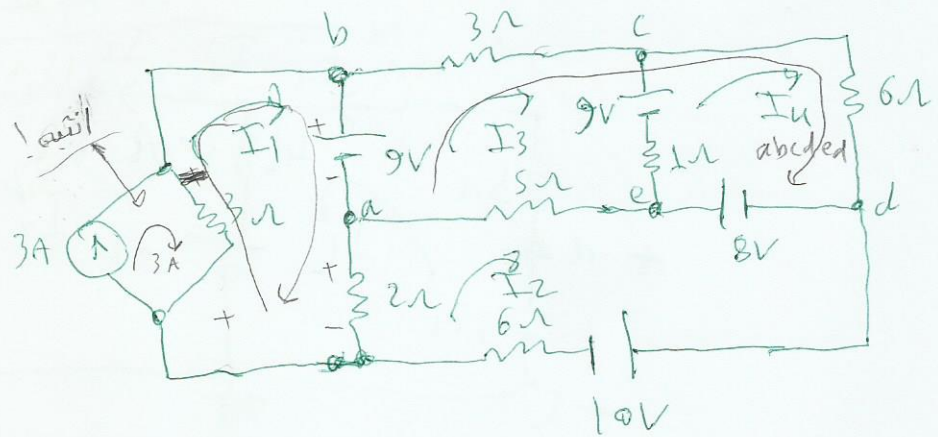

18.

$$(3+2)I_1 - 2I_2 + 9V - (3A \times 3\Omega) = 0$$

$$\rightarrow 5I_1 - 2I_2 = -9 + 9 = 0$$

$$\rightarrow \underline{5I_1 - 2I_2 = 0}$$

19.

$$-2I_1 + (2+5+6)I_2 - 5I_3 + 8V = 0$$

$$\rightarrow \underline{-2I_1 + 13I_2 - 5I_3 = -18}$$

20.

$$-9V + 3I_3 + 6I_4 + 5(I_3 - I_2) = 0$$

$$\underline{= -5I_2 + 8I_3 + 6I_4 = 17}$$