

In the circuit shown in Fig. P3.25, both diodes have  $n = 1$ , but  $D_1$  has 10 times the junction area of  $D_2$ . What value of  $V$  results? To obtain a value for  $V$  of  $10\text{ mV}$ , what current  $I_2$  is needed?

