33.5 The RLC series circuit

In the previous sections we considered individual elements connected to an AC source. Here, we will adopt a circuit that contains a combination of circuit elements: a resistor, an indicator, and a capacitor.



The instantaneous applied voltage is

$$\Delta v = V_{max} \sin \omega t$$

The current also varies as

$$i = I_{max} \sin(\omega t - \phi)$$
 33.10

where φ is some phase angle between the current and the applied voltage. Based on our discussion in chapter 28, the current everywhere in the circuit must be the same, while the voltage across each element has a different amplitude and phase.

$$\Delta v_R = I_{\max}R = \Delta V_R \sin \omega t$$
$$\Delta v_L = I_{\max}X_L \sin\left(\omega t + \frac{\pi}{2}\right) = \Delta V_L \cos \omega t$$
$$\Delta v_C = I_{\max}X_C \sin\left(\omega t - \frac{\pi}{2}\right) = -\Delta V_C \cos \omega t$$

Phase relationships between the voltage and current phasors for (a) a resistor, (b) an indicator, and (c) a capacitor connected in series are shown in following figure.



Because the phasors are rotating vectors, the voltage phasors can be combined using vector addition as in the following figure.



From this figure, we conclude that,

$$\Delta V_{\text{max}} = \sqrt{\Delta V_{\text{R}}^{2} + (\Delta V_{\text{L}} - \Delta V_{\text{C}})^{2}} = \sqrt{(I_{\text{max}}R)^{2} + (I_{\text{max}}X_{\text{L}} - I_{\text{max}}X_{\text{C}})^{2}}$$

$$\Delta V_{\text{max}} = I_{\text{max}}\sqrt{R^{2} + (X_{\text{L}} - X_{\text{C}})^{2}}$$

$$I_{\text{max}} = \frac{\Delta V_{\text{max}}}{\sqrt{R^{2} + (X_{\text{L}} - X_{\text{C}})^{2}}} = \frac{\Delta V_{\text{max}}}{Z}$$

$$33.12$$

Where $Z = \sqrt{R^2 + (X_L - X_C)^2}$ and is called the impedance of the circuit.

From the figure, one can also find the phase angel $\boldsymbol{\phi},$



Exercise:

Based on the phase angle in eq. (33.13), discuss the following situations:

- 1- When $X_L > X_C$
- 2- When $X_L < X_C$
- 3- When $X_L = X_C$

5 Phase Angle and Frequency in RLC Circuits

In an **RLC series AC circuit**, the **phase angle** (ϕ) between the current and the voltage depends on the relationship between **inductive reactance** (**X**_L) and **capacitive reactance** (**X**_C):

♦ 1. When X_L>X_C

- This occurs at **high frequencies**.
 - The net reactance is inductive, so:
 - The **current lags** behind the voltage.
 - The phase angle φ is positive.
- We say the circuit is **inductive**.

♦ 2. When X_L<X_C

- This occurs at **low frequencies**.
 - The net reactance is capacitive, so:
 - The current leads the voltage.
 - The phase angle φ is negative.
- The circuit is **capacitive**.

44 3. When XL=XC

- The inductive and capacitive effects cancel out.
- The circuit is **resonant** or **purely resistive**.
- The **phase angle is zero**:
 - Voltage and current are in phase.

Summary Table:

Inductive reactance: $X_L = \omega L = 2\pi f L$

Capacitive reactance: $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$

Condition	φ (Phase Angle)	Behavior
X _L >X _C	Positive	Inductive: current lags
XL <xc< td=""><td>Negative</td><td>Capacitive: current leads</td></xc<>	Negative	Capacitive: current leads
X _L =X _C	Zero	Purely resistive

Example-1:

A series RLC circuit has R = 425 V, L = 1.25 H, and C = 3.50 mF. It is connected to an AC source with f = 60.0 Hz and $\Delta V_{max} = 150$ V.

- (A) Determine the inductive reactance, the capacitive reactance, and the impedance of the circuit.
- (B) Find the maximum current in the circuit.
- (C) Find the phase angle between the current and voltage.
- (**D**) Find the maximum voltage across each element.
- (E) What replacement value of L should an engineer analyzing the circuit choose such that the current leads the applied voltage by 30° rather than 34° ? All other values in the circuit stay the same.

Quiz-1:

Examine the Figure, which includes diagrams labeled (a), (b), and (c).

For each part, determine the correct relationship between the inductive reactance X_L and the capacitive reactance X_C .

Label each as one of the following:

- X_L>X_C
- X_L<X_C
- X_L=X_C

Indicate which condition corresponds to each part: (a), (b), and (c).



(*a*)

- Current leads voltage (phasor is ahead in rotation direction).
- \checkmark This means $X_L < X_C$ (capacitive behavior).

(b)

- Current and voltage are **in phase**.
- \checkmark This means $X_L = X_C$ (resonance).

(c)

- Voltage **leads** current.
- \checkmark This means $X_L > X_C$ (inductive behavior).

Quiz-2: In a series RLC circuit, increasing the frequency of the source causes which of the following to decrease?

- A. Inductive reactance X_L
- B. Capacitive reactance X_C
- C. Resonant frequency
- D. Total impedance near resonance