

28.3 Kirchhoff's rules:

As we discussed that we can analyze simple circuits using the expression $V = IR$ and the rules for series and parallel combinations of resistors. However, it is not often possible to reduce a circuit to a single loop.


-The procedure for analyzing more complex circuits is greatly simplified if we use two principles called Kirchhoff's rules:

Rule 1:

The sum of electric current entering any junction in a circuit must equal to the sum of electric current leaving that junction as given by:

$$\sum I_{in} = \sum I_{out}$$

$$I_1 = I_2 + I_3$$

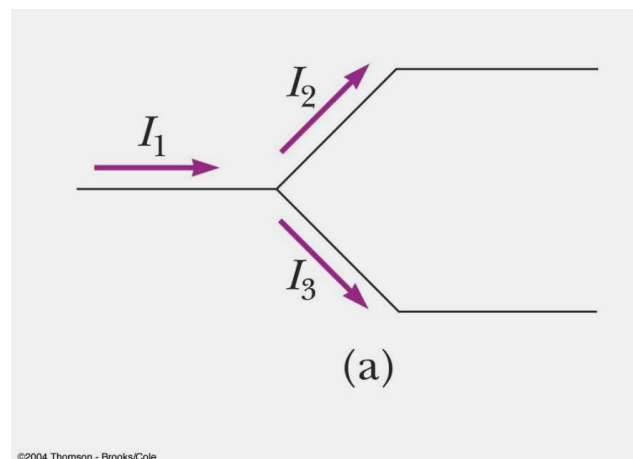

The charge that passes through some circuit elements must equal the sum of the decreases in energy as it passes through other elements. The potential energy decreases whenever the charge moves through a potential drop IR across a resistor or whenever it moves in the reverse direction through a source of emf. The potential energy increases whenever the charge passes through a battery from the negative terminal to the positive terminal.

Rule 2:

The sum of the potential difference across all electric elements around any closed circuit loop must equal zero,




$$\sum \nabla V = 0$$

Let us imagine moving a charge around the loop. When the charge returns to the starting point, the charge–circuit system must have the same energy as when the charge started from it.

The sum of the increases in energy in some circuit elements must equal the sum of the decreases in energy in other elements.

The potential energy decreases whenever the charge moves through a potential drop IR across a resistor or whenever it moves in the reverse direction through a source of emf. The potential energy increases whenever the charge passes through a battery from the negative terminal to the positive terminal.

Each circuit element is traversed from left to right \longrightarrow
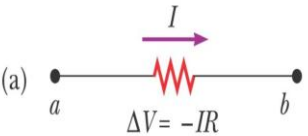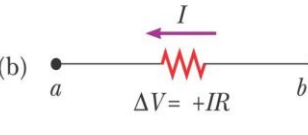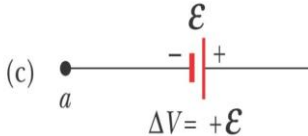
| | |
|--|--|
| <p>(a) </p> <p><small>©2004 Thomson - Brooks/Cole</small></p> | <ul style="list-style-type: none">• Because charges move from the high-potential end of a resistor to the low-potential end, if a resistor is traversed in the direction of the current, the change in potential V across the resistor is $-IR$ |
| <p>(b) </p> <p><small>©2004 Thomson - Brooks/Cole</small></p> | <ul style="list-style-type: none">• If a resistor is traversed in the direction opposite the current, the change in potential V across the resistor is $+IR$ |
| <p>(c) </p> <p><small>©2004 Thomson - Brooks/Cole</small></p> | <ul style="list-style-type: none">• If a source of emf (assumed to have zero internal resistance) is traversed in the direction of the emf (from $-$ to $+$), the change in potential V is $+\epsilon$. The emf of the battery increases the electric potential as we move through it in this direction. |

$$-4I_2 - 14 + 6I_1 - 10 = 0$$

$$6I_1 - 4I_2 - 24 = 0 \quad 3$$

Substituting (1) in (2):

$$10 - 6I_1 - 2(I_1 + I_2) = 0$$

$$-8I_1 - 2I_2 + 10 = 0 \quad 4$$

Multiply each term in Equation (3) by 4 and each term in Equation (4) by 3:

$$-96 + 24I_1 - 16I_2 = 0 \quad 5$$

$$30 - 24I_1 - 6I_2 = 0 \quad 6$$

Add Equation (6) to Equation (5) to eliminate I_1 and find I_2 :

$$-66 - 22I_2 = 0 \quad \implies I_2 = -3A$$

Use this value of I_2 in Equation (3) to find I_1 :

$$-24 + 6I_1 - 4 * (-3) = 0$$

$$-24 + 6I_1 + 12 = 0$$

$$I_1 = 2 A$$

$$I_3 = I_1 + I_2 = 2 - 3 = -1 A$$

Because our values for I_2 and I_3 are negative, the directions of these currents are opposite those indicated in the Figure.

The numerical values for the currents are correct. Despite the incorrect direction, we must continue to use these negative values in subsequent calculations because our equations were established with our original choice of direction.