33.6 Power in an AC Circuit

In chapter 28, we found that the power delivered by a battery to an dc circuit equals to:

$$P=I^2R=\Delta V.I$$

Similarly, the power delivered by an ac generator to RLC circuit can be calculated as:

$$P = I.\Delta V = (I_{max}sin(\omega t - \phi)).(\Delta V_{max}sin(\omega t))$$

Also, we can express the average power P_{av} as follows:

$$P_{av.} = \frac{1}{2} I_{max} \Delta V_{max} \cos(\phi) = I_{rms} \Delta V_{rms} \cos(\phi)$$

where $cos(\phi)$ is called the power factor, an indicator of how effectively power is being used.

This Equation shows that the power delivered by an AC source to any circuit **depends on the phase**, a result that has many interesting applications. For example, a factory that uses large motors in machines, generators, or transformers has a large inductive load (because of all the windings). To deliver greater power to such devices in the factory without using excessively high voltages, technicians introduce capacitance in the circuits to shift the phase. (More explanations are shown below)

Special case:

When $\phi = 0 \rightarrow cos_{(0)} = 1$,

Then:

$$P_{av.} = \frac{1}{2} I_{max} \Delta V_{max} = I_{rms} \Delta V_{rms}$$

Moreover, we can write the average power as:

$$P_{av} = I_{rms}^2 R$$

We can conclude that:

- ✓ No power losses are associated with pure capacitors and pure inductors in an AC circuit. Why?
 - In an ideal capacitor or ideal inductor, no energy is permanently consumed or lost.
- The average power delivered by the source is converted to internal energy in the resistor.
 - A resistor converts electrical energy into heat continuously.

33.7 Resonance in a series RLC circuit

In the RLC circuit, the resonance frequency occurs when the driving frequency is such that the rms current has **its maximum value**.

$$I_{\rm rms} = \frac{\Delta V_{\rm rms}}{Z} = \frac{\Delta V_{\rm rms}}{\sqrt{R^2 + (X_{\rm L} - X_{\rm C})^2}}$$
 33.14

The angular frequency ω_0 at which $X_L - X_C = 0$ is called the resonance frequency of the circuit.

$$X_{L} = X_{C}$$

$$\omega_{0}L = \frac{1}{\omega_{0}C}$$

$$\omega_{0}^{2} = \frac{1}{LC}$$

$$\omega_{0} = \frac{1}{\sqrt{LC}}$$

33.15

- ★ At resonance, the circuit behaves like a pure resistor.
- ✓ The current is **maximum** because impedance is **minimum**.
- ✓ The current is in phase with the voltage because the inductor and capacitor cancel each other's effects.
- $\checkmark Z = \sqrt{R^2 (X_L X_C)^2}$; since: $X_L = X_C$; Then, Z = R

A plot of I_{rms} current versus angular frequency (ω) for a series *RLC* circuit is shown in the Figure below. The data assume a constant $\Delta V_{\rm rms} = 5.0$ mV, L = 5.0 mH, and C = 2.0 nF.



- ✓ All curves peak sharply at ω_0 , confirming that **maximum current occurs at** resonance.
- \checkmark As R increases, the **maximum current decreases**.
- ✓ Lower resistance (e.g., R=3.5 Ω) results in a **sharper and taller peak**, indicating a **higher Q factor** (better resonance).
- \checkmark Higher resistance makes the curve flatter (broader resonance).
- The average power as a function of frequency for a series RLC circuit as:

$$P_{\rm av.} = \frac{(\Delta V_{rms})^2 R \omega^2}{R^2 \omega^2 + L^2 (\omega^2 - \omega_0^2)^2}$$

• When $\omega = \omega_0$, the average power is **maximum**.

The power factor Q can also be computed as following:

$$Q = \frac{\omega_0}{\Delta \omega} = \frac{\omega_0 L}{R}$$

Where $\Delta \omega$ is the width of the curve measured between the two values of ω for which P_{avg} has one-half its maximum value, called the *half-power points*.

Right Plot (b):

- Power Peaks at Resonance ω₀:
- Just like current, **power is maximized** when the driving frequency equals the resonance frequency.
- ✓ Sharper Peak with Lower Resistance:
- Lower resistance produces a **narrower**, taller peak, which means more efficient power transfer near ω_0 , but less outside that frequency.
- The quantity $\Delta \omega$ (bandwidth) is **smaller** for smaller R, indicating a higher selectivity or **sharper resonance**.
- ✓ Power Decreases with Higher Resistance:
- For R=10, the peak power is lower and more spread out, showing that resistance reduces power output and broadens the response.

Exercise-I:

A series RLC circuit is connected to an AC source with the voltage:

 $v(t) = 200 \sin(314t)$, $i(t) = 8 \sin(314t - 0.643)$

Given:

- L=0.5 H
- R=20 Ω

Q-1: What is the total impedance of the circuit?				
a) 1600 Ω	b) 157 Ω	c) 142 Ω	d) 25 Ω	

Q-2: What is the power factor of the circuit?			
a) 1	b) 0.25	c) 0.8	d) Zero

Q-3: Based on the given values, which of the following is true about the phase relationship in the circuit?

- a) Voltage leads the current
- b) Current and voltage are in phase
- c) Current leads the voltage
- d) Current is perpendicular to the voltage

Q-4: At resonance, what happens to the resonance frequency if the resistance **R** in the circuit is decreased?

- a) Remains constant
- b) Increases
- c) Decreases
- d) Changes as a sinusoidal wave

Q-5: What is the capacitive reactance X_C of the circuit?

•	L		
a) 1600 Ω	b) 157 Ω	c) 142 Ω	d) 25 Ω

Exercise-II:

A sinusoidal voltage source is described by:

 $\Delta v(t) = 100 \sin(1000t)$

where t is in seconds and Δv is in volts. This voltage is applied to a series RLC circuit with the following parameters:

- Resistance: $R=400\Omega$
- Capacitance: C=5µF
- Inductance: L=0.5H

Q-1:	What is the total impeda	nce Z of the circ	uit (in ohms)?
a) 50	b) 100	c) 500	d) 1000

Q-2: In reference to Q-1, by how many degrees does the **voltage lead the current** in the RLC circuit? a) 26.0° b) 42.2° c) 64.5° d) 85.2°

a) 36.9°	b) 43.2°	c) 64.5°	d) 85.3°
----------	----------	----------	----------

Q-3: Based on the same RLC circuit, what is the resonance angular frequency $\omega 0 \setminus omega_0 \omega 0$ of the circuit (in rad/s)?a) 59.3b) 264.3c) 417.5d) 632.5

Q-4: In a series RLC AC circuit, the instantaneous voltage and current are given as:

 $\Delta v(t) = 100 \sin(\omega t),$ $i(t) = 100 \sin(\omega t + 3\pi)$

where t is in seconds, Δv is in volts, and i is in amperes.

What is the average power consumed by the circuit (in kilowatts)?a) 1.5b) 2.5c) 5.5d) 10.5



Average Power in AC Circuits

The formula:

Solution Second Seco

- P_{av}: Average power delivered to the circuit (in watts)
- I_{max} , ΔV_{max} : Maximum current and voltage
- I_{rms} , ΔV_{rms} : RMS (root mean square) values of current and voltage
- $\cos(\phi)$: **Power factor** a crucial indicator of how effectively power is being used

4 What the Equation Tells Us:

- Power delivery in an AC circuit **depends on the phase difference** ϕ between voltage and current.
- If voltage and current are in phase (φ=0°), cos(φ)=1, and maximum power is delivered.
- If voltage and current are **out of phase** (like in inductive or capacitive loads), cos(φ)<1, and **less real power is delivered**, even though current and voltage are still present.

Real-World Example — Industrial Settings:

Factories using:

- Large motors
- Transformers
- Generators

... often deal with **inductive loads** due to the coils in these machines. Inductance causes the **current to lag** behind the voltage, resulting in a **low power factor**.

To **improve the power factor** and make the system more efficient:

- Capacitors are added to the circuit.
- Capacitors cause **current to lead voltage**, which **offsets** the lag from the inductors.
- This reduces the phase angle φ and increases cos(φ), allowing more real power to be delivered without increasing the voltage or current dangerously.

C Why This Matters:

Improving the power factor means:

- Less energy wasted
- Lower electricity bills
- Smaller voltage drops
- Better performance of electrical systems

Exercise:

Plotting Irms and Pav vs Frequency for a Series RLC Circuit using Python

Given:

- L=5.0 μ H
- C=2.0 nF
- $\Delta Vrms=5.0 \text{ mV}$
- Test three resistance values: $R=3.5 \Omega$, 5.0 Ω , and 10.0 Ω
- Angular frequency range: 8×10^6 to 12×10^6 rad/s

Starter Python Code:

```
import numpy as np
import matplotlib.pyplot as plt
# Constants
L = 5e-6 # H
C = 2e-9 # F
Vrms = 5e-3 # V
omega = np.linspace(8e6, 12e6, 1000) # Angular frequency range
# Resistance values
R values = [0.50, 5.0, 50.0]
# Set up plots
fig, (ax1, ax2) = plt.subplots(1, 2, figsize=(12, 5))
for R in R values:
    # Reactances
    XL = omega * L
    XC = 1 / (omega * C)
    # Impedance
    Z = np.sqrt(R^{*}2 + (XL - XC)^{*}2)
    # RMS Current
```

```
Irms = Vrms / Z
    # Average Power
    P avg = Irms^{*2} R
    # Plotting
    ax1.plot(omega / 1e6, Irms * 1e3, label=f"R = {R} \Omega")
ax2.plot(omega / 1e6, P_avg * 1e6, label=f"R = {R} \Omega")
# Labels and titles
ax1.set_title("RMS Current vs Frequency")
ax1.set_xlabel("Angular Frequency (Mrad/s)")
ax1.set_ylabel("I_rms (mA)")
ax1.grid(True)
ax1.legend()
ax2.set_title("Average Power vs Frequency")
ax2.set_xlabel("Angular Frequency (Mrad/s)")
ax2.set_ylabel("P_avg (µW)")
ax2.grid(True)
ax2.legend()
plt.tight layout()
plt.show()
```