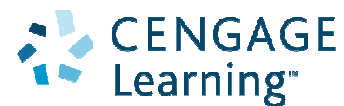


Chapter 5


Electrical circuits



Basic Electrical Circuits & Components

Basic Electrical & Electronics

Electrical Circuit Terminology

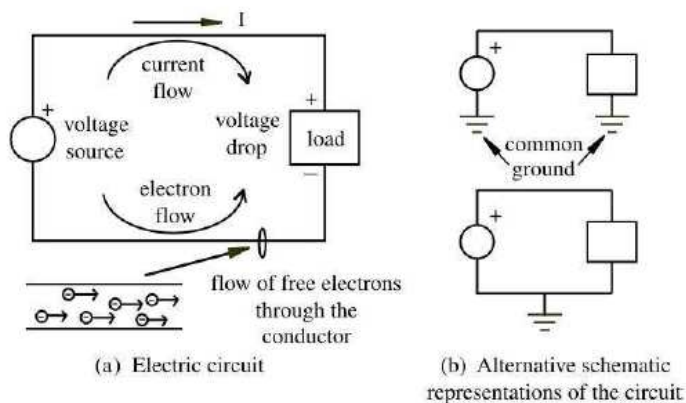

e581.eps


- *Anode* : +ve side of source where electrons are attracted.
- *Cathode* : -ve side from where electrons are released.
- *Ground* : a reference point where voltage is assumed zero.
- *Load* : network of circuit elements that dissipate or store electrical energy.



Basic Electrical Circuits & Components

Basic Electrical & Electronics

Basic Electrical Elements

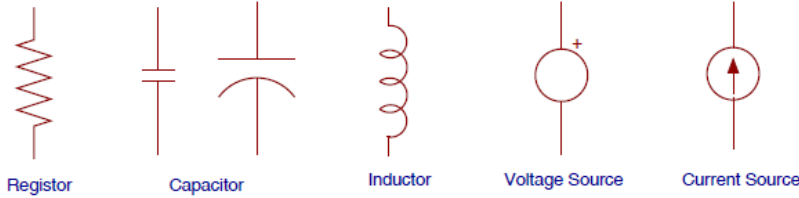

- There are three basic passive elements: the resistor (R), capacitor (C) and inductor (L).
- Passive elements require no additional power supply, as active elements such as integrated circuits.
- There are two types of ideal energy sources: a voltage source (V) and a current source (I).
- Ideal sources contain no internal resistance, inductance or capacitance.



Basic Electrical Circuits & Components

Basic Electrical & Electronics

Resistor

□ Resistor dissipates electrical energy into heat.

$$V = IR \quad P = I^2 R \quad R = ab \cdot 10^c \pm tol$$

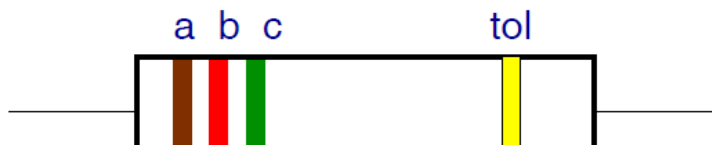


Table: a, b, and c Bands

Color	Black	Brown	Red	Orange	Yellow	Green	Blue	Violet	Gray	White
Value	0	1	2	3	4	5	6	7	8	9

Table: tol Band

Color	Gold	Silver	Nothing
Value	±5%	±10%	±20%

INTRODUCTION



Basic Electrical Circuits & Components

Basic Electrical & Electronics

Capacitor

- Capacitor is a passive element that stores energy in the form of an electric field, resulted from a separation of electrical charge.
- An ideal capacitor generates a voltage potential difference between its two nodes proportional to the stored electrical charge.

$$v_C(t) = \frac{Q(t)}{C} = \frac{1}{C} \int_0^t i(\tau) d\tau \quad i(t) = C \frac{dv_C}{dt}$$


where, C = Capacitance (Farad = Coulomb/Volt)

- Since the voltage across a capacitor is the integral of the displacement current the voltage cannot change instantaneously.
- An ideal capacitor induces a 90° phase angle between its voltage and current across its terminals due to the integral function.




Basic Electrical Circuits & Components

Basic Electrical & Electronics

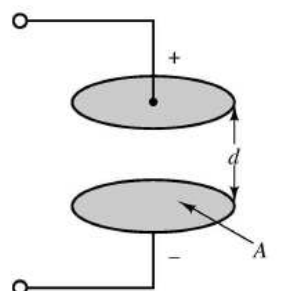

Parallel-plate capacitor with air gap d (air is the dielectric)

e433.eps

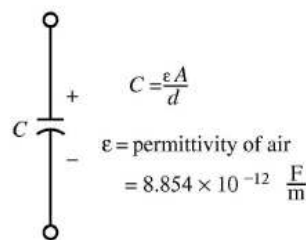

Circuit symbol

e434.eps

- Capacitance is a property of the dielectric material, the plate geometry and separation.
- Capacitors block DC voltage and pass the AC voltage. DC voltage will build a potential difference in the capacitor until they are equal. AC voltage simply alternates the charge and discharge of the capacitor and is passed, not blocked, in a circuit.



Basic Electrical Circuits & Components

Basic Electrical & Electronics

Inductor

- Inductor is a passive energy storage element that stores energy in the form of a magnetic field.
- An ideal inductor generates a potential difference proportional to the rate of change of current passing through it.

$$v_L(t) = L \frac{di}{dt} = \frac{d\lambda}{dt} \quad i(t) = \frac{1}{L} \int_0^t v_L(\tau) d\tau$$


λ = Magnetic flux through the coil due to current (Weber),
 L = Inductance of the coil (Henry), assumed to be constant.

↔ Current through an inductor cannot change instantaneously because it is an integral of the voltage. Motor, electromagnetic relays or solenoids have large inductance, so it is difficult to turn these ON or OFF very fast.



Basic Electrical Circuits & Components

Basic Electrical & Electronics

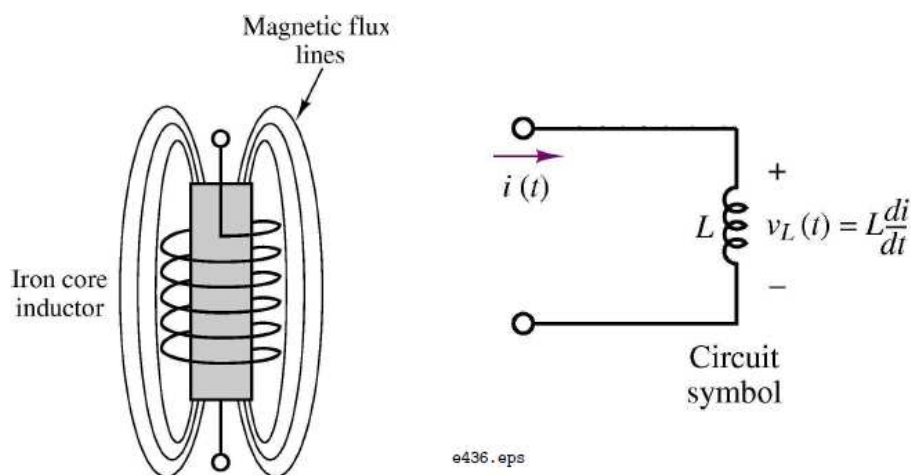

e435 . eps


The inductor is made by a coil of conductor around a core like a solenoid.



Basic Electrical Circuits & Components

Circuit


Node & Loop

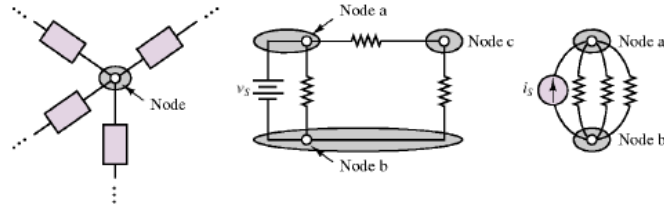

e385.eps

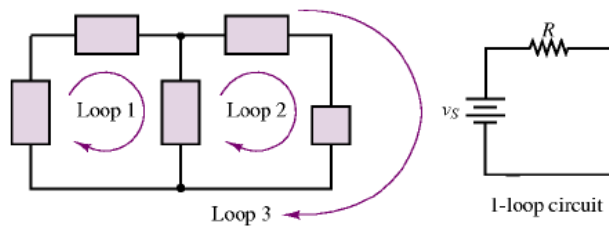Examples of nodes in practical circuits

A node is the junction of 2 or more branches.



e386.eps

A loop is any closed connection of branches.




CENGAGE Learning

Basic Electrical Circuits & Components

Circuit

Kirchoff's Voltage Law (KVL)

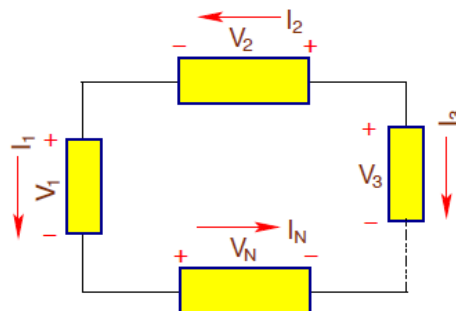- Sum of voltages around a closed loop is zero, $\sum_{i=1}^N V_i = 0$
- In clockwise or counterclockwise loop direction, form the sum of the voltages across each element, assign to each voltage the first algebraic sign encountered at each element.



$$-V_1 - V_2 + V_3 + \dots - V_N = 0$$

introduction




CENGAGE Learning

Basic Electrical Circuits & Components

Circuit

Kirchoff's Current Law (KCL)

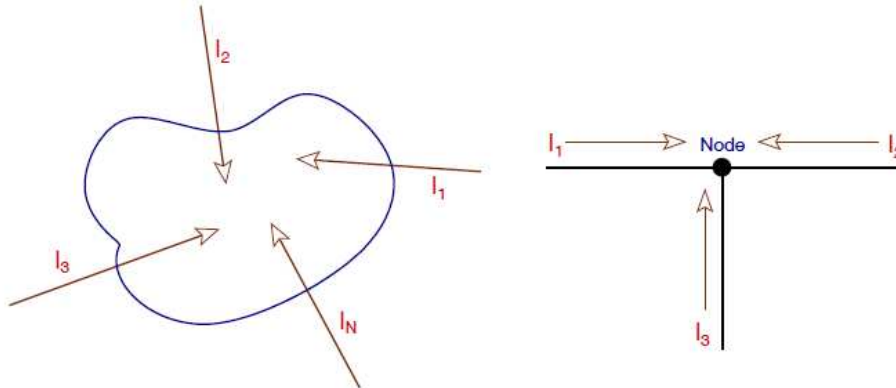- Sum of the currents flowing into a closed surface or node is zero, $\sum_{i=1}^N I_i = I_1 + I_2 + \dots + I_N = 0$.



- If the calculated result for a current is negative, the current actually flows in opposite direction.


Introduction



Basic Electrical Circuits & Components

AC Signals & Impedance

Sinusoidal Waveform

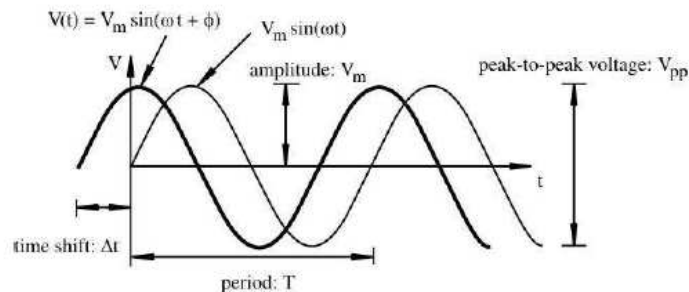

- frequency: $f = \frac{1}{T} = \frac{\omega}{2\pi}$ time shift: $\Delta t = \frac{\phi}{\omega}$
- if ϕ is +ve \rightarrow occurs earlier on time axis \rightarrow lagging.
- $V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t) dt} = \frac{V_m}{\sqrt{2}}$
- $I_{rms} = \sqrt{\frac{1}{T} \int_0^T I(t)^2 dt} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t - \theta) dt} = \frac{I_m}{\sqrt{2}}$
- $P(t) = V(t)I(t) = 2V_{rms}I_{rms} \cos(\omega t) \cos(\omega t - \theta)$
- $P_{av} = \frac{1}{T} \int_0^T P(t) dt = V_{rms}I_{rms} \cos \theta$

