

PHYS 221

Electromagnetism (1)
2nd semester 1446


Prof. Omar Abd-Elkader

Problems 9

Chapter 33 Problems

3, 10, 17, 21, 22, 26, 32, 33, 37

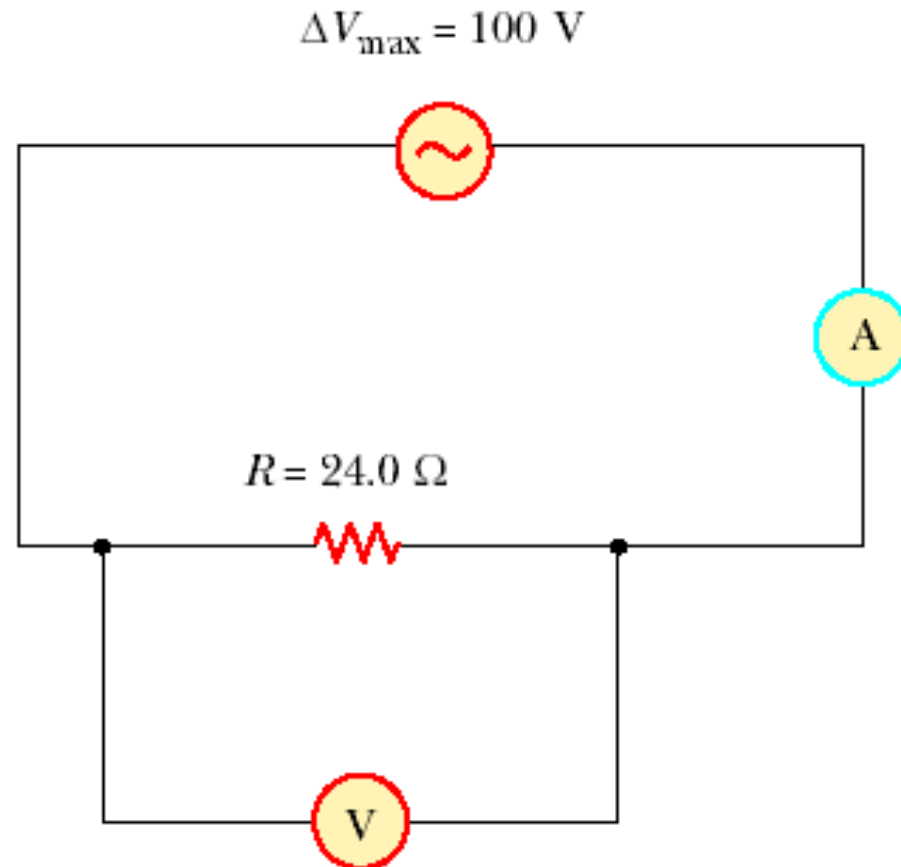3. An AC power supply produces a maximum voltage $\Delta V_{\max} = 100 \text{ V}$. This power supply is connected to a $24.0\text{-}\Omega$ resistor, and the current and resistor voltage are measured with an ideal AC ammeter and voltmeter, as shown in Figure P33.3. What does each meter read? Note that an ideal ammeter has zero resistance and that an ideal voltmeter has infinite resistance.



Each meter reads the rms value.

$$\Delta V_{\text{rms}} = \frac{100 \text{ V}}{\sqrt{2}} = \boxed{70.7 \text{ V}}$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{R} = \frac{70.7 \text{ V}}{24.0 \Omega} = \boxed{2.95 \text{ A}}$$

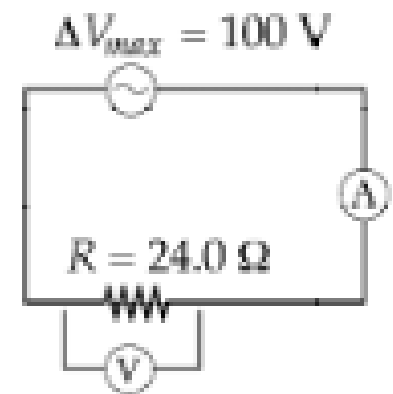


FIG. P33.3

10. An inductor has a $54.0\text{-}\Omega$ reactance at 60.0 Hz . What is the maximum current if this inductor is connected to a 50.0-Hz source that produces a 100-V rms voltage?

$$\text{At } 50.0\text{ Hz, } X_L = 2\pi(50.0\text{ Hz})L = 2\pi(50.0\text{ Hz})\left(\frac{X_L|_{60.0\text{ Hz}}}{2\pi(60.0\text{ Hz})}\right) = \frac{50.0}{60.0}(54.0\ \Omega) = 45.0\ \Omega$$

$$I_{\max} = \frac{\Delta V_{\max}}{X_L} = \frac{\sqrt{2}(\Delta V_{\text{rms}})}{X_L} = \frac{\sqrt{2}(100\text{ V})}{45.0\ \Omega} = \boxed{3.14\text{ A}}.$$

17. What maximum current is delivered by an AC source with $\Delta V_{\max} = 48.0$ V and $f = 90.0$ Hz when connected across a $3.70\text{-}\mu\text{F}$ capacitor

$$I_{\max} = (\Delta V_{\max})\omega C = (48.0 \text{ V})(2\pi)(90.0 \text{ s}^{-1})(3.70 \times 10^{-6} \text{ F}) = \boxed{100 \text{ mA}}$$

21. A series AC circuit contains the following components: $R = 150 \, \Omega$, $L = 250 \, \text{mH}$, $C = 2.00 \, \mu\text{F}$ and a source with $\Delta V_{\text{max}} = 210 \, \text{V}$ operating at $50.0 \, \text{Hz}$. Calculate the (a) inductive reactance, (b) capacitive reactance, (c) impedance, (d) maximum current, and (e) phase angle between current and source voltage.

$$(a) \quad X_L = \omega L = 2\pi(50.0 \, \text{s}^{-1})(250 \times 10^{-3} \, \text{H}) = \boxed{78.5 \, \Omega}$$

$$(b) \quad X_C = \frac{1}{\omega C} = \left[2\pi(50.0 \, \text{s}^{-1})(2.00 \times 10^{-6} \, \text{F})\right]^{-1} = \boxed{1.59 \, \text{k}\Omega}$$

$$(c) \quad Z = \sqrt{R^2 + (X_L - X_C)^2} = \boxed{1.52 \, \text{k}\Omega}$$

$$(d) \quad I_{\text{max}} = \frac{\Delta V_{\text{max}}}{Z} = \frac{210 \, \text{V}}{1.52 \times 10^3 \, \Omega} = \boxed{138 \, \text{mA}}$$

$$(e) \quad \phi = \tan^{-1}\left[\frac{X_L - X_C}{R}\right] = \tan^{-1}(-10.1) = \boxed{-84.3^\circ}$$

22. A sinusoidal voltage $\Delta v(t) = (40.0 \text{ V}) \sin(100t)$ is applied to a series RLC circuit with $L = 160 \text{ mH}$, $C = 99.0 \mu\text{F}$, and $R = 68.0 \Omega$. (a) What is the impedance of the circuit? (b) What is the maximum current? (c) Determine the numerical values for I_{max} , ω , and ϕ in the equation $i(t) = I_{\text{max}} \sin(\omega t - \phi)$.

$$(a) \quad Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{68.0^2 + (16.0 - 101)^2} = \boxed{109 \Omega}$$

$$X_L = \omega L = (100)(0.160) = 16.0 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{(100)(99.0 \times 10^{-6})} = 101 \Omega$$

$$(b) \quad I_{\text{max}} = \frac{\Delta V_{\text{max}}}{Z} = \frac{40.0 \text{ V}}{109 \Omega} = \boxed{0.367 \text{ A}}$$

$$(c) \quad \tan \phi = \frac{X_L - X_C}{R} = \frac{16.0 - 101}{68.0} = -1.25 :$$

$$\phi = -0.896 \text{ rad} = -51.3^\circ$$

$$\boxed{I_{\text{max}} = 0.367 \text{ A}}$$

$$\boxed{\omega = 100 \text{ rad/s}}$$

$$\boxed{\phi = -0.896 \text{ rad} = -51.3^\circ}$$

26. An AC source with $\Delta V_{\text{max}} = 150 \text{ V}$ and $f = 50.0 \text{ Hz}$ is connected between points a and d in Figure P33.26. Calculate the maximum voltages between points (a) a and b , (b) b and c , (c) c and d , and (d) b and d .



$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi(50.0)(65.0 \times 10^{-6})} = 49.0 \Omega$$

$$X_L = \omega L = 2\pi(50.0)(185 \times 10^{-3}) = 58.1 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(40.0)^2 + (58.1 - 49.0)^2} = 41.0 \Omega$$

$$I_{\max} = \frac{\Delta V_{\max}}{Z} = \frac{150}{41.0} = 3.66 \text{ A}$$

(a) $\Delta V_R = I_{\max} R = (3.66)(40) = \boxed{146 \text{ V}}$

(b) $\Delta V_L = I_{\max} X_L = (3.66)(58.1) = 212.5 = \boxed{212 \text{ V}}$

(c) $\Delta V_C = I_{\max} X_C = (3.66)(49.0) = 179.1 \text{ V} = \boxed{179 \text{ V}}$

(d) $\Delta V_L - \Delta V_C = 212.5 - 179.1 = \boxed{33.4 \text{ V}}$

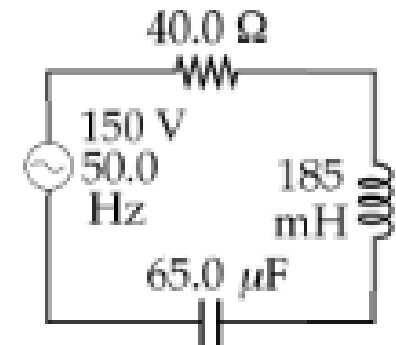


FIG. P33.26

32. A series RLC circuit has a resistance of 45.0Ω and an impedance of 75.0Ω . What average power is delivered to this circuit when $\Delta V_{\text{rms}} = 210 \text{ V}$?

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \text{ or } (X_L - X_C) = \sqrt{Z^2 - R^2}$$

$$(X_L - X_C) = \sqrt{(75.0 \Omega)^2 - (45.0 \Omega)^2} = 60.0 \Omega$$

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right) = \tan^{-1}\left(\frac{60.0 \Omega}{45.0 \Omega}\right) = 53.1^\circ$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{Z} = \frac{210 \text{ V}}{75.0 \Omega} = 2.80 \text{ A}$$

$$\mathcal{P} = (\Delta V_{\text{rms}}) I_{\text{rms}} \cos \phi = (210 \text{ V})(2.80 \text{ A}) \cos(53.1^\circ) = \boxed{353 \text{ W}}$$

33. In a certain series RLC circuit, $I_{\text{rms}} = 9.00 \text{ A}$, $\Delta V_{\text{rms}} = 180 \text{ V}$, and the current leads the voltage by 37.0° . (a) What is the total resistance of the circuit? (b) Calculate the reactance of the circuit ($X_L - X_C$).

(a) $\mathcal{P} = I_{\text{rms}}(\Delta V_{\text{rms}}) \cos \phi = (9.00)180 \cos(-37.0^\circ) = 1.29 \times 10^3 \text{ W}$

$\mathcal{P} = I_{\text{rms}}^2 R$ so $1.29 \times 10^3 = (9.00)^2 R$ and $R = \boxed{16.0 \ \Omega}$.

(b) $\tan \phi = \frac{X_L - X_C}{R}$ becomes $\tan(-37.0^\circ) = \frac{X_L - X_C}{16}$: so $X_L - X_C = \boxed{-12.0 \ \Omega}$.

37. An *RLC* circuit is used in a radio to tune into an FM station broadcasting at 99.7 MHz. The resistance in the circuit is 12.0 Ω , and the inductance is 1.40 μH . What capacitance should be used?

$$\omega_0 = 2\pi(99.7 \times 10^6) = 6.26 \times 10^8 \text{ rad/s} = \frac{1}{\sqrt{LC}}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(6.26 \times 10^8)^2 (1.40 \times 10^{-6})} = \boxed{1.82 \text{ pF}}$$