

PHYS 111

1st semester 1446


Prof. OMAR H. M. ABD-ELKADER

Lecture 7

RC Circuits


RC circuits contain both a resistor R and a capacitor C (duh).

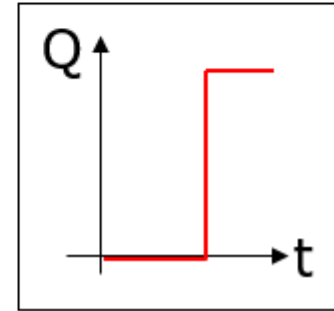Until now we have assumed that charge is instantly placed on a capacitor by an emf.



The approximation resulting from this assumption is reasonable, provided the resistance between the emf and the capacitor being charged/discharged is small.

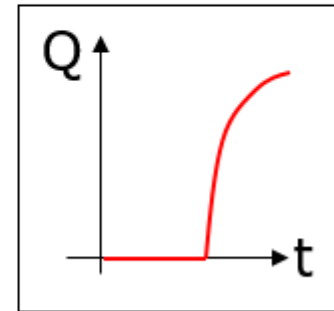If the resistance between the emf and the capacitor is finite, then the capacitor does not change instantaneously.



Charging a Capacitor


Switch open, no current flows.

Close switch, current flows.

Apply Kirchoff's loop rule*
(green loop) at the instant
charge on C is q .

$$\varepsilon - \frac{q}{C} - IR = 0$$

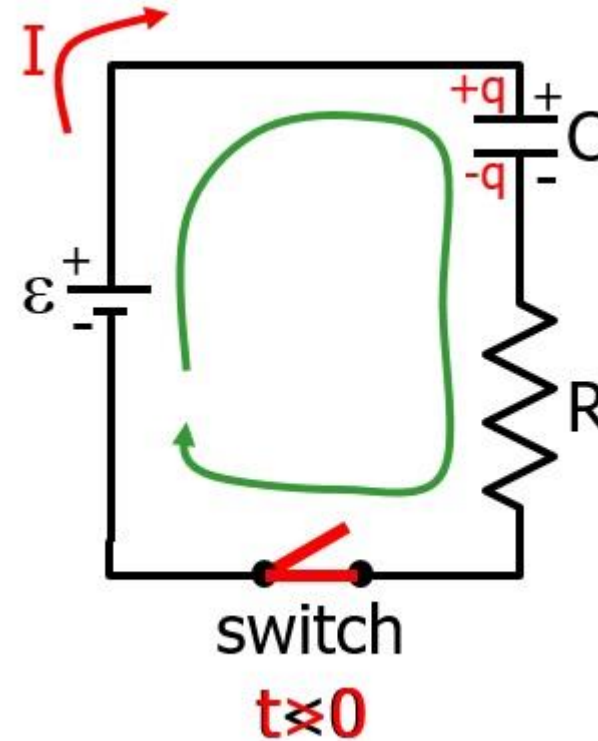This equation is
deceptively
complex because
 I depends on q
and both depend
on time.




*Convention for capacitors is "like" batteries: negative if going across from + to -.

Limiting Cases

$$\varepsilon - \frac{q}{C} - IR = 0$$

When $t=0$, $*q=0$ and $I_0=\varepsilon/R$.

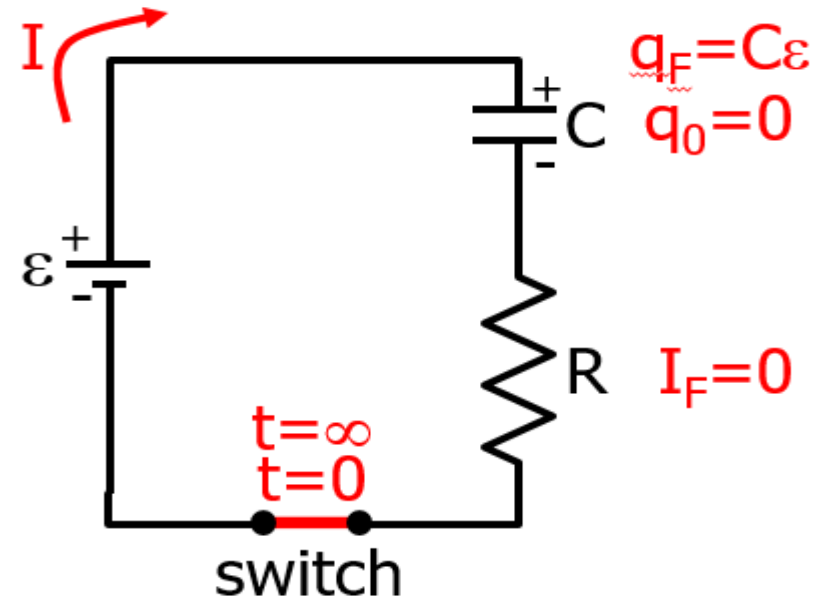When t is "large," the capacitor is fully charged, the current "shuts off," and $Q=C\varepsilon$.



$*q=0$ at $t=0$ only if the capacitor is initially uncharged (read the problems carefully!)

$\varepsilon = IR$ is true only at time $t=0$ or when $q=0$! $V_R = IR$ is always true, but V_R is the potential difference across the resistor, which you may not know. Using $V = IR$ to find the voltage across the capacitor is likely to lead to mistakes unless you are very careful.

Math:

$$\varepsilon - \frac{q}{C} - IR = 0$$

$$I = \frac{\varepsilon}{R} - \frac{q}{RC}$$

$$\frac{dq}{dt} = \frac{\varepsilon}{R} - \frac{q}{RC} = \frac{C\varepsilon}{RC} - \frac{q}{RC} = \frac{C\varepsilon - q}{RC}$$

$$\frac{dq}{C\varepsilon - q} = \frac{dt}{RC}$$

$$\frac{dq}{q - C\varepsilon} = -\frac{dt}{RC}$$

More math:

$$\int_0^q \frac{dq}{q - C_\varepsilon} = - \int_0^t \frac{dt}{RC}$$

$$\ln(q - C_\varepsilon) \Big|_0^q = - \frac{1}{RC} \int_0^t dt$$

$$\ln\left(\frac{q - C_\varepsilon}{-C_\varepsilon}\right) = - \frac{t}{RC}$$

$$\frac{q - C_\varepsilon}{-C_\varepsilon} = e^{-\frac{t}{RC}}$$

$$q - C_\varepsilon = -C_\varepsilon e^{-\frac{t}{RC}}$$

Still more math:

$$q = C\varepsilon - C\varepsilon e^{-\frac{t}{RC}}$$

$$q = C\varepsilon \left(1 - e^{-\frac{t}{RC}} \right)$$

$$q(t) = Q \left(1 - e^{-\frac{t}{RC}} \right)$$

Why not just solve this for q and I?

$$\varepsilon - \frac{q}{C} - IR = 0$$

$$I(t) = \frac{dq}{dt} = C\varepsilon \left(\frac{1}{RC} e^{-\frac{t}{RC}} \right) = \frac{C\varepsilon}{RC} e^{-\frac{t}{RC}} = \frac{\varepsilon}{R} e^{-\frac{t}{RC}} = \frac{\varepsilon}{R} e^{-\frac{t}{\tau}}$$



$\tau = RC$ is the "time constant" of the circuit; it tells us "how fast" the capacitor charges and discharges.

Charging a capacitor; summary:

$$q(t) = Q_{\text{final}} \left(1 - e^{-\frac{t}{RC}} \right)$$

recall that this is I_0 ,
also called I_{max}

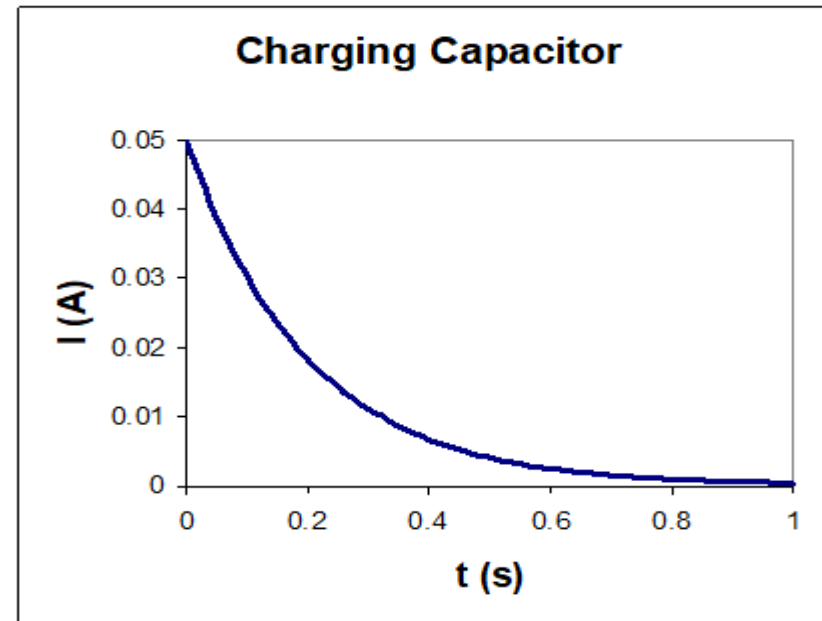
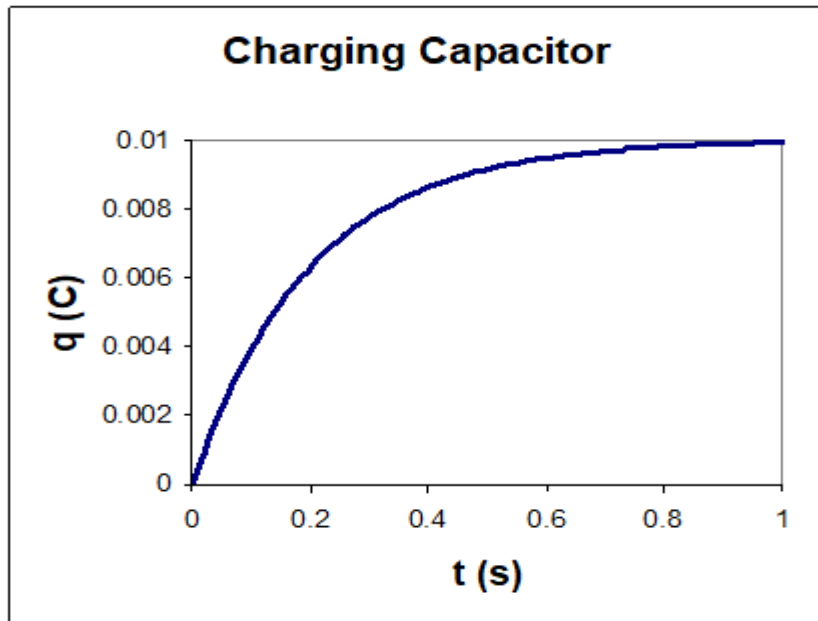
$$I(t) = \frac{\varepsilon}{R} e^{-\frac{t}{RC}}$$



Sample plots with $\varepsilon=10$ V, $R=200$ Ω , and $C=1000$ μF .
 $RC=0.2$ s

In a time $t=RC$, the capacitor charges to $Q(1-e^{-1})$ or 63% of its capacity...

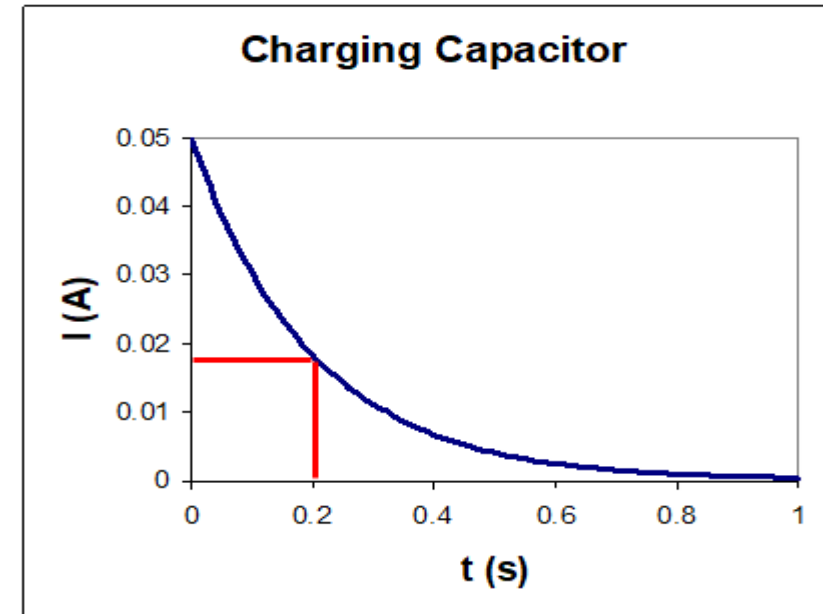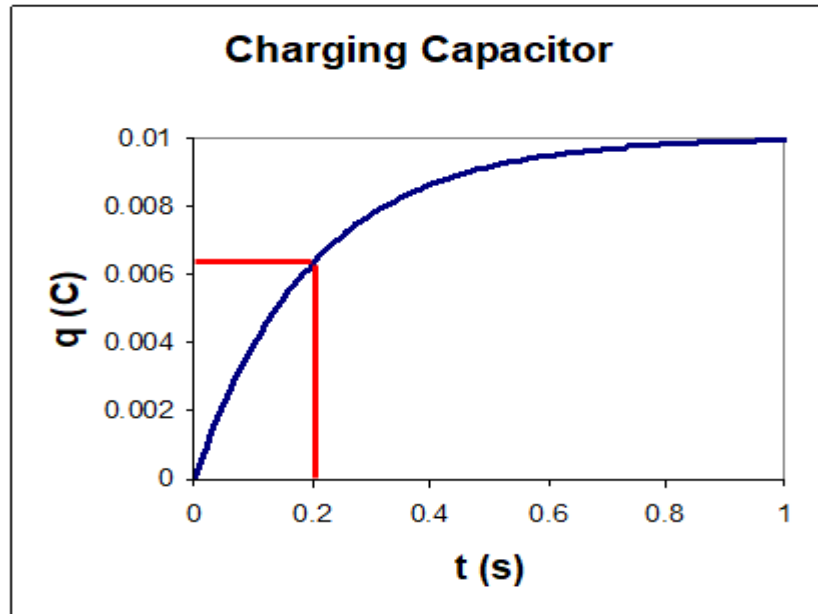...and the current drops to $I_{\max}(e^{-1})$ or 37% of its maximum.



$$RC = 0.2 \text{ s}$$

$$\tau = RC$$

is called the **time constant** of the RC circuit


Discharging a Capacitor

Capacitor charged, switch open, no current flows.

Close switch, current flows.

Apply Kirchoff's loop rule* (green loop) at the instant charge on C is q .

$$\frac{q}{C} - IR = 0$$

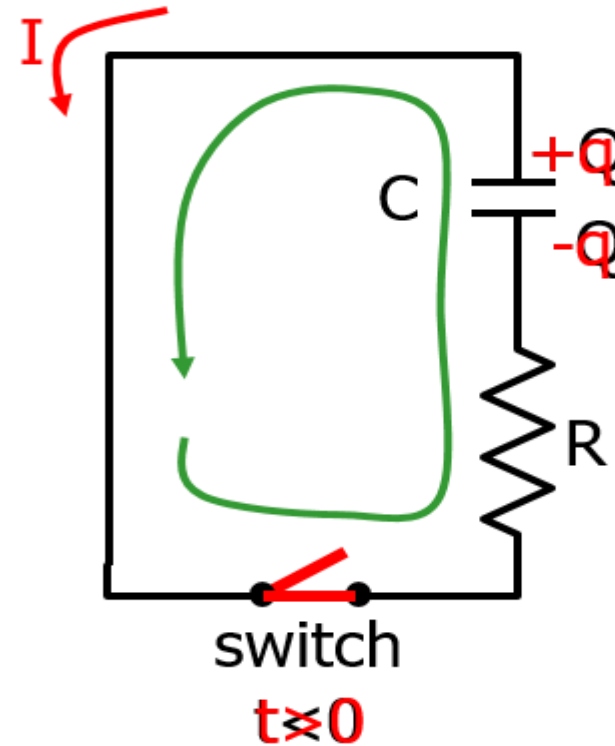

*Convention for capacitors is "like" batteries: positive if going across from - to +.


Discharging a Capacitor

Capacitor charged, switch open, no current flows.

Close switch, current flows.

Apply Kirchoff's loop rule* (green loop) at the instant charge on C is q .

$$\frac{q}{C} - IR = 0$$

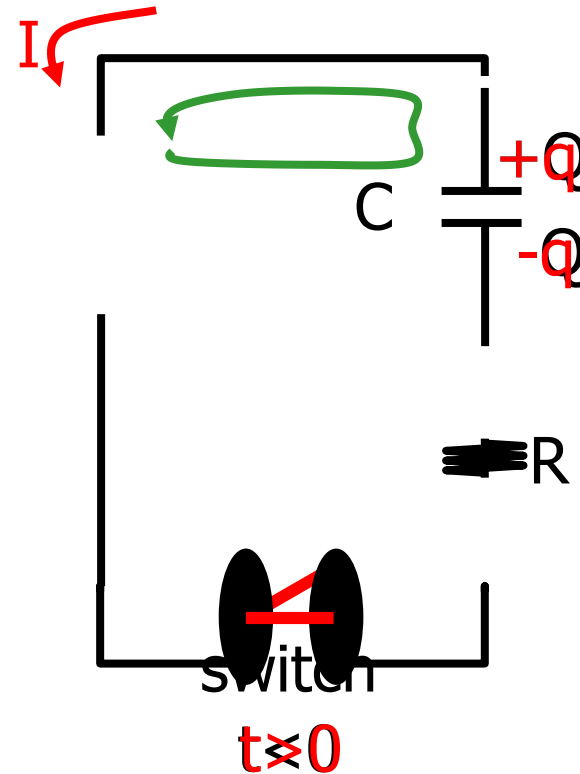

*Convention for capacitors is "like" batteries: positive if going across from - to +.

Math:

$$\frac{q}{C} - IR = 0$$

$$IR = \frac{q}{C}$$

$$I = -\frac{dq}{dt}$$

negative because
charge decreases

$$-R \frac{dq}{dt} = \frac{q}{C}$$

$$\frac{dq}{q} = -\frac{dt}{RC}$$

More math:

$$\int_Q^q \frac{dq}{q} = - \int_0^t \frac{dt}{RC} = - \frac{1}{RC} \int_0^t dt$$

$$\ln(q)|_Q^q = - \frac{1}{RC} \int_0^t dt$$

$$\ln\left(\frac{q}{Q}\right) = - \frac{t}{RC}$$

$$q(t) = Q e^{-\frac{t}{RC}}$$



$$I(t) = - \frac{dq}{dt} = \frac{Q}{RC} e^{-\frac{t}{RC}} = I_0 e^{-\frac{t}{RC}}$$

same equation
as for charging

Discharging a capacitor; summary:

$$q(t) = Q_0 e^{-\frac{t}{RC}}$$



$$I(t) = I_0 e^{-\frac{t}{RC}}$$

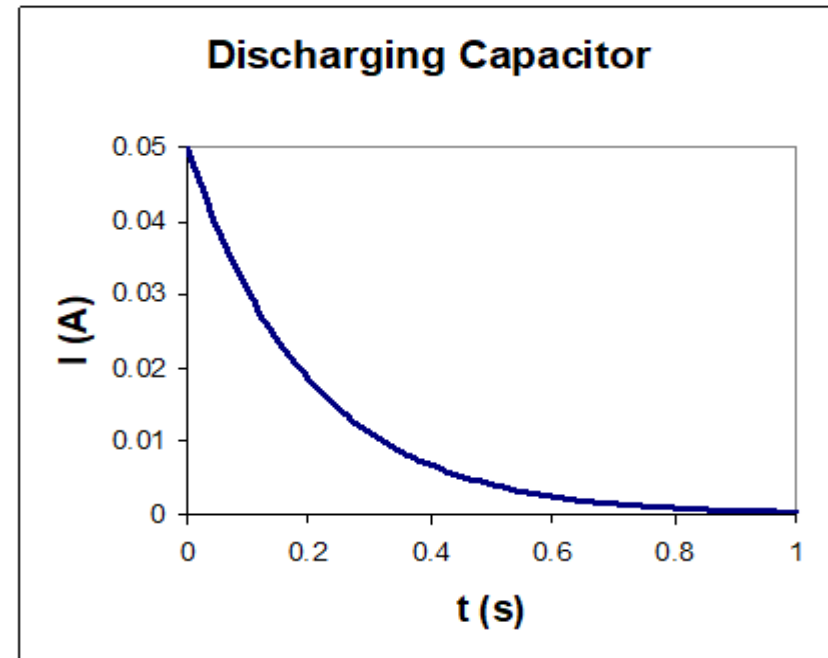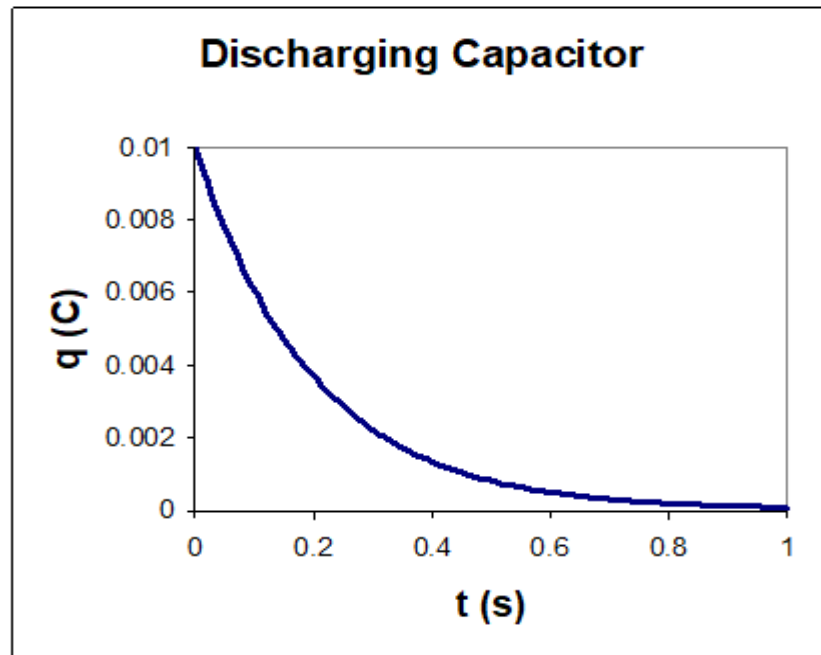

Sample plots with $\varepsilon=10$ V, $R=200$ Ω , and $C=1000$ μF .
 $RC=0.2$ s

In a time $t=RC$, the capacitor discharges to Qe^{-1} or 37% of its capacity...

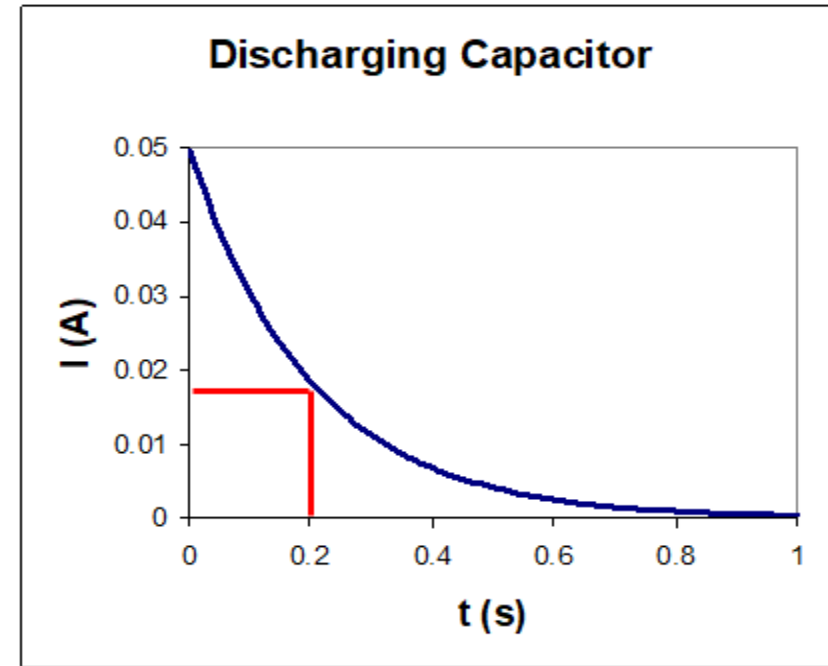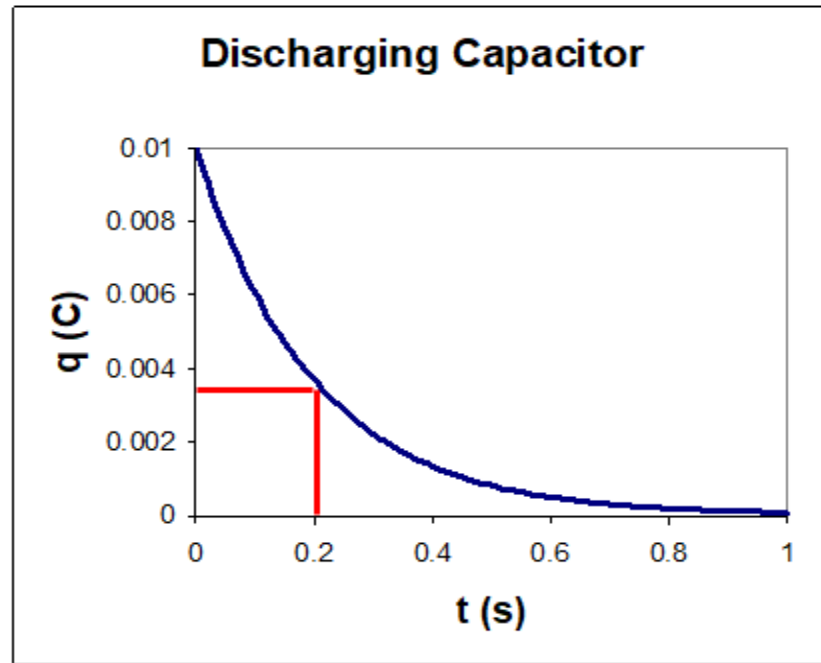...and the current drops to $I_{\max}(e^{-1})$ or 37% of its maximum.



$$RC=0.2 \text{ s}$$

Notes

$$I(t) = \frac{\varepsilon}{R} e^{-\frac{t}{RC}}$$

This is for charging a capacitor.
 $\varepsilon/R = I_0 = I_{\max}$ is the initial current,
and depends on the charging emf
and the resistor.

$$I(t) = I_0 e^{-\frac{t}{RC}}$$

This is for discharging a capacitor.
 $I_0 = Q/RC$, and depends on how
much charge Q the capacitor
started with.

I_0 for charging is equal to I_0 for discharging only if the discharging capacitor was fully charged.

Notes

In a series RC circuit, the same current I flows through both the capacitor and the resistor. Sometimes this fact comes in handy.

In a series RC circuit, where a source of emf is present (so this is for capacitor charging problems)...

$$V_R + V_C = \Delta V$$

$$V_R = \Delta V - V_C = IR \quad V_C \text{ and } I \text{ must be at the same instant in time for this to work.}$$

$$I = \frac{\Delta V - V_C}{R}$$

Any technique that begins with a starting equation and is worked correctly is acceptable, but I don't recommend trying to memorize a bunch of special cases. Starting with $I(t) = dq(t)/dt$ always works.

Notes

In a discharging capacitor problem...

$$V_R = V_C = IR$$

$$I = \frac{V_C}{R}$$

So sometimes you can “get away” with using $V = IR$, where V is the potential difference across the capacitor (if the circuit has only a resistor and a capacitor).

Rather than hoping you get lucky and “get away” with using $V = IR$, I recommend you understand the physics of the circuit!