



Name: ..... Student Id: .....

### Quiz #3

A single-loop circuit contains two resistors and two batteries, as shown in figure below. Answer the following questions:

- 1) Find the current in the circuit.
- 2) What power is delivered to each resistor?

